RACTICAL

ELECTRONICS

¢50

ARCH 1974

RHYTHM GENERATOR

ustralia	50c
ew Zealand	50c
outh Africa	45c
hodesia	45c
Nigeria	K.40
Sweden	Kr. 3.50
Malaysia	$1.80
Malta	22c5
Norway	Kr. 5.10

Also...

FREE! IN THIS ISSUE...

Our BLUEPRINT *for combating the* FUEL/POWER CRISIS

- SCORPIO Mk2 CAR IGNITION SYSTEM
- FLUORESCENT LAMP INVERTER

Write the Specification of your perfect iron

and compare it with an Antex

MODEL X25 Soldering Iron 220-240 or 100-120 Volts. The leakage current of the NEW X25 is only a few micro-amps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". **Totally enclosed element. Ceramic and** steel shaft. Bits do not "freeze" and can easily be removed. **PRICE £2·05** **(rec. retail)** P & P 10p. **Suitable for** production work and as a general purpose iron.

MODEL CCN
220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16" 1/4" and 3/64" including Heat Shield. **PRICE £2·48** (rec. retail) P & P 10p.

as selected for the DESIGN CENTRE LONDON

MODEL C Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64", to 3/16". Voltages 240, 220, 110, 50 or 24. **PRICE £2·05** (rec. retail) P & P 10p.

MODEL G 18 watt miniature iron, fitted with long-life iron-coated bit 3/32". Voltage 240, 220 or 110. **PRICE £2·26** (rec. retail) P & P 10p.

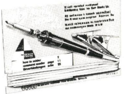

MODEL MLX KIT
Battery operated 12v.
25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet and with booklet "How to Solder".
PRICE £2·54 (rec. retail)
P & P 12p.

MODEL SK.2 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" **heat sink, solder and** "How to Solder" booklet.
PRICE £3·25 (rec. retail)
P & P 10p.

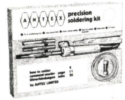

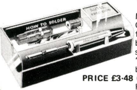

MODEL SK.1 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.
PRICE £3·48 (rec. retail)
P & P 12p.

ST3 Stand – This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands. The two sponges at the side which are easily replaceable, serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration.
PRICE: £1·00 (rec. retail) P & P 10p.

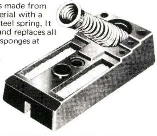

ALL PRICES include VAT at 10%

ANTEX

☐ **Please send the following:**

____

____

☐ Please send the ANTEX colour catalogue

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:
ANTEX LTD. FREEPOST
PLYMOUTH PL1 1BR
(no stamp required) Tel 0752 67377.

I enclose cheque/P.O./Cash (Giro No. 258 1000) ______________

NAME ______________

ADDRESS ______________

____

______________ PE3

PRACTICAL ELECTRONICS

VOLUME 10 No. 3 MARCH 1974

CONSTRUCTIONAL PROJECTS

RHYTHM GENERATOR *by Brice Ward*
A programmable source for 64,000 rhythmic patterns 228

***FLUORESCENT LAMP INVERTER** *by C. J. Mills*
Emergency lighting from a 12V supply. Blueprint design for 8, 13 and 20W units 237

ELECTRONIC SNAP *by C. J. Allen*
End those arguments about who answered first with this novelty circuit 246

***P.E. SCORPIO Mk 2 IGNITION SYSTEM** *by D. S. Gibbs & I. M. Shaw*
Electronic ignition system. Blueprint design for 6 or 12V cars 248

A.C. DETECTOR PROBE *by B. Bowles*
A simple circuit for detecting the presence of oscillations 253

CRYSTAL CALIBRATION OSCILLATOR *by R. A. Penfold*
A highly stable fixed frequency oscillator for calibration purposes 258

BOOLEAN ALGEBRA—1 *by B. J. Wood*
An introduction to switching theory 264

GENERAL FEATURES

CONSTANT CURRENT GENERATORS—1 *by C. R. Masson*
First of a two part series on the design and use of these versatile circuits 242

INGENUITY UNLIMITED
Optical Communications System—Boiler Gas Valve Operation—
Slow Timebase Oscillator—Tape Guide 260

NEWS AND COMMENT

EDITORIAL—Inspiring Times 227

SPACEWATCH *by Frank W. Hyde*
Skylab Mission—Pioneer 10 and Jupiter 241

ON THE FRINGE *by Gerry Brown*
The more unusual aspects of electronics 252

BOOK REVIEWS
Selected new books we have received 269

ESP etc. *by B. H. Baily*
Unexplained happenings and phenomena 270

INDUSTRY NOTEBOOK *by Nexus*
What's happening inside industry 273

PATENTS REVIEW
Thought provoking ideas on file at the British Patents Office 274

*SPECIAL FREE BLUEPRINT

FLUORESCENT LAMP INVERTER—P.E. SCORPIO Mk 2 IGNITION SYSTEM

Our April issue will be published on Friday, March 8, 1974

© IPC Magazines Limited 1974. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, Inland £3·25, Overseas £3·50. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

Henry's

PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS
IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS
You need a catalogue! 55p post paid complete with Discount Vouchers

TEST EQUIPMENT

MULTIMETERS

(carr., etc. 30p)
M210 20k/V Slimline, **£6·75**
THL33D 2k/V Robust, **£7·50**
U437 10k/V Steel case. A.C. up to 40kHz, **£4·95**
U4324 20k/V with A.C. current ranges, **£8·00**
AF105 50k/V, **£11·95**
U4313 20k/V A.C. current. Steel case, **£10·50**
U4341 Plus built in transistor tester, **£10·50**
Model 500 30k/V, **£9·95**

OTHER EQUIPMENT

SE250B Pocket Signal Injector, **£2·10.** Carr. 15p
SE500 Pocket Signal Tracer, **£1·70.** Carr. 15p
TE15 Grid Dip Meter 440kHz—280MHz, **£15·00.** Carr. 30p
TE40 A.C. Millivoltmeter 1·2MHz, **£18·95.** Carr. 35p
TE65 28 Range Valve Voltmeter, **£19·95.** Carr. 40p
TE20D 120kHz—500MHz RF Generator, **£17·95.** Carr. 40p
TE22D 20Hz—200kHz Audio Generator, **£18·95.** Carr. 40p
SE350A Deluxe Signal Tracer, **£12·50.** Carr. 20p
SE400 Volts/ohms/R-C sub./RF field/RF gen., **£14·75.** Carr. 20p

New Revolutionary Supertester 680R

680R Multi-tester, **£18·50**

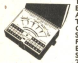

Accessories	
Transistor tester	**£11·00**
Electronic voltmeter	**£18·00**
Ampclamp	**£11·95**
Temperature probe	**£11·95**
Gauss meter	**£11·95**
Signal Injector	**£5·95**
Phase sequence	**£5·95**
EHT Probe	**£5·95**
Shunts 25/50/100A	**£4·50** each

A SELECTION OF INTERESTING ITEMS

C3025 Compact transistor tester, **£6·30.** P. & P. 15p
E1300 Mono mag cart preamp, **£2·75.** P. & P. 15p
E1310 Stereo mag cart preamp, **£4·62.** P. & P. 25p
Easiphone telephone amplifier, **£7·95.** P. & P. 25p
D1203 Teleamp with PU coil, **£4·40.** P. & P. 20p
LL1 Door Intercomm. and chime, **£7·95.** P. & P. 25p
Chattalite (lights as you talk), **£13·90.** P. & P. 20p
1kW Dimmer/controller, **£3·00.** P. & P. 10p
9in Twin spring unit, for Reverbs, **£3·30.** P. & P. 15p
16in Twin spring unit, for Reverbs, **£6·85.** P. & P. 25p
Car Tachometer Electronic, **£8·95.** P. & P. 15p
VHF Aircraft band corrector, **£4·50.** P. & P. 15p
B2005 4 Ch. mic. mixer, **£3·75.** P. & P. 15p
B2004 2 Ch. stereo mixer, **£5·95.** P. & P. 15p
PK3 Kit. Etch your own printed circuits, **£1·50.** P & P. 20p

EXCLUSIVE: SPECIAL OFFERS

MW/LW CAR RADIO + or − earth with speaker and fixings. **£6·50** carr/packg. 30p.

8 TRACK CAR STEREO (− earth) with speakers, in pods and fixings. **£12·50** carr/packg. 40p.

Portable Battery Cassette tape player **£7·25**.

Car Lighter Plug and adaptor for all cassette and radio 6/7½/9 volt output (state width). **£1·95** each.

Rotel Stereophones

RH630	**£4·50**
RH700	**£6·75**
RH430	**£3·30**

Rotel RA310 15 + 15 watt Stereo Amplifier (List £52·00) **£34·52.**

Wein W500 Battery/Mains Cassette Recorder **£12·75.**

AKAI GXC40 stereo cassette recorder **£59·95** carr/packg. 50p,

Pair Akai ADM microphones. **£6·95** carr/packg. 20p.

PORTABLE CASSETTE TAPE PLAYER — for car or carry around. **£7·25** carr/packg. 20p.

HANIMAX BC808 POCKET CALCULATOR with % key. **£28·95.**

Hanimax BC811M Memory Version **£37·50.**

Mains Unit for BC808, BC811M **£2·85** (state model).

Hanimax H101 Stereo Compact Record Player 2×7w. Complete with speakers (List £54·50). Price **£39·95.** Plus free pair of stereo phones.

BUILD THIS RADIO

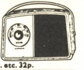

PORTABLE MW/LW RADIO KIT using Mullard RF/IF module. Features MW—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts **£7·98** (battery 22p). Carr. etc. 32p.

SPECIAL PURCHASES

UFH TV TUNERS CHANNELS 21 to 64. Brand new transistorised geared tuners for 625 Line Receiver IF output. **£2·50.** Post 20p.

EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

Model No.		£
310	Radio control receiver	2·98
300	4-channel R/C transmitter	5·95
345	Superhet R/C receiver	5·95
455	AM signal generator	12·33
65	Simple transistor tester	1·40
115	8W amplifier	3·90
120	12W amplifier	4·70
125	Stereo control unit	5·70
130	Mono control unit	3·60
605	Power supply for 115	4·55
610	Power supply for 120	4·55
615	Power supply for 2 × 120	5·73
230	AM/FM aerial amplifier	2·93
240	Auto packing light	5·90
275	Mic. preamplifier	6·08
570	LF generator 10Hz—1mHz	15·80
575	Sq. wave generator 20Hz–20kHz	14·60
590	SWR meter	12·85
620	Ni–CAD Charger 1·2–12V	8·00
630	STAB. Power supply 6–12V 0·25–0–1A	8·15
690	D.C. motor speed Gov.	2·87
700	Electronic Chaffinch	7·00
705	Windscreen wiper timer	6·80
760	Acoustic switch	10·75
780	Metal Detector (electronics only)	9·65
790	Capacitive burglar alarm	6·85
835	Guitar preamp	4·25
840	Delay car alarm	6·15
875	CAP. Discharge ignition for car engine (–Ve Earth)	13·15
80	Scope calibrator	2·25
255	Level indicator	6·15
525	120—160mHz VHF timer	11·30
715	Photo cell switch	7·70
795	Electronic continuity tester	4·30
860	Photo timer	13·25
871	Slide projector auto feed control	7·15
235	Acoustic alarm for driver	7·60
465	Quartz XTAL checker	8·75
220	Signal Injector	2·30
390	VOX	15·50
432	Testakit	19·30
670	Buffer Battery Charger	6·55
885	Capacitive Contact Alarm	6·25
850	Electronic Keyer	18·75
820	Electronic Digital Clock	58·50

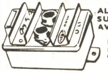

ALL KITS OFFERED SUBJECT TO STOCK AVAILABILITY

Prices correct at time of preparation, subject to change without notice.

BUILD THIS TUNER

MW/LW Radio tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built-in battery. Excellent results. Size: 7in × 2¾in × 3¾in. All parts **£4·85.** Carr. 15p.

MULTI-USE AND RADIONIC KITS

		£
10–1	10 Projects	3·60
50–1	50 Projects	8·00
150–1	150 Projects	13·20
Telephone Communicator		7·20
X20	20 (Elec) Projects	4·95
X40	40 (radio) Projects	9·45

(Carr./Packing 40p)

ALL TRANSISTOR CIRCUITS WITH HANDBOOKS

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post, etc. 15p per order unless stated.

GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/erase heads. Wind and rewind controls. Takes up to 4in spools. Brand new complete with head circuits. **£9·50.** Carr. 30p.

TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).

Singles Log and Lin
5kΩ, 10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1 Meg. **45p** each.

Ganged Log and Lin
10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ. **65p** each.
(Quantity discounts available). Complete with knobs.

MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO
'17' High Impedance, **£2·00;** '18' Med. Impedance, **£2·00;** Erase Heads for '17' and '18', **75p;** '63' 2 track mono-Hi imp., **£1·75;** '43' Erase Head for '63', **75p.** (Post, etc. 15p any quantity).

R730/E73 2 Track Mono Record Erase Low Imp., **75p** pair.

Sinclair, Miniature Amplifiers & Tuner/Decoder

AMPLIFIERS (Carr. etc. 20p).		£
4–300	0·3 watt 9 volt	1·75
104	1 watt 9 volt	2·80
304	3 watt 9 volt	2·95
555	3 watt 12 volt	3·10
E1208	5 watt 12 volt	5·10
608	10 watt 24 volt	4·10
410	10 watt 28 volt	4·95
E1206	30 watt 45 volt	9·95
E1210	2½ + 2½ watts 12 volt	6·25
RE500	5 watt IC mains operated Amplifier with controls	6·30
SAC14	7 + 7 watt Stereo with controls	8·70
SAC30	15 + 15 watt Stereo with controls	11·75

SINCLAIR PROJECT 60 (Carr. 20p)	£
Z30 3·57 Z50	4·37
Stereo 60 Preamplifier	7·97
PZ5	3·97
PZ6	6·37
PZ8 (for Z50)	4·77
TRANS.	3·95
AFU	4·45

NEW SINCLAIR PROJECT 80	£
Stereo Preamplifier	11·95
Audio Filter Unit	6·95
Z40 15 Watt Amplifier	5·45
Z60 25 Watt Amplifier	6·95
PZ5 Model for 1 on 2 Z40	4·98
PZ6 Model (S. Tab.) 1 on 2 Z40	7·98
PZ8 Model (S. Tab.) 1 on 2 Z60	7·98
TRANSFORMER FOR PZ8	2·95
Project 605 Kit	19·95
Project 805	£26·95
SP40-5 2Z40/Stereo 80/PZ5	£25·00
SP40-6 2Z40/Stereo 80/PZ6	£27·75
SP60 2Z60/Stereo 80/PZ8	£30·45

(Transformer PZ8 **£3·95**)

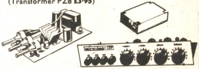

POWER SUPPLIES FOR EVERY PURPOSE

(All cased unless stated chassis)
470C 6/7½/9V 300mA, (Includes Multi-Adaptor for Tape Recorders, etc.), **£2·15.** Post 20p
Car Lighter Voltage Adaptors 300mA (State Voltage 6V, 7½V, 9V), **£1·95** each. Post 25p
SC202 3/6/7½/9V 400mA, **£3·35.** Carr. 30p
HC244R Stabilised version, **£4·35.** Carr. 30p
P500 9V 500mA, **£2·90.** Post 20p
P11 24V 500mA (chassis), **£2·90.** Post 20p
P15 26/28V 1 amp (chassis), **£2·90.** Post 20p
P1080 12V 1 amp (chassis), **£4·25.** Post 20p
P1081 45V 0·9 amp (chassis), **£7·50.** Post 20p
P12 4½—12V 0·4—1 amp, **£7·15.** Post 30p
SE101A 3/6/9/12V 1 amp (Stab.), **£10·30.** Post 25p
RP164 6/7½/9/12 1 amp (Stab.), **£10·20.** Post 30p

FIBRE OPTICS

0·01 dia. Mono Filament, **£1·50** per 25 metre reel.
0·13 dia. 64 Fibres Sheathed, **£1·00** per metre.
SPRAYS 15mm dia. Mares Tails, **£9·50.**

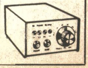

Henry's RADIO LIMITED

EDGWARE ROAD, W2

SEE FACiNG PAGE FOR ADDRESSES

Henry's

UK'S LARGEST RANGE OF TRANSISTORS, IC'S RECTIFIERS, ALL SEMICONDUCTOR DEVICES

BEST PRICES · RETAIL · TRADE · EXPORT & INDUSTRIAL

FREE BOOKLET

All types of
TRANSISTORS • RECTIFIERS
BRIDGES • SCR's • TRIACS
INTEGRATED CIRCUITS
F.E.T. • LIGHT DEVICES
OVER **1500** DIFFERENT DEVICES

MORE DEVICES
NEW PRICES
NEW RANGES
THIS IS A MUST
FOR ALL
SEMI-CONDUCTOR
USERS!

ENTIRELY NEW 1973 EDITION (ask for Booklet No. 36)

SEND FOR YOUR FREE COPY TODAY!

INTEGRATED CIRCUITS. VERY IMPORTANT—**ONLY** BRANDED I.C's ARE TO THE **FULL** MANUFACTURERS' SPECIFICATIONS. **ALL** OTHERS ARE NOT. HENRY'S SELL *ONLY* BRANDED INTEGRATED CIRCUITS . . . FROM **TEXAS . . . I.T.T. . . . FAIRCHILD . . . SIGNETICS** . . . SO WHY BUY ALTERNATIVES OR UNDER SPEC. DEVICES WHEN YOU CAN PURCHASE THE GENUINE ARTICLE FROM US EX STOCK . . . NEED WE SAY MORE!

Type	1–11 £p	12–29 £p	30–99 £p	Type	1–11 £p	12–29 £p	30–99 £p
SN7400N	20	18	16	SN7446N	2·16	2·16	1·89
SN7401N	20	18	16	SN7447AN	1·80	1·80	1·57
SN7401AN	38	38	33	SN7448N	1·50	1·27	1·13
SN7402N	20	18	16	SN7450N	20	18	16
SN7403N	20	18	16	SN7451N	20	18	16
SN7403AN	38	38	33	SN7453N	20	18	16
SN7404N	24	21	18	SN7454N	20	18	16
SN7405N	20	18	16	SN7460N	20	18	16
SN7405AN	44	44	38	SN7470N	33	30	27
SN7406N	40	38	35	SN7472N	38	38	34
SN7407N	40	38	35	SN7473N	44	41	37
SN7408N	25	22	19	SN7474N	48	48	42
SN7409N	33	33	28	SN7475N	59	55	51
SN7409AN	44	44	38	SN7476N	45	36	32
SN7410N	20	18	16	SN7480N	80	70	50
SN7411N	25	23	21	SN7481N	1·25	1·10	95
SN7412N	28	28	25	SN7482N	87	80	72
SN7412AN	38	38	33	SN7483N	1·20	1·10	1·00
SN7413N	30	27	25	SN7485N	1·87	1·87	1·63
SN7414N	72	72	63	SN7486N	50	50	44
SN7416N	30	27	25	SN7489N	4·32	4·32	3·78
SN7417N	30	27	25	SN7490N	75	70	63
SN7420N	20	18	16	SN7491AN	1·10	1·00	90
SN7422N	28	28	25	SN7492N	75	70	63
SN7422AN	38	38	33	SN7493N	75	70	63
SN7423N	37	34	32	SN7494N	85	80	75
SN7425N	37	37	32	SN7495N	85	80	75
SN7427N	37	37	32	SN7496N	1·00	90	83
SN7428N	43	43	37	SN74100N	2·16	1·89	1·89
SN7430N	20	18	16	SN74104N	60	53	45
SN7432N	37	37	32	SN74105N	60	53	45
SN7433N	43	43	38	SN74107N	51	51	45
SN7433AN	57	57	50	SN74110N	57	57	50
SN7437N	43	43	37	SN74111N	86	86	75
SN7438N	43	43	37	SN74116N	2·16	2·16	1·89
SN7438AN	57	57	50	SN74118N	1·00	90	83
SN7440N	20	18	16	SN74119N	1·92	1·92	1·68
SN7441AN	85	79	73	SN74120N	1·05	1·05	92
SN7442N	85	79	73	SN74121N	57	57	50
SN7443N	1·50	1·27	1·13	SN74122N	80	80	70
SN7444N	1·50	1·27	1·13	SN74123N	1·44	1·44	1·26
SN7445N	2·16	2·16	1·89	SN74125N	69	69	60

Type	1–11 £p	12–29 £p	30–99 £p
SN74126N	69	69	60
SN74132N	72	72	63
SN74136N	63	63	55
SN74141N	1·00	90	80
SN74142N	2·88	2·88	2·52
SN74145N	1·44	1·44	1·26
SN74147N	2·30	2·30	1·83
SN74148N	2·01	2·01	1·63
SN74150N	2·30	2·30	2·01
SN74151N	1·15	1·15	1·00
SN74153N	1·09	1·09	95
SN74154N	2·30	2·30	2·01
SN74155N	1·55	1·55	1·00
SN74156N	1·09	1·09	1·00
SN74157N	1·09	1·09	95
SN74159N	2·44	2·44	2·14
SN74160N	1·58	1·58	1·38
SN74161N	1·58	1·58	1·38
SN74162N	1·58	1·58	1·38
SN74163N	1·58	1·58	1·38
SN74164N	2·01	2·01	1·76
SN74165N	2·01	2·01	1·76
SN74166N	2·16	2·16	1·89
SN74167N	4·10	4·10	3·59
SN74170N	2·88	2·88	2·52
SN74172N	5·76	5·76	5·04
SN74173N	1·66	1·66	1·45
SN74174N	1·80	1·80	1·57
SN74175N	1·29	1·29	1·13
SN74176N	1·44	1·44	1·26
SN74177N	1·44	1·44	1·26
SN74180N	1·44	1·44	1·26
SN74181N	5·18	5·18	4·53
SN74182N	1·44	1·44	1·26
SN74184N	2·16	2·16	1·89
SN74185AN	2·16	2·16	1·89
SN74188N	6·48	6·48	5·67
SN74190N	2·30	2·30	2·01
SN74191N	2·30	2·30	2·01
SN74192N	2·30	2 30	2·01
SN74193N	2·30	2·30	2·01
SN74194N	1·72	1·72	1·51
SN74195N	1·44	1·44	1·26
SN74196N	1·58	1·58	1·38
SN74197N	1·58	1·58	1·38
SN74198N	3·16	3·16	2·77
SN74199N	2·88	2·88	2·52

PRICING OF SN7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX

SN74 (HIGH POWER), SN74 (LOW POWER) series in stock. Send for List 36 free on request. Low Profile Sockets, 14 pin, **15p**, 16 pin, **17p**, 8 pin, **14p**.

TRANSISTORS—A selection

For *full* list send for booklet 36 today

Type	£ p	Type	£ p	Type	£ p	Type	£ p	Type	£ p	Type	£ p
AAZ13	10	BC169C	14	BY100	15	OC36	65	V405A	25	2N3614	59
AC107	35	BC182	12	BY127	15	OC44	18	ZTX108	10	2N3702	11
AC128	20	BCY32	85	BYZ13	35	OC45	18	ZTX300	14	2N3714	1·60
AC187	20	BCY39	1·00	C106D	55	OC71	15	ZTX302	18	2N3771	1·75
ACY17	35	BCY55	2·50	GET111	55	OC72	25	ZTX500	15	2N3773	2·25
ACY39	65	BCY70	15	GET115	75	OC77	55	2G301	40	2N3790	2·25
AD149	50	BCY71	20	GET880	55	OC81	28	2N697	15	2N3819	35
AD161	39	BCY72	13	LM309K	1·87	OC83	25	2N706	10	2N3866	75
AD162	39	BD124	80	MAT121	25	OC140	65	2N930	20	2N3903	15
AF117	20	BD131	45	MJE340	50	OC170	25	2N987	45	2N4062	14
AF118	50	BF115	22	MJE520	65	OC200	55	2N1132	25	2N4126	15
AF139	33	BF180	33	MJE305S	75	OC202	90	2N1304	22	2N4871	35
AF186	40	BF194	13	MPF105	46	OCP71	1·00	2N1613	20	2N5457	36
AF239	44	BFX13	25	NKT217	45	ORP12	55	2N1671	1·00	2S001	3·00
ASY27	30	BFX34	55	NKT404	60	ORP60	45	2N2147	75	2S026	8·90
BA115	10	BFX88	22	OA5	60	P346A	20	2N2160	69	2S303	70
BAX13	5	BFY50	20	OA81	10	TIL209	25	2N2926	10	40250	45
BC107	15	BFY51	20	OA200	8	TIP29A	49	2N3053	20	40361	45
BC108	15	BFY64	45	OA202	10	TIP30A	58	2N3054	45	40362	40
BC109	15	BFY90	75	OC16	85	TIP31A	61	2N3055	45	40408	50
BC109C	14	BLY36	6·25	OC20	1·25	TIP41A	74	2N3440	50	40486	75
BC113	16	BSX20	15	OC28	65	TIP42A	90	2N3442	1·10	40636	1·00
BC147	12	BU105	2·20	OC35	55	TIS43	26	2N3525	80	40430	85

TBA 800 5 WATT I.C.

Suitable alternative to SL403D. 5/30 volt operated. 8/16 ohm 5 watt output.
With circuits and data **£1·50.**

SINCLAIR IC12

With circuits and data. 6 W IC with printed circuit board 28V operated, **£2.**

ZN414 IC

Integrated circuit radio as featured by many magazines. (PW Jan. 73 Reprint Ref. No. 19 for **10p**), **£1·20.**

STROBE TUBE ZFT4A/XTF2

Suitable for Dec. '73 Pract. Electronics, **£2·50**

ST2 (D32) DIAC **25p**
CRS1/40 SCR **45p**

ULTRASONIC TRANSDUCERS

Operate at 40kHz up to 100 yds. Ideal remote switching and signalling, complete with data transmitter and receiver, new I.C. circuits. Per pair, **£5·90.**
TA 960 I.C. with socket **£1·80.**

3015F 7 SEC.

IC size complete with data price **£1·70** each.
(Digital clock circuits Ref. No. 31, **15p**).

TRANSISTORS—SPECIAL OFFERS

2N3055

25	**47p** each
100	**42p** each
500	**39p** each
1000	**34p** each

BY127

25	**12p** each
100	**10p** each
500	**9p** each
1000	**8p** each

AF117

25	**15p** each
100	**13p** each
500	**12p** each
1000	**10p** each

OC35

25	**46p** each
100	**42p** each
500	**38p** each
1000	**34p** each

ZENER DIODES

400m/w BZY88/BZX83. From 3·3V—33V, **10p** each.
1·3W 5% Miniature Tubulars IN4700 series. From 3·3V—33V, **18p** each.
10W. Stnd. Mounting ZS series 6·8V—100V 5%, **40p** each.

LINEAR I.C.

LINEAR I.C.	£ p
702C (T05)	75
709C (T05)	39
709C (DIL)	39
723C (T099)	90
723C (DIL)	90
728C (DIL)	45
728C (T099)	45
741C (T05)	50
741C (DIL)	50
747C (T099)	1·00
747C (DIL)	1·00
748C (DIL)	61

SILICON RECTIFIERS

1 amp series. IN4001 to IN4007. From **6p** each.
1·5 amp. PL4001 to PL4007. From **8p** each.
3 amp. PL7001/IN5400. From **14p** each.
Send for full list 36.

SEMI-CONDUCTOR QUANTITY DISCOUNTS

10% 12+, 15% 25+, 20% 100+
All one type except where quantity discounts shown.
Min. order £1·00 please.

MORE OF EVERYTHING AT HENRY'S

See pages 202, 203 and Back Cover of this magazine.

BEST VALUE

10% VAT

TO BE ADDED TO ALL ORDERS

TRIACS—Stud Mounting with accessories

Type	P.I.V.	Price ea. 1–11
3 AMP RANGE		
SC35A	100V	80p
SC35B	200V	85p
SC35D	400V	90p
SC35E	500V	£1·20
6 AMP RANGE		
SC40A	100V	90p
SC40B	200V	95p
SC40D	400V	£1·20
SC40E	500V	£1·50
10 AMP RANGE		
SC45A	100V	£1·05
SC45B	200V	£1·15
SC45D	400V	£1·45
SC45E	500V	£1·85
15 AMP RANGE		
SC50A	100V	£1·45
SC50B	200V	£1·65
SC50D	400V	£1·95
SC50E	500V	£2·25

TRIACS—Additional Types

40430 TRIAC (T066) **85p**
40669 TRIAC (Plastic) **90p**
40486 TRIAC (T05) **75p**

NEW RANGES BRIDGE RECTIFIERS

FEATURES SMALL SIZE & LOW COST

250 M/A ¼ AMP P.I.V.

B025/05	50	16p
B025/10	100	18p

¼ × ¼ × ⅛in dia.

Type	P.I.V.	Price ea. 1–11
½ AMP		
B05/05	50V	20p
B05/10	100V	22p
B05/20	200V	23p
B05/40	400V	25p
B05/60	600V	27p

½H × ½L × $\frac{3}{16}$in. dia.

1 AMP

B1/05	50V	25p
B1/10	100V	25p
B1/20	200V	28p
B1/60	600V	30p

½H × ½L × $\frac{3}{16}$in. dia.

1 AMP

W005	50V	29p
W01	100V	30p
W02	200V	32p
W06	600V	35p

⅜ × ⅜in. tubular

2 AMPS

B2/05	50V	35p
B2/10	100V	40p
B2/20	200V	45p
B2/60	600V	50p
B2/100	1000V	55p

½H × ½L × $\frac{3}{16}$in. dia.

4 AMPS

B4/100	100V	55p
B4/200	200V	59p
B4/400	400V	65p
B4/600	600V	75p
B4/800	800V	£1·00

½H × ½L × $\frac{3}{16}$in. dia.

6 AMPS

B6/05	50V	65p
B6/10	100V	70p
B6/20	200V	80p
B6/40	400V	90p
B6/60	600V	£1·00

½H × ½L × $\frac{3}{16}$in. dia.

SILICON CONTROLLED RECTIFIERS

Type	P.I.V.	1–11
1 AMP (TO5)		
CRS 1/05AF	50V	30p
CRS 1/10AF	100V	30p
CRS 1/20AF	200V	35p
CRS 1/40AF	400V	45p
CRS 1/60AF	600V	55p
3 AMP (TO48)		
CRS 3/05AF	50V	40p
CRS 3/10AF	100V	40p
CRS 3/20AF	200V	45p
CRS 3/40AF	400V	55p
CRS 3/60AF	600V	65p
5 AMP	400V	60p
CRS	5/400V	60p
7 AMP (TO48)		
CRS 7/100	100V	60p
CRS 7/200	200V	67p
CRS 7/400	400V	85p
CRS 7/600	600V	95p

All types offered subject to availability. Prices correct at time of press. E. & O.E. U.K. post, etc. 15p per order.

Henry's RADIO LIMITED
EDGWARE ROAD, LONDON W2

404-406 Electronic Components and Equipment 01-402 8381
309 PA – Disco – Lighting High Power Sound 01-723 6963
303 Bargains Store (Callers only)
Home and Car Entertainment Centres. London and branches now open.
120 Shaftesbury Avenue, London W1 01-437 9692
104 Burnt Oak Broadway, Burnt Oak, Edgware 01-952 7402
190-194 Station Road, Harrow, Middlesex 01-663 7788/9
354-356 Edgware Road, London W2 01-402 5854/4736

All mail to
303 Edgware Road,
London W2 1BW
All stores open 9 am to 6 pm six days a week
Hi-Fi – Tape Equipment Discount Stock List Free at all stores

Mk III Sound to Light Unit Chassis Version

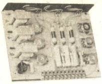

The audio drive voltage is derived directly from the amplifier output or across the speaker load. The unit converts the audio-frequency signals into a three-coloured light display when used with coloured flood lamps or similar; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.
Max. power 1·5kW per channel at 240V a.c.
Complete assembly built and tested. Size: 9in × 7in × 3in. Price **£27·50.**

MN3 3 Channel I.C. Mixer Kit

Three channel I.C. audio mixer kit MN3 is specially designed for the home constructor or educational project. Suitable for use in domestic audio, discotheque and simple p.a. applications. The MN3 mixer kit has the following features: Advanced design using 5 ICs; Slider fader level controls mounted directly to p.c. board; Full range Bass and Treble controls; Uses top grade components with fibreglass ready-drilled and tinned printed circuit board and the unit may be operated from twin 9V batteries (PP3) if required.

As optional extras, an attractive ready-punched facia panel and control knobs are available. The unit is available as a ready built mixer with facia.

Size: 9.5in × 4·8in × 1·5in (with facia).

Construction manual available separately at 25p.

Kit Price **£11.**

STL/1 Single Channel Sound to Light Unit

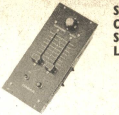

Single channel "Sound to Light" unit with 60mm slider fader controls for audio trigger level and background load dimmer.
This unit is switchable for response to High, Mid. and Low frequency audio signals, selected by facia control. A D.J. "pulse-flash" push button is fitted for manual flashing of the lamp load together with neon load indicator.
Maximum Load: 1kW at 240V a.c.
Size: 8in × 3·6in × 3in. Price **£14·30.**

Practical Electronics "Scorpio" Electronic Ignition System Kit

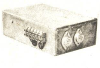

This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc.
Case size: 7·25in × 4·5in × 2in approx.
Complete assembly and wiring manual **25p.**
Price **£12·10.**

STL/3 Sound to Light Unit

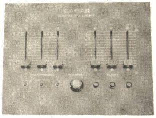

The performance of this unit is similar to the Mk III chassis version above, but is provided with an attractive black anodised facia panel and designed to mount directly into equipment desks or cabinets. High, Mid. and Low frequency channel sensitivity controls employ 60mm slider faders for present-day attractive appearance and ease of use. Size: 11in × 8·5in × 4in. Price **£42·35.**

AUDIO EFFECTS

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES, ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9V BATTERY (not supplied). COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD AND FULL INSTRUCTIONS. KIT PRICE **£2·86.**

All prices quoted include postage and VAT.
S.A.E. for further details.

DABAR ELECTRONIC PRODUCTS
98 LICHFIELD STREET, WALSALL
STAFFS WS1 1UZ

The Pictorial Method

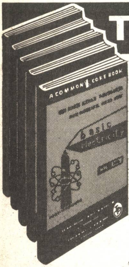

BASIC **ELECTRICITY**(5vols) **ELECTRONICS**(6vols) **TELEVISION**(3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

There is one fault, that being the great difficulty in putting the books down once you begin reading. *Y.T.O.. King's Lynn*

These manuals have played an important part in my career. *K.W.. West Drayton*

My only regret is that I should have purchased these manuals years ago. *C.B.. West Wickham*

I have studied many books but have learned more from Part One than from anything else. *B.A.. Reading*

These books create a sound basis on which to build a successful future. *R.G.. Gt. Yarmouth*

I am well pleased with the series. Everything is well set out in self-explanatory diagrams. *D.D.. West Ham*

POST NOW FOR THIS OFFER!

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES,
BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £............
BASIC ELECTRICITY 5 parts £5·30 ☐
BASIC ELECTRONICS 6 parts £6·40 ☐
BASIC TELEVISION 3 parts £3·60 ☐
Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME ....
BLOCK LETTERS
FULL POSTAL..
ADDRESS ....
....

I.L.P. (Electronics) Ltd

SECOND GENERATION 25 WATT HYBRID

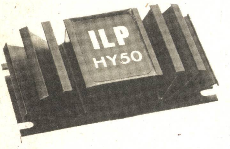

A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices.

We have now finally reduced the modular audio amplifier to a simple input/output device requiring only the addition of a basic unstabilized (split line) power supply.

The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of "King-size" cigarettes.

Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

SPEC.

OUTPUT POWER:	25W RMS, 50W peak music power.
LOAD IMPEDANCE:	4–16Ω into 8Ω
INPUT SENSITIVITY:	0dB (0·775V RMS).
INPUT IMPEDANCE:	47kΩ.
TOTAL HARMONIC DISTORTION:	Less than 0·1% at 25W typically 0·05.
SIGNAL/NOISE RATIO:	better than 75dB.
FREQUENCY RESPONSE:	10Hz–50kHz ± 1dB.
SUPPLY VOLTAGE:	±25V.
SIZE:	105 × 50 × 25mm.

Price £5·80 mono £11·60 stereo. Price inclusive of VAT & P. & P.

NEW HY5 PREAMPLIFIER

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids.

Like the HY50, the new HY5 has no external components and has been redesigned to run off a split power line with improvements in signal/noise, overload capability and reduced distortion. The output has been increased to match the power module (0dB), and share the same power supply.

Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 and power supply only potentiometers are required to complete a simple mono amplifier with input and output facilities expected to be found on Hi-Fi amplifiers.

The combination of two HY5's two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.

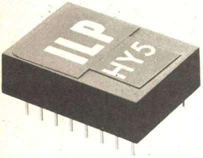

SPEC.

INPUTS
Magnetic Pick-up 3mV (within 1dB RIAA curve)
Ceramic Pick-up up to 3mV.
Microphone 10mV.
Tuner 250mV.
Auxiliary 3–100mV.
Input impedance 47kΩ 1 kHz

OUTPUTS
Tape 100mV.
Main output. 0dB (0·775V).

ACTIVE TONE CONTROLS
Treble ± 12dB at 10kHz
Bass ± 12dB at 100Hz

OVERLOAD CAPABILITY
(equalization stage) 40dB on most sensitive input.

OUTPUT NOISE LEVEL
(below 10mV magnetic input) 68dB.

DISTORTION 0·05% at 1kHz.
SUPPLY VOLTAGE ± 16–25V.
SUPPLY CURRENT 15mA.

Price £4·51 mono £9·02 stereo. Price inclusive of VAT & P. & P.

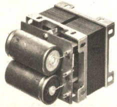

POWER SUPPLY PSU50

The new PSU50 has a low profile look being only 2¼in high and can be used for either mono or stereo systems.

SPEC.
OUTPUT VOLTAGE ± 25V.
INPUT VOLTAGE 210–240V.
SIZE: L. 70 D. 90 H. 60mm.
Price £5·23. Price inclusive of VAT & P. & P.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
OPEN 6 DAYS A WEEK. 9.00 a.m.-6.00 p.m.

TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION COMPANY LTD.
DEPT. E
163 MITCHAM ROAD, LONDON SW17 9PG
01-672 3137/9080

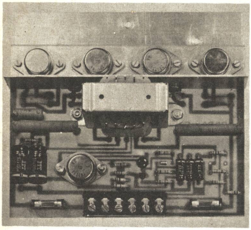

NEW TUAC POWER MODULES

TP125 illustrated
£15·25
★ 125 watts RMS continuous sine wave output
★ 4 RCA 150 watt 15 amp output transistors
★ Special layer wound driver transformer
★ Short, open, and thermal overload protection
★ Compact size: 7 x 6½ x 3 in.

TL100
£11·50
★ 100 watts RMS sine wave
★ 2 RCA 15 amp output transistors
★ Rugged transformer driver
★ Full thermal overload protection
★ Compact size: 5 x 5 x 3 in.

TL60
£9·75
★ 60 watts RMS sine wave
★ RCA 115 watt output transistors
★ Only six connections to make
★ Same size as TL100

TL30
£7·50
★ 30 watts RMS sine wave
★ Rugged transformer driver
★ 2 RCA output transistors
★ Full thermal overload protection

Power supplies vacuum impregnated Transformers with supply board incorporating stabilised pre-amp supply:

PS 125 ±50 volts for one TP125	£8·75
PS 100 ±45 volts for one TL100	£8·00
PS 60 ±40 volts for one TL60	£6·75
PS 30 ±30 volts for one TL30	£4·50
PSU 2 for supplying disco mixer	£3·50

Specification on all three power modules:
All output power rating ±1dB. Output impedance 8–15 ohms. THD at full power 1% typically 0·5%. Input sensitivity 60mV into 10kΩ. Frequency response 10Hz–25kHz ±2dB. Hum and noise better than −75dB.

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING
ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER.
H.P. ARRANGED THROUGH PAYBONDS.

Digital Clock Kits

SPACE RESEARCH NOW BRINGS YOU A DIGITAL CLOCK–WITH NO MOVING PARTS–FOR YOU TO BUILD.

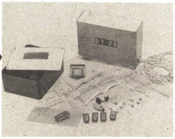

CHOOSE FROM TWO EASY TO BUILD KITS –

KIT O All components, including P.C.B. designed for easy home assembly – Bright and clear digits. Tough A.B.S. plastic case with contrasting front panel.
PRICE – **£23·00** plus £2·30 V.A.T.
Total **£25·30** inc. post and package

KIT M Smaller digits than that in kit O. All components and steel case covered in blue and white plastic (as made up in illustration).
PRICE – **£21·00** plus £2·10 V.A.T.
Total **£23·10**
inc. post and package.

Only our advanced designed techniques make these low prices possible. Both kits are tested before they leave us and are covered by the P.E.A. money back guarantee.

P.E.A. Ltd.
35 High Street
WELWYN
Herts. AL6 9EE

Please send details of: Kit O ☐ Kit M ☐
Please send me: Kit O ☐ Kit M ☐
I enclose PO/Cheque to the value of £ ____________
NAME ____________
ADDRESS ____________
____

MULTIMETER Model C-7081 GN Range Doubler 50,000 ohm/volt High Sensitivity Meter **£14·40.**

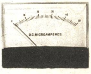

4½in × 3½in METER. 30μA, 50μA or 100μA, **£3·65.**

TAPE RECORDER LEVEL METER
500μA, 70p

MULTI-METER
Model 200H
20,000 ohm/volt, £6·50.

CARDIOID DYNAMIC MICROPHONE
Model UD-130. Frequency response 50–15,000c/s. Impedance Dual 50K and 600 ohms, **£6·40.**

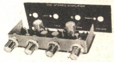

3 WATT STEREO AMPLIFIER
£4·30

All above prices include 10% V.A.T. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 6. Special prices for quantity quoted on request.

M. DZIUBAS
158 Bradshawgate • Bolton • Lancs. BL2 1BA

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic ASTRAD 17 and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! THIS ONE SUPERSEDES ALL EARLIER MODELS! It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for **both** battery and mains use! We're almost giving them away at only **£18·50—a mere fraction of even today's Russian miracle price!** We challenge you to compare performance and value with **£80** radios! ***Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call.** Volume controlled from a whisper to a roar that would fill a hall! **Much wider band spread for absolute "pinpoint" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity!** Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. **Yes, EVERY WAVEBAND** instantly at your fingertips **including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. VHF: FM/USW, AM: LW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world! Expensive TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! **Press-button dial illumination! Take it anywhere—** runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 in approx. **It's also a fabulous CAR RADIO. Can also be used through extension amplifier, tape recorder or public address system. SIZE 13in × 10in × 4½in** overall approx. Magnificently designed, in highly polished cases. Made to give years of perfect service. Purer & sweeter tone than ever. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With WRITTEN GUARANTEE, manual with simple operating instructions & circuit diagram. **PLUS ultra sensitive earphone for personal listening. ONLY £18·50** (with mains/battery eliminator **£2·25** extra) **BOX, POST, ETC. 45p. NO MORE TO PAY! *BUT WAIT, for only 75p extra** you get the sensational **"COMPUTERISED" WORLD TUNING GUIDE** (it enables you to zone and time in a flash for transmissions the whole world over—even a child can do it in a flash—**it even lets you know when to tune into the U.K. when abroad.** NO GUESSING! NO MESSING!) **PLUS Standard 'longlife' batteries and Converter Plug.** (Sorry—We cannot change these new radios for any earlier model already purchased.) Send quickly to Uxbridge Road address, or call at either Store. But HURRY!
SHOPERTUNITIES SAVE YOU £££'s & £££'s!

THOUSANDS of MILES REDUCED to INCHES?
LATEST RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD!*COMPUTERISED?
THIS FANTASTIC EARTH SHRINKER
BRAND NEW FABULOUS ASTRAD 17
PORTABLE RADIO & COMMUNICATIONS RECEIVER
WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!
"MAGIC EYE" tuning level indicator
YES, 24,901 miles SHRUNK TO ONLY 13 x 10 x 4½ inches approx?
28 TRANSISTORS AND DIODES!
WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM. FM. MW. LW. USW.)
*MUST YOU PAY UP TO £80?
FIRST TIME EVER!
*NOW AVAILABLE WITH fabulous 'COMPUTERISED' WORLD TUNING GUIDE!
NO MORE GUESSWORK–
INSTANT DATA at your fingertips – enables you to ZONE & TIME IN A FLASH for transmissions the world over!
THIS OFFER ONLY FROM US!
BATTERY MODEL £18·50 BOX POST ETC. 45p
MAINS/BATTERY ELIMINATOR £2·25 extra

BUY ONE FROM US!
SAVE £23·03 NOW!
fabulous BRAND NEW SOLID STATE
This equipment's got EVERYTHING!
BATTERY/MAINS AC
Combined V.H.F AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER
"MAGIC EYE"
WITH REMOTE CONTROL MICROPHONE
RECOMMENDED RETAIL PRICE £44
OUR PRICE £20·97 CARR. ETC. 50p

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!). We've snapped up 500 magnificent machines. **Latest sensation in the world of-sound!** First-class makers! Fabulous **VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains.** (Simply plug in the 220/240V AC line cord). **Record and play back anything, anywhere! IMPORTERS RECOMMENDED RETAIL PRICE £44! WE OFFER AT UNDER HALF PRICE!** Wonderful features: ★ **Press-button Keyboard Control Panel or latest MASTER SWITCH CONTROL!** ★ **"MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller!** ★ **Separate ON/OFF and HI-LO volume controls!** ★ **Heavy duty built-in speaker!** ★ **Earphone** (for personal listening or "monitoring") **and extension speaker sockets!** ★ **Remote control microphone!** ★ **Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.)** Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. **AND the amazing built-in full circuit VHF, AM/FM Radio** gives you superb clarity of tone, incredible station **selection.** Unique rotating Station Selector Dial—gets, locally, local city and regional stations in every part of the country, plus B.B.C. National, VHF. Picks up dozens of foreign stations. **Fabulous in your car!** You could pay £££'s more for a Car Radio or Car Cassette player ALONE! **£20·97, carr. etc., 50p— NO MORE TO PAY! Complete with simple instructions, remote control microphone with on/off switch and microphone stand. WITH WRITTEN GUARANTEE.** Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call.
BONUS OFFER: Batteries and Cassette Tape 28p extra if required.

FIRST TIME EVER! *SAVE £16·02!
BRAND NEW AC/DC BATTERY/MAINS
Cassette TAPE RECORDER & PLAYER
FIRST CLASS MAKERS
With remote control microphone.
WE COULD CHARGE UP TO £26·97!
OUR PRICE £10·95 POST ETC. 50p

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! **NOW** a superb de-luxe portable **BATTERY/MAINS** tape recorder and player—and incredible **Shopertunities** bring it to you for ONLY **£10·95.** Due to our cut price we cannot name first-class makers—but rest assured **you're getting one of the BEST!** Expensive **"PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) AND AUTOMATIC LEVEL CONTROL.** No fiddling with awkward tape and reels, **just "slap-in" a cassette and off you go!** (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere.) **Amazing** performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Complete—**record anywhere,** indoors or out! **Runs on standard batteries AND 220/240V AC mains.** Separate jacks for remote control microphone, etc. Size 9½in × 5in × 2½in approx. Design can vary slightly. With carry handle. WRITTEN GUARANTEE and full instructions. (Importers recommended selling price £26·97!) **OUR PRICE ONLY £10·95, post, etc. 50p. NO MORE TO PAY! Send and test, on mail order 7 day approval from receipt of goods—refund if not delighted.** Or call at either of our stores. **BONUS OFFER** (Rationed one per customer)—Cassette tape, Standard batteries **AND** microphone stand **55p** extra if required.

Order by post to Uxbridge Road address or call at either store.
Bargains galore at both stores.—**(COMMERCIAL TRAVELLERS PLEASE NOTE:** Merchandising office at Holborn Store.)

Callers: ACCESS & BARCLAY CARDS ACCEPTED AT BOTH STORES

SHOPERTUNITIES LTD.

Dept. PE/NC/36, 164 UXBRIDGE RD. (facing Shepherds Bush Green), **LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN** (opposite Chancery Lane), **LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.**

Don't miss

SOUND 74 international

BLOOMSBURY CENTRE HOTEL

Coram Street, Russell Square
London W.C.1

12-14 MARCH 1974

Tues/Wed 10.00-18.00 hrs.
Thurs 10.00-17.00 hrs.

THE ONLY EXHIBITION IN EUROPE EXCLUSIVELY FEATURING

PUBLIC ADDRESS & ALLIED EQUIPMENT

There will also be Lectures and Demonstrations

Tickets and information from the organisers

THE ASSOCIATION OF PUBLIC ADDRESS ENGINEERS
6 Conduit Street, London
WIR 9TG ENGLAND
TEL. 01-493 5256

NOW AVAILABLE IN THE U.K!

CHINAGLIA

ONE OF ITALY'S LEADING TEST EQUIPMENT MAKERS

PRESENT **THE CORTINA MINOR**

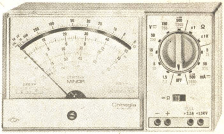

One of a range of professional quality instruments now available to U.K. users

● SENSITIVITY 20,000 Ω/VOLT (D.C.), 4,000 Ω/VOLT (A.C.) ● ROBUST DIODE PROTECTED PRECISION MOVEMENT ● 33 RANGES D.C. VOLTS 0–100mV, 1·5V, 5V, 15V, 50V, 150V, 500V, 1,500V. D.C. CURRENT 0–50μA, 5mA, 50mA, 500mA, 2·5A. A.C. VOLTS, 0–7·5V, 25V, 75V, 250V, 750V, 1,500V, A.C. CURRENT 0–25mA, 250mA, 2·5A, 12·5A. dB RANGES, −10 to + 69. RESISTANCE RANGES 10k Ω, 10M Ω F.S.D. CAPACITANCE RANGES 100μF, 1F F.S.D ● ACCURACY—RESISTANCE, D.C. VOLTAGE AND CURRENT, 2·5%. A.C. VOLTAGE AND CURRENT 3·5% ● OHMS RANGES POWERED BY INTERNAL BATTERIES ● COMPACT SIZE: 150 × 85 × 40mm 350gr ● CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR ● PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT ● FULLY GUARANTEED FOR 12 MONTHS ● AFTER SALES SERVICE AND SPARES FACILITIES ● SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET ● SPECIAL 30kV PROBE FOR D.C. MEASUREMENT AVAILABLE AS AN OPTIONAL EXTRA.

PRICE £13 (p & p 80p) **PROBE £7·50 inc. of VAT**

For full details of the Chinaglia range contact:

CHINAGLIA (U.K.) LTD.
19 MULBERRY WALK, LONDON, S.W.3 Tel. 01-352 1897

EEMI ELECTRONIC ORGAN KITS

There are four excellent quality models for the do-it-yourself enthusiasts

★Portable—4 octave keyboard with 10 voices, 3 pitches— vibrato, **£145·29.** ★Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built-in amplifier and speaker **£250·93.** ★Console—2 × 4 octave keyboards and 13 note pedal board, 29 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, **£406·00.** ★Console—2 × 5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, 3 Couplers, etc., at **£572·55.**

V.A.T. please add 10%—show separately on order.

All components can be bought separately. Send 50p for 24-page catalogue which includes details of specialised components plus free vouchers worth 50p.
Also available-WIRELESS WORLD SOUND SYNTHESISER KITS complete with reprinted instructions.

ELVINS

ELECTRONIC MUSICAL INSTRUMENTS

Components suppliers to the music industry

12 Brett Road, Hackney, London, E.8
Tel. 01-986 8455

8 Putney Bridge Road, London, SW18 1HU
Tel. 01-870 4949

Trannies

All orders sent to our new retail shop at:
4 Bush House, Bush Fair,
HARLOW, ESSEX.
Tel. 37739. P/P 10p. Catalogue 10p.

ALL PRICES FULLY INCLUSIVE OF VAT

74 Series TTL

(National Semiconductors and I.T.T.)
LOW PRICES, HIGH QUALITY

100 plus less 10% on the 25+ column

Nos.	1+	25+
7400	20p	16p
7401	20p	18p
7402	20p	18p
7403	20p	18p
7404	21p	19p
7405	21p	19p
7406	54p	49p
7407	54p	48p
7408	29p	24p
7409	29p	24p
7410	20p	18p
7411	23p	21p
7412	40p	33p
7413	31p	29p
7416	49p	47p
7417	57p	53p
7420	20p	18p
7422	60p	58p
7423	60p	58p
7425	60p	53p
7426	35p	31p
7427	55p	51p
7428	35p	79p
7430	20p	18p
7432	42p	33p
7435	97p	91p
7437	77p	74p
7438	77p	74p
7440	20p	18p
7441	81p	78p
7442	81p	78p
7443	£1·40	£1·32
7444	£1·57	£1·52
7445	£2·31	£2·18
7446	£2·31	£2·18
7447	£1·48	£1·37
7448	£1·98	£1·81
7450	20p	16p
7451	20p	19p
7453	20p	19p
7454	20p	18p
7460	20p	18p
7470	33p	27p
7472	33p	30p
7473	46p	42p
7474	44p	40p
7475	63p	57p
7476	55p	51p
7480	£1·10	99p
7481	£1·37	£1·26
7482	£1·10	99p
7483	£1·32	£1·29
7484	£1·32	£1·21
7485	£2·75	£2·64
7486	49p	41p
7489	£4·95	£4·29
7490	82p	71p
7492	84p	65p
7493	82p	66p
7494	£1·04	93p
7495	£1·14	£1·03
7496	£1·25	£1·15
74100	£2·75	£2·58
74104	£1·18	£1·14
74105	£1·18	£1·14
74107	48p	46p
74110	67p	65p
74111	£1·52	£1·40
74118	£1·10	80p
74119	£1·64	£1·54
74121	47p	42p
74122	£1·70	£1·59
74123	£3·35	£3·28
74141	£1·10	99p
74145	£1·65	£1·48
74150	£3·30	£2·75
74151	£1·21	£1·15
74153	£1·32	£1·15
74154	£2·20	£1·87
74155	£1·65	£1·21
74156	£1·65	£1·21
74157	£1·54	£1·43
74160	£2·18	£2·05
74161	£2·18	£2·05
74162	£4·84	£4·54
74163	£4·84	£4·54
74164	£2·73	£2·63
74165	£2·73	£2·63
74166	£4·28	£3·94
74174	£2·78	£2·66
74175	£1·94	£1·81
74176	£1·99	£1·87
74177	£2·75	£2·64
74180	£2·75	£2·64
74181	£6·49	£6·05
74182	£2·16	£2·02
74184	£2·69	£2·42
74190	£3·08	£2·69
74191	£2·30	£2·24
74192	£2·53	£2·30
74193	£2·53	£2·30
74194	£3·27	£3·15
74195	£2·42	£2·30
74196	£2·18	£2·06
74197	£2·18	£2·06
74198	£6·65	£6·05
74199	£6·65	£6·05
74200	£26·40	£21·12

Linear Integrated Circuits

301	DIL	50p
301	TO99	55p
301	8 PIN DIL	46p
301A	DIL	69p
301A	TO99	69p
301A	8 PIN DIL	66p
307	DIL	69p
307	TO99	69p
307	8 PIN DIL	66p
308	TO99	6·45p
308A	TO99	6·40p
709c	DIL	35p
709c	TO99	31p
723c	DIL	99p
723c	TO99	95p
741c	8 PIN DIL	38p
741c	14 PIN DIL	39p
741c	TO99	41p
747c	DIL	46p
748c	DIL	39p
748c	TO99	41p

THE FERRANTI RADIO IC

ZN414 £1·32

Electrolytic Capacitors

4 VOLT

47µF	6½p
100µF	6½p
200µF	6½p
320µF	6½p
1000µF	13p
4700µF	29p

6·3 VOLT

33µF	6½p
68µF	6½p
150µF	6½p
470µF	11p
680µF	13p
1500µF	18p
2200µF	18p
3300µF	26p

10 VOLT

22µF	6½p
47µF	6½p
100µF	6½p
220µF	8p
330µF	10p
470µF	10p
1000µF	11p
1500µF	20p
2200µF	24p

16 VOLT

15µF	6½p
33µF	6½p
150µF	6½p
150µF	8p
220µF	9p
680µF	17p
1000µF	17p
1500µF	25p
2000µF	43p

25 VOLT

10µF	6½p
22µF	6½p
47µF	6½p
100µF	8p
150µF	8p
220µF	10p
470µF	13p
680µF	20p
1000µF	22p
2200µF	39p
5000µF	68p

40 VOLT

6·8µF	6½p
15µF	6½p
33µF	6½p

40 VOLT

47µF	6½p
68µF	10p
100µF	9p
220µF	11p
470µF	19p
680µF	25p
1000µF	25p
2200µF	44p

63 VOLT

1µF	6½p
2·2µF	6½p
4·7µF	6½p
6·8µF	6½p
10µF	6½p
22µF	6½p
68µF	10p
100µF	11p
150µF	18p
220µF	19p
330µF	22p
470µF	26p
1000µF	44p

VOLUME CONTROLS
Potentiometers

Carbon track 500Ω to 2·2MΩ. Log or Linear.
Single **13p.** Dual gang (stereo) **44p.**
Single type with D.P. switch **13p** extra.

CARBON SKELETON PRESETS

Small high quality type (linear only). All valves 100·5 meg ohms.
—1 watt **6p** each
—2·5 watt **6½p** each

THYRISTORS

P.I.V.	50	100	200
1 Amp	28p	35p	41p
3 Amps	44p	50p	60p
P.I.V.		300	400
1 Amp		44p	53p
3 Amps			60p

SLIDE SWITCH

SPST **11p** each. D.P.D.T. **13p** each.

MINIATURE NEON LAMPS

240V or 110V 1–4 **5p.** 5 plus **4½p** each.

Mullard Polyester Capacitors

C280 SERIES

250V P.C. mounting: 0·01µF, 0·015, 0·022 **3½p.** 0·033, 0·047, 0·068 **4p.** 0·1 **4½p.** 0·15, 0·22 **5½p.** 0·33 **7p.** 0·47 **9½p.** 0·68 **12p.** 1µF **14p.** 1·5µF **22p.** 2·2µF **27p.**

C296 SERIES

400V: 0·001µF, 0·0015, 0·0022, 0·0033, 0·0047 **3p.** 0·0068, 0·01, 0·015, 0·022, 0·033 **3½p.** 0·047, 0·068, 0·1 **4½p.** 0·15 **6½p.** 0·22 **8½p.** 0·33 **12p.** 0·47 **14½p.**
160V: 0·01µF, 0·015, 0·022, 0·033, 0·047, 0·068 **3½p.** 0·1 **4p.** 0·15 **4p.** 0·1 **4½p.** 0·15, 0·22 **5½p.** 0·33 **7p.** 0·47 **9½p.** 0·68 **12p.** 1µF **14½p.** 1·5µF **22p.** 2·2µF **24p.**

AMTRON KITS

We have been appointed stockist of Amtron high quality construction kits (20p P.&P. on all kits)

	£
UK65 Transistor tester	2·60
UK120 Hi-Fi amplifier 12W	5·20
UK110 Stereo amplifier 5 + 5W	11·07
UK115 Hi-Fi amplifier 8W	4·31
UK220 Signal injector	2·57
UK300 Four-channel radio control transmitter	6·55
UK310 Radio control receiver	3·28
UK325 "GCX2" channel splitting unit, 1,000 and 2,000Hz	7·86
UK330 "GCX2" channel splitting unit, 1,500 and 2,500Hz	7·86
UK415 Resistor box	8·69
UK425 Capacitor box	8·39
UK515 MW radio receiver	7·86
UK790 Capacitive burglar alarm	7·57

Many other kits available. Send for the free Amtron catalogue.

These kit prices include VAT

OUR NEW RETAIL SHOP IS NOW OPEN

Mon. to Sat. 7—5.30

Fri. late opening 6 p.m.

VEROBOARD

	0·1	0·15
2½ × 3¾	24p	19p
2½ × 5	27p	23p
3¾ × 3¾	27p	23p
3¾ × 5	31p	31p
17 × 2½	82p	63p
17 × 3¾	£1·10	87p
17 × 5 (Plain)		90p
Pin insertion tool	57p	57p
Spot face cutter	46p	46p
Pk 36 Pins	20p	20p

Resistors

¼ watt 5% carbon	1p
½ watt 5% carbon	1p
1 watt 10% carbon	2½p

range 10 ohms to 4·7 megohms.

½ watt m/o 2%	4p

range 10 ohms to 1 megohms.

MINITRON DIGITAL INDICATOR TYPE 3015F

Read 0·9 and decimals. ONLY **£1·65**

400mW ZENER DIODES

BZY88 Series 3·3 volt to 33 volt.

1–99	100 plus
7p	6p

£1 Bargain Packs

£1	10 Silicon *npn* power transistors (2N3055), tested/unmarked.
£1	30 Plastic FET'S, unmarked/untested. Similar to 2N3819.
£1	20 TO5 transistors *npn* 2 to 5A, untested/unmarked.
£1	20 TO18 transistors *pnp* like BC178, BC179, etc., untested/unmarked.
£1	30 Plastic 2N3055, unmarked/untested. TO220 case.
£1	10 General purpose, fully tested FET's.
£1	500 Carbon resistors, ¼, ½, 1, 2W.
£1	100 Electrolytic condensers.
£1	250 Ceramic Polystyrene, silver mica, etc., condensers.
£1	250 Polyester, Polycarbonate, paper, etc., condensers.
£1	25 Potentiometers, assorted.
£1	250 High Stab. 1%, 2%, 5%, resistors.
£1	1lb Assorted nuts, bolts, washers, spacers, etc.
£1	25 Assorted switches, rotary, lever, micro, toggle, etc.
£1	50 Presets Potentiometers.

Any 5 Packs **£4.** P. & P. 10p for *each* pack.

Transformers

Primary 200-220-240V.

			£	P./P.
MT111	12V	0·5A	1·11	16p
MT111/3	24V	0·25A	1·35	20p
MT71	12V	2A	1·76	22p
MT71/B	24V	1A	1·76	22p
MT18	12V	4A	2·47	36p
MT18/8	24V	2A	2·47	36p

30V transformers

Prim. 200–220–240V. Secondary voltage, 12, 15, 20, 24, 30V or 12–0–12V or 15–0–15V.

		£	P./P.
MT112	0·5A	1·32	22p
MT79	1A	1·80	36p
MT3	2A	2·96	36p
MT20	3A	3·30	42p
MT51	5A	4·84	49p

50V transformers

Prim. 200–220–240V. Secondary voltage, 19, 25, 33, 40, 50V or 25–0–25V.

		£	P./P.
MT102	0·5A	1·76	30p
MT103	1A	2·58	38p
MT105	3A	4·84	52p
MT106	4A	6·02	22p

60V transformers

Prim. 200–220–240V. Secondary voltage, 24, 30, 40, 48, 60V or 24–0–24V or 30–0–30V.

		£	P./P.
MT124AT	0·5A	1·76	38p
MT126AT	1A	2·47	34p
MT127	2	3·90	44p

Miniature transformers

Prim. 220V			£	P./P.
BT606	100mA	6–0–6V	0·98	15p
BT909	100mA	9–0–9V	0·98	15p
BT12012	100mA	12–0–12V	1·08	15p
BT24024	100mA	24–0–24V	1·95	15p

Transistors/ Diodes

AC107	16p
AC126	14p
AC127	13p
AC128	13p
AC142K	22p
AC141K	20p
AC176	15p
AC187	18p
AC187K	20p
AC188	18p
AC188K	20p
ACY17	24p
ACY18	21p
ACY19	25p
ACY20	22p
ACY21	23p
ACY22	18p
ACY30	68p
AD140	40p
AD142	44p
AD143	39p
AD149	38p
AD150	60p
AD161	38p
AD162	38p
AF114	18p
AF115	18p
AF116	18p
AF117	18p
AF118	92p
AF124	27p
AF139	39p
AF239	41p
AL100	77p
AL102	66p
AL103	55p
BC107	11p
BC108	11p
BC109	11p
BC113	15½p
BC116	16p
BC125	16p
BC126	25p
BC132	16p
BC134	16p
BC135	16p
BC137	16p
BC138	36p
BC142	33p
BC143	33p
BC144	30p
BC145	26p
BC147	9p
BC148	9p
BC149	9p
BC153	16p
BC154	17p
BC157	13p
BC158	12p
BC159	14p
BC167	13p
BC168	11p
BC169	11p
BC177	15p
BC179	15p
BC182L	10p
BC183L	11p
BC184L	11p
BC186	33p
BC212L	11p
BC213L	11p
BC214L	11p
BC258	9p
BC259	9p
BC267	14p
BC268	15p
BC300	40p
BC301	32p
BC302	30p
BC303	50p
BC304	40p
BCY70	17p
BCY71	37p
BCY72	17p
BD131	68p
RD132	90p
BD135	42p
RD136	50p
BD141	£1·87
BD142	50p
BF159	33p
BF173	29p
BF177	28p
BF178	29p
BF179	35p
BF194	15p
BF195	17p
BF244	27p
BF260	29p
BF329	18p
BF330	18p
BF390	37p
BFY84	28p
BFX85	35p
BFX86	22p
BFX87	28p
BFX88	26p
BFY50	21p
BFY51	17p
BFY52	17p
BFY64	39p
BFY90	72p
BSX20	19p
C407	22p
C426	33p
C428	31p
C480	17p
MP8111	35p
MP8112	42p
MP8113	35p
MP8121	33p
MF8122	44p
MP8123	50p
NKT211	28p
NKT212	28p
NKT214	25p
NKT217	55p
NKT261	23p
NKT271	20p
NKT274	20p
NKT275	25p
NKT403	71p
NKT405	83p
NKY603F	66p
NKT613G	33p
NKT674	26p
NKT677C	24p
NKT713	32p
NKT773	27p
OC19	55p
OC20	55p
OC23	49p
OC25	45p
OC28	50p
OC29	50p
OC35	50p
OC36	50p
OC44	14p
OC45	14p
OC70	23p
OC71	14p
OC72	14p
OC81	14p
OC83	22p
OC84	28p
TIP29A	53p
TIP30A	64p
TIP31A	64p
TIP32A	78p
TIP33	£1·05
TIP34A	£1·54
TIP35A	£2·53
TIP36A	£3·19
TIP41A	79p
TIP42A	91p
2N706	13p
2N930	23p
2N1131	22p
2N1132	28p
2N1613	22p
2N1711	26p
2N2904	40p
2N2904A	44p
2N2905	46p
2N2924	18p
2N2926	10p
2N3053	26p
2N3054	55p
2N3055	52p
2N3702	11p
2N3703	11p
2N3704	11p
2N3705	11p
2N3706	11p
2N3707	11p
2N3708	11p
2N3709	11p
2N3710	11p
2N3711	9p
2N3794	17p
2N3819	28p
40361	50p
40362	50p
40636	50p

Diodes & Rectifiers

1N914	8p
1N916	8p
1N4148	8p
1844	10p
1N4007	22p
1S113	17p
RA100	16p
BA102	25p
BA115	8p
BA144	14p
BA145	22p
BA154	14p
BAX13	14p
BAX16	14p
BAY18	19p
BAY31	9p
BY100	19p
BY126	16p
BY127	19p
BYX10	24p
OA5	19p
OA10	24p
OA47	9p
OA70	8p
OA73	11p
OA79	8p
OA81	9p
OA85	11p
OA90	8p
OA81	8p
OA95	8p
OA200	11p

NEW VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH.

74 Series TTL

INTERNATIONALLY
KNOWN BRANDS
Ist. GRADE DEVICES AT NEW
ROCK BOTTOM PRICES

SN7400	**18p**	SN7447	**£1·10**
SN7401	**18p**	SN7473	**41p**
SN7402	**18p**	SN7474	**41p**
SN7404	**18p**	SN7475	**50p**
SN7408	**20p**	SN7476	**44p**
SN7410	**18p**	SN7490	**82p**
SN7413	**31p**	SN7492	**84p**
SN7420	**18p**	SN7493	**82p**
SN7430	**18p**	SN74100	**£2·37**
SN7441	**81p**	SN74121	**50p**
SN7442	**81p**	SN74141	**£1·10**
		SN74192	**£2·15**

BRIDGE RECTIFIERS

P.I.V.	1 amp	R.M.S.	2 amp
100V	**20p**	50V	**35p**
200V	**22p**	100V	**40p**
600V	**25p**	200V	**45p**
1000V	**38p**	400V	**50p**

RECTIFIERS

P.I.V.		1 amp		3 amp
50	1N4001	**6½p**	1N5400	**15½p**
100	1N4002	**7½p**	1N5401	**16½p**
200	1N4003	**9p**	1N5402	**17½p**
400	1N4004	**9p**	1N5404	**22p**
600	1N4005	**11p**	1N5406	**26½p**
800	1N4006	**13½p**	1N5407	**30p**
1000	1N4007	**16½p**	1N5408	**33p**

BY100	**16½p**	BY133	**23p**
BY103	**22p**	BY164	**55p**
BY105	**16½p**	BY176	**£1·65**
BY126	**16p**	BY182	**£1·65**
BY127	**16½p**	BY250	**25½p**

PRICE BARRIER SLASHED

LED LITRONIX DL707 SERIES
READOUTS

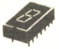

0·3in high characters
14 pin Dil
Ref. LED 1.
ALSO +1 REF. LED1A

£1·99 + 20p VAT = £2·19

OR
FILAMENT INDICATOR
MINITRON **3015** F & G

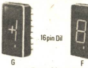

at ***BREAKTHROUGH PRICE £1·49***

Cheapest Opto yet *GaAsp* LED's

RED
LED 2. 0·125″ 26p
LED 3. 0·175″ 17p

GREEN
LED 4. 0·125″ 69p
LED 5. 0·175″ 75p

Remember **Vat Inclusive Prices**

Veroboard

	Copperclad 0·1in	Plain 0·15in	0·15in	Extra P & P
2½in × 1in	**7p**	**7p**	—	—
2½in × 3¾in	**24p**	**18p**	**12p**	—
2½in × 5in	**26½p**	**23p**	**13p**	—
3¾in × 3¾in	**26½p**	**23p**	—	—
3¾in × 5in	**30p**	**30p**	**22p**	—
17in × 2½in	**82p**	**63p**	**45p**	10p
17in × 3¾in	**£1·10**	**86p**	**60p**	10p
17in × 5in	—	—	**90p**	10p

Dip Breadboard **115p**
Verostrip **28p**
Spot Face Cutter **44p**
Pin Insertion tool **55p**
Terminal Pins (packs of 50), state size... **55p**

DIGITAL CLOCK on a chip

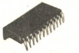

just imagine, one MOS LSI I.C. eliminating 15 MSI I.C.s and numerous other components. Either

12 or 24 hour, 4 or 6 digit 50 or 60Hz operation leading zero supression single voltage supply similar to DIGITRONIC in P.W. March 1973.
Only **£7·99**

With 4 LED's £16·59
With 6 LED's £20·75

I.C. SOCKETS

DUAL IN LINE: 8 pin **13½p**, 14 pin **15½p**, 16 pin **17½p**, 24 pin **26½p**, | 28 pin **39½p**, , 36 pin **41p**, 40 pin **44p**.
ZIG ZAG: 14 pin **19½p**, 16 pin **21p**.

HEAT SINKS

TV2 for T0-66 15p. 5F for T0-5
TV3 for T0-3 16p. 18F for T0-18

5½p.

TV4 for T0-126
TV5 for T0-220

DIP10/2 for SL403D
DIP14/5 for EA1,000

14p

16p

10DN400 4 4Y-1 4

46p

35p

CHROMASONIC electronics

RESISTORS

Rating	Type	Tolerance		Range	Price Each
⅛/¼ watt	Carbon Film	±5%	E12 Series	5Ω to 330KΩ	**1½p**
½ watt	Metal Oxide Film	±2%	E12 Series	10Ω to 1MΩ	**4½p**
½ watt	"Cermet" Thick Film	±2%	E12 Series	56Ω to 150KΩ	**8p**
½ watt	Carbon Film	±5%	E24 Series	10Ω to 10MΩ	**1½p**
½ watt	Carbon Composition	±0·5Ω	(2·2Ω) 2·7Ω: 3·3Ω: 3·9Ω: 4·7Ω:		**4½p**
1 watt	Carbon Composition	±10%	(5·6Ω) 6·8Ω: 8·2Ω		**5½p**
1 watt	Carbon Film	±5%	E12 Series	10Ω to 10MΩ	**3p**
2 watt	Carbon Film	±5%	E12 Series	10Ω to 10MΩ	**6p**
2½ watt	Wire Wound	±10%	E12 Series	0·22Ω to 0·47Ω	**10p**
2½ watt	Wire Wound	±5%	E12 Series	1Ω to 270Ω	**10p**
5 watt	Wire Wound	±5%	~ E12 Series	0·5Ω to 8·2KΩ	**10p**
10 watt	Wire Wound			0·5Ω to 6·8KΩ	**11p**
10 watt	Wire Wound	±5%	10KΩ: 15KΩ: 20KΩ: 25KΩ		**17p**
15 watt	Wire Wound			10Ω to 6·8KΩ	**13½p**

DISCOUNTS: 10% on any 100 or more mixed value or wattage, 25% on any 100 or more same value and same wattage.

TRANSISTORS and DIODES

AC107	**16p**	ASY26	**33p**	BC328	**24½p**	BF180	**33p**	BSY95A	**14p**	TIP41A	**81p**								
AC126	**13p**	BC107	**11p**	BCY70	**17p**	BF181	**33p**	BU105	**£1·75**	TIP42A	**99p**								
AC127	**13p**	BC108	**11p**	BCY72	**17p**	BF184	**28p**	BU105 02	**£1·92**	TIS43	**36½p**								
AC128	**13p**	BC109	**11p**	BCZ10	**28p**	BF185	**28p**	D13V	**53p**	TIS73	**£2·10**								
AC176	**15p**	BC114	**15½p**	BCZ11	**28p**	BF194	**15p**	MJ4000	**£1·49**	TIS91	**33p**	2N3054	**51p**	2N4289	**19p**	AAZ13	**11p**	BAX13	**9p**
AC187	**22p**	BC117	**22p**	BD115	**74p**	BF195	**17p**	MJ4010	**£1·49**	2N697	**16½p**	2N3055	**52p**	2N4441	**87p**	BA100	**10p**	BAX16	**10p**
AC187K	**20p**	BC147	**10p**	BD124	**82p**	BF196	**16p**	MJE340	**52p**	2N706	**13p**	2N3391A	**29p**	2N4442	**£1·06**	BA102	**27½p**	BAY38	**41p**
AC188	**22p**	BC148	**10p**	BD131	**55p**	BF197	**16p**	MJE2955	**£1·82**	2N708	**16½p**	2N3566	**18p**	2N4443	**£1·45**	BA110	**45p**	BB105	**42p**
AC188K	**25p**	BC149	**10p**	BD132	**66p**	BF200	**32p**	MJE3055	**92p**	2N914	**24½p**	2N3638	**20p**	2N4444	**£2·09**	BA111	**55p**	BB141	**99p**
ACY19	**25p**	BC157	**13p**	BD131/2	**£1·19**	BF200	**27½p**	MPF102	**27½p**	2N1302	**20p**	2N3702	**13p**	2N4871	**60p**	BA112	**99p**	BB142	**82p**
ACY20	**22p**	BC158	**12p**	BD133	**72p**	BF244B	**27p**	MPF103	**41p**	2N1303	**24p**	2N3703	**12p**	2N5129	**16½p**	BA114	**9p**	OA5	**99p**
AD140	**49p**	BC159	**14p**	BD135	**42p**	BF262	**25p**	MPF104	**45p**	2N1304	**24p**	2N3704	**13p**	2N5172	**11p**	BA115	**19p**	OA10	**94p**
AD149	**49p**	BC168B	**11p**	BD136	**44p**	BF263	**25p**	MPF105	**45p**	2N1305	**24p**	2N3705	**12½p**	2N5459	**69p**	BA116	**9p**	OA47	**11p**
AD161	**29p**	BC189	**12p**	BD137	**50p**	BF272	**£1·21**	MPF106	**49½p**	2N1306	**24p**	2N3706	**14p**	2N5777	**47p**	BA128	**11p**	OA79	**10p**
AD162	**29p**	BC171	**20p**	BD138	**55p**	BF390	**37p**	OC28	**50p**	2N1307	**27½p**	2N3707	**12p**	2N6076	**16½p**	BA129	**23p**	OA81	**8p**
AD161/2 PR	**59p**	BC172	**17½p**	BD139	**61p**	BFS28	**£1·01**	OC35	**50p**	2N1308	**35p**	2N3708	**10p**	3N140	**£1·01**	BA143U	**75p**	OA85	**10p**
AF114	**17p**	BC174B	**35p**	BD140	**66p**	BFW10	**66p**	OC36	**50p**	2N1309	**35p**	2N3709	**10p**	3N141	**89p**	BA143V	**67p**	OA90	**8p**
AF115	**17p**	BC177	**22p**	BD201	**£1·55**	BFW11	**67p**	OC44	**14p**	2N1613	**22p**	2N3710	**11p**	3N152	**101p**	BA144	**20p**	OA91	**8p**
AF116	**17p**	BC178	**22p**	BD202	**£1·37**	BFW87	**38p**	OC45	**14p**	2N1711	**26p**	2N3711	**11p**	3N153	**89p**	BA145	**22p**	OA95	**9p**
AF117	**17p**	BC179	**24p**	BD203	**£1·55**	BFX29	**43p**	OC71	**14p**	2N1893	**52½p**	2N3771	**£1·82**	40360	**51p**	BA148	**22p**	OA200	**11p**
AF118	**92p**	BC182L	**11p**	BD204	**£1·37**	BFX30	**37½p**	OC72	**14p**	2N2160	**£1·54**	2N3772	**£2·75**	40361	**50p**	BA154	**20p**	OA202	**12p**
AF124	**27p**	BC183L	**12p**	BF109	**75p**	BFX88	**26p**	OC75	**15p**	2N2219	**41p**	2N3773	**£2·20**	40362	**50p**	BA155	**15½p**	OA210	**19½p**
AF125	**27p**	BC184L	**12p**	BF115	**25p**	BFY50	**22p**	OC81	**14p**	2N2646	**55p**	2N3819	**28p**	40408	**55p**	BA156	**16½p**	OA211	**30p**
AF126	**27p**	BC187	**27½p**	BF160	**25½p**	BFY51	**22p**	OC83	**25p**	2N2905	**46p**	2N3823	**99p**	40430	**£1·39**	BA182	**26½p**	IN914	**8p**
AF127	**27p**	BC212L	**12p**	BF167	**24p**	BFY52	**22p**	OC140	**22p**	2N2924	**16p**	2N3903	**16½p**	40432	**£2·17**	BA220	**7p**	IN916	**10p**
AF139	**35p**	BC213L	**13p**	BF173	**24p**	BR100	**43p**	OC170	**28p**	2N2925	**16p**	2N3904	**19p**	40673	**55p**	BA221	**7p**	IN4148	**5½p**
AF172	**25p**	BC2144	**11p**	BF177	**28p**	BRY39	**44p**	OC171	**33p**	2N2926 all	**10p**	2N3905	**23p**	AA119	**10p**	BA222	**7½p**		
AF179	**71½p**	BC268	**15p**	BF178	**29p**	BSX20	**18p**	TIC44	**46p**	2N3053	**19p**	2N3906	**25p**	AA120	**10p**	BAV10	**11p**		
AF239	**41p**	BC327	**26½p**	BF179	**33p**	BSX21	**22p**	TIC226D	**£1·97**			2N4058	**13½p**	AA129	**10p**	BAW62	**10p**		

CAPACITORS

MULLARD C333, 629 and 630 series —Ceramic Plate. E12 series from 1·8pF to 0·002μF, **5½p.**

CERAMIC DISC—LOW VOLTAGE— 0·01μF, 0·022μF, 0·047μF, **5½p;** 0·1μF, 0·22μF, **6½p.**

POLYSTYRENE (160V)—From 10pF to 0·01μF in multiples of 10pF; 15pF; 22pF; 33pF; 47pF and 68pF, **4½p.**

MYLAR PLATE (100V)—1000 PF, 2000pF, 5000pF, **2½p,** 0·01μF, 0·02μF, 0·04μF, 0·05μF, **3½p;** 0·068μF, 0·1μF, **5p;** 0·2μF, **6½p.**

MULLARD C280 (250V POLYESTER) —0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, **3½p;** 0·068μF, **4p;** 0·1μF, 0·15μF, **4½p;** 0·22μF, **5½p;** 0·33μF, **7p;** 0·47μF, **9p;** 0·68μF, **12p;** 1·0μF, **14½p;** 1·5μF, **22p;** 2·2μF, **26½p.**

new *stabilised* POWER PACK/CONVERTER

Switched 3, 6, 7½ or 9 volts.
Up to 400mA Output

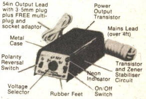

Our Price **£3·99** + P. & P. 16p.
Unstabilised Version of above .. **£2·99**
Other Eliminators (unstabilised)*
6 volts at up to 50mA .. .. **£1·65**
9 volts at up to 50mA .. .. **£1·65**
9 volts (miniature) up to 50mA .. **£2·09**
6 + 6 volts at up to 50mA .. .. **£2·75**
9 + 9 volts at up to 50mA .. .. **£2·75**
7½ volts for Cassette Players (small) **£2·20**
3, 4½, 6, 7½, 9, 12 volts up to ½A .. **£3·75**
Fully Stabilised* Car Battery Converter, giving switched outputs of 6, 7½ or 9 volts .. .. **£5·49**
P. & P. on all models 16p.

ZENERS

All 5% tolerance

BZY88, 400mW, 3·3V to 33V	**11p**
1ZS, 1W, 3·3V to 100V	**18p**
BZX70, 2·5W, 7·5V to 75V	**27p**

VAT INVOICES ON REQUEST

UNLESS SHOWN OTHERWISE P&P ON U.K. ORDERS IS 8p. OVERSEAS ORDERS AT COST

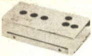

Mullard LP1186

Varactor diode tuned F.M. tuning heart, **£4·15,** as described in P.E. May 1973.
LP1185 matching I.F. strip, **£4·85.**

THE TEXAN

20 + 20 Watt Integrated Stereo Amplifier Kit. Superb state-of-the-art design by engineers of Texas Instruments, **£31·35** + P. & P. 49p.

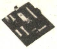

SGS EA1000

3 watt amplifier module. Price including handbook and FREE heatsink.
Our price £2·49.
Quantity discounts.

A1005S

F.M. tuner chassis, fully transistorised. 9 Volt positive earth operation.
Our Price £6·35.

A1018

F.M. tuner, similar to A1005S but in oiled walnut cabinet, etc.
Our Price £9·38.

A1005MS

Multiplex Stereo Decoder, fully built and aligned, to match A1005S.
Our Price £5·95.

AUDIO I.C'S

Audio I.C. Leaflet No. 12. FREE (only with I.C.'s—10p separately.

Pre-Amplifiers

Dual, MC1303L **£1·89**
Low Noise Dual, MC1339P **£1·29**

Amplifiers

250mW, MFC4000A **49p**
1 watt, TAA300 **£1·79**
2 watt, LM380 **£1·40**
3 watt, SL414 **£1·76**
5 watt, TBA800 £1·59
7 watt, TBA8105 **£1·70**
15 watt, BHA0002 **£3·95**
35 watt driver, NE540L **£1·32**

NEW SL414 pin for pin = SL403D 3 watt **£1·76**

3½ decade DVM

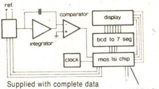

- Maximum Display + or – 1·999V
- Minimum Display + or – 1mV
- Can be scaled up to read 1.999V
- Automatic Polarity Detection
- Dual Ramp Integration
- Automatic Overange Indication
- Up to 50 readings per second
- Chopper Output provided.

Supplied with complete data
All this on a single 16 pin DIL packed MOS LSI Integrated Circuit

A State-of-the-Art Digital Voltmeter I.C. for only £7·79

Coil·less Phase·Locked Loop
I.C. Stereo Decoder

Motorola MC1310, supplied complete with our FREE leaflet No. 11
Our Price £3.05

MC1312 decodes CBS. SQ. Free leaflet No. 11 gives full circuit and details. ***Our Price £6·49***

QUADRISONICS

Inc. all parts for decoder, inc. Veroboard, V.A.T., P. & P. (Leaflet alone 10p.)

Linears

	8pin Dip	TO99	14pin Dil
709	34p	40p	35p
710	35p	40p	39p
711	—	45p	39p
723	—	96p	95p
741	42p	45p	43p
747	—	—	92p
748	42p	45p	43p

CA3046	95p	MVR5V(L0005)	£1·65
CA3075	£1·65	MVR12V(L005)	£1·65
CA3082	£1·65	MVR15V(L037)	£1·65
LM101H	£1·99	NE555	85p
LM201H	£1·15	NE560B	£4·92
LM301	£1·05	NE561B	£4·92
LM307N	66p	NE562B	£4·92
LM308N	£1·45	NE565	£2·80
LM309K	£2·69	NE566	£2·75
LM3900	77p	NE567	£2·80
MC1330	88p	SG3402N	£3·08
MC1350	83p	SL440	£2·89
MC1351	£1·10	TAA263	99p
MC1352	£1·10	TAA293	99p
MC1357	£1·59	TAA310	£1·37
MC1358	£1·69	TAA320	99p
MC1456G	£1·75	TAA350	£2·54
MC1458CPI	£2·42	TAA370	£5·15
MC1495	£5·65	TAA550	81p
MC1496N	£1·49	TAA570	£1·65
MC3401	77p	TAA700	£4·49
MFC4010A	61p	TAD100	£1·55
MFC4060	78p	TAD110	£1·65
MFC6030A	83p	TBA651	£2·00
MFC6040	£1·10	ULN2111A	£1·59

the component people

Dept. 2.
56, Fortis Green Road, London, N10 3HN.
telephone: 883 3705

INDUCTORS

MULLARD block filter LP1175 as used with TAD100 now only **£1·49**

R.F. CHOKES, 0·1µH to 19mH. For full details ask for List No. 5. P.&P. 5p.

DENCO COILS

Transistor Range: Series 1T to 5T inclusive Blue, Yellow, Red and White all **44p** each.
I.F. Transformers: IFT13, 14, 16 and 17, **55p** each; IFT 15, **76p;** IFT18, **73p.**

Dual Purpose Range: Series 1 to 7 inc. Blue, Yellow, Red and White, **44p** each.
1 to 5 Green. List No. 5 gives full details.
Ferrite Aerials: Medium and Long—state 300pF or 500pF tuning, **87p** each

Tuning Gangs

Type C804

5pF	**61p**	50pF	**66p**
10pF	**61p**	60pF	**79p**
15pF	**61p**	75pF	**79p**
20pF	**66p**	100pF	**75p**
25pF	**61p**		

Type 0

365pF **80p**
365 + 365pF **96p**

Type 00

208 + 176pF with screen and trimmers. **99p**

P. & P. all types 10p

NEW FERRANTI RANGE

ZN414

The Radio I.C. in a TO18 can. Supplied with our data leaflet No. 10. Giving circuits and component information. (Leaflet alone 10p.)

Our Price £1.32

BFS59	15p	ZTX302	17p	ZTX450	17p	ZS121	10p	ZS272	18p
BFS60	20p	ZTX303	14p	ZTX451	17p	ZS122	13p	ZS274	19p
BFS61	20p	ZTX304	21p	ZTX500	12p	ZS123	16p	ZS276	26p
BFS96	15p	ZTX310	9p	ZTX501	13p	ZS124	18p	ZS278	37p
BFS97	23p	ZTX311	10p	ZTX502	17p	ZS140	25p		
BFS98	20p	ZTX312	10p	ZTX503	14p	ZS141	43p		
		ZTX313	11p	ZTX504	43p	ZS142	33p		
ZTX107	10p	ZTX314	13p	ZTX510	17p	ZS170	10p		
ZTX108	10p	ZTX320	31p	ZTX530	21p	ZS171	13p		
ZTX109	15p	ZTX330	15p	ZTX531	22p	ZS172	16p		
ZTX212	14p	ZTX331	16p	ZTX550	17p	ZS174	17p		
ZTX213	14p	ZTX341	22p	ZTX551	17p	ZS176	23p		
ZTX214	15p	ZTX382	13p			ZS178	38p		
ZTX300	12p	ZTX383	15p	**DIODES**		ZS270	11p		
ZTX301	13p	ZTX384	18p	ZS120	8p	ZS271	16p		

KSO30A Zener Series as BZY88 Series **11p** each.

ELECTROLYTICS

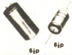

µF	4V	6·3V	10V	16V	25V	40V	63V	100V	160V	450V
1							6½p		8½p	15p
1·5							6½p			
2·2							6½p		8½p	
3·3							6½p			
4·7							6½p		8½p	17p (4µF)
6·8						6½p	6½p	8½p		
8										21p
10					6½p		6½p	8½p		
15				6½p		6½p	6½p			24p (16µF)
22			6½p		6½p		6½p	11p		
33		6½p		6½p		6½p				33p (32µF)
47	6½p		6½p	6½p	6½p	6½p	8p			25p (50µF)
68		6½p		6½p			11p			(350V)
100	6½p		6½p		6½p	8p	14p	25p		
150		6½p		6½p	8p	11p	14p			
220	6½p		6½p	8p	11p	14p	19p	31p		
330	6½p		8p	11p			25p	44p		
470		8p	11p		14p	20p	26p	47p		
680		10p		14p	20p	25p		59p		
1000	13p		14p	19p	22p	25p	44p	79p		
1500		18p	19p	25p						
2200		18p	24p		39p	44p	79p	149p		
3300		26p								
4700	25p			44p	68p	79p	149p	252p		
6800				75p						

Potentiometers

5kΩ 250kΩ
10kΩ 500kΩ
25kΩ 1MΩ
50kΩ 2MΩ
100kΩ

Log or lin less switch (and 1kΩ lin)	13p
Log or lin with switch	26p
Dual less switch	44p
Dual with switch 10kΩ, 100kΩ and 1MΩ, log only	57p
10kΩ log + 10kΩ antilog less switch	44p

10kΩ Single
25kΩ **40p**
50kΩ Dual
100kΩ **60p**

New Silver and Black Knob, **16½p**

Presets

Vertical or Horizontal

0·1 watt **5½p** 0·25 watt **7p**

100Ω	1kΩ	10kΩ	100kΩ	1MΩ
250Ω	2·5kΩ	25kΩ	250kΩ	2·5MΩ
500Ω	5kΩ	50kΩ	500kΩ	5MΩ

Cermet Type to 1MΩ only. **41p.**

VDR's & Thermistors

A15B	98p	GL23	£1·21
CZ1	16½p	R53	£1·49
CZ4	18p	R54	£1·61
CZ13A	18p	VA1005	16p
CZ19	18p	VA1026	16p
E298CD A258	13p	VA1033	16p
E298ED A258	13p	VA1034	16p
E298ED A260	13p	VA1039	16p
E298ED A262	13p	VA1040	16p
E298ED A265	13p	VA1053	16p
E298ED P268	13p	VA1055S	16p
E298ZZ 05	13p	VA1056S	16p
E298ZZ 06	13p	VA1066S	17p
E299DD P336	14p	VA1067S	19p
E299DD P338	14p	VA1077	19p
E299DD P342	14P	VA1098	21p
E299DD P348	14p	VA1104	31p
GL16	£1·21	VA1107	29p

Other types obtainable upon application

GENESIS

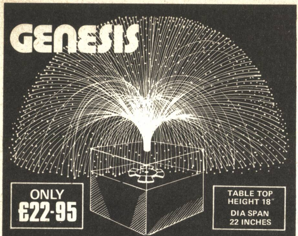

At the head of our fibre optic kingdom stands the unique genesis. This fantastic model incorporates the largest mares tail you can buy.
Now combined with the most sensational kinetic light base ever designed in this field. This lamp is unique in the way that the base is opaquely translucent. The tinted upper section allows one to see a slowly rotating eight coloured sculptured wheel, that seems to be floating on a blue haze, that radiates a warm mystic glow.
Thousands of optical fibres energized with colour. Fibre tips flash like stars, bright with all the changing colours of the rainbow. Available in blue or green. M.M. Discount price £22.95 inc p.p. and VAT.

CASCADE Height 18".
Cascade, the fibre optic that's also a beautiful corner light, M.M. Discount price £16.65 inc p.p. and VAT.

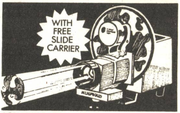

AQUARIUS 100
A star for home parties, this budget priced 100-watt projector will transform your room into a swirling image of continuously changing liquid colour of reds, blues, yellows and greens.
This machine is supplied with one six inch liquid wheel and includes lamp and lead. Complete with free 2 x 2 slide projection carrier.
M & M discount price £19.95 post free.

LITTLE GEM
Little Gem, complete with the smaller mares tail, (8mm approx, 18" x 10" high, overall height from table approx 14"). With a single white light display, housed in a red translucent base, cowled with a special moulded three dimensional filter that throws light in array. It's amazing, we have completely shattered the style of conventional optics with the fabulous little gem. ONLY £10 inc post and VAT.

OILWHEEL PROJECTORS
Multi-coloured,
For projecting psychedelic colours 6" or 4" diameter
Ideal for fibre optics
6" oil wheel £5.00 + p.p. 15p.
4" (suitable for optics) £2.65 + p.p. 10p.

D.I.Y. SECTION

THE SENSATIONAL MARES TAIL
Three sizes to choose from:
18mm ferrule, 11" high x 22" dia.
7,500 fibres, £10.50 +20p p.p.
12mm ferrule, 10" high x 19" dia.
4,800 fibres £7.85 +12p p.p.
8mm ferrule, 10" high x 18" dia.
2,900 fibres £4.95 +10p p.p.
Complete instructions supplied.

Display bunching of various types of fibres at low cost. TYPE A 1320. Fibres contained in a tough flexible sheath. Makes delightful displays. M.M. Discount Price 40p per ft. £1.10 per yd. +5p p.p.
TYPE B. Light guides comprising of 64 fibres. Each fibre .010 inch diameter in a flexible sheath 1/8 inch. 45p per ft. £1.28 per yd +5p p.p.
TYPE C. Monofilament .040 dia, single strand flexible plastic that enables heat bending for combined use with type A or type B. 22p per ft. min order 3ft 66p +5p p.p.

SLOW SPEED MAINS MOTOR
to rotate oil wheel and static wheel 70p inc p.p.

STATIC COLOUR DISC
M.M. Discount price £1.40 inc post. Specially made for optics. Complete with metal boss. To fit motor. 4" dia, seven prominent colours contained in separate sections.

Bulb and batton kit plus 6ft of flex
75p inc post and VAT.

Terms: C.W.O. cheques/po's
C.O.D. please send 50 pence when ordering

BUY WITH CONFIDENCE FROM A FIRM WITH A NATIONAL REPUTATION

MIDLAND MATERIALS

OPTICS, 7 QUEENS STREET, WELLINGBOROUGH, NORTHANTS. TEL: 79831.

LONDON COLLEGE OF FURNITURE

41 Commercial Road,
London E1 1LA

Department of Musical Instrument Technology

Full Time Courses Certificate Courses in:

Piano Tuning, Construction, Repair and Maintenance
Early Stringed Keyboard Instrument Construction: Harpsichord, Clavichords
Fretted Instruments: guitars, lutes, viols, etc.
Violin Making: violins, violas and cellos
Electronic Musical Instruments.

Part Time Courses Block Release or Day Release

Stringed Keyboard Instrument Design and Manufacture
Violin Making
Early Fretted Instrument Making
Piano Tuning and Maintenance
Woodwind Instrument Maintenance

Further information from:
Senior Administrative Officer
Tel: 01-247 1953

ilea

KEEP WARM AT A COOL PRICE.

Slash central heating costs with AMKIT.

If you can put in electric wiring, you can install Amkit. The unique nylon pipe hot water central heating system, that you install yourself in hours.

Look at these advantages:
- No soldering
- No 'T' junctions
- No special equipment
- No leaks, no lagging, no corrosion
- No structural upheaval

Just reliable, effective central heating (Guaranteed 25 years) at a saving of between £150 & £250. This famous system has been successfully marketed since 1968.

Clip the coupon, and we'll tell you more.

To Autocon Manufacturing Co.
Spring House, 10, Spring Place, London, NW5, 3BH
Please send your brochure telling me all about Amkit.
Name
Address

PE7 AMC

or see for yourself at: THE AMKIT D.I.Y. CENTRE,
15, Procter St., London, W.C.1. (opp Holborn Undgnd).
Open Mon-Fri 9.30 am-5-30 pm. Sat 9 am-1 p.m.

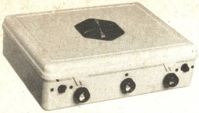

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN—PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio.
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

TOTAL BUILDING COSTS

£7·23 (+10% VAT 72p) **P.P. & INS. 44p (Overseas P.P. £1·85p)**

Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 3½″ Loudspeaker ● Earpiece ● Mica Baseboard
- 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs
- Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeving, etc.
- Parts price list and plans 50p (free with parts)

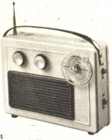

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9½in × 7in × 2¾in approx. Parts price list and plans **30p** (FREE with parts).

TOTAL BUILDING COSTS £6·95 (+10% VAT 69p) **P.P. & INS. 44p (OVERSEAS P. & P. £1·85)**

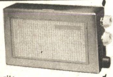

POCKET FIVE

3 Tunable wavebands. MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive Black and Gold Case. Size 5½in × 1½in × 3½in approx. Plans and parts price list **15p** (FREE with parts).

Total Building Costs £2·28 (+10% VAT 22p) **P.P. & Ins. 26p (Overseas P. P. £1·25)**

TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list **15p** (FREE with parts).

Total Building Costs £2·50 P.P. & Ins. 26p (+10% VAT 25p) **(Overseas P. & P. £1·25)**

NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes. MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9in × 5½in × 2¾in approx. Parts price list and plans **15p** (FREE with parts).

TOTAL BUILDING COSTS £2·73 (+10% VAT 27p) **P.P. & INS. 30p (OVERSEAS P. & P. £1·25)**

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3″ loudspeaker, etc., MW/LW coverage. Push Pull Output. Parts price list and plans **15p** (FREE with parts.)

TOTAL BUILDING COSTS £3·60 (+10% VAT 36p) **P.P. & INS. 30p (OVERSEAS P. & P. £1·25)**

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3″ Loudspeaker. Parts price list and easy build plans, **20p.** Free with parts.

TOTAL BUILDING COSTS £4·08 (+10% VAT 40p) **P.P. & INS. 31p (OVERSEAS P. & P. £1·85p)**

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7. TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4″ 2 watt Ferrite Magnet loudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in × 7in × 4in approx. Easy to follow instructions and diagrams. Parts price list and plans **25p** (FREE with parts).

TOTAL BUILDING COSTS £6·98 (+10% VAT 69p) **P.P. & INS. 47p (OVERSEAS P. & P. £1·85)**

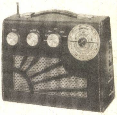

ROAMER TEN

WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND

Latest 4″ 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in × 7in × 4in.

Easy to follow instructions and diagrams. Parts price list and plans **30p** (FREE with parts).

TOTAL BUILDING COSTS £8·50 (+10% VAT 85p) **P.P. & INS. 52p (OVERSEAS P. & P. £1·85)**

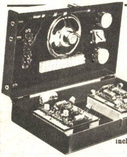

EDU-KIT

Build Radios, Amplifiers, etc., from easy stage diagrams.

Five units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone 3″ moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three ½in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans **25p** (FREE with parts).

TOTAL BUILDING COSTS £5·50 (+10% VAT 55p) **P.P. & INS. 33p (OVERSEAS P. & P. £1·85)**

TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW. and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in × 5½in × 2¾in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker Parts. price list and plans **25p** (FREE with parts).

TOTAL BUILDING COSTS £4·48 (+10% VAT 44p) **P.P. & INS. 33p (OVERSEAS P. & P. £1·25)**

ROAMER SIX

CASE AND LOOKS AS TRANS EIGHT 6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in × 5½in × 2¾in approx. Plans and parts price list **25p** (FREE with parts).

TOTAL BUILDING COSTS £3·98 (+10% VAT 39p) **P.P. & IN. 31p (OVERSEAS P. & P. £1·85)**

RADIO EXCHANGE LTD

*Callers side entrance "Lavells" shop
*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.

To **RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 ISA**
Tel. 0234 52367 Reg. No. 788372

I enclose £ ______________ for ______________________________

Name ____

Address ____

P.E.61

NOW! A FAST *EASY* WAY TO LEARN BASIC RADIO & ELECTRONICS

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified **HOME STUDY** method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

RADIO AND TELEVISION

General Radio and TV Engineering
Radio servicing, maintenance and repairs
Television Maintenance and Servicing
Colour TV
Practical TV
Electronic Engineering
Radar Technology
Practical Radio and Electronics (Technatron)
Applied Electronics
Radio Amateurs
City and Guilds Radio and TV Electrical Mech.
Elementary Electronics Course for Radio
Elementary Physics Course for Radio

BRITISH SCHOOL OF ENGINEERING TECHNOLOGY

Dept. BPE 70, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

NAME.. AGE .... BPE 70
(block capitals)
ADDRESS ....

....

SUBJECT OF INTEREST ....

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

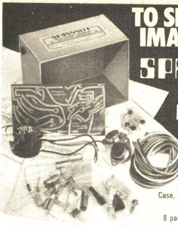

TO SPARK YOUR IMAGINATION! the SPARKRITE Electronic Ignition Kit only £9·35

Kit comprises EVERYTHING:
Case, cables, coil connectors,
Silicon grease,
8 page instruction leaflet.

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

• Sustained peak performance. • Up to 20% fuel saving. • Instant all-weather starting. Faster acceleration, higher top speed. • Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: **£9·35** inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available **£11·55** inc. V.A.T. and postage.

GUARANTEED 5 YEARS

ORDER NOW—SEND P.O./Cheque direct to:
ELECTRONICS DESIGN ASSOCIATES, Dept. PE3
82 Bath St., Walsall WS1 3DE. Phone: 33652

"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR

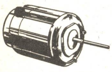

Type SS15. These fine motors are easily reversed, starting and stopping in less than 5^0 without electrical or mechanical braking. Simple relay circuit can be applied to give DC., to winding for a maximum holding torque of 300oz/in with 35v at 0·35 amps through winding. For AC. (synchronous) operation at 120r., 50Hz. Speed 60 rpm at 60Hz., 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution witn accuracy of 0·1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions: dia. 4", body length 4¾", spindle length 2¼" x $\frac{5}{16}$" dia. Weight 6½ lbs. BRAND NEW in maker's packing. Offered at less than ½ maker's price OUR PRICE ONLY **£15**

MAINS SOLENOID by MAGNETIC DEVICES LTD.

A beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1½" x 1½". Pull is approximately 2lbs., plunger travel 1¼". Fixing eye takes up to ½" bolt, plunger non-captive. NEW in original maker's boxes. **£1·20**. P. & P. 20p. Large number available, special price for quantity.

SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately ½" between divisions. Panel mounting with chrome bezel 3¾" dia. **£1·40**. 15p P. & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x ½"; (80 DB) ⅜" x 5/32" x ⅜". Ex-equipment, all tested. **£1·20** each. P. & P. FREE.

MAINS SOLENOID

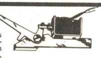

This little unit gives vertical lift of approximately 1" through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm, 2½". 240V AC. Pull at coil is approximately 1lb. **£1**. FREE P. & P. Special quotes for quantities.

SOLENOIDS by WESTOOL

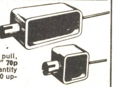

240AC type MM6. 3lb. pull, 2¾" x 1" x 1¼". Travel 1". **90p.** each. P. & P. 10p. 240AC type MM4. 2lb. pull, 1½" x 1¾" x 1". Travel ¾" **70p** each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.

OPEN FRAME shaded pole GEARED MOTORS

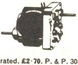

(Dural gear case) 240 AC., 28rpm. NEW HIGH TORQUE, approx. overall size: 3½" x 3¼" x 2¾" + spindle ¼" dia. as illustrated. **£2·70**. P. & P. 30p.
Similar to above, 19rpm. **£2·70**. P. & P. **30p.**
110rpm with pressed steel gear, case (similar to above but slightly smaller). **£2·70**. P. & P. 30p.

NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant, ideal for P.C.'s etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12"; 24" x 12"; 24" x 24"; FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". **£1** per sq. ft. Cut sizes (1-10 sq. ft.) 25p. P. & P. Full Sheet **£8** each. Carr. £1 for 1st sheet plus 25p each additional sheet.

SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v. 1½amp at 240v. Size: (approx.) 1$\frac{7}{16}$" long x ¼" dia. Ideal for burglar alarms, security systems etc., and wherever non-mechanical switching is required. 10 for **£2·10**; P. & P. 15p. 50 for **£8**; 100 for **£16·50**. FREE P. & P. over 10.

AMPEX 7·5v. D.C. MOTOR

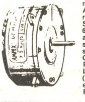

This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600rpm ± speed adjustment. Internal AF/RF suppression. ¼" dia. x 1" spindle, motor 3" dia. x 1⅜". Original cost £16·50. OUR PRICE **£3·30**. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available **75p** each. FREE P. & P.

ALL PRICES NOW INCLUDE V.A.T. UNLESS OTHERWISE STATED

All items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2·50 C.W.O., please. Company orders under £2·50, surcharge 60p unless C.W.O.

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD,
LONDON, W2.
Tel: 01-723 5667 01-402 5580

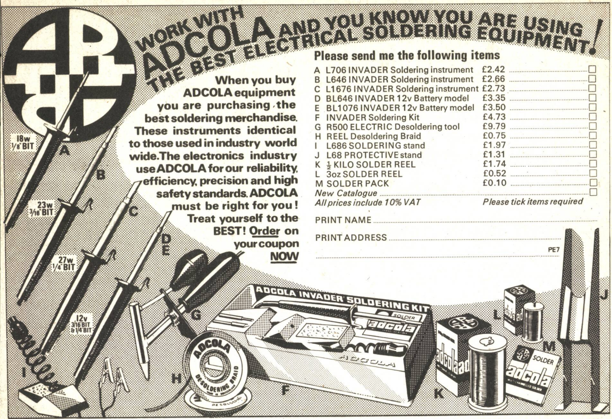
WORK WITH ADCOLA AND YOU KNOW YOU ARE USING THE BEST ELECTRICAL SOLDERING EQUIPMENT!
18w 1/8" BIT
A
B
23w 3/16" BIT
C
27w 1/4" BIT
D
E
12v 3/16" BIT & 1/4" BIT
G
I
H
F
K
L
M
J
ADCOLA INVADER SOLDERING KIT
adcola
ADCOLA DESOLDERING BRAID
SOLDER

When you buy ADCOLA equipment you are purchasing the best soldering merchandise. These instruments identical to those used in industry world wide. The electronics industry use ADCOLA for our reliability, efficiency, precision and high safety standards. ADCOLA must be right for you! Treat yourself to the BEST! Order on your coupon NOW

Please send me the following items

A	L706 INVADER Soldering instrument	£2.42	☐
B	L646 INVADER Soldering instrument	£2.66	☐
C	L1676 INVADER Soldering instrument	£2.73	☐
D	BL646 INVADER 12v Battery model	£3.35	☐
E	BL1076 INVADER 12v Battery model	£3.50	☐
F	INVADER Soldering Kit	£4.73	☐
G	R500 ELECTRIC Desoldering tool	£9.79	☐
H	REEL Desoldering Braid	£0.75	☐
I	L686 SOLDERING stand	£1.97	☐
J	L68 PROTECTIVE stand	£1.31	☐
K	½ KILO SOLDER REEL	£1.74	☐
L	3oz SOLDER REEL	£0.52	☐
M	SOLDER PACK	£0.10	☐
New Catalogue			☐

All prices include 10% VAT *Please tick items required*

PRINT NAME ....

PRINT ADDRESS ....

PE7
....

Post to ADCOLA PRODUCTS LTD. ADCOLA HOUSE GAUDEN ROAD LONDON SW4 6LH VAT REGD No. 235 6153 72 REGD No. 442762

CF

GIRO NO. 331 7056
C.W.O. only. P. & P. 10p on orders below £5
Discount: £10–10%, £20–15% (except net items)
Export Order enquiries welcome (VAT free)

Official Orders accepted from
Educational & Government Departments
ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS

10E12 ¼W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), **£3·10** net
10E12 ½W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%), **£3·20** net
25E12 ¼W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), **£7·20** net
25E12 ½W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%), **£7·35** net
20E12 ½W KIT: 20 of each E12 value, 10 ohms—1M, a total of 1220 (METAL FILM 5%), **£7·50** net
15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), **£8·15** net
10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), **£12·65** net

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. Mounting: 0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, **3½**p. 0·068μF, 0·1μF, **4½**p. 0·15μF, **4½**p. 0·22μF, **5½**p. 0·33μF, **8**p. 0·47μF, **9**p. 0·68μF, **11**p. 1μF, **15**p. 1·5μF, **22**p. 2·2μF, **25**p.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, **2½**p. 0·0068μF, 0·01μF, 0·015μF, 0·022μF, 0·033μF, **3½**p. 0·047μF, 0·068μF, 0·1μF, **4½**p. 0·15μF, **6½**p. 0·22μF, **8½**p. 0·33μF, **12**p. 0·47μF, **14**p.
160V: 0·01μF, 0·015μF, 0·022μF, **2½**p. 0·047μF, 0·068μF, **3½**p. 0·1μF, 0·15μF, **4½**p. 0·22μF, **5**p. 0·33μF, **6**p. 0·47μF, **7½**p. 0·68μF, **11**p. 1μF, **12½**p.

MINIATURE CERAMIC PLATE CAPACITORS

50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (μF) 0·01, 0·015, 0·022, 0·033, 0·047, **2½p.** each. 0·1, 30V, **4½p.**; 0·1; 100V, **5½p.**

POLYSTYRENE CAPACITORS 160V 5%

(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, **4p.** 6800, 10,000, **4½p.**

RESISTORS

CF—High Stab Carbon Film 5% MF—High Stab Metal Film, 5%.

W.	Type	Range	1-9	10-49	50-99	100-249	250-499	500-999	1000+	Size mm
⅛	CF	22-1M	1	0·8	0·65	0·62	0·55	0·5	0·45	2·4×7·5
¼	CF	22-2M2	1	0·8	0·65	0·62	0·55	0·5	0·45	3·9×10·5
½	CF	22-1M	1	0·8	0·65	0·62	0·55	0·5	0·45	5·5×16
¼	MF	10-2M7	1	0·9	0·8	0·7	0·65	0·65	0·6	3×7
½	MF	10-2M2	1	0·9	0·8	0·7	0·65	0·65	0·6	4·2×10·8
1	MF	10-10M	1·5	1·25	1·25	1·1	1	0·95	0·8	6·6×18
2	MF	10-10M	3	2·5	2·5	2	1·75	1·75	1·6	8×17·5

For value mixing prices, please refer to our catalogue. (price in pence each)
VALUES AVAILABLE—E12 Series only. Net prices above 100.

PRESET SKELETON POTENTIOMETERS

MINIATURE 0·25W Vertical or horizontal **6p** each
1K, 2K2, 4K7, 10K, etc. up to 1MΩ
SUB-MIN 0·05W Vertical, 100Ω to 220KΩ **5p** each

Wavechange Switches
1P, 4W; 1P, 12W; 2P, 2W
2P, 4W; 2P, 6W; 3p, 3W
4P, 2W; 3P, 4W; 4P, 3W.
26½p

B. H. COMPONENT FACTORS LTD.

(P.E.) 61 CHEDDINGTON ROAD, PITSTONE,
NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ
Tel.: Cheddington 668446 (Std. Code 0296)
PLEASE WRITE FOR FREE CATALOGUE

Miniature Mullard Electrolytics

1·0μF	63V	**6p**	68μF	16V	**6p**
1·5μF	63V	**6p**	68μF	63V	**12p**
2·2μF	63V	**6p**	100μF	10V	**6p**
3·3μF	63V	**6p**	100μF	25V	**6p**
4·0μF	40V	**6p**	100μF	63V	**14p**
4·7μF	63V	**6p**	150μF	16V	**6p**
6·8μF	63V	**6p**	150μF	63V	**15p**
8·0μF	40V	**6p**	220μF	6·4V	**6p**
10μF	16V	**6p**	220μF	10V	**6p**
10μF	25V	**6p**	220μF	16V	**8p**
10μF	63V	**6p**	220μF	63V	**21p**
15μF	16V	**6p**	330μF	16V	**12p**
15μF	63V	**6p**	330μF	63V	**25p**
16μF	40V	**6p**	470μF	6·4V	**9p**
22μF	25V	**6p**	470μF	40V	**20p**
22μF	63V	**6p**	680μF	16V	**15p**
32μF	10V	**6p**	680μF	40V	**25p**
33μF	16V	**6p**	1000μF	16V	**20p**
33μF	40V	**6p**	1000μF	25V	**25p**
32μF	63V	**6p**	1500μF	6·4	**15p**
47μF	10V	**6p**	1500μF	16V	**25p**
47μF	25V	**6p**	2200μF	10V	**25p**
47μF	63V	**8p**	3300μF	6·4	**26p**

VEROBOARD	0·1	0·15
2½ × 5"	**28p**	**28p**
2½ × 3¾"	**26p**	**19p**
3¾ × 5"	**32p**	**33p**
3¾ × 3¾"	**28p**	**28p**
2½ × 1"	**7p**	**7p**
2½ × 5" (Plain)	—	**14p**
2½ × 3¾" (Plain)	—	**12p**
5 × 3¾" (Plain)	—	**22p**
Insertion tool	**59p**	**59p**
Track Cutter	**44p**	**44p**
Pins, Pkt. 25	**10p**	**10p**

TRANSISTORS

AC127	**16½p**	BC212L	**12p**
AC128	**22p**	BC213L	**12p**
BC107	**11p**	BC214L	**17p**
BC108	**12p**	OC44	**18p**
BC109	**13p**	OC71	**13p**
BC148	**12p**	OC81	**16p**
BC149	**12p**	OC170	**23p**
BC182L	**12p**	TIS43	**33p**
BC183L	**12p**	2N2926	**11p**
BC184L	**13p**	2N3702	**11p**

POTENTIOMETERS

Carbon Track 5K Ω to 2M Ω, log or lin. Single, **16½p.** Dual Gang **46p.** Log Single with Switch **26p.** Slider Pots. 10K, 100K, 500K. 30mm, **34p.** 45mm, **47p.** 60mm, **55p.**

DIODES	
IN4001	**6½p**
IN4002	**7½p**
IN4003	**9p**
IN4004	**9½p**
IN4005	**12p**
IN4006	**14p**
IN914	**7p**
IN916	**7p**
BA100	**10p**
OA5	**42p**
OA47	**9p**
OA81	**11p**
OA200	**8p**

PLUGS	
DIN 2 Pin	**12p**
3 Pin	**13p**
5 Pin 180°	**15p**
Std. Jack	**14½p**
2.5mm Jack	**11p**
Phono	**5½p**

SOCKETS	
DIN 2 Pin	**10p**
3 Pin	**10p**
5 Pin 180°	**12p**
Std. Jack	**14½p**
2.5mm Jack	**11p**
Phono	**5½p**

ELECTROLYTIC CAPACITORS. Tubular & Large Cans

(uF/V): 2·2/25, 2·2/63, 4·7/10, 4·7/25, 4·7/63, 22/10, 22/25, 22/63, **5p.** 2/10, 10/10, 50/10, 100/10, 10/25, 50/25, 10/50, **5½p.** 200/10, 100/25, 50/50, **6½p.** 500/10, 200/25, 100/50, **9p.** 1000/10, 500/25, 200/50, **11p.** 2000/10, 1000/25, 500/50, **16½p.** 1000/50, **39p.** 1000/100, **66p,** 2000/25, **27p.** 2500/12, **17p.** 2500/25, **33p.** 2500/50, **62p.** 3000/50, **72p.** 5000/25, **66p.** 5000/50, **94p.** 7000/50, **60p.** 25,000/25, **74p.** HI-VOLT: 8/350, **14p.** 16/350, **19p.** 32/350, **25p.** 50/250, **18p** 100/500, **33p.**

METALLISED PAPER CAPACITORS

250V: 0·05μF, 0·1μF **4½p,** 0·25μF, **5½p,** 0·5μF, **6½p,** 1μF, **9p.** 500V: 0·025μF, 0·05μF, **4½p.** 0·1μF, **5½p,** 0·25μF, **6½p.** 0·5μF, **9p.** 1000V: 0·01μF, **10p.** 0·022μF, **12p.** 0·047μF, 0·1μF, **16p.** 0·22μF, **31p,** 0·47μF. **39p.**

Integrated Circuits	
μA709C	**50p**
μA741C	**55p**
μA723C	**£1**
μL914	**35p**

Screened Wire, Metre	**5½p**
Twin Screened Wire, Metre	**10p**
Stereo Screened Wire, Metre	**10p**
Connecting Wire, All colours, Metre	**2½p**
Neon Bulb, 90V Wire Ended	5 for **24p**
Panel Neon, 240V, Red, Amber, Clear	**16½p**

QUANTITY DISCOUNT
SPECIAL BULK BUY PRICES
ARE AVAILABLE BY
QUOTATION FOR LARGE
PROJECTS AND TRADE

ALL SPEAKERS NEED TO BE PUT IN THERE PLACE

16-PAGE EXTRA!

"YOUR HOME WITH HI-FI"

TELLS YOU WHERE

An acoustic guide on how to make your home a better place to listen in.

PLUS

- Snobs' guide to hi-fi
- Multi-track tape-recording
- Choosing a microphone
- Hints and tips on tuners
- **AUDIO talks to Frank Muir about his choice of music and the equipment he uses**
- Tests: **Garrard Zero 100 SB**
  Sonab R4000 Stereo Receiver
  Sony TC 161 D Cassette Recorder
  Building and testing the **Goodmans DIN20** loudspeaker kit.

ALL IN THE MARCH

Audio

ON SALE MID-FEB. 25p

Subject to the current national industrial situation at the time of going to press

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS

Prim. 120/240V. Sec 120/240V Centre Tapped and Screened

ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb	oz	Size cm.	P & P £	p
07	20	1	8	7·0 × 6·0 × 6·0	2·32	30
149	60	3	12	9·9 × 7·7 × 8·6	3·45	36
150	100	5	8	9·9 × 8·9 × 8·6	3·79	52
151	200	8	0	12·1 × 9·3 × 10·2	6·45	52
152	250	13	12	12·1 × 11·8 × 10·2	8·41	67
153	350	15	0	14·0 × 10·8 × 11·8	11·20	82
154	500	19	8	14·0 × 13·4 × 11·8	16·25	*
155	750	29	0	17·2 × 14·0 × 14·0	22·10	*
156	1000	38	0	17·2 × 16·6 × 14·0	29·87	*
158	2000	60	0	21·6 × 15·3 × 18·1	49·25	*

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb	oz	Size cm.	Auto Taps	P & P £	p
113	20	1	0	5·8 × 5·1 × 4·5	0-115-210-240	1·22	22
64	75	2	4	7·0 × 6·7 × 6·1	0-115-210-240	2·40	30
4	150	3	4	8·9 × 7·7 × 7·7	0-115-200-220-240	2·89	36
66	300	6	4	9·9 × 9·6 × 8·6	,, ,,	5·63	52
67	500	12	8	12·1 × 11·2 × 10·2	,, ,,	8·36	67
84	1000	19	8	14·0 × 13·4 × 14·3	,, ,,	15·19	82
93	1500	30	4	14·0 × 15·9 × 14·3	,, ,,	21·99	*
95	2000	32	0	17·2 × 16·6 × 14·0	,, ,,	28·70	*
73	3000	40	0	21·6 × 13·4 × 18·1	,, ,,	39·17	*

CASED AUTO TRANSFORMERS

115 500W enclosed transformer, with mains lead and two 115V outlet sockets, **£9·49**, P & P 67p. 20W version, **£2·02**, P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)
PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps. 12V	24V	Weight lb	oz	Size cm.	Secondary Windings	P & P £	p
111	0·5	0·25		8	4·8 × 2·9 × 3·5	0-12V at 0·25A × 2	1·22	22
213	1·0	0·5	1	4	6·1 × 5·8 × 4·8	0-12V at 0·5A × 2	1·44	22
71	2	1	1	12	7·0 × 6·4 × 6·1	0-12V at 1A × 2	1·90	22
18	4	2	2	12	8·3 × 7·7 × 7·0	0-12V at 2A × 2	2·68	36
70	6	3	3	8	8·9 × 8·0 × 7·7	0-12V at 3A × 2	3·20	42
108	8	4	5	8	9·9 × 8·9 × 8·6	0-12V at 4A × 2	3·60	52
72	10	5	6	4	9·9 × 9·6 × 8·6	0-12V at 5A × 2	4·25	52
116	12	6	6	12	9·9 × 10·2 × 8·6	0-12V at 5A × 2	5·10	52
17	16	8	8	12	12·1 × 9·9 × 10·2	0-12V at 8A × 2	6·56	52
115	20	10	11	8	14·0 × 9·6 × 11·8	0-12V at 10A × 2	8·36	67
187	30	15	15	8	14·0 × 12·1 × 11·8	0-12V at 15A × 2	15·40	82
226	60	30	32	0	17·2 × 15·3 × 14·0	0-12V at 30A × 2	28·44	*

30 VOLT RANGE

Ref. No.	Amps	Weight lb	oz	Size cm.	Secondary Taps	P & P £	p
112	0·5	1	4	6·1 × 5·8 × 4·8	0-12-15-20-24-30V	1·42	22
79	1·0	2	4	7·0 × 6·7 × 6·1	,, ,,	1·92	36
3	2·0	3	4	8·9 × 7·7 × 7·7	,, ,,	2·90	36
20	3·0	4	8	9·9 × 8·3 × 8·6	,, ,,	3·58	42
21	4·0	6	4	9·9 × 9·6 × 8·6	,, ,,	4·25	52
51	5·0	6	12	12·1 × 8·6 × 10·2	,, ,,	5·30	52
117	6·0	8	0	12·1 × 9·3 × 10·2	,, ,,	6·31	52
88	8·0	12	0	12·1 × 11·8 × 10·2	,, ,,	8·18	67
89	10·0	13	12	14·0 × 10·2 × 11·8	,, ,,	10·33	67

50 VOLT RANGE

Ref. No.	Amps.	Weight lb	oz	Size cm.	Secondary Taps	P & P £	p
102	0·5	1	12	7·0 × 6·4 × 6·1	0-19-25-33-40-50V	1·90	30
103	1·0	2	12	8·3 × 7·4 × 7·0	,, ,,	2·80	36
104	2·0	5	8	7·9 × 8·9 × 8·6	,, ,,	3·87	42
105	3·0	6	12	9·9 × 10·2 × 8·6	,, ,,	5·26	52
106	4·0	10	0	12·1 × 10·5 × 10·2	,, ,,	6·99	52
107	6·0	12	0	14·0 × 10·2 × 11·8	,, ,,	10·35	67
118	8·0	18	0	14·0 × 12·7 × 11·8	,, ,,	13·51	97
119	10·0	25	0	17·2 × 12·7 × 14·0	,, ,,	16·95	*

60 VOLT RANGE

Ref. No.	Amps.	Weight lb	oz	Size cm.	Secondary Taps	P & P £	p
124	0·5	2	4	7·0 × 6·7 × 6·1	0-24-30-40-48-60V	1·93	36
126	1·0	3	4	8·9 × 7·7 × 7·7	,, ,,	2·70	36
127	2·0	6	4	9·9 × 9·6 × 8·6	,, ,,	4·25	42
125	3·0	8	12	12·1 × 9·9 × 10·2	,, ,,	6·46	52
123	4·0	13	12	12·1 × 11·8 × 10·2	,, ,,	8·36	67
40	5·0	12	00	14·0 × 10·2 × 11·8	,, ,,	9·85	67
120	6·0	15	8	14·0 × 12·1 × 11·8	,, ,,	12·14	82
121	8·0	25	00	14·0 × 14·7 × 11·8	,, ,,	13·65	*
122	10·0	25	0	17·2 × 12·7 × 14·0	,, ,,	20·09	*
189	12·0	29	00	17·2 × 14·0 × 14·0	,, ,,	22·49	*

MINIATURE TRANSFORMERS WITH SCREENS

Ref. No.	mA	Weight lb	oz	Size cm.	Volts	P & P £	p
238	200		2	2·8 × 2·6 × 2·0	3-0-3	1·31	10
212	1A, 1A	1	4	6·1 × 5·8 × 4·8	0-6, 0-6	1·52	22
13	100		4	3·9 × 2·6 × 2·9	9-0-9	1·12	10
235	330, 330		4	4·8 × 2·9 × 3·5	0-9, 0-9	1·52	10
207	500, 500	1	00	6·1 × 5·4 × 4·8	0-8-9, 0-8-9	2·03	22
208	1A, 1A	1	12	7·0 × 6·4 × 6·1	0-8-9, 0-8-9	2·73	30
236	200,200		4	4·8 × 2·9 × 3·5	0-15, 0-15	1·52	10
214	300, 300	1	4	6·1 × 5·8 × 4·8	0-20, 0-20	1·60	22
221	700 (d.c.)	1	8	7·0 × 6·1 × 6·1	20-12-0-12-20	1·41	30
206	1A, 1A	2	12	8·3 × 7·7 × 7·0	0-15-20, 0-15-20	3·08	38
203	500,500	2	4	8·3 × 7·0 × 7·0	0-15-27, 0-15-27	2·82	38
204	1A, 1A	3	4	8·9 × 7·7 × 7·7	0-15-27, 0-15-27	2·86	38

*Carriage via B.R.S.

PLEASE ADD 10% FOR V.A.T.
INCLUDING P. & P.

BARRIE electronics

3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS ALDGATE & ALDGATE EAST

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORY

Better built
Better performance
Better value

SAXON HI-FI POWER AMPS IN THREE USEFUL SIZES FOR DOMESTIC & COMMERCIAL APPLICATIONS

New versions using 3A "Plastic Power" Driver Transistors now available.

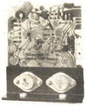

To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.

SA35 35W RMS uses 7 transistors and 7 diodes. Carr. paid. **£4·45**

SA50 50 watt RMS
7 transistors, 7 diodes
Carr. paid **£5·65**

SA100 makes an ideal unit in disco assemblies

A real glutton for work. Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid. **£10·90**

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15–40,000Hz ± 1dB
Distortion	0·2% at 1kHz
Loads	4 to 16 ohms
Quiescent current	15mA
Noise	Better than −75dB
Supply voltage	SA35–45V SA50 45/65V SA100 40–70V
Size	4½in × 4in × 1in (SA100) 4in × 3in × 1in (SA35/SA50)

All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in its SA100

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES
FOR THE SA35, SA50 AND SA10 POWER AMPS. ABOVE

PU45	Unstabilised supply for 2 SA35's	**£4·90**	
PU70	Unstabilised supply for one or two SA50 or SA100	**£7·75**	carr. 40p
PS45	Stabilised module for two SA35's or one SA50	**£3·50**	carr. free
MT45	Transformer for above, heavy duty	**£2·85**	carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted	**£3·50**	carr. 20p
PS70	Stabilised supply module for one or two SA100's	**£4·90**	carr. free
MT70	Transformer for PS70	**£4·90**	carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

SAXON PA MIXER-CONTROL UNITS

In extra slimline easy-fit case.

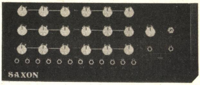

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master control on output of M6HL. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos, etc. Standard jack sockets, compact design. In strong metal cases. All Units guaranteed for 3 years.

- **HIGH AND LOW IMPEDANCE INPUTS**
- **BASS/TREBLE/VOLUME ON EACH PAIR**
- **MASTER CONTROL ON OUTPUT**

- **M4H**
  4 high Z, 4 low Z inputs, 4 sets of controls. Case 10″ × 8″ and only 2½in deep. Carr. paid. **£18·50** + **V.A.T.**
- **M6HL**
  12 inputs (6 high Z, 6 low Z) 18″ × 8″ × 2½″ Carr. paid **£27·50** + **V.A.T.**

Channel section modules, for building your own: gain—16 × (24dB). Tone controls—18dB swing. Carr. paid. **£3·50** + **V.A.T.**

CONTROL UNITS UNBEATABLE FOR QUALITY AND VALUE

EXCITING NEW STEREO VERSION. MK. II with stereo over-ride and case. (Carr. 30p). **£19·75**
Mono (as shown).

For 9 v. battery operation. As stereo model, less mic. input. Carr. 20p. **£6·50**

Two decks, and full headphone monitoring. The unit is mains operated and measures 17½in × 3in × 4in deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass treble, mains on/off. Comparable to units at over twice the price.

AKG HEADPHONES

World famous D.190C—the one the professionals use—at special bargain price of **£19·50** Plus V.A.T.

GENERAL PURPOSE MIC.

Dynamic professional quality. Carr. pd. **£9·90**

120 W HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.

SPECIFICATION
Power output, 120W into 8 ohms
Freq. response, 20–20,000Hz ± 2dB
Input sensitivity, 200mV into 10K
Construction, Fibreglass board
Size, 8in × 4in × 4in (5in with supply)
Low distortion parallel push-pull output stage.

Module and power supply (Carr. 40p) **£18·95**

- **160 watts version with power supply (Carr. 50p)** **£27·90**

SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kW (3,000W) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.

3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls, 2 amplifier sockets eliminate need for split leads. Up to 3kW lighting load. Suitable for free standing or panel mounting. **£19·75** Carr. 30p.

SINGLE CHANNEL UNIT

Operates from 5–100W amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£7·50**

COMPLETE AMPLIFIERS CSE 100

This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100W RMS and continuous signal outputs of 70W. Two individually controlled inputs with wide range bass and treble controls.

£34·90 carr. free

SAXON 100 **£48·50** carr. free

With an RMS output of 120W speech and music, 100W continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!
12in 25W 8/15 ohms **£6·95** carr. 30p. 15in 50W 8/15 ohm **£14·50** carr. 50p. 12in 40W 15,000 gauss magnet system 8/15 ohm **£11·50** carr. 40p.

V.A.T. **Please add 10% to total value of order (including carr.) for Value Added Tax.**

Please include S.A.E. with written enquiries

Prices subject to alteration without notice. E. & O.E.

Order and personal shoppers to:
SAXON ENTERTAINMENTS LTD., 329 Whitehorse Road, W. Croydon, Surrey CRO 2HS
Telephone 01-684 6385
From 9.30 a.m.-5.30 p.m.

Prices quoted do not include V.A.T. 10% must be added on to total value of order for V.A.T

TRADE AND EXPORT ENQUIRIES INVITED

TERMS OF BUSINESS
Cash with order (C.W.O.). For C.O.D. please add 35p extra, cash by regd. letter please.

R T V C

Remember! one of the Top Ten Accessory Awards from Motor *magazine*

PUSH BUTTON CAR RADIO KIT

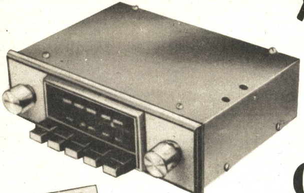

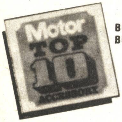

BUILD YOUR OWN TOURIST PUSH BUTTON CAR RADIO

Technical specification:

1.) **Output** 2.5 watts R.M.S. into 8 ohms. For 12 volt operation on negative or positive earth.
2.) **Integrated circuit** output stage, pre built three stage IF Module.

Controls Volume, manual tuning and five push buttons for station selection, illuminated tuning scale covering full medium and long wave bands.

Size Chassis 7 ins. wide, 2 ins. high and 4$\frac{5}{16}$ ins. deep approx.

NOTE: The ability to solder on a printed circuitboard is necessary to complete this kit successfully. Circuit diagram and comprehensive instructions 55p free with kit.

Car Radio Kit
£6.60 + 55p. postage & packing.

Speaker including baffle and fixing strips
£1.65 + 23p. postage & packing.

Recommended **Car Aerial** – fully retractable and locking.
£1.35 post paid.

STEREO 21

QUALITY SOUND FOR LESS THAN £19·00

Stereo 21 easy to assemble audio system kit, – no soldering required. Includes:—

BSR 3 speed deck, automatic, manual facilities together with ceramic cartridge.

Two 8" × 5" speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

For the technically minded:—

Specifications:

Input sensitivity 600mV:Aux. input sensitivity 120mV: Power output 2.7 watts per channel: Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs – radio, tape, etc., and outputs for taping discs. **Overall Dimensions.** Speakers approx. 15½" × 8" × 4". Complete deck and cover in closed position approx. 15½" × 12" × 6". Complete only **£18·45 + 16p. p & p**

Extras if required.

Optional Diamond Styli **£1.37**

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance, **£3.85.**

DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties.

Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.

1) Crystal Mic or Guitar 9mV. 2) Moving coil Mic or Guitar 8mV. 3), 4), 5) Medium output equipment (Gram. Tuner, Monitor, Organ, etc.) – all 250mV sensitivity.

Size approx. 12½ ins. × 6 ins. × 3½ ins.
£13.50 + 60p.
postage & packing.

8 TRACK CARTRIDGE PLAYER

Elegant self selector push button player for use with your own stereo system. Compatible with Viscount III system, the Stereo 21 and the Unisound module.

Technical specification.

Mains input, 240V. Output sensitivity 125mV

Comparable unit sold elsewhere at £24·00 approx.

Yours for only £10·60 + 90p. p & p

BUILD YOUR OWN STEREO AMPLIFIER

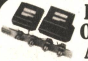

For the man who wants to design his own stereo —here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.

£7·64 + 55p. p & p

P.E. TAPE LINK CONSTRUCTORS

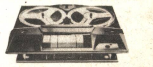

A suitable 3 speed tape deck, less heads. Caters up to 5¾ ins. spools. 240V AC mains.

Unused but store soiled hence no warranty. £4.00 + £1.00 p & p

£49·00

40 Watt Amplifier.
Viscount III – R102 now 20 watts per channel.
System I includes,
Viscount III amplifier – volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification
20 watts per channel into 8 ohms.
Total distortion @ 10W @ 1kHz 0·1%. *P.U.1* (for ceramic cartridges) 150mV into 3 Meg. *P.U.2* (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within 1dB R.I.A.A. *Radio* 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. *Tone controls and filter characteristics*. Bass: 12dB to –17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble 12dB to –12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) –58dB.
Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13¾″ × 9″ × 3¾″.

Garrard SP. 25 Mk III deck with magnetic cartridge, plinth and cover.

Two Duo Type II matched speakers – Enclosure size approx. 17″ × 10½″ × 6½″ in simulated teak. Drive unit 13″ × 8″ with parasitic tweeter. **Complete System £49·00**

£65·00

System II
Viscount III amplifier (As System I)
Garrard SP. 25 Mk III deck (As System I)
Two Duo Type III matched speakers – Enclosure size approx. 23½″ 11½″ 9½″. Finished in teak veneer. Drive units approx. 13½″ 8¼″ with 3¼″ HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz.

Complete System £65·00

PRICES: SYSTEM 1

Viscount III R 102 amplifier	£24·20	£1 p &-p
2 Duo Type II speakers	£14·00	£2·20 p & p
Garrard SP25 Mk. III with MAG. cartridge plinth & cover	£18·00	£1·75 p & p
total	£56·20	

Available complete for only £49·00 £3·50 p. & p.

PRICES: SYSTEM 2

Viscount R 102 amplifier	£24·20	£1 p & p
2 Duo Type III speakers	£32·00	£3·30 p & p
Garrard SP25 Mk III with MAG. cartridge plinth & cover	£18·00	£1·75 p & p
total	£74·20	

Available complete for £65·00 £4 p. & p.

THE ULTIMATE COMPLETE SPEAKER SYSTEM EMI LE 315

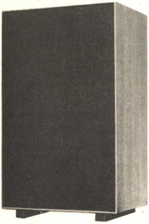

A professional standard five way speaker system with enclosure giving top quality performance.

Enclosure Dimensions
approx. (3 ft. × 2 ft. × 1 ft.).

Drive Units
Hand built – 15″ diameter bass with 3″ voice coil,
– two 5″ diameter Mid Range units,
– two 3¼″ HF. units,
plus matching crossover panel with two variable potentiometers for mid and high frequency adjustment.

Powder Handling
Continuous rating 35 W rms., Peak power rating 70 W.

Frequency Response
20 Hz 20,000 Hz.

Recommended retail selling price, £86·00.

Our price £45·00 + £3.50 postage & packing.

EMI SPEAKERS

FANTASTIC REDUCTION

15″ 14A/780. Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3″ voice coil.

Recommended retail price £40·80.

OUR PRICE £18·70 + £1·50 p & p

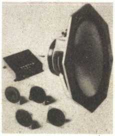

950 Kit – Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.
Huge 19″ × 14″ (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.

The four 10,000 gauss tweeters, each 3¼″ dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2″, others 0·5″. Recommended list price £44·00.

OUR PRICE £25·00 + £1·50 p & p
Special Offer.

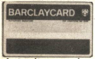

Just write your order giving your credit card number
DO NOT SEND YOUR CARD

- **Mail orders to Acton. Terms C.W.O. All enquires Stamped Addressed Envelope. Goods not despatched outside U.K.**
- **Leaflets available for all items listed.* Send stamped addressed envelope.**

***No leaflet available on Reliant Mk 1V Mono Amplifier**

R T-V C

Radio and TV Components (Acton) Ltd.
21 High Street, Acton, London W3 6NG (D)
323 Edgware Road, London W2
Edgware: 9 a.m.-5.30 p.m. Half day Thurs.
Acton: 9.30 a.m.-5 p.m. Closed all day Wed.

SINCLAIR CALCULATORS
Subject to the maker's full guarantee. An incomparably fast and comprehensive after sales service is provided by Sinclair's famous service department.

Cambridge Kit **£23·95** (£3)
Cambridge Assembled **£25·95** (£3)
Executive **£33·95** (£3·70)

FERRANTI ZN414
Fabulous integrated circuit radio chip supplied with instructions **£1·20** (23p). Also available a kit of parts to construct a MW and LW radio. Send S.A.E. for free leaflet.

SINCLAIR EQUIPMENT

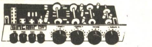

Z40 **£4·25** (63p); Project 605 **£18·95** (£2·30);
Z60 **£5·38** (74p) Stereo; 80 Pre-amp **£9·45** (£1·05);
Q16 **£5·90** (79p); Project 80 Tuner **£8·95** (£1·10);
PZ5 **£3·47** (57p); Project 80 Decoder **£5·69** (77p);
PZ6 **£5·95** (99p); Project 80 AFU **£5·38** (74p);
PZ8 **£6·20** (84p); Trans. for PZ8 **£2·95** (50p).

SINCLAIR SUPER IC12
6W r.m.s. power with 44-page booklet and printed circuit **£2·10** (43p).

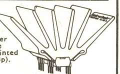

SWANLEY IC TOMORROW **£2·60** (47p)
The world's most powerful IC amplifier. Similar appearance to the IC12 but rated at 10W r.m.s. power. Supplied with data but no printed circuit board.

BATTERY ELIMINATOR BARGAIN **£3.75** (60p)
The most versatile battery eliminator ever offered. Switched output of 3V, 4·5V, 6V, 7·5V, 9V and 12V at 500mA.

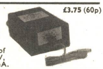

ZIPPY CABINETS
Attractive plastic instrument cabinets in 4 sizes. P1 80 × 50 × 30mm **60p** (25p); P2 115 × 65 × 40mm **87p** (30p); P3 155 × 90 × 50mm **£1·20** (35p); P4 210 × 125 × 70mm **£1·80** (45p).

IC RADIO CHIP TBA651 **£2·10** (32p)
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data **£2·10** (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for **£1·75** (29p).

S-DECS and T-DECS

S-DECS	**£1·98** (31p)
T-DECS	**£3·63** (47p)
μ-DEC A	**£3·99** (51p)
μ-DEC B	**£6·99** (81p)
16 dil IC carriers	**£1·77** (25p)

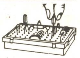

DE LUXE KIT FOR THE IC12
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version **£1·55** (26p). Stereo model with balance control **£3·50** (46p).

IC12 POWER KIT
Supplies 28V 0·5A **£2·47** (50p).

LOUDSPEAKERS FOR THE IC12
5in 8 ohm **£1·10** (27p). 5in × 8in 8 ohm **£1·55** (37p).

PREAMPLIFIER KITS FOR THE IC12
Type 1 for magnetic pickups, mics. and tuners. Mono model **£1·30** (24p). Stereo model **£2·30** (34p). Type 2 for ceramic or crystal pickups. Mono **60p** (17p). Stereo **£1·20** (23p).

SEND S.A.E. FOR FREE LEAFLET ON KITS.

ECONOMICAL QUADRAPHONICS **£9·95** (£1·30)
Napolex Quadraphonic Synthesizer. Complete, self-contained matrix system in attractive cabinet. Just feed ordinary 2 channel stereo into it and connect outputs to 4 loudspeakers to obtain the latest experience in sound.

SWANLEY ELECTRONICS

32 Goldsel Road, Swanley, Kent

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools etc. welcome. Mail order only. No callers, please.

No VAT on overseas orders which are most welcome.

P.E. SOUND SYNTHESISER

Complete kits or individual components.

741C mini DIL **37p;** 748CS mini DIL **48p.**
4-Quadrant Multipliers
SG3402N **£1·74;** SG3402T **£1·74;** SG1495D **£2·90.**
Electronic Attenuator
MFC6040 **£1.**
Noise Diodes
Z1J **50p;** Z1M Wideband **£1·20.**
Zener Diodes BZY88 series
3·3V; 3·6V; 3·9V; 5·1V; 6·8V; 7·5V; 11V; 12V. All at **22p** each.
Voltage Regulators
MVR15–15V 450mA—TO3 **£1·80.**
μA723 (Equiv.) adjustable 8–37V–TO5 outline **£1·80.** μA7815—15V-TO66 outline **£2·20.**
Bridge Rectifiers
Rec. 41a, 100 PIV 2·2A **£1·20.**
Rec. 70, 400 PIV 800 mA **40p.** ML3046P **75p.**
Transistors/Diodes
BC184; BC182; BC213 all at **9p** each.
BC209C *npn* 150mW **9p;** BC204 *pnp* 150mW **9p;** AC176 *npn* Ger **24p;** 2N2219 *npn* 800mW **22p;** 2N2905 *pnp* 800mW **27p;** 2N3819 f.e.t. **46p;** 1N914 **5p;** 1SJ50 **12p;** 1GP7 **10p.**
Hook-up Wire
1m each, 20 diff. colours **60p.**
1m each, 36 diff. colours **£1·07.**
Supplied in longer lengths by request.
Screened Cable. Low noise 7/.02 Cap.92pF/m. Nom. imp. 50 ohm. **15p/metre.**
Lacing Cord
Rayon cored black p.v.c. **2p**/m.
McMurdo's, New stocks—Low prices
8 pole plug RP8 **30p;** 8 pole skt. RS8 **48p.**
2mm plugs/skts. 7·5p/35p for 5.
Black, blue, red, green, yellow, white.
Mains Transformers
Miniature Type
Secs. 0–12V, 0–12V @ 3VA each **£1·38.**
Secs. 0–20V, 0–20V @ 3VA each **£1·38.**
Regulator Type 634
Sec. 17·5V @ 1·6A **£2·15.**
MT102 AT (Douglas)
Sec. 0–19, 25, 33, 40, 50 @ 500mA **£2·35.**

Potentiometers
Min. Moulded Carbon. Lin. Tracks:
5kΩ; 10kΩ; 25kΩ; 50kΩ; 100kΩ; 1MΩ **18p;** Log. Tracks. 10kΩ **18p.**
Ganged
5kΩ log; 10kΩ; 100kΩ lin. **64p.**
Carbon Presets. Horiz. Type.
10kΩ; 47kΩ; 100kΩ; 470kΩ **10p.**
Cermet Presets. Horiz. Type
100; 500; 1kΩ; 10kΩ; 50kΩ; 100kΩ **35p.**
15 Turn Cermet Trimmers
10kΩ **£1·20.**
Semi-precision Wirewound Pot.
1kΩ **52p.**
Precision 10 Turn Miniature
10kΩ (Spectrol) 23mm dia. × 19mm **£3;** 1kΩ (R.S.) 13mm dia. × 40mm **£3.**
10 Turn Counting Dial (Amphenol) £2.
Rotary Switches
2P 6W; 3P 4W; 4P 3W; 6P 2W **37p.**
Min. push to make buttons 30p.
Sub-miniature toggles
S.P.S.T. **75p;** D.P.D.T. **£1.**
Stripboards. Cu. strips drilled 0·1" crs. 115×34 ways. **95p.**
Hutchinson Tone Control. 1/16" epoxy glass, roller tinned PCB. **95p.**
Resistors
2% metal oxide Mullard/Electrosil **16p** for 5.
5% carbon film Mullard/Erie **9p** for 5.
Capacitors
Tantalum bead, Silver Mica, Polyester, Polystyrene, Ceramic, Electrolytic.
4½p stamp brings latest lists.

Access
Buy it with Access

Simply send exact details of name and number copied from the face of your Access Card and leave the rest to us.

EATON AUDIO

P.O. Box No. 3, ST. NEOTS
HUNTINGDON PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2.
Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P. All prices subject to V.A.T.

TELEPRINTER HANDBOOK

AN RSGB PUBLICATION

Price **£5·25**

HANDBOOK OF IC CIRCUIT PROJECTS by J. Ashe. Price **£1·50.**

HOW TO USE INTEGRATED CIRCUITS LOGIC ELEMENTS by J. W. Streater. Price **£1·50.**

T.V. ENGINEERS' POCKET BOOK by P. J. McGoldrick. Price **£2·60.**

2nd BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES by B. B. Banbani. Price **£1·05.**

SERVICING WITH THE OSCILLOSCOPE by G. J. King. Price **£2.**

BASIC ELECTRONIC TEST PROCEDURES by I. Gottlieb. Price **£2·15.**

ELECTRONICS POCKET BOOK by J. P. Hawker. Price **£1·70.**

HI FI YEAR BOOK 1974 by C. Sproxton. Price **£1·75.**

BASIC ELECTRONIC CIRCUITS SIMPLIFIED by N. W. Hibbs. Price **£2.**

THE MAZDA BOOK OF PAL RECEIVER SERVICING by D. J. Seal. Price **£4.**

TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard. Price **£1·90.**

*** ALL PRICES INCLUDE POSTAGE ***

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185
Closed Saturday 1 p.m.

4-STATION INTERCOM

£13·95

Solve your communication problems with this **4-Station Transistor Intercom** system (**1 master** and **3 Subs**), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from **Master** to **Subs** and **Subs** to **Master.** Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 47p.

MAINS INTERCOM (new model)

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price **£21·95** per pair. P. & P. 60p extra.

INTERCOM/BABY ALARM

£5·95

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft connecting wire. Complete with battery. P. & P. 35p.

Transistor TELEPHONE AMPLIFIER

£4·95

Why not **boost** business efficiency with this incredible De-Luxe **Telephone Amplifier.** Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/3)
169 KENSINGTON HIGH STREET, LONDON, W.8

Marshall's

A. Marshall & Son (London) Limited
42 Cricklewood Broadway London NW2 3HD, Telephone 01-452 0161
& 65 Bath Street Glasgow G2 2BX, Telephone 041-332 4133

months best buy ex-stock
All British made 'Calcate' calculator
One of the first electronic calculators in the world with no mechanical switches or moving parts. Touch button operation using latest MOS integrated circuitry. Complete with charger and case. 1 years quarantee. 140mm x 80mm.
Our price £29·00 excluding VAT
Recommended price £42·50. P&P 30 pence UK

Transistors

2G301	0·15	2N3392	0·13	3N187	1·55	ASY29	0·36	BCY72	0·13	BFY11	0·45
2G302	0·15	2N3393	0·13	3N200	2·49	ASY50	0·20	BCY87	3·54	BFY17	0·90
2G303	0·25	2N3394	0·13	3N201	1·12	ASY55	0·15	BCY88	2·42	BFY18	0·35
2G306	0·30	2N3402	0·18	40050	0·78	BC107	0·16	BCY89	0·97	BFY19	0·35
2G309	0·30	2N3403	0·19	40251	0·81	BC108	0·15	BCZ10	0·35	BFY20	0·50
2G345B	0·25	2N3404	0·24	40309	0·30	BC109	0·19	BCZ11	0·50	BFY29	0·40
2G371	0·15	2N3405	0·27	40310	0·50	BC113	0·13	BD115	0·75	BFY37	0·20
2G374	0·15	2N3414	0·10	40313	0·92	BC114	0·12	BD116	0·75	BFY41	0·43
2N174	1·40	2N3415	0·10	40316	0·50	BC115	0·15	BD121	0·75	BFY43	0·65
2N404	0·43	2N3416	0·15	40318	0·92	BC116	0·15	BD123	0·82	BFY50	0·22½
2N456	0·75	2N3417	0·21	40360	0·46	BC116A	0·18	BD124	0·67	BFY51	0·18½
2N456A	0·75	2N3570	1·25	40361	0·48	BC117	0·21	BD131	0·40	BFY52	0·20½
2N457A	0·80	2N3571	1·12½	40362	0·50	BC118	0·11	BD132	0·50	BFY53	0·16
2N491	3·58	2N3572	0·97	40363	0·61	BC119	0·29	BD135	0·43	BFY56	0·34
2N696	0·15	2N3702	0·11	40389	0·46	BC121	0·23	BD136	0·49	BFY64	0·41½
2N697	0·15	2N3703	0·12	40394	0·56	BC125	0·15	BD137	0·55	BFY75	0·40
2N698	0·25	2N3704	0·14	40395	0·65	BC126	0·20	BD138	0·63	BFY76	0·22
2N699	0·29	2N3705	0·12	40406	0·44	BC132	0·30	BD139	0·71	BFY77	0·24
2N706	0·16	2N3706	0·09	40407	0·33	BC134	0·11	BD140	0·87	BFY78	0·36
2N706A	0·18	2N3707	0·13	40408	0·50	BC135	0·11	BDY10	1·25	BFY90	0·60
2N708	0·14½	2N3708	0·70	40409	0·52	BC136	0·15	BDY11	1·50	BRY39	0·28
2N709	0·38	2N3709	0·11	40410	0·52	BC137	0·15	BDY17	1·50	BSX19	0·13
2N711	0·30	2N3710	0·12	40411	2·25	BC138	0·24	BDY18	1·75	BSX20	0·20½
2N718	0·21	2N3711	0·11	40414	3·55	BC140	0·34	BDY19	1·97	BSX21	0·20½
2N718A	0·49	2N3712	0·96	40467	0·69	BC141	0·29	BDY20	1·05	BSX26	0·49
2N720	0·50	2N3713	1·20	40468A	0·44	BC142	0·23½	BDY38	0·65	BSX27	0·34
2N721	0·55	2N3714	1·38	40600	0·69	BC143	0·21	BDY60	0·85	BSX28	0·25
2N914	0·22	2N3715	1·50	40601	0·67	BC144	0·24	BDY61	1·25	BSX29	0·47
2N916	0·41	2N3716	1·80	40602	0·46	BC145	0·21	BDY62	1·00	BSX60	0·54
2N918	0·47	2N3773	2·65	40603	0·58	BC147	0·12	BF115	0·25	BSX61	0·42
2N929	0·30	2N3779	3·15	40604	0·56	BC148	0·13	BF116	0·23	BSX76	0·15
2N930	0·48	2N3790	2·40	40636	1·10	BC149	0·12	BF117	0·43	BSX77	0·20
2N1090	0·30	2N3791	2·35	40673	0·70	BC153	0·18	BF119	0·58	BSX78	0.25
2N1091	0·32	2N3792	2·69	AC107	0·25	BC154	0·18	BF121	0·25	BSW70	0·28
2N1132	0·54	2N3794	0·10	AC113	0·16	BC157	0·14	BF123	0·27	BSY24	0·20
2N1302	0·18½	2N3819	0·37	AC117	0·20	BC158	0·13	BF125	0·25	BSY25	0·20
2N1303	0·18½	2N3820	0·38	AC121	0·13	BC159	0·14	BF152	0·20	BSY26	0·20
2N1304	0·24	2N3823	1·42	AC126	0·25	BC160	0·37	BF153	0·21	BSY27	0·15
2N1305	0·24	2N3824	1·33	AC127	0·25	BC167B	0·13	BF154	0·16	BSY28	0·15
2N1306	0·31	2N3826	0·23	AC128	0·25	BC168B	0·13	BF158	0·23	BSY38	0·19½
2N1307	0·22	2N3854	0·18	AC141K	0·30	BC168C	0·11	BF159	0·27	BSY39	0·19½
2N1308	0·25	2N3854A	0·16	AC142K	0·25	BC169B	0·13	BF160	0·23	BSY51	0·25
2N1309	0·35½	2N3855	0·19	AC151V	0·14	BC169C	0·13	BF161	0·41½	BSY52	0·25
2N1483	0·90	2N3855A	0·20	AC152V	0·17	BC170	0·11	BF163	0·31½	BSY53	0·25
2N1507	0·30	2N3856	0·19	AC153	0·25	BC171	0·13	BF166	0·31½	BSY54	0·30
2N1613	0·33	2N3856A	0·20	AC153K	0·25	BC172	0·11	BF167	0·21	BSY56	0·79
2N1631	0·38	2N3858	0·16	AC154	0·20	BC182	0·12	BF173	0·24	BSY65	0·15
2N1637	0·36	2N3858A	0·19	AC176	0·18	BC182L	0·12	BF177	0·29	BSY78	0·40
2N1638	0·32	2N3859	0·14	AC176K	0·25	BC183	0·09	BF178	0·35	BSY79	0·40
2N1701	1·19	2N3859A	0·19	AC187K	0·28	BC183L	0·09	BF179	0·43	BSY790	0·45
2N1702	2·15	2N3860	0·19	AC188K	0·34	BC184	0·11	BF180	0·35	BSY95A	0·10½
2N1711	0·45	2N3866	1·09	ACY17	0·35½	BC184L	0·11	BF181	0·34	BU104	1·42
2N1893	0·81	2N3877	0·25	ACY18	0·24	BC186	0·25	BF182	0·40	BU105	2·25
2N2102	0·30	2N3877A	0·26	ACY19	0·27	BC187	0·27½	BF183	0·40	C111	0·53
2N2147	0·70	2N3900	0·21	ACY20	0·22	BC207	0·12	BF184	0·17	D40N3	0·55
2N2148	0·94	2N3900A	0·21	ACY21	0·26	BC208	0·11	BF185	0·17	GET111	0·45
2N2192	0·40	2N3901	0·32	ACY22	0·17	BC212K	0·10	BF194	0·16	GET113	0·25
2N2192A	0·40	2N3903	0·24	ACY28	0·20	BC212L	0·16	BF195	0·17	GET114	0·20
2N2913	0·40	2N3904	0·27	ACY30	0·42	BC214L	0·21	BF196	0·15	GET115	0·50
2N2193A	0·61	2N3905	0·24	ACY39	0·65½	BC237	0·09	BF197	0·15	GET119	0·35
2N2194	0·73	2N3906	0·27	ACY40	0·17	BC238	0·09	BF198	0·18	GET120	0·40
2N2194A	0·30	2N4036	0·62½	ACY41	0·17	BC239	0·09	BF199	0·18	GET535	0·20
2N2218A	0·86	2N4037	0·42	ACY44	0·31	BC251	0·20	BF200	0·40	GET536	0·20
2N2219	0·57	2N4058	0·16	AD136V	0·96	BC252	0·18	BF224J	0·14	GET538	0·20
2N2219A	0·86	2N4059	0·09	AD142	0·50	BC253	0·23	BF225J	0·19	GET873	0·12
2N2220	0·45	2N4060	0·11	AD143	0·45	BC257	0·09	BF237	0·22	GET875	0·15
2N2221	0·41	2N4061	0·11	AD149V	0·66	BC258	0·09	BF238	0·22	GET880	0·35
2N2221A	0·83	2N4062	0·11	AD150	0·63	BC259	0·13	BF244	0·16	GET883	0·20
2N2222	0·60	2N4302	0·25	AD161	0·45	BC261	0·20	BF245	0·33	GET887	0·20
2N2222A	0·91	2N4303	0·47	AD162	0·45	BC262	0·18	BF246	0·43	GET890	0·25
2N2368	0·31	2N4916	0·11	AD161 }	Pr.	BC263	0·23	BF247	0·49	GET895	0·25
2N2369	0·37	2N4917	0·17	AD162 }	1·05	BC300	2·12	BF254	0·16	TIP29A	0·49
2N2369A	0·41	2N4918	0·73	AF109R	0·40	BC301	0·34	BF255	0·17	TIP30A	0·58
2N2646	0·77	2N4919	0·84	AF114	0·25	BC302	0·29	BF257	0·47	TIP31A	0·62
2N2647	1·12	2N4920	0·99	AF115	0·24	BC303	0·54	BF258	0·59	TIP32A	0·74
2N2711	0·13	2N4921	0·73	AF116	0·25	BC307	0·10	BF259	0·55	TIP33A	1·01
2N2712	0·12	2N4922	0·84	AF117	0·20	BC307A	0·10	BF270	0·21	TIP34A	1·51
2N2713	0·17	2N4923	0·83	AF118	0·50	BC308	0·09	BF272	0·53	TIP35A	2·90
2N2714	0·18	2N5172	0·12	AF121	0·22	BC308A	0·12	BF273	0·15	TIP36A	3·70
2N2904	0·55	2N5174	0·22	AF124	0·24	BC308B	0·09	BF274	0·17	TIP41A	0·79
2N2904A	0·70	2N5175	0·26	AF125	0·20	BC309	0·10	BF457	0·53	TIP42A	0·90
2N2905	0·71	2N5176	0·32	AF126	0·19	BC309A	0·10	BF458	0·65	TIP2955	0·98
2N2905A	0·88	2N5190	0·92	AF127	0·20	BC309B	0·10	BFS21A	2·30	TIP3055	0·60
2N2906	0·65	2N5191	0·95	AF139	0·38	BC327	0·21	BFS28	0·92	ME0401	0·18
2N2906A	0·70	2N5192	1·24	AF170	0·25	BC328	0·19	BFS61	0·27	ME0402	0·20
2N2907	0·38	2N5195	1·46	AF172	0·25	BC337	0·19	BFS98	0·20	ME0404	0·13
2N2907A	0·41	2N5245	0·43	AF178	0·55	BC338	0·19	BFW11	0·61	ME0411	0·17
2N2923	0·12	2N5457	0·49	AF179	0·65	BCY30	0·43	BFX13	0·23	ME0412	0·18
2N2924	0·14	2N5458	0·45	AF180	0·50	BCY31	0·51½	BFX29	0·30	ME0413	0·14
2N2925	0·17	2N5459	0·49	AF186	0·40	BCY32	1·15	BFX30	0·25	ME1120	0·25
2N2926		3N128	0·73	AF200	0·35	BCY33	0·34	BFX37	0·33	ME4001	0·09
Green	0·12	3N138	1·65	AF239	0·51	BCY34	0·36½	BFX44	0·33	ME4002	0·11
Yellow	0·11	3N139	1·42	AF240	0·72	BCY38	0·52½	BFX63	2·48	ME4003	0·14
Orange		3N140	0·92	AF279	0·54	BCY39	1·05	BFX68	0·30	ME6101	0·10
	0·11	3N141	0·81	AF280	0·54	BCY40	0·87	BFX84	0·24	ME4102	0·11
2N3053	0·32	3N142	0·58	AFY42	0·74	BCY42	0·15	BFX85	0·30	ME4103	0·10
2N3054	0·86	3N143	0·75	AL102	0·75	BCY43	0·15	BFX86	0·25½	ME4104	0·11
2N3055	0·75	3N152	0·92	AL103	0·70	BCY58	0·21	BFX87	0·28	ME4101	0·14
2N3390	0·26	3N153	0·81	ASY26	0·30	BCY59	0·22	BFX88	0·25	ME6102	0·16
2N3391	0·28	3N154	0·84	ASY27	0·36	BCY70	0·17	BFX89	0·45	ME8002	0·17
2N3391A	0·29	3N159	1·17	ASY28	0·28	BCY71	0·22	BFY10	0·35	ME8003	0·16

Open
9.30 am - 5.30 pm
Mon to Sat
'Return of post' service
Barclaycards accepted

Litronix LED's

RL-2 02 03 04	46p
RL54	13p
RL55	42p
RL209	33p
RL4484	31p
RL4850	31p
DL707 (Alphanumeric)	2.35

Litronix LED's
Sescocem semi-conductors.
Full range of Cosmos
Capacitors - Siemens Nitsuko Ducati

Zener Diodes
Sesocem and Mullard

400mw	11p
1w	17p
1½w	25p
10w	40p
20w	52p

Components supplied for most projects in this magazine

Our full range is in our catalogue available now - price 20pence

Post and Packing **13p** per order. Europe 25p. Commonwealth (Air) 65p (MIN). Matching charge (audio transistors only) 15p extra per pair. Prices subject to stock availability.

Kellner Construction Kits

We are the sole distributors in U.K.

ES3 3 watt Mono Transistor Amplifier Kit	**£4·08**
ES15 15 watt Hi-Fi Transistor Amplifier Kit [two for stereo] with Tone Control and Pre-Amp	**£13·20**
ES30 30 watt Mono Hi-Fi Power Amplifier	**£9·20**
ES50 50 watt Mono Hi-Fi Power Amplifier	**£10·53**
EV3 Distortion Compensated Pre-Amplifier	**£4·00**
AV7 Aerial Amplifier. LW, SW, MW, VHF, T/V Channels 2–12	**£2·04**
UHS70 FM Transmitter Kit. 65mHz–145mHz. A GPO Licence is required	**£2·79**
MUE7 Short Wave and VHF Receiver Kit. Companion to UHS70 25mHz–150mHz	**£3·22**
EW18 Electronic Dice Kit	**£6·53**
EW20 Electronic Dice with Sensor Button	**£7·79**
ST800 Strobe Light Kit, 120W/S	**£7·86**
LO1000 Psychedelic Light Control, single channel	**£7·00**
LO350 Psychedelic Light Control, three channel	**£13·50**
NT15 Power Supply—4 to 30V, 1·5W	**£7·46**
NT85 Professional Stabilized Power Supply, 5 to 70V, 2A	**£12·53**
D800 800W Light Dimmer Speed Control	**£2·98**
WT7 Aircraft Communications Tuner 110–130mHz. Built and aligned	**£15·46**
WT9 Transmitter VFO for 2 meters [144mHz–146mHz]. Built and aligned	**£15·46**

All prices plus 10% VAT and plus 15p post and packing. All kits with easy to follow instructions and covered by a full guarantee.

Bridge Rectifiers

	Plastic				Metal—Professional quality			
	£	£	£	£	£	£	£	£
	1A	2A	4A	6A	5	15	25	50A
50	0·24	0·32	0·60	0·62	2·22	2·64	3·36	12·30
100	0·36	0·37	0·70	0·75	2·24	3·00	3·60	12·36
200	0·30	0·41	0·75	0·80	2·82	3·78	4·32	14·40
400	0·36	0·45	0·85	1·10	3·72	4·20	5·40	16·38
600	0·40	0·52	0·95	1·25				

AB Potentiometers—carbon

Rotary type 45: Singles (Log and linear) **15p.** Single switched (Log and linear) **21p.** Doubles (Log and linear) **38p.**

Slider type 58: Singles (Log and linear) **30p.** Doubles (Log and linear) **50p.**

Presets: 0·1 watt **6p,** 0·2 watt **6p,** 0·3 watt **7½p.** Please specify vertical or horizontal.

Diodes and Rectifiers

PIV	50	100	200	400	600	800	1000
1·5	8p	9p	10p	11p	12p	15p	20p
3	15p	17p	20p	22p	25p	27p	30p
10	—	35p	40p	47p	56p	—	—
35	84p	92p	£1·18	£2·15	£2·52	£3·65	£4·20

Cathode Stud Only

IN3766 (35A 800pv)	**£3·65**	IN3786 (35A 1000pv)	**£4·20**

IN34A	10p	BA141	17p	BY237	12½p	OA79	7p
IN914	7p	BA142	17p	BYZ10	35p	OA81	8p
IN916	7p	BA144	12p	BYZ11	32p	OA85	10p
AA119	7p	BA145	17p	BYZ12	30p	OA90	7p
AA129	15p	BA154	12p	OA9	10p	OA91	7p
BA100	15p	BY100	15p	OA10	20p	OA95	7p
BA102	25p	BY126	15p	OA47	7½p	OA200	7p
BA110	25p	BY127	17½p	OA70	7½p	OA202	10p
BA115	7p	BY140	£1	OA73	10p	OA210	27p

Integrated Circuits

Each month we will show a different range of i.c.'s which are kept in stock.

CA3000	2·28	CA3028b	1·17	CA3054	1·19	CD4010ae	1·07
CA3001	3·38	CA3029	0·52	CA3055	1·44	CD4011ae	0·51
CA3002	2·26	CA3029a	0·63	CA3059	1·84	CD4012ae	0·51
CA3004	2·26	CA3030	1·08	CA3060	4·91	CD4013ae	0·99
CA3005	1·50	CA3030a	1·64	CA3062	2·97	CD4014ae	2·66
CA3006	3·47	CA3033	2·92	CA3064	1·42	CD4015ae	2·66
CA3007	3·28	CA3033a	4·93	CA3065	1·42	CD4016ae	1·02
CA3008	1·98	CA3034	1·65	CA3066	2·61	CD4017ae	2·66
CA3008a	3·24	CA3035	1·52	CA3067	2·72	CD4018ae	2·66
CA3010	0·56	CA3036	0·90	CA3068	3·01	CD4019ae	1·23
CA3010a	0·69	CA3037a	2·60	CA3070	2·15	CD4020ae	2·96
CA3011	0·92	CA3038	2·60	CA3071	2·01	CD4021ae	2·70
CA3012	1·11	CA3038a	3·40	CA3072	2·07	CD4022ae	2·58
CA3013	1·30	CA3039	1·00	CA3075	1·46	CD4023ae	0·51
CA3014	1·52	CA3040	2·95	CA3076	1·67	CD4024ae	4·95
CA3015	1·40	CA3041	1·30	CA3078	3·19	CD4025ae	0·51
CA3015a	1·82	CA3042	1·30	CA3080	0·58	CD4027ae	1·58
CA3016	2·61	CA3043	1·73	CA3080a	1·90	CD4028ae	2·34
CA3016a	3·90	CA3044	1·42	CA3086	0·46	CD4029ae	3·79
CA3018	0·88	CA3045	1·50	CA3088e	1·38	CD4037ae	1·93
CA3018a	1·19	CA3046	0·86	CA3089e	2·18	CD4042ae	2·11
CA3019	0·94	CA3047	1·59	CA3090q	4·70	CD4043ae	2·11
CA3020	1·55	CA3047a	2·92	CD4000ae	0·51	CD4044ae	2·11
CA3020a	2·01	CA3048	2·34	CD4001ae	0·51	CD4045ae	2·65
CA3021	1·90	CA3049	1·96	CD4002ae	0·51	CD4046ae	2·84
CA3022	1·61	CA3050	2·28	CD4006ae	2·45	CD4047ae	1·65
CA3023	1·55	CA3051	1·73	CD4007ae	0·51	CD4049ae	0·90
CA3026	1·25	CA3052	1·80	CD4008ae	2·53		
CA3028a	0·88	CA3053	0·52	CD4009ae	1·07		

Car Radio,
Kit K/CR-9502.

Metal
Locator,
Kit K/GD-348

Electronic
Calculator,
Kit K/IC-2108.

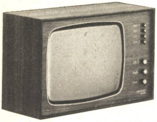

Black and White
Portable Television,
Kit K/GR-9900.

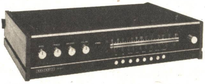

Hi-Fi Stereo
Receiver,
Kit K/AR-1214

Get the Heathkit Catalogue..and save

Handcrafted electronics with built-in quality and kit form savings.
Hundreds of models to choose from.
Heath offer you outstanding specifications and plus values that will impress you, your family and friends. Want to know more? Send for your personal introduction to the international world of Heathkit electronics . . . the Free Heathkit Catalogue.

Free

Please send me the FREE Heathkit Catalogue & details of Monthly budget plans.

NAME ____________________

ADDRESS ____________________

____

HEATH
Schlumberger

HEATH (GLOS.) LTD. DEPT. PE/03/74
Bristol Road,
Gloucester GL2-6EE

YOU AIN'T HEARD NOTHIN' YET!!

. . . UNTIL YOU TUNE IN TO STEREO PERFECTION WITH 'VARICAP'

'p.e.' f.m.
varicap stereo tuner

Size approx.
8¾" × 2¾" × 6½"

This elegant and practical stereo tuner features push button 'spot-on' tuning with up to five simple pre-set stations (no difficult tuning dial and drive cord). Its easy 'no problem' construction requires only a few simple setting adjustments with a D.C. Voltmeter. It incorporates NEW pre-set modules for R.F. and I.F. circuits, this eliminates the need for the usually difficult circuit alignment.
All this, coupled with the latest Motorola high efficiency, Integrated Circuit 'phase lock loop' stereo decoder and automatic stereo lamp indicator, ensures perfect stereo reception.
The 'Varicap' is, in our opinion, THE most easily constructed stereo tuner available which will achieve professional results.
The kit comprises Fibre glass P.C. board, elegant slimline teak veneer cabinet, brushed aluminium front panel, push buttons, instructions, in fact everything you need.
We also supply any of these kit components as separate items.

Total kit price ONLY £28·50 (inclusive of VAT and postage).

IDEAL FOR USE WITH THE 'TEXAN', 'GEMINI' OR ANY OTHER GOOD QUALITY STEREO AMPLIFIER.

PARTS FOR PRACTICAL WIRELESS PROJECTS:
After many requests, Electro Spares are supplying lists of components for ALL projects featured in 'Practical Wireless' from July 1973 issue onwards. We regret that we cannot supply lists for projects published before this date.
All you have to do is send us a stamped addressed envelope, not less than 9" × 4", stating which project is of interest to you. We will then forward you an individually priced list of the components required, there is, of course, no necessity to purchase a full kit, you may purchase only the parts you require at any one given time.
We believe this method of 'one source' buying can save you time and postage—**AND THAT MEANS MONEY!!**
ALL COMPONENTS SUPPLIED BY ELECTRO SPARES ARE NEW, BRANDED PRODUCTS OF REPUTABLE MANUFACTURERS AND THEREFORE CARRY THE MAKERS' FULL GUARANTEE.

'P.E.' 'GEMINI' STEREO AMPLIFIER
The 'Gemini' is a quality hi-fi stereo amplifier for the home constructor, featuring a genuine 30 watt R.M.S. per channel output into 8 ohms. Total harmonic distortion of 0·02% and a frequency response (−3dB) 20Hz–100kHz, at all power levels.
We are continuing to supply components for this fabulous amplifier, which is now recognised as practically THE ultimate in High-Fidelity.
We know no better unit for the home constructor—hundreds have been supplied throughout the world.
Electro Spares have available a booklet containing full specification, complete constructional information, wiring diagrams and fault finding guide, etc.
The price is 55p + 4p postage, along with which we will send you our new **LOW PRICE LIST.** Price list available separately on receipt of a large S.A.E. Our new Mail Order department address is set below. We aim for quick, efficient service—or why not pay us a call, we make all enthusiasts welcome and there are no parking problems.

ELECTRO SPARES

288 Ecclesall Road, Sheffield
S11 8PE. Tel: (0742) 668888

'THE COMPONENT CENTRE OF THE NORTH'

es

COMPREHENSIVE HOME CONSTRUCTOR KITS

AS SPECIFIED IN THE P.E. RONDO

COMPLETE QUADRAPHONIC HI-FI SYSTEM

CBS SQ* MATRIX DECODER *TM CBS	Complete kit. Post Free. Inc. CBS Licence Fee + VAT 80p	**£8.00**
PREAMPLIFIER BOARD	Complete kit. Post Free. + VAT 30p	**£3.00**
MASTER VOL./TONE/BALANCE BOARD	Complete kit. Post Free. + VAT 85p	**£8.50**
POWER AMP BOARD AND HEATSINK (Stereo Pair)	Complete kit. Per Board. Post Free + VAT 75p	**£7.50**
POWER SUPPLY BOARD COMPLETE	Post Free. + VAT 50p	**£5.00**
MAIN SMOOTHING CAPACITORS (TWO reqd.)	Post Free. + VAT 15p	**£1.50** Per Pair
MAINS TRANSFORMER	Post Free. + VAT 62p	**£6.25**
CHASSIS-PUNCHED AND DRILLED WITH SCREENS	Post Free. + VAT 32p	**£3.25**
RONDO CASE	Post Free. + VAT 17p	**£1.75**
HARDWARE PACK	Post Free. + VAT 20p	**£2.00**
CONTROL SECTION FASCIA	Post Free. + VAT 35p	**£3.50**
STEREO DECODER KIT	Post Free. + VAT 59p	**£5.95**
STEREO DECODER READY BUILT AND TESTED	Post Free. + VAT 69p	**£6.95**
GOLDRING G101/2 TURNTABLE Less Cartridge	Post Free. + VAT £2·39	**£23.90**
DEUTSCHE ELAC STS 144/17 CARTRIDGE	Post Free. + VAT 69p	**£6.90**

All component parts for "Rondo" loudspeaker assemblies are available, including special precision machined wrapround cabinets for very easy construction and perfect professional finish—as shown in fig. 5.9 of January 1974 issue.

READY BUILT LOUDSPEAKERS	(Teak or White Veneer) Post £2·00. + VAT £4·40	**£42.00** Per Pair
COMPLETE SPEAKER KIT WITH 4 DRIVE UNITS, CROSSOVER WADDING, ETC. (Four kits reqd. for Rondo) INCLUDES CABINETS	Per Pair Post £1·00. + VAT £3·55	**£34.50**
	Per Four Post £2·00. + VAT £6·40	**£62.00**
BASS DRIVE UNITS (2 per cabinet)	Post Free. + VAT 39p	**£3.95** EACH
TWEETERS (2 per cabinet)	Post Free. + VAT 12p	**£1.20** EACH
CROSSOVER KIT (1 per cabinet)	Post Free. + VAT 25p	**£2.50** EACH

SONAX

ELECTRONICS

SPENCER HOUSE
BRETTENHAM ROAD
EDMONTON
LONDON, N.18

TRADE ENQUIRIES WELCOME

PLEASE SEND ME

PLEASE TICK BOX

CBS SQ DECODER ☐
PREAMPLIFIER BOARD ☐
MASTER VOLUME BOARD ☐
POWER AMP BOARDS ☐
POWER SUPPLY BOARDS ☐
SMOOTHING CAPACITORS ☐
MAINS TRANSFORMER ☐
CHASSIS ☐
STEREO DECODER KIT ☐
STEREO DECODER BUILT ☐
READY BUILT LOUDSPEAKER TEAK CABINET ( ) ☐
READY BUILT LOUDSPEAKERS WHITE CABINET ( ) ☐

BASS DRIVE UNITS ( ) ☐
TWEETERS ( ) ☐
CROSSOVER KIT ( ) ☐
CABINET KIT WHITE ( ) ☐
CABINET KIT TEAK ( ) ☐
COMPLETE SPEAKER KIT WITH DRIVE UNITS CROSSOVER WADDING, ETC. WITH WHITE CABINET ( ) ☐
DITTO WITH TEAK CABINET ( ) ☐
GOLDRING G101 TURNTABLE LESS CARTRIDGE ☐
ELAC 144 CARTRIDGE ☐

RONDO CASE ☐
HARDWARE PACK ☐
CONTROL SECTION FASCIA ☐

MONEY ENCLOSED

£ ....

CHEQUE
P.O.
MONEY ORDER

Please insert quantity in open brackets

BLOCK CAPITALS PLEASE DETAILS OF ANCILLARY KITS ☐

NAME ....

ADDRESS ....

....

.... P.E.3/4

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER
STEREO & MONO

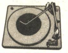

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V. Size 18½ × 11¼in.
Above motor board 3¼in. Below motor board 2½in.

with STEREO and MONO XTAL **£6·25** Post 25p.

PORTABLE PLAYER CABINET

Modern design. Black rexine covered. Silver front grille. Padded Lid. Chrome fittings. Size 18in × 11in.
Few only in red rexine.
Motor board cut for BSR deck **£4·50** Post 25p

4 Transistor Mono Amplifier

Powerful 3 watt output. 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make.
Size 8in wide × 4in deep × 3in high.
Suitable 7in × 4in speaker, £1. **£5·95** Post 25p

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono compatible cartridge. **£4·95**

GARRARD DECCA HI-FI DECK

Single play Stereo/
Mono Deram
transcription
head and arm.
Four speeds.
10½in turntable.
Anti-rumble filter.
Bias compensation.
Laboratory motor.

SPECIAL PRICE **£18·50** Post 25p Ideal for Disco Decks

METAL PLINTH AND PLASTIC COVER

Cut out for most Garrard or B.S.R.
Most will play with cover in position.
12½ × 14¾ × 7½in.
Covered in black leatherette. **£4·95** Post 35p

ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH—AT SAME PRICE

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13¾ × 10 × 3¾in. Player unit clips to loudspeakers making it extremely compact, overall size only 13¾ × 10 × 8½in., 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls.
240V AC Mains.

Attractive
Teak finish
Weight 13 lb.

Bargain Price
£25
85p Carriage

SPECIAL OFFER!
SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0 TO 60 MINUTES

Single pole two-way Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Fully insulated. Makers' last list price £4·50. Brand new and fully guaranteed. OUR PRICE **£1·65** or **£3** pair. Post 25p

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2½in sides 6 × 4in 45p; 8 × 6in 53p; 10 × 7in 65p; 12 × 8in 85p; 14 × 9in 90p; 16 × 6in 90p; 12 × 3in 50p; 16 × 10in £1.
ALUMINIUM BOXES 3 × 3 × 3in 60p; 4 × 4 × 4in 70p; 6 × 4 × 4in 80p; 9 × 4 × 4in £1; 12 × 4 × 4in £1·30.
ALUMINIUM PANELS 18 s.w.g. 6 × 4in 9p; 8 × 6in 15p; 14 × 3in 16p; 10 × 7in 19p; 12 × 5in 20p; 12 × 8in 28p; 16 × 6in 28p; 14 × 9in 34p; 12 × 12in 40p; 16 × 10in 50p.
PAXOLIN PANEL 10 × 8in 15p.
1¼ inch **DIAMETER WAVECHANGE SWITCHES**, 25p.
2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way, 25p each.
1 p.1. 2-way, or 4 p. 2-way, or 4 p. 3-way, 25p.
TOGGLE SWITCHES, sp. 14p; dp. 22p; dp. dt. 22p.
Sub-miniature, sp. 30p; dp. 37p; dp. dt. 45p.

BRITISH FM/VHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors ready aligned —requires 10·7 Mc/s I.F. Complete with tuning gang. Connections supplied but some technical experience essential. **Our price £3·95** Post 20p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less
PLEASE STATE VOLTAGE REQUIRED. **£2·20** Post 20p
Details S.A.E. Size 3½ × 1½ × 1⅜in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1¾ x 1½ x ½ in. Response 25 c/s to 25 kc/s. 26 dB gain.
For use with valve or transistor equipment. Full instructions supplied. Details S.A.E. **99p** Post 10p

NEW TUBULAR ELECTROLYTICS				CAN TYPES	
2/350V	14p	250/25V	14p	50+50/300V	50p
4/350V	14p	500/25V	20p	60+100/350V	85p
8/450V	18p	1000/25V	35p	32+32/250V	20p
16/450V	22p	1000/50V	47p	32+32/450V	60p
32/500V	50p	8+8/450V	22p	350+50/325V	55p
25/25V	10p	8+16/450V	25p	16+16+16/275V	45p
50/50V	10p	16+16/450V	40p	100+50+50/350V	55p
100/25V	10p	32+32/350V	40p		

LOW VOLTAGE ELECTROLYTICS.
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.
CERAMIC 1pF to 0·01mF, 4p. Silver Mica 2 to 5000pF, 4p.
PAPER 350V-0·1 4p; 0·5 13p; 1mF 15p; 2mF 150V 15p. 500V-0·001 to 0·05 4p; 0·1 5p; 0·25 8p; 0·47 25p.
SILVER MICA. Close tolerance 1%. 2·2-500pF 8p; 560-2,200pF 10p; 2,700-5,600pF 20p; 6,800pF-0·01, mfd 30p each.
TWIN GANG. "0-0" 208pF + 176pF, 65p.
Slow motion drive 365pF + 365pF with 25pF + 25pF, 50p; 500pF standard 65p; small 3-gang 500pF £1·60.
SHORT WAVE SINGLE. 10pF, 30p; 25pF, 55p; 50pF, 55p.

SHORT WAVE SINGLE GANG. Precision Silver Plated Gangable Tuning Condensers.
Values up to 100pF. **50p** each
Section Couplers supplied FREE with two or more gangs.

NEON PANEL INDICATORS 250V AC/DC. Amber 20p.
RESISTORS. ¼W, ½W, 1W. 20% 1p; 2W, 5p. 10Ω to 10M.
HIGH STABILITY. ½W 2% 10 ohms to 6 meg., 10p.
Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.
WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 0·5 ohm to 8·2 ohms 10p.
TAPE OSCILLATOR COIL Valve type 35p.
FERRITE ROD 8 × ⅜in 20p; 6 × ⅜in 20p; 3 × ⅜in 10p.

MAINS TRANSFORMERS

ALL POST 25p each

Eagle MT12 12-0-12V 50mA	90p
250-0-250 80 mA. 6·3V 3·5A 6·3V 1A or 5V 2A	£2·50
350-0-350 80 mA 6·3V 3·5A, 6·3V 1A or 5V 2A	£3·00
300-0-300V 120mA, 6·3V 4A C.T.; 6·3V 2A	£3·25
MINIATURE 200V 20mA, 6·3V 1A 2½ × 2½ × 2in	75p
MIDGET 220V 45mA, 6·3V 2A 2¾ × 2½ × 2in	90p
HEATER TRANS. 6·3V 3A	60p

GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £2·80
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £2·25
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £3·80
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8·75
3 amp, 5, 8 and 13V £1·00; Ditto 5 amp £1·20. 3 amp, 3, 5, 8, 10, 13 and 5-0-5V £1·30, Ditto 5 amp. £1·50; 6-0-6V 500mA 90p 9V 1 amp 95p 12V 300mA 75p 12V 500mA 85p 12V 750mA 95p. 40V 1 amp £1·75.
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £2·80; 500W £6·25; 750W £10; 1000W £15
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12V, 1½ amp £1·50; 2 amp £1·80; 4 amp £2·50
BATTERY CHARGERS. Ready built with leads and clips 1½ amp £2; 4 amp £4; 5 amp. £4·50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs. 1½ amp 40p; 2 amp 55p; 4 amp 85p.

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V 3 amps 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. Famous make (Value £19) OUR PRICE **£10** Carr. 50p
Can be used as 800 watt auto transformers 240-110V.

SET OF 3 MOTORS FOR COLLARO STUDIO TAPE DECK

£2·50 Post 50p

VOLUME CONTROLS

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. Edge 5K. S.P. Transistor 25p.

80 Ohm Coax 4p yd.

BRITISH AERIALITE
AERAXIAL-AIR SPACED
40 yd £1·40; 60 yd £2.
FRINGE LOW LOSS **10p** per yd
Ideal 625 and colour.

Wire Wound controls 1¼in diam. 3 Watts. 10 ohms to 100K British Made with long spindles ¼in dia. 45p each.
HELICAL POT 10K LIN. List £3. Bargain 75p.
DUAL CONCENTRIC POT 500K LOG AND 500K LIN D.P. switch. Inner spindle 3¼in; outer spindle 2¼in 75p.

E.M.I. 13½ × 8in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. **£4·50** Post 25p

With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. **£2·75** Post 25p

Bookshelf Cabinet 16 × 10 × 9in. Teak finish **£5·50** Post 25p

GOODMANS 6½in. HI-FI WOOFER

8 ohm. 10W. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. **£4**
Suitable Cabinet 12 × 8 × 6 £4 Suitable Tweeter £2

ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3½ × 3½ × 2in deep. Rating 10W, 3 ohm.
Crossover £1·25 **£1·90** Post 20p.

GOODMANS 8 in. WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass resonance 35 cps. Frequency response 30-8,000 cps. Ideal bass unit for Hi-Fi system. **£3·75**

SPECIAL OFFER LOUDSPEAKERS

3 ohm, 2½in; 2¾in; 3½in; 5in.
8 ohm, 2¼in; 2¾in; 5in × 3in; 5in.
15 ohm, 3½in; 5in; 6 × 4in; 7 × 4in; 8 × 5in.
25 ohm, 2½in; 3in; 5 × 3in; 5in.
35 ohm, 2in; 3in; 5in.
80 ohm, 2¼in; 2¾in.

£1 EACH

LOUDSPEAKERS P.M. 3 OHMS. 7 × 4in £1·25; 6½in £1·50; 8 × 5in £1·60; 8in £1·75; 10 × 6in £1·90; 10in £2·00.
RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in diameter 4W £2·50, 10 in diameter 5W £2·50; Post 25p. 12in diameter, 6W, £2·95; 3 or 8 or 15 ohm models.
SPEAKER COVERING MATERIALS. Samples Large S.A.E.
Horn Tweeters 2-16Kc/s. 8W 8 ohm or 15 ohm £2·20.
De Luxe Horn Tweeters 2-18Kc/s, 15W, 15 ohm £3·50.
TWO-WAY 3,000 c.p.s. CROSSOVERS 3, 8 or 15 ohm £1·25.

TWO-WAY CROSSOVER NETWORK 3,000 c/s

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5½in × 4in with control knob, tweeter and woofer leads and input terminals. Suitable for 3 to 8 ohm impedance. **£2·20** Post 20p

VALVE OUTPUT TRANSFORMER 25p.
MIKE TRANSFORMER MU metal 100-1 £1·25.
5 WATT MULTI RATIO. 3, 8 and 15 ohms, 80p.
PUSH-PULL VALVE OUTPUT TRANSFORMERS.
50 watt............£12·50   100 watt........ £15·00

ELECTRO MAGNETIC PENDULUM MECHANISM

1·5V d.c. operation over 200 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, strobe, etc. **95p** Post 20p

R.C.S. RECORD PLAYER AMPLIFIER

2 stage triode pentode valve. 3 watts output. Volume on/off and tone controls. Printed circuit A.C. mains complete and tested. **£4·50** Post 25p

COAXIAL PLUG 10p. **PANEL SOCKETS** 10p. **LINE** 18p
OUTLET BOXES, SURFACE MOUNTING 25p.
BALANCED TWIN RIBBON FEEDER 300 ohms, 5p yd.
JACK SOCKET Std. open-circuit 14p. closed circuit 23p; Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p
JACK PLUGS Std. Chrome 20p; 3·5mm Chrome 12p **DIN SOCKETS** Chassis 3-pin 10p; 5-pin 10p **DIN SOCKETS** Lead 3-pin 18p; 5-pin 15p. **DIN PLUGS** 3-pin 18p; 5-pin 25p.
VALVE HOLDERS 5p; **CERAMIC** 8p; **CANS** 5p.

ALL PRICES INCLUDE VAT   MINIMUM POST AND PACKING ● CALLERS WELCOME ●

RADIO COMPONENT

Illustrated Colour Brochure, Radio Books & Components Lists 10p Written guarantee.

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

£5·75 THE PAIR, Post 25p. (Available separately. Woofer £4·25; Tweeter £1·90)

Comprising a fine example of a Woofer $10\frac{3}{4} \times 6\frac{1}{2}$in with a massive Ceramic Magnet, 44oz Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter $3\frac{1}{4}$in square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard	8 ohms
Maximum power	12 watts
Useful Response	35 to 18,000 cps
Bass Resonance	45 cps

SUITABLE ENCLOSURE 20 × 13 × 9in. MODERN DESIGN. TEAK WOOD FINISH. **£9·90** Post 25p

8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50–16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8in. 10 watts, 10in, 12 watts. **£3·75**

TEAK VENEER HI-FI SPEAKER CABINETS
Fluted Wood Fronts

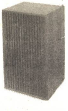

MODEL "A". 20 × 13 × 9in For 12 in. dia. or 10in speaker. **£9·90** Post 25p

MODEL "B". 16 × 10 × 9in For 13 × 8in. or 8 in. speaker **£5·50** Post 25p
MODEL "B" 2 ditto. Triangular Corner Version.

MODEL "C". 16 × 8 × 6in. For 8 × 5in. speaker **£4.40** Post 25p

LOUDSPEAKER CABINET WADDING 18in wide, 15p ft.

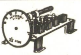

BARGAIN AM TUNER. Medium Wave. Transistor Superhet Ferrite aerial. 9 volt. **£4·95**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£3·95**
STEREO VERSION OF ABOVE £5·95.

BARGAIN FM TUNER. 88-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 × 5 × 4in. **£12·85**

BARGAIN FM TUNER. As above less cabinet. **£8·85**

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£4·50**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. **£3·50** Post 20p

WAFER THIN HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size $10\frac{7}{8} \times 8\frac{1}{4} \times \frac{1}{16}$in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopiers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p** EACH (FOUR FOR **£1·50**)

ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12″ £9·90

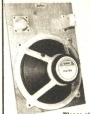

Post Free

30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. Post Free **£12·50**

Please state 3 or 8 or 15 ohms. Post free

BAKER "BIG SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" 12in 25 watt 3, 8 or 15 ohms. **£8·80** Post Free

GROUP "35" 12in 35 watt 3, 8 or 15 ohms. **£9·90** Post Free

GROUP "50" 15in. 50 watt 8 or 15 ohms. **£22·00**

NEW 12in VERSION £17·60

MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E. **£49** Carr. £1·00

CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 and 15 ohm Loudspeaker matching. **£69**

Q MAX CHASSIS CUTTERS
A die, punch and Allen Screw

Sizes	
$\frac{3}{8}$″	74p
$\frac{7}{16}$″	83p
Key "T" for above	6p
$\frac{1}{2}$″, $\frac{9}{16}$″, $\frac{5}{8}$″	90p
$\frac{11}{16}$″, $\frac{3}{4}$″	92p
$\frac{13}{16}$″, $\frac{7}{8}$″	99p
Key "A" for above	6p
$\frac{15}{16}$″, 1″, $1\frac{1}{16}$″, $1\frac{1}{8}$″	£1·00
$\frac{13}{16}$″, 1 7/32″, $1\frac{1}{4}$″	£1·15
$1\frac{15}{16}$″, $1\frac{3}{8}$″	£1·20
$1\frac{1}{2}$″	£1·35
$1\frac{5}{8}$″	£1·55

Sizes	
$1\frac{3}{4}$″	£1·70
Key "B" for above	10p
2″	£2·25
2 3/32″	£2·50
$2\frac{1}{2}$″	£3·30
Key "C" for above	13p
$2\frac{5}{8}$″	£4·50
$2\frac{3}{4}$″	£5·75
3″	£9·00
Key "E" for above	20p
1″ Square, with key	£2·10

SPECIAL OFFER

100 ohm Rheostat $2\frac{1}{2}$in dia. Ceramic former screw terminals $\frac{1}{4}$in dia. spindle. 95p. Post 25p.

SPECIAL OFFER

3in Panel Meter 50 μA. Unusual scale requires re-calibration. £1·75. Post 25p.

WEYRAD COILS

P50/1AC	40p	RA2W	85p
P50/2CC	38p	OPT1	65p
P50/3V	38p	LFDT4	65p
PCA1	60p	Twin gang	75p

DELUXE 4 POLE MOTOR

1,400 r.p.m. reversible 42 Watt, spindle $1\frac{1}{4}$in × 7/32in, size $3\frac{1}{2}$in × 3in. As illustrated. 240V a.c. mains. **£1·95** Post 25p

E.M.I. GRAM MOTOR

120V or 240V a.c. 2,400 rpm. 2-pole 70mA. Size $2\frac{7}{8} \times 2\frac{1}{4} \times 2\frac{1}{4}$in. **£1·00** Post 25p

BAKER HI-FI SPEAKERS
HIGH QUALITY—BRITISH MADE

REGENT
12in. 15 watts

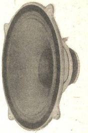

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance	45cps
Flux Density	12,000 gauss
Useful response	45-13,000cps

3 or 8 or 15 ohm models.

£8·80 Post Free

DE-LUXE Mk II
12in. 15 watts

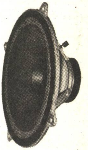

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance	30cps
Flux Density	14,000 gauss
Useful response	25-16,000cps

8 or 15 ohms models.

£11 Post Free

SUPERB
12in. 20 watts

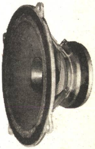

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance	25cps
Flux Density	16,500 gauss
Useful response	20-17,000cps

8 or 15 ohms models.

£16·50 Post Free

AUDITORIUM
12in. 25 watts

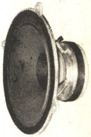

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs, Ideal for Hi-Fi and Discotheques.

Bass Resonance	35cps
Flux Density	15,000 gauss
Useful response	25-16,000cps

8 or 15 ohms models.

£15·40 Post Free

AUDITORIUM
15in 35 watts

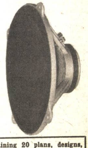

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Bass Resonance	35cps
Flux Density	15,000 gauss
Useful response	20-14,000cps

8 or 15 ohms models.

£22 Post Free

Hi-Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free.

CUSTOMERS FREE CAR PARK • **OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closed for Lunch 1.15-2.30)**

SPECIALISTS 337 WHITEHORSE ROAD · CROYDON

(Export: Remit cash and extra postage.) *Buses 50, 68, 159. Rail Selhurst* **Telephone 01-684-1665**

look! electronics really mastered

...practical
...visual
...exciting!

no previous knowledge
no unnecessary theory
no "maths"

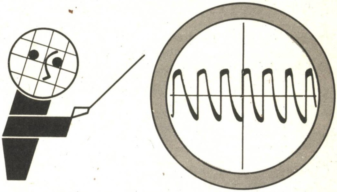

RAPY

BUILD, SEE AND LEARN
step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS

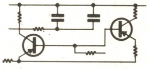

as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE **POST NOW for BROCHURE**

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME BLOCK CAPS

ADDRESS PLEASE EL34

special free gift also to all our students

PE

INSPIRING TIMES

If necessity be the mother of invention, we are now surely entering upon a period of prolificity in circuit creation and adaptation.

It is the amateur designer and experimenter who so often has the knack of hitting upon the right kind of solution to a sudden problem affecting everyday life. And problems there certainly are at this present time when restrictions in the use of electricity, if not complete cuts in the supply, affect all households; and soaring prices, if no actual shortage of petrol, make every motorist that more efficiency conscious.

This month's *Ingenuity Unlimited* includes a novel circuit devised by one of our readers and it is likely to be of interest to those with electrically controlled gas fired heating systems. A fore-runner, no doubt, of other crisis inspired ideas. We shall be happy, indeed consider it to be our duty, to publish other circuit ideas which may help overcome hardships or inconvenience experienced at home or on the road.

There already exist, of course, many circuits and systems that have relevance in the present difficult times. As a service to our readers we have prepared a special Blueprint for inclusion in this issue. It gives details for constructing two extremely useful and topical projects.

One side of this Blueprint carries details of the *P.E. Scorpio Mk 2 Ignition System*. The great success of the first Scorpio ignition system coupled with a continuing demand for copies of the original article made it quite clear that publication of an up-dated version would be highly welcomed; and in actual fact, could be a genuine service to the car owning public. The merits of the capacitor discharge ignition system are now well established, but they are, in any case, summarised in the article which complements the information given on the Blueprint.

The other side of the Blueprint is devoted to a design for a lamp inverter. Such devices are not by any means novel, but since design information may not be immediately to hand at the crucial moment, we expect a number of readers will appreciate the appearance of this useful design.

NEW PRICE

We ourselves, alas, are not immune from the effects of rising prices and shortages of raw materials, and we regret having to end this month with the following domestic note.

An apology is due to our readers for the lack of advance warning with regard to an increase in price of Practical Electronics. This increase to 25p takes effect as from this (March) issue. Unfortunately it was not possible to make an earlier announcement in this respect.

We trust all our readers will understand that the current high cost of materials, especially paper, makes this new price for P.E. unavoidable.

F.E.B.

Editor
F. E. BENNETT

Editorial
R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.
J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager
D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW
Phone: 01-634 4210

C. R. BROWN, *Classified*
Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.,
London EC4A 4AD
Phone: *Editorial* 01-634 4452
Advertisements 01-634 4202

RHYTHM GENERATOR

BY BRICE WARD

PROBABLY the simplest rhythm generator is the old fashioned metronome. This device maintains the player's tempo but it cannot emphasise the down beat or create any special effects.

Down beat enhancement can be achieved electronically but for more entertaining rhythm accompaniment it is more satisfying to tie the output of an electronic metronome to electronic percussion generators in a selected sequence or rhythm pattern such as Waltz, Cha-cha, etc.

All commercially available switched rhythm generators have fixed rhythms which cannot be changed except by rewiring the switches. The generator to be described has no such limitations, it can produce any rhythm pattern of 16 pulses, for a total of 64,000 patterns, to be used to drive any one of eight percussion generators. Details for setting up the common rhythm patterns will be given.

Four time signature switches select 4/4, 3/4, 6/8 or 9/8 time for the 16 available pulses and when programming a rhythm pattern the pulse order can be monitored using a Minitron indicator. Because circuit layout is not particularly critical detailed constructional information has been omitted and instead use has been made of photographs annotated where necessary, to provide rudimentary guidelines for assembly.

BLOCK DIAGRAM

Fig. 1 shows the block diagram for the Rhythm Generator. The tempo generator is an assymetrical astable multivibrator. It will start when power is applied and run at all times from that point on. The frequency is controlled by the tempo control VR1.

The output of this generator is fed to a divide by four circuit. This expedient was used to keep the size of the tempo generator components to reasonable levels and insure more reliable operation of that part of the circuit. The tempo generator runs then at an effective 64 beats per measure.

The four bit binary counter is used to generate 16 binary numbers which are decoded for the address information (storage address) and applied to IC6 for decoding and application to the Minitron indicator. IC5 decoding chip is used to supply reset pulses to the counter for 9 and 12 counts giving 9/8 time and 3/4 or 6/8 time respectively.

The step generator is switched to the input of the counter when the "Stop/Run" switch is placed in the "Stop" position. The divide by four output is removed at that time and the counter can be manually stepped from 0 through 15.

MEMORY CHIPS

The storage section for the programmed rhythms is made up of two SN7489, 64 bit bipolar memory chips (IC7/IC8). Each of these contains 64 flip-flops capable of storing a binary 0 or 1 (0 volts or 4 volts respectively). The particular group of four flip-flops selected per chip (eight for both chips) is controlled by the address lines which get their information from the counter. Thus 16 registers of eight bits each are available.

Each of these 16 registers is operated or selected in turn when the counter is running or being manually stepped and the contents of each can be controlled by the input switches to store either a binary 0 or 1. The actual output of each bit is inverted and is reoriented by the output gates, IC9/IC10.

Besides the address lines, input lines and output lines, there is a "chip select" and a "write" line.

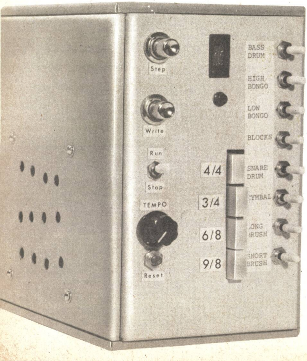

Cover photograph by courtesy of SPECTRUM COLOUR LIBRARY

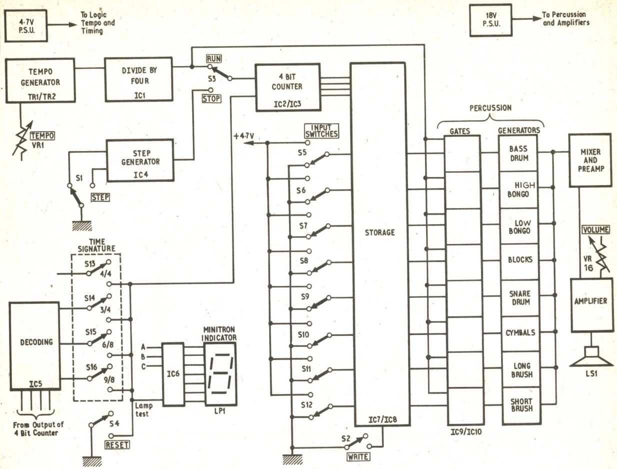

Fig. 1. Block diagram of rhythm generator

The chip select line is permanently grounded in this application because it simply makes the output available. The "write" line is used to write new information into storage when programming the rhythm generator. Setting the input switches as desired (S5 through 12) and pressing the "Write" switch will cause the new information to be stored, otherwise, the input does not effect the condition of the storage locations.

The output of the instrument gates is controlled by the output of the storage section and the divide by four counter. The result is a positive pulse of voltage initiated when the counter changes state if, in the new count position, a "1" has been stored for that instrument.

- ***Rhythms can be programmed by the user***
- ***Eight percussion generators***
- ***Can produce any 16 pulse rhythms up to 64,000***
- ***Four time signature switches for 4/4, 3/4, 6/8 or 9/8 measures***
- ***Pulse order can be observed using a Minitron Indicator***

PERCUSSION GENERATORS

The percussion generators make use of various circuits to generate the sounds of drums, bongos and so forth.

The bass drum generator, for example, contains an input amplifier which converts the 5 volt input pulse to 18 volts, shapes it and applies it to a twin-T ringing oscillator. The circuitry for the bongos and blocks is similar.

The snare drum, cymbal and brushes make use of a noise diode the output of which is shaped and filtered, mixed with some basic frequency and applied to the mixer. The first four instruments are applied to a single f.e.t. stage. The final four are applied to individual f.e.t. stages and the output of these five f.e.t.s is applied to a source follower as an output stage to the amplifier.

The output of the 18 volt power supply is regulated to reduce hum and noise while the 4·7V supply is held reasonably level with a Zener diode. The volume control, VR16, is located on the back panel of the complete instrument.

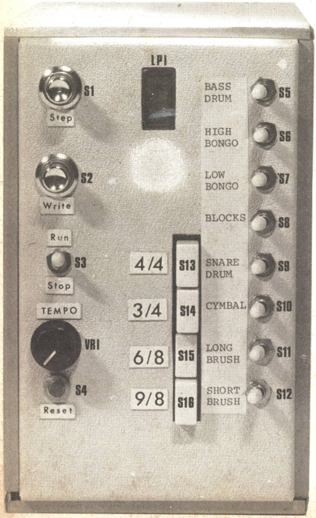

COMPONENTS . . .

TEMPO, TIMING AND LOGIC

Resistors

R1 1kΩ
R2 22kΩ
R3 15kΩ
R4 1kΩ
All 10% ½ watt carbon

Capacitors

C1 0·01µF ceramic 100V
C2 10µF elect. 25V
C3–C6 0·01µF polyester (4 off)

Integrated Circuits

IC1–IC3 SN7473 (3 off)
IC4 SN7400
IC5 SN7420
IC6 SN7447
IC7–IC8 SN7489 (2 off)
IC9–IC10 SN7402 (2 off)

Transistors

TR1–TR2 BC108

Switches

S1–S2 Single pole change over, break before make push-button.
S3 Single pole change over miniature toggle
S4 Single pole change over, break before make push-button
S5–S12 Single pole change over miniature toggle (8 off)
S13–S16 Bank of four, four pole change over switches
All switches available from Home Radio

Potentiometer

VR1 250kΩ carbon lin.

Lamp

LP1 Minitron 3015F 7 segment indicator

Miscellaneous

Contil Mod 2B case (West Hyde Developments)
2 plug in Veroboards 5·1in×3·744in, 0·1in matrix to suit 32 contact edge connectors, type B

POWER SUPPLY UNIT

Resistors

R5 7Ω 2W
R6 270Ω ½W

Capacitors

C7 2,000µF elect. 25V
C8 1,000µF elect. 15V

Transistors

TR3 2N3054

Diodes

D1 ZL4·7 4·7V Zener 1W
D2 ZL18 18V Zener 500mW

Bridge Rectifiers

D3–D6 MDA 942A1 Motorola
D7–D10 MDA 942A1 Motorola

Transformer

T1 Pri-240V, Sec. 1 18V, 0·35A; Sec. 2 6·3V 0·7A (Henry's Radio)

Miscellaneous

FS1—200mA cartridge fuse S17–Double pole main toggle switch

BASS DRUM

Resistors

R7	4·7k Ω	R13–R14	56k Ω (2 off)
R8	1M Ω	R15	1·2M Ω
R9	2·7k Ω	R16	100 Ω
R10	82k Ω	R17	68k Ω
R11	2·2k Ω	R18	10k Ω
R12	2·7k Ω		

All 10% ½W carbon

Capacitors

C9	0·1µF
C10	0·02µF
C11–C15	0·1µF (5 off)

Potentiometers

VR3	5k Ω miniature preset
VR4	50k Ω miniature preset

Transistors

TR4–TR5 BC109

HIGH AND LOW BONGOS

Resistors

R19–R20	4·7k Ω (2 off)
R21–R22	2·7k Ω (2 off)
R23–R24	1M Ω (2 off)
R25–R26	27k Ω (2 off)
R27–R28	2·2k Ω (2 off)
R29–R30	6·8k Ω (2 off)
R31–R34	56k Ω (4 off)
R35–R36	1·2M Ω (2 off)
R37–R38	68k Ω (2 off)
R39–R40	100 Ω (2 off)
R41–R44	82k Ω (4 off)

All ½W 10% carbon

Capacitors

C16–C17	0·01µF (2 off)
C18–C23	0·015µF (6 off)
C24*	0·033µF (High bongo only)
C25*	0·1µF (Low bongo only)
C26–C27	0·05µF (2 off)
C28–C29	0·01µF (2 off)

Transistors

TR6–TR9 BC109 (4 off)

Potentiometers

VR5–VR6	5k Ω miniature preset (2 off)
VR7–VR8	50k Ω miniature preset (2 off)

BLOCKS

Resistors

R45	4·7k Ω	R50	68k Ω
R46–R47	27k Ω (2 off)	R51–R52	22k Ω
R48	150k Ω	R53	15k Ω
R49	390k Ω	R54	2·7k Ω

All 10% ½ watt carbon

Capacitors

C30	0·1µF
C31–C33	0·002µF (3 off)
C34	0·1µF
C35	500pF

Potentiometers

VR9 50k Ω miniature preset

Transistors

TR10–TR12 BC109 (3 off)

SNARE DRUM

Resistors

R55–R56	4·7k Ω	R61	12k Ω
R57	3·3k Ω	R62	120k Ω
R58	1k Ω	R63	2·2k Ω
R59	120k Ω	R64	3·9k Ω
R60	100k Ω	R65	15k Ω

All ½ watt 10% carbon

Capacitors

C36	1µF elect. 15V
C37	10µF elect. 15V
C38	0·1µF
C39	0·0022µF
C40	0·022µF
C41	220pF
C42	1·5µF elect. 15V
C43	500pF

Potentiometer

VR10 100k Ω miniature preset

Transistors

TR13–TR14 BC109 (2 off)

Diodes

D11	1N914
D12	Z1J (Semitron)

Inductor

L1 OL130 transformer (Henry's Radio)

CYMBAL

Resistors

R66	3·3k Ω	R73	120k Ω
R67	10k Ω	R74	100k Ω
R68	470kΩ	R75	120k Ω
R69	47k Ω	R76–R77	10k Ω
R70	10k Ω	R78	2·2k Ω
R71	1·5M Ω	R79	1M Ω
R72	680 Ω	R80	10k Ω

All ½ watt 10% carbon

Capacitors

		C47	0·05µF
C44	2µF elect. 15V	C48	1µF elect. 15V
C45	8µF elect. 15V		
C46	0·1µF	C49	0·05µF

Transistors

TR15–TR17 BC109 (3 off)

Diodes

D13–D14	1N914 (2 off)
D15	Z1J (Semitron)

Inductor

L2 OL130 transformer

LONG BRUSH

Resistors

R81	4·7k Ω	R88	100k Ω
R82–R83	22k Ω	R89–R90	10k Ω
R84	1·2M Ω	R91	2·2k Ω
R85	390 Ω	R92	150k Ω
R86	100k Ω	R93	82k Ω
R87	68k Ω		

All ½ watt 10% carbon

Capacitors

		C53	0·01µF
C50	4µF elect. 15V	C54	2·5µF elect. 15V
C51	0·1µF		
C52	0·02µF	C55	0·22µF

Transistors

TR18–TR20 BC109 (3 off)

Diodes

D16	1N914	D17	Z1J (Semitron)

SHORT BRUSH

Resistors

R94	4·7k Ω
R95–R96	22k Ω (2 off)
R97	1·2M Ω
R98	390 Ω
R99	100k Ω
R100	68k Ω
R101	100k Ω
R102–R103	10k Ω (2 off)
R104	2·2k Ω
R105	150k Ω
R106	82k Ω

All ½ watt 10% carbon

Capacitors

C56	1µF elect. 15V
C57	0·1µF
C58	0·02µF
C59	0·01µF
C60	2·5µF elect. 15v
C61	0·22µF

Transistors

TR21–TR23 BC109 (3 off)

Diodes

D16	1N914
D17	Z1J (Semitron)

MIXER AND PRE-AMPLIFIERS

Resistors

R107	4·7k Ω
R108–R112	2·2k Ω (5 off)
R113	10k Ω
R114	2M Ω
R115	10k Ω
R116	2·2k Ω

All ½ watt 10% carbon

Capacitors

C62–C66	0·01µF (5 off)
C67	0·05µF

Potentiometers

VR11–VR15 2·5M Ω miniature preset (5 off)

Transistors

TR24–TR29 2N3819 (6 off)

AMPLIFIER

Resistors

R117	330k Ω	R121	39k Ω
R118	39k Ω	R122	3·3k Ω
R119	18k Ω	R123	22 Ω
R120	150k Ω	R124	1k Ω

All ½ watt 10% carbon

Capacitors

C68	0·1µF	C71	0·1µF
C69	0·002µF	C72	50µF elect. 15V
C70	500µF elect. 15V		

Potentiometer

VR16 25k Ω

Integrated Circuit

IC1 PA263 (Jermyn)

Loudspeaker

LS1 8 Ω, 5 watt 4in loudspeaker

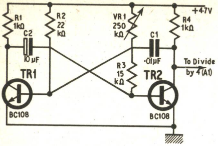

Fig. 2. Circuit of tempo generator

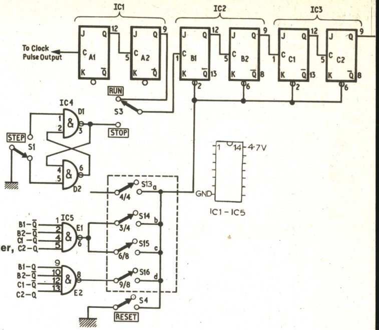

Fig. 3. Circuit of divide by four, four bit counter, time signature decoder and step generator

TEMPO GENERATOR

The circuit for the tempo generator is shown in Fig. 2. If the multivibrator capacitors were of equal value, the output would be a symmetrical square wave but C1 is 1/1000 the value of C2 creating a pulse of very short duration at a repetition rate determined largely by the value of C2. The output period is made variable by VR1 and gives a sufficient range of tempo to cover most requirements.

The output feeds a divide by four counter stage (IC1) composed of flip-flops A1 and A2 as shown in Fig. 3. The output of this counter is a symmetrical square wave with a period variable from 2 seconds to 25 milliseconds. This output is the basic timing waveform for the entire system.

FOUR BIT COUNTER

The four flip-flops labelled B1, B2, C1 and C2 (IC2, IC3) make up a four bit binary counter. Drive for this counter is obtained either from the output of the divider in the "Run" position of S3, the "Stop/Run" switch, or from the bistable latch (D1 and D2) in the "Stop" position. This allows the counter to be stepped through the count sequence manually with S1, the "Step" switch.

All four flip-flops can be reset by grounding the reset pins (2 and 6 of each chip). To reset the counter in the "Stop" position, the "Reset" switch S4 is pressed. This forces the counter to binary 0000.

In the 4/4 position of the "Time Signature" switch S13, the counter will count through 16 counts and automatically return to 0000. In the 3/4 and 6/8 positions, the counter must be forced back to 0000 after 12 counts.

This is done by applying the $\overline{Q}$ outputs of B1 and B2 and the Q outputs of C1 and C2 to the input of NAND gate E1 (IC5). When this count is reached, the output of that gate will go immediately to 0 and the counter will be reset.

For 9/8 time, only 9 counts are allowed and the counter is then reset with NAND gate E2.

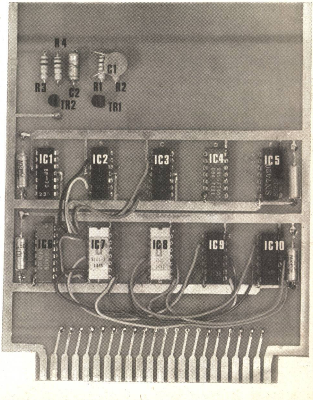

Prototype p.c.b. including tempo, timing and logic assembly. Four 0·01μF capacitors must be included for decoupling the chip supply lines

STORAGE, OUTPUT AND INDICATOR

Fig. 4 shows the logic diagram for the storage, indicator and output gates. The four counter Q outputs from IC2/IC3 are applied to the A, B, C and D inputs of each of the memory chip address select lines.

S5 through S12 are the instrument input switches and S2 is the "Write" switch. The chip select inputs (pins 2) on both IC7 and IC8 are permanently grounded which simply means that the output will always be available.

The output of these storage or memory chips is applied to the inputs of eight NOR gates (IC9/IC10) and gated with the output of the divider IC1 to give a positive pulse out for each position and time segment that an instrument is to sound.

IC6 uses outputs A, B and C of the counter to decode the correct sequence of grounds to be applied to the Minitron indicator.

LOGIC ASSEMBLY

Although the prototype used plug-in printed circuit boards, 0·1in plug-in Veroboards can be successfully substituted for the logic and percussion circuitry.

While no constructional details are included sufficient information for this should be gleaned from the photograph of the prototype logic card showing the disposition of the tempo generator and logic chips. Note carefully the use of four 0·01μF capacitors connected between the supply and ground lines. These should be added to prevent spurious triggering.

Point to point wiring on the board should be carried out according to the circuit diagrams given. It really boils down to wiring between the i.c. pin numbers shown and taking off external wiring, such as to control switches and percussion generators, to those copper strips which will mate with the Veroboard's edge connector.

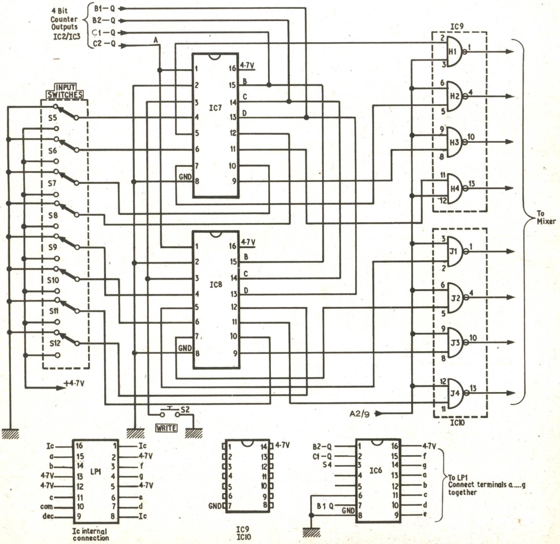

Fig. 4. Circuit for storage, lamp driver and percussion gates

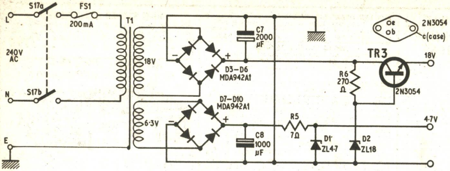

Fig. 5. Circuit of power unit

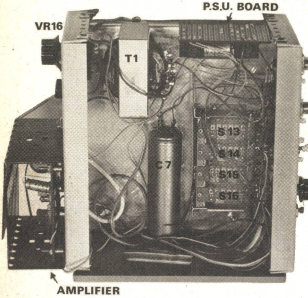

Part of the component assembly within the case. The amplifier is outboard mounted and the speaker connected to the removed plate

Once connections have been made and verified breaks in the copper should be made where appropriate. Finally check all wiring according to the circuits and make sure that there are no solder bridges or loose bits of wire around to cause future trouble.

POWER SUPPLY

The power supply is made up on a $2\frac{1}{2}$in × $2\frac{1}{2}$in, 0·15in matrix Veroboard. With the transformer and large electrolytic C7 these are all finally mounted on the Contil case chassis plate. With the wiring completed for this connect to the mains and ensure that the line output voltages are correct.

At this point it is a good idea to cut and drill those holes for the control panel switches and indicator. The locations for these are indicated in the photograph.

The 4·7V power lines can now be connected to the logic board edge connector and the appropriate connections to the control panel switches made. A number of tests can now be made.

First plug in the board and switch on. In the "Stop" position of S3, press the "Reset" button. The Minitron indicator should show a figure eight. This is a lamp test feature and assures that all seven segments of the indicator work correctly. With the switch released the indicator should read 0. With S3 now in the "Run" position the Minitron indicator should go through 0 to 7 repetitively. The "Tempo" control can slow this process right down so that single digit changes can be easily observed.

If these tests are satisfactory, the unit is sound to this point. There are other tests that could be made but they would require additional instruments and are not really worth including.

Next month details for the percussion generators, mixer and amplifier will be given.

PA and PE
Sound '74
INTERNATIONAL

The Public Address Engineers' Exhibition, Bloomsbury Centre Hotel, Russell Square, London WC1
12-14th March, 1974.
Tuesday, Wednesday 10 a.m. to 6 p.m. Thursday 10 a.m. to 5 p.m.

Visit the Practical Electronics Stand and see our latest audio equipment (including the Rhythm Generator) designed specially for the home constructor.
Tickets available from Editorial Dept., Practical Electronics, Fleetway House, Farringdon St., London E.C.1. Please enclose S.A.E.

PRICES INCLUDE VAT

SUPERSOUND 13 HI-FI MONO AMPLIFIER

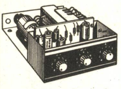

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz—30KHz ± 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8–15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3in high × 6in wide × 7½in deep. A.C. 200/250V.

PRICE £11·60 P. & P. 40p.

DE LUXE STEREO AMPLIFIER

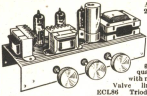

A.c. mains 200–240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 × ECL86 Triode Pentodes. 1 × EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300m/v for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w × 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price £9·90.** P. & P. 50p.

NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 7½V and 9V and 12V at 1 amp on load.
Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6″ × 3½″ × 2¼″. Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £5 P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2⅝in × 3in approx. **28p** pair. P. & P. 6p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL × 3½inW × 3inD. Price **£2·31.** P.&P. 40p

MAINS TRANSFORMER. For transistor power supplies.
Pri. 200/240V Sec. 9-0-9 at 500mA. **£1·10** P. & P. 25p.
Pri. 200/240V Sec. 12-0-12 at 1 amp. **£1·21** P. & P. 26p.
Pri. 200/240V Sec. 10-0-10 at 2 amp. **£1·82** P. & P. 35p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9–18V. Battery or from H.T. line 200/300V. Frequency response 15Hz–25KHz. Gain 26dB. Solid encapsulation size 1⅜ × 1½ × ⅜in. Brand new — complete with instructions. Price **£1.** P. & P. 15p.

3 REFERENCE ENCYCLOPEDIAS FOR ELECTRONIC ENGINEERS AND DESIGNERS, covering between them, transistor characteristics, diode and transistor equivalents. Many thousands of up-to-date European types listed.

Diode Equivalents	**80p**	
Transistor Equivalents	**90p**	
Transistor Characteristics	**£1·20**	
All three together	**£2·60**	POST FREE

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY **40p.** Post 5p.

8 pole 3 way 2 bank low loss Yaxley type switches 1¼″ sections. Standard spindle. 2 switches **66p** + 10p P. & P.

NEW ISSUE—Thyristor, Triac, Diac, etc. encyclopedias **95p** Post Free.

FOR PERSONAL CALLERS ONLY! Limited number of Stereo Radiogram chassis covering LW/MW/FM bands. Mono radio and stereo gram. Overall size approx. 16½″W, 6¾″H, 8″D. 4 Watts per channel output. ONLY **£16·50.**

RECORD PLAYER BARGAINS

Mains models. All brand new in maker's packing.

LATEST B.S.R. C109/C129 AUTOCHANGER UNITS. With latest stereo/mono compatible cartridge **£7·60** plus 60p P. & P.

B.S.R. MODEL C123 Auto unit deluxe with stereo cartridge. **£8·60** plus 60p P. & P.

PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12½in × 14¼in × 3½in high (approx. 7½in high, including rigid smoked acrylic cover). P. & P. 70p. **Now only £4·95**

LATEST ACOS GP91/1SC Mono Compatible Cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. **£1·50.** P. & P. 15p.

SONOTONE 9TAHC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY **£2·30.** P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. **£2·80.** P. & P. 15p.

LATEST RONETTE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. **£1·63.** P. & P. 15p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono/stereo records on mono equipment **£1·50.** P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. × 3 d. × 6 h. Ready built and tested. PRICE **£4·40.** P. & P. 50p. ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE **£5·85.** P. & P. 60p.

SPECIAL OFFER!!

HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16in high × 10½in wide × 6in deep. Fitted with E.M.I. Ceramic Magnet 13in × 8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £9·25 Carr. 75p.

CABINET AVAIL. SEPARATELY **£4·95.** Carr. 65p. Also available in 8 ohm with EMI 13in × 8in. bass speaker with parasitic tweeter. **£7·15.** Carr. 75p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3·5 watts. Volume and tone controls. Chassis size only 7in. wide × 3in. deep × 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.

OUR ROCK BOTTOM BARGAIN PRICE **£3·30** P. & P. 40p

LOUDSPEAKER BARGAINS

5in 3 ohm **£1·25,** P. & P. 15p. 7 × 4in 3 ohm **£1·40,** P. & P. 20p. 10 × 6in 3 or 15 ohm **£2·10,** P. & P. 30p. E.M.I. 8 × 5in 3 ohm with high flux magnet **£1·70,** P. & P. 20p. E.M.I. 13½ × 8in with high flux ceramic magnet with parasitic tweeter 3, 8, or 15 ohm **£3·50.** P. & P. 30p. E.M.I. 13 × 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network **£4·65.** P. & P. 30p.

EMI CERAMIC MAGNET HEAVY DUTY TWEETER. pprox. 3½in. Av. 3 or 8 or 15 ohms. **£1·25** plus 20p p. & p.

BRAND NEW. 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly **£7·50.** Guitar models: 25w **£7·50.** 35w **£9·35.** P. & P. 45p each.

SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10″ TWIN CONE LOUDSPEAKERS. With large ceramic magnet and plasticised cone surround. 8 ohm impedance.

£3·70. P. & P. 35p.

Also available specification as above but size 10″ × 6″ **£2·70** and size 8″ round **£2·60** P. & P. 35p.

LIMITED NUMBER EMI 2¼″ 8 ohm Tweeters. Mounted on flat bracket, size 2½″ wide × 7¾″ long. Ex equipment but new and tested. **70p** per pair plus 15p P.& P.

12in "RA" TWIN CONE LOUDSPEAKER

10 watts peak handling. 3, 8 or 15 ohm, **£2·45.** P. & P. 36p.

35 ohm SPEAKERS 3″. ONLY **70p.** P. & P. 25p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11¾in × 14$\frac{11}{16}$in × 1$\frac{7}{16}$in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz–20kHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only **£6·55** each. P. & P. 34p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam earmuffs. Wired and fitted with standard stereo ¼in jack plug. Frequency response 30–15,000Hz. Matching impedance 8–16 ohms. Easily converted for mono. PRICE **£3·30.** P. & P. 25p.

HAVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT

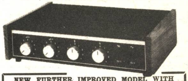

NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response ± 3dB 12–30,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth ± 3dB 12–15,000Hz. Bass boost approx. to ± 12dB. Treble cut approx. to −16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1·0 amp. Overall size—12″ wide × 8″ deep × 2¾″ high.

Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES	AMPLIFIER KIT,	**£11·55**	P. & P. 25p.
	(Magnetic input components 33p extra)		
	POWER PACK KIT,	**£3.30**	P. & P. 35p.
	CABINET,	**£3·30**	P. & P 35p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, **£23·10.** Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.

3-VALVE AUDIO AMP. HA34 MK II

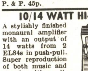

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7½in w. × 4in. d. × 4¾in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4½ watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£5·50.** P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **£4·50.** P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

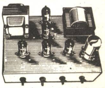

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3–15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet **15p** plus S.A.E. (Free with parts). **All parts sold separately.** ONLY **£8·80.** P. & P. 60p. Also available ready built and tested **£12·10.** P. & P. 70p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. **Our price £1·10 yd.** length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

Open 9-5.30 Mon. to Fri.
9-5 Sat. Early closing Wed.

A few minutes from South Wimbledon Tube Station.

HARVERSON SURPLUS CO. LTD.

Dept. PE, 170 High St., Merton, London, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

TRAMPUS

MONEY BACK IF NOT SATISFIED
all brand new, full spec. Top grade.
Free fabulous NEW catalogue. Send S.A.E.

red+ data 1/8" pin source **LED's 17p!** **Til209** & clip 22p
BIG 1/4" panel clip & RED LED 28p. GREEN & clip 59p
INFRA RED LED £1. IC photo amp 44p. & amp/switch 85p

Digital Display LED 1/3" 0-9DP.DIL. £1·69
Minitron type 0-9dPDIL £1·19. SOCKETS 13p.

Calculator batt/mains from £25

IC DIGITAL CLOCK CHIPS.
Texas etc with 4 displays £12. 6 displays & chip £14. pcb £1·49
Mostek date & alarm chips with 6 displays £19.
kit: All parts & case. National chip. 4 digit £20. 6 x £23.

with data **integrated circuits**

GAS sensor TGS 308 £2
KIT £4·69
fully built £8

741: 8pin 29p, to99 & 14pin 27p 748 33p 709 21p
710 35p 723 59p. 555 timer 79p ZN414 rx. £1·10
703 rf if 28P mc1310 & led £2·76 mc1339 £1·20 TAD100 & if £2
1AMP+ REGULATOR 7805,5(&7-20)V. also 12 & 15V £1·49
AUDIO AMPS: mfc4000 50p; 1&2W £1·19; 3W £1·29; 6W---

gates 7400 etc 16P 7413 32P 7447 £1·25
7470/72 32P 7474/76 39P 7490 63P
7492 69P 74121 49P. & all others in cat.
NEW 16pin counter/driver 90/47 £2·25

74n TTL low prices.

DALO p.c.b. PEN 69p.
DIL SOCKETS: Profesional / gold P. Pins hi or lo Profile 8,14,16 Pin 13p

2N3055 33p. four £1. **BC107, BC108, BC109 all 7p ea**

IN914 3p ZENERS BZY88 8p. 1A RECTS 50v 3½P 400v 5p. BRIDGE 20p
FETS: 2N3819 19p 2N3823E 20p 4416E 25P BC182/3/4 10P
BC212/3/4 11p BCY70 13p BD131/2 35p ea. BFY51/2/3 15p TIS43 25p
2N2926 Oy 7p 2N3053 15p 2N3702/3/4/5/6/7/8/9/10/11 all 9p ea
2N3904/6 14p HEATSINKS 5f/TO5 18f/TO18 5p. TO3: 4YL 29p TV3 14p
CAPACITORS 25v10,50,100uf 5p. DISCS 4p. PRESETS 5p. CARBON-POTS 11P. Switch+11P. Dual 55P. ULTRASONIC TRANSDUCERS £2 ea
FLUORESCENT LIGHTS, 8W. 13" 12VOLT £2·59

Trampus electronics
ADD 10% VAT TO PRICES. P.&P. 10P. CWO.
P.O. BOX 29, BRACKNELL, BERKS.

TRANSISTORS

AC126	14p	AF180	45p	BC158	14p	BF180	32p	BFY51	21p
AC127	16p	AF181	43p	BC159	14p	BF181	32p	2N3053	23p
AC128	14p	AF239	44p	BC177	20p	BF184	35p	2N3054	57p
AC141K	24p	BC107	12p	BC183L	14p	BF185	35p	2N3055	60p
AC142K	24p	BC108	10p	BC184L	12p	BF186	45p	TIP29	66p
AC176	20p	BC109	12p	BC187	22p	BF194	15p	TIP30	75p
AC187	18p	BC113	25p	BC294	16p	BF195	15p	TIS91	48p
AC187K	24p	BC114	30p	BC440	50p	BF196	15p		
AC188K	24p	BC115	20p	BC460	68p	BF197	15p		
AD142	45p	BC116	20p	BD124	80p	BF200	32p		
AD149	45p	BC117	15p	BD131	60p	BF258	40p		
AD161	34p	BC125	14p	BD132	60p	BF259	40p		
AD162	34p	BC142	25p	BD139	63p	BF337	23p		
AF115	21p	BC143	25p	BDX32	£2·00	BFT42	44p		
AF116	21p	BC147	13p	BF115	25p	BFT43	44p		
AF117	21p	BC148	13p	BF121	35p	BFX84	40p		
AF118	49p	BC149	13p	BF158	19p	BFX88	30p		
AF139	40p	BC154	20p	BF167	20p	BFX89	67p		
AF178	45p	BC157	14p	BF179	39p	BFY50	21p		

DIODES AND AND RECTIFIERS

OA91	7p
OA202	9p
1N4148	4p
BY127	11p
1N4006	8p

RESISTORS METAL FILM 5% TOL.

⅛W, ¼W, ½W, E12 values to 2·7M all **1p** each.
1W to 10M E12 values **3p** each; **2W** to 10M E12 values **4p** each; **5W** wire wound, **10W** wire wound **8p** and **9p** each. See Cat. for values.

POTENTIOMETERS-CARBON TRACK

5K, 10K, 25K, 50K, 100K, 250K, 500K, 1M.

Log or lin less switch	11p
Log or lin with switch	23p
Dual log less switch 250K, 500K, 1M, 2M, only	39p
Dual lin less switch 5K, 10K, 25K, 50K, 100K, only	39p
Dual log with switch 10K, 100K, 250K, 500K, 1M only	55p

JACK PLUGS AND SOCKETS

Standard insulated **11p**; Standard screened **18p**; Stereo insulated **22p**; Stereo screened **30p**; 3·5mm insulated **8p**; 3·5mm screened **12p**; Standard socket switched **17p**; Stereo socket switched **21p**; 3·5mm socket switched **6p**; Standard line socket **15p**; Stereo line socket **22p**; 3·5mm line socket **10p.**

PHONO-D.I.N. PLUGS AND SOCKETS

Phono plug insulated **7p**; Phono plug screened **11p**; Phono line socket screened **12p**; Metal coax plug **8p**; 2, 3, 5 pin 180°, 240°, D.I.N. plugs **12p**; 4, 6, 7 pin plugs **15p**; 2, 3, 5 pin 180° line sockets **13p**; 2, 3, 5 pin 180° chassis sockets **7p.**

CABLES AND SCREENED WIRES

Min. mike cable single **7p**/metre; Min. twin mike cable **11p**/metre; Pick up wire single **7p**/metre; Pick up wire twin **11p**/metre; Stereo screened twin **10p**/metre; 4 core individually screened **14p**/metre; Speaker wire twin coded **6p**/metre.

E. A. HALL (ELECTRONICS)

The Manse, Little Brington, Northampton NN7 4HX

Mail Order Only. C.W.O. Postage and packing 10p per order. Detailed Catalogue 6p. Please add V.A.T. on total order incl. postage and packing. Many other items in our catalogue.

Which type of Shopper are YOU?

Shopper A, enthusiastic to a fault, is determined to track down the components he needs for his next project. We'll overlook the fact that he'll probably end up with pneumonia!

Shopper B learnt his lesson long ago—now he simply sits back and orders all his requirements from his Home Radio Components' catalogue. The worst that could happen to him is that, being so absorbed in the catalogue, he might burn his toast! That's a small price to pay though for the comfort, convenience and economy of ordering components this way.

You too can join the blissful "B's"—there must be about 100,000 of them! To get your catalogue (240 large pages packed with 6,800 items, 1,770 of them illustrated) simply post the coupon with your P.O. or cheque for 77p. (55p plus 22p post and packing.) Every catalogue contains 5 vouchers, each worth 10p when used as directed. **Send now.**

Please write your Name and Address in block capitals

Name ______________________

Address ______________________

____

____

____

HOME RADIO (Components) LTD. Regd. No. 912966 London
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

FLUORESCENT LAMP INVERTER

By C. J. MILLS

High efficiency light source from a 12V d.c. supply

WITH power cuts an annual recurrence the construction of an inverter to drive a fluorescent lamp from a 12V d.c. supply, such as a car battery, is a worthwhile investment.

Although one basic circuit is described, with minor component changes the inverter is capable of driving either an 8W, 13W or 20W lamp.

HIGH FREQUENCY OPERATION

The choice of an operating frequency above 20kHz for the inverter means a reduction in transformer size, increased lamp efficiency and the elimination of audible whistles.

The unit incorporates transistor protection against lamp removal by automatically stopping the oscillator. Diode protection against supply polarity reversal is also included.

CIRCUIT DESCRIPTION

The circuit shown in Fig. 1 is developed from the well-known Hartley oscillator. The primary winding of the pot core transformer T1 is in the emitter circuit so that the collector of the transistor TR1 can be earthed. This arrangement means that the feedback winding must give a greater voltage than the primary winding and therefore has more turns.

The feedback winding provides the drive to the transistor base via a limiting resistor R1, one of the lamp heaters and C3.

The voltage across the secondary winding is sufficient to strike the tube and the leakage inductance in conjunction with the base resistor limits the tube running current. This is necessary because the fluorescent tube tends to maintain a constant voltage.

Heater current for the tube is provided at one end by the drive current and at the other by a few extra turns on the secondary winding. The bypass capacitor across the transistor limits the peak collector emitter voltage to a safe value. This is not normally required in the 8W version.

POSITIVE AND NEGATIVE EARTH

If the circuit is being constructed in a separate metal case and used with a positive earthed supply system the transistor can be mounted directly on to the case. If the supply is negative earthed a mica washer and plastic bushes should be used to insulate the transistor which should be protected from possible shorts to earth by a plastic cover.

The circuit board should now be cut and drilled to fit the case and the components mounted as shown. The transformer leads can be connected to the printed circuit via pins and further pins can

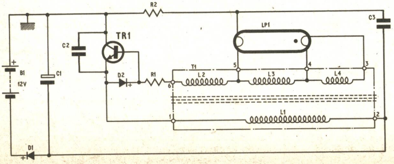

Fig. 1. Circuit diagram of fluorescent lamp inverter

A P.E. BLUEPRINT FEATURE

be used for connecting leads to the transistor and the fluorescent lamp.

When the wiring-up is completed the circuit should be carefully checked before it is connected to the voltage supply to ensure that both diodes and the transistor are connected the right way round and that copper breaks in the Veroboard have been cleanly cut and that there are no shorts between strips due to surplus solder.

TESTING

Testing should start with a low voltage battery or a gradually increasing voltage supply with a series ammeter to check that the current consumption is not excessive and that the transistor is not overheating.

The fluorescent tube must be connected to complete the bias circuit and if the circuit is oscillating a glow will be seen from the heaters at the ends of the tube. When the full voltage is applied the lamp should strike and light up but during preliminary testing the lamp will strike easier if a fine wire is stretched between the metal end caps and connected to one of the heater pins.

If the circuit does not oscillate L1 may be reversed or there may be some shorted turns in the transformer. When operating normally with a 13 watt tube this inverter consumes about 1·4 amps at 12 volts. This current and the light output can be varied slightly by small adjustments to R1 and/or C3.

PRECAUTIONS

All metal parts, including the metal end caps on the tube, should be earthed and the fine wire connected to the heater pin during tests should be removed. The voltage across the tube is high enough to provide a nasty shock and should be treated with respect.

TRANSFORMER WINDING

The winding order is identical for the 8 watt, 13 watt or 20 watt versions of the inverter. Start by winding the primary L1 on the bobbin according to the relevant data given in the Components List. Lead ends on each coil should be colour coded for later identification.

Insulate with plastic adhesive tape and then add L2 again insulating the winding with tape. Finally add L3 and L4. The direction of winding for all coils is the same.

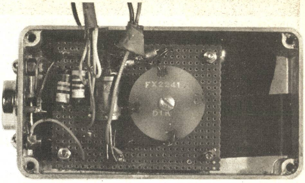

Interior assembly of 13W inverter

Before bolting the two halves of the Ferroxcube pot core together onto the Veroboard, two paper spacing washers should be cut and fitted between them.

CONSTRUCTION

The Ferroxcube transformer and majority of circuit components are mounted on a 2in × $2\frac{1}{4}$in, 0·1in matrix Veroboard with the transistor connected to case.

The mounting of the fluorescent lamp will depend on the application and to a certain extent on the constructor's preferences. For example an 8 watt tube can be used in a caravan mounted flush with the roof and components separate or on a channel support with the components mounted in the channel.

Alternatively an attractive table or hanging lamp can be constructed with the fluorescent lamp in a vertical Perspex tube with the components in a suitable case at one end of the tube.

Another idea is to construct a portable lamp using two 6V lantern batteries in a suitable case with the lamp and reflector mounted on the outside. Leads can then be connected via a plug and socket for external battery supplies such as a car battery. This makes an ideal camping light but the lantern batteries should be isolated from the car battery by diodes or a switch. ★

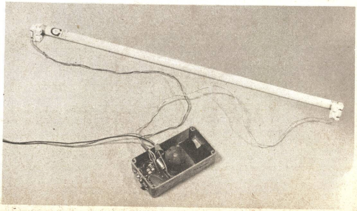

The 13W inverter with output leads terminated with clips and lamp

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0–260V

All Types

SHROUDED TYPE

0·5 KVA (2½ amp)	**£10·00**
1 KVA (5 amp)	**£14·70**
2 KVA (10 amp)	**£28·10**
3 KVA (15 amp)	**£31·25**
4 KVA (20 amp)	**£72·50**
37·5 amp	**£102·50**

CARRIAGE AND PACKING EXTRA

L.T. TRANSFORMERS

All primaries 220–240V

Type No.	Sec. Taps	Price	Post
1	30, 32, 34, 36V at 5A	**£4·70**	+45p
2	30, 40, 50V at 5A	**£6·90**	+60p
3	10, 17, 18V at 10A	**£5·00**	+50p
4	6, 12V at 20A	**£6·50**	+60p
5	17, 18, 20V at 20A	**£7·30**	+60p
6	6, 12, 20V at 20A	**£6·90**	+60p
7	24A at 10A	**£5·30**	+50p
8	4, 6, 24, 32V at 12A	**£7·20**	+60p
9	6 and 12V at 10A	**£3·80**	+40p

VOLTAGE CHANGING TRANSFORMER

M.f.g. to highest W.D. spec. Auto wound, and tapped 0–130–160–200–250 at least 2kVA. Can also be used as 230–240V input, 115V out for U.S.A. equipment, or reverse to obtain 240V from 115V. The ideal transformer for making up solid state constant voltage unit, by use of taps the following voltages may be obtained 30–40–50–70–90V at 10 amps. Weight 40lb, length, 260mm, height 190mm, width 230mm. In original maker's wooden case, **£8.** Carr. £1.

PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS

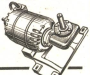

30 r.p.m. 40 lb. ins. Position of drive spindle adjustable to 3 different angles, Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of makers' price. **£7·48.**

AEI A.C. MOTOR

Smooth running, powerful, continuously rated, reversible motor. 230/250V a.c., 50 cycle 1/50 H.P., 0·25A. **£3·50** post 30p.

4 BANK 3c/o PUSH BUTTON ASSEMBLY

Black rectangular buttons. 5 units (min. order) **85p.** Post 15p.

600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. **£2·75.** Post 25p.

2000 WATT POWER CONTROL

For Power toois. Heating, Sewing Machines, Lighting, etc. **£8·00.** Post 27p.

VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp contacts. Fitted diecast case. Tested and in perfect condition **£4·75.** Post 25p.

FOOT SWITCH

Suitable for Motors, Drills, etc., etc. 5 amp. 250 volt. Price **75p.** Post 15p.

UNISELECTOR SWITCHES

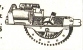

NEW **4 Bank 25 Way,** 24V d.c. operation. **£6·90.** Post 30p. **6 Bank 25 Way,** 24V d.c. **£7·90.** Post 30p. **8 Bank 25 Way,** 24V d.c. operation. **£9·50.** Post 40p.

TRIACS
GENERAL ELECTRIC POWER-GLAS TRIACS

10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC146D 10 amp, 400 PIV, **£1.** Post 5p. Type SC146E 10 amp, 500 PIV, **£1·30.** Post 5p. (Inclusive of data and application sheet.) Suitable Diac **18p.**

All Mail Orders—Callers—Ample Parking
Dept. PE3, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid **state** timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions **£6·30.** Post 30p.

INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s.
Approx. ¼ output of Hy-Lyght. Price **£12·00.** Post 50p.

HY-LYGHT STROBE MK III
For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. **£12.** Post 50p.

THE 'SUPER' HY-LYGHT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe.

- Variable speed from 1-13 flash per sec.
- Reactor control circuit producing an intense white light. ONLY **£20.** Post 75p.

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Lyght Kit including reflector **£4·75.** Post 25p.
Super Hy-Lyght Kit including reflector **£7.** Post 60p.

7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price **55p.** Post 15p.

RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Lyght or Super Hy-Lyght Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: **£18.** Post 50p. Send S.A.E. for details.

COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel. 100 watt lamp. 200/240V AC. Features extremely efficient optical system. **£18·50.** Post 50p.

6 INCH COLOUR WHEEL
As used for Disco lighting effects, etc. Price **£4.** Post 30p.

BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp.
Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb **£16.** Post £1.
Spare bulb **£7.** Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES
4ft 40 watt. Price **£5·50.** Post 30p. **2ft 20 watt, £4·25.** Post 25p. (For use in standard bi-pin fittings.)
MINI. **12in 8 watt, £1·60.** Post 15p. **9in 6 watt, £1·30.** Post 15p. Complete ballast unit and holders for 9in and 12in tube, **£1·70.** Post 25p. (9in and 12in measures approx.)

50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price **£7·75.** P. & P. 25p.

PROGRAMME TIMERS

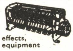

230/240V a.c. 15 r.p.m. Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays, etc. Ex equipment tested.

4 cam model.	**£2·50**	post 30p.
6 cam model.	**£3·25**	post 30p.
12 cam model.	**£4·00**	post 35p.

All prices are subject to
10% VAT. (10p in the £)
To all orders add 10% VAT to total value of goods including carriage/packaging.

SERVICE TRADING CO

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/300/500/1k/ohm **£1·15.** Post 10p.
50 WATT 1/5/10/25/50/100/250/500/1k/1·5k/ohm **£1·60.** Post 10p.
100 WATT 1/5/10/25/50/100/250/500/1k/1·5k/2·5k/3·5k/5k ohm **£2·35.** Post 15p.
Black Silver, Skirted knob calibrated in Nos. 1-9. 1½in. dia. brass bush. Ideal for above Rheostats, **22p** each.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1) Coil ohms	1	2	3	4
	52	4–6	6M	**60p***
Col. (2)	58	5–9	6 c/o	**80p**
Working	150	4–9	2 c/o	**70p***
d.c. volts	185	8–12	6M	**60p***
Col. 3	230	6–12	2 c/o	**70p***
Contracts	308	9–14	4 c/o	**75p***
Col. (4)	410	10–18	4 c/o	**70p***
Price	700	16–24	4M 2B	**60p***
	700	16–24	4 c/o	**80p***
HD =	700	15–35	2 c/o HD	**70p***
Heavy duty	700	6–12	1 c/o HD	**50p***
	700	20–30	6 c/o	**80p**
*Incl. Base	2,500	36–45	6M	**60p***
	2,400	30–48	4 c/o	**60p**
	5,800	24–26	2 c/o	**60p***
All prices	9,000	40–70	2 c/o	**60p***
incl. P. & P.	15k	85–110	6M	**60p***

6 VOLT D.C. 1 make contacts **35p.** Post 5p.
6 VOLT D.C. 2 make contacts **75p.** Post 5p.

9 VOLT D.C. RELAY
3 c/o 5 amp contacts. 70 ohm coil. **75p.** Post 5p.

12 VOLT D.C. RELAY
3 c/o 5 amp contacts. **75p.** Post 5p.

24 VOLT D.C. 3 c/o **75p.** Post 5p.

230 VOLT A.C. 'DIAMOND H' RELAYS (Unused)

Three sets c/o contacts rated at 5 amps.
PRICE: **55p.** Post 5p.

100 VOLT A.C.
2 c/o seated type, octal base **£1.** Post 10p.
24 VOLT A.C. 3 c/o **55p.** Post 5p.

CLARE-ELLIOTT TYPE RP7641 G8
Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. **70p** post paid.

HEAVY DUTY A.C. SEALED RELAYS

230/240 V. 2 c/o. 20 amp contacts. 110 Volt. 2 c/o 20 amp contacts. Either type **£1·25.** Post 10p.

DRY REED RELAYS

Mfg. by ERG, 12 volt d.c. encapsulated.
Single c/o **65p,** post paid. Two c/o **85p,** post paid.
STC 280 ohm coil 6/12V d.c. 3 make metal shrouded. **60p** post paid.
Large range of other types, details on request.

"HONEYWELL" PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

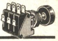

Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob 1 in. Fixing hole ⅝ in. ONE bank **30p;** TWO bank **40p;** THREE bank **50p.** Quote for quantity.

VERY SPECIAL OFFER

Micro Switch. 5 amp c/o contacts. M.f.g. bg. Honeywell. NEW. **Twenty** for **£1·50.** Post 10p (min. 20).

'HONEYWELL' LEVER OPERATED MICROSWITCH

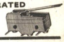

10 amps 250 volt A.C. c/contacts. In maker's carton.
PRICE: 10 for **£1·90.** Post 15p.

INSULATION TESTERS *NEW!*

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in, W.4in, H.6in, weight 6lb. **1,000V,** 1,000 megohms, **£34.** Post 60p. **500V,** 500 megohms, **£28.** Post 60p.

BALANCE/LEVEL METERS

100-0-100 Micro Amp. Size 1½in + 1½in + ⅞in. Price only **70p.** Post 5p.

METERS NEW! 2½in. Flush round. Available in D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 1, 5, 10, 15, 20, both types **£2·00.** Post 15p. Voltmeter **0-300V** A.C. **£2.** Post 15p.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

P.E. RONDO

FULL SPECIFICATION KITS

Complete designer approved kits. Full data and even solder included. Top quality PCBs and components.

- * **CBS-SQ MATRIX DECODER £8.** Post Free + 80p VAT.
- * **READY BUILT £11.** Post Free + £1·10 VAT.
- * **PRE-AMP BOARD, COMPLETE £3.** Post Free + 30p VAT.
- * **MASTER VOL/TONE/BAL. BD. £8·50.** Post Free + 85p VAT.
- * **POWER AMP BOARD HEATSINK.** Two reqd. for Rondo **£7·50.** Post Free + 75p VAT.
- * **POWER SUPPLY BOARD £5.** Post Free + 50p VAT.
- * **MAIN SMOOTHING CAPS £1·50** per pair. Post Free + 15p VAT.
- * **MAINS TRANSFORMER £6·25.** Post Free + 62p VAT.
- * **PUNCHED CHASSIS £3·25.** Post Free + 32p VAT.
- * **RONDO CASE £1·75.** Post Free + 17p VAT.
- * **HARDWARE PACK £2.** Post Free + 20p VAT.
- * **CONTROL SECTION FASCIA £3·50.** Post Free + 35p VAT.
- * **STEREO DECODER KIT £5·95.** Post Free + 59p VAT.
- * **STEREO DECODER BUILT AND TESTED £6·95.** Post Free + 69p VAT.
- * **GOLDRING G101/2 TURNTABLE Less Cartridge £22·90.** Post £1.
- * **DEUTSCHE ELAC CARTRIDGE STS 144/17 £6·90.** Post Free + 69p VAT.
- * **READY BUILT LOUDSPEAKERS** (Teak or white veneer) per pair **£42.** Post £2 + £4·40 VAT.
- * **COMPLETE SPEAKER KIT WITH DRIVE UNITS CROSS OVER, WADDING, ETC.** (Four reqd. for Rondo) **£18·50** each. Post 50p + £1·90 VAT.
- * **COMPLETE SPEAKER KIT WITH DRIVE UNITS CROSS OVER WADDING, ETC.** per pair **£35·50.** Post £2 + £3·75 VAT.
- * **COMPLETE SPEAKER KIT WITH DRIVE UNITS CROSS OVER WADDING, ETC.** per pair **£62.** Post £4 + £6·60 VAT.
- * **BASS DRIVE UNITS** (2 per cabinet) **£4·25** each. Post Free + 42p VAT.
- * **TWEETERS** (2 per cabinet) **£1·20** each. Post Free + 12p VAT.
- * **CROSS OVER UNIT** (1 per cabinet) **£2·50** each. Post Free + 25p VAT.

Details of ancilliary parts and author's note available soon.

TRADE GLADLY SUPPLIED

STUDIO ELECTRONICS

P.O. BOX No. 18. HARLOW. ESSEX CM18 6SH
Telephone: Harlow (0279) 25457

ORDER—PLEASE SEND

CBS-SQ DEC ☐
CBS-SQ DEC BUILT ☐
PRE-AMP ☐
MASTER VOL. ☐
POWER AMPS ☐
POWER SUPPLY ☐
CAPACITORS ☐
TRANSFORMER ☐
RONDO CASE ☐
HARDWARE ☐
CONTROL FASCIA ☐
STEREO DECODER KIT ☐
STEREO DECODER Built ☐
BUILT SPEAKER Teak ( ) ☐
BUILT SPEAKER White ( ) ☐
BASS DRIVE UNITS ( ) ☐
TWEETERS ( ) ☐
CROSS OVER KIT ( ) ☐
COMPLETE SPEAKER KIT White ( ) ☐
COMPLETE SPEAKER KIT Teak ( ) ☐
GOLDRING G101 TURNTABLE Less cart. ☐
ELAC 144 CARTRIDGE ☐
Notes ☐

Please insert quantity in open brackets

ENCLOSED £............ CHEQUE/P.O.

NAME ....

ADDRESS ....

....

....

.... PE 3/4

A DEXTER DIMMASWITCH

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.

600 watt **£3.52**	Kit form **£2.97**
300 watt **£2.97**	Kit form **£2.42**

All plus 12p post and packing
Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY
1 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED TO H.M. GOVERNMENT DEPARTMENTS, HOSPITALS, LOCAL AUTHORITIES, ETC.

I-N-T-E-R-L-O-C-K-I-N-G PLASTIC STORAGE DRAWERS

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/ 1D and 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins × 2¼ins × 2¼ins). **£1·40** DOZEN.

DOUBLE UNITS (2D) (5ins × 4½ins × 2¼ins). **£2·30** DOZEN.

TREBLE (3D) £2·50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case **(6D2), £3·60** for 8, **EXTRA LARGE SIZE (6D1) £3·40** for 8.

PLUS QUANTITY DISCOUNTS!

Orders £10 and over DEDUCT 5% in the £
Orders £20 and over DEDUCT 7½% in the £
Orders £50 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES

Please add 10% V.A.T. to total remittance

FLAIRLINE SUPPLIES
(Dept. PE3) 124 Cricklewood
Broadway, London, N.W.2
Tel. 01-450 4844

PARTRIDGE MAINS ISOLATION TRANSFORMER, Pri: 105-250V, 5V steps, Sec: 240V, 13 amps. **£15,** carr. pack. £1·50.

PARMEKO MAINS TRANSFORMER isolated windings. Pri: 200-250V. Sec: 90-120V at 4·5 amp., **£4,** carr. pack. 75p.

GARDNER'S POTTED TRANSFORMER, 0-250V. Pri. 200-250V. Sec. Input: 18V 500m/n, 50V 150m/a, 6V 250m/a output. Size: 3in × 2¾in × 2¾in, **£1,** p.p. 28p. Ex equip. tested.

RIPLEY MAINS TRANSFORMER, Pri: 110V-240V, Sec: 12·5V: 0:12·5V 750m/A 7V:0:7 V1A, **£1,** p.p. 25p.

MAINS TRANSFORMER, Pri: 100-250V, Sec: 22:0:22 200m/A. 22:0:22 100m/A 0:24V 20m/A, **80p,** p.p. 25p.

MAINS TRANSFORMER, Pri: 230V, Sec: 14V, 120 amps. **£15,** p.p. £1·50.

MAINS TRANSFORMER, Pri: 100-240V a.c. 36·5-0-36·5V, 27 m/A, 0-21·5, 260 m/A, **80p,** p.p. 25p.

TRANSISTOR OUTPUT TRANSFORMER, Ratio 8:1, 120mH. Centre tap 2 watts. output, **20p,** p.p. 8p.

SMOOTHING CHOKE, 11MH, 1¾in × 1¼in × 1½in, **20p,** p.p. 8p.

FINNED ALUMINIUM HEATSINK, 4¾in × 6in × 1in, 2 × 2N3055, **£1,** p.p. 13p.

GOODMANS 8in SPEAKERS 3 Ω **£1·50,** p.p. 28p.

FINNED ALUMINIUM HEATSINK. 9in × 8in × 1½in. in C.: 4 × 2N3055, **£2,** p.p. 29p.

GARRARD MAG. TAPE DECKS: 1⅞i.p.s., 50V, solenoid operated brakes, etc. Mains voltage motors **£7·50** each, p.p. 60p.

MOTEK 3 speed tape deck (1⅞in × 3¾in × 7½in) reel to reel 7in mains operated, **£7·50,** p.p. 63p.

10 REED SWITCHES operated by push buttons and magnets, **50p,** p.p. 25p.

COMPONENT PANEL, 6 scr's (300V, 1·6A) 6 cond., 12 resistors, 6 diodes, **45p,** p.p. 8p.

COMPONENT PANEL, 6 s'crs (200V 4 amps), 6 condensers, 12 resistors, **30p,** p.p. 8p.

COMPONENT PANEL (9 ICs FJH131) (1-CA300), 1 crystal 7·68kHz + various other components, **£1,** p.p. 8p.

COMPONENT PANEL, 2 × 500mF 50V, 3 × 100mF 25V, cap. 1 × 2N2612, 2 × 2N404, 3 diodes plus various other components, **10p,** p.p. 9p.

COMPONENT PANEL, 24 0A81 diodes, **10p,** p.p. 6p.

VEEDER ROOT ELECTRICAL IMPULSE COUNTER NON-RESETTABLE, A.C. 200-250V, **£1·10,** p.p. 13p.

GEC MAINS CIRCUIT BREAKERS, 2 amp or 5 amp, **£1** each, p.p. 14p.

LEVER ACTION P.O. 1000 TYPE SWITCHES
Lock 4-pole changeover, **15p,** p.p. 4p. Ex equip.
Lock 2-pole changeover, **10p,** p.p. 4p. Ex equip.

MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500µF 64V, 7,100µF 40V, **50p** each. 20,000 30V, 25,000 25V, 35,000 15V, **30p** each, p.p. 21p.

MULLARD FULLWAVE RECTIFIERS
6-48V, 15 amp, **75p,** p.p. 10p.

BELLING LEE 1·5 amp in-line rubber covered interference suppressor, **25p,** p.p. 8p.

RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.

SOLENOIDS 12 VOLT PULL ACTION
2in × 1in × ¾in, **40p,** p.p. 8p.

SOLENOIDS 12-24V d.c. pull action 1⅝in × 1⅝in × 1½in, **40p,** p.p. 5p.

SOLENOIDS 240V a.c. pull action 2½in × 1⅝in × 1½in, **50p,** p.p. 9p.

SANGAMO WESTON TIME LAPSED METER
Mains operated. 1½in × 1½in × 2in, **£1·50** p.p. 7p.

SCR WITH HEAT SINK (600V 15 amp), **50p,** p.p. 5p.

OMRON MK2 MIDGET POWER RELAY, 12V d.c. Double pole changeover. New, **70p,** p.p. 5p.

STC VARLEY, miniature relays 700 Ω, 17·5-37V, perspex cover, 4 pole changeover, **40p,** p.p. 5p.

POTTER BRUMFIELD 12V d.c. 3 pole changeover with base, contacts rated 7A d.c., **£1,** p.p. 10p.

I.T.T. LOW PROFILE RELAYS. 4 pole c/overs. 500 Ω 12-18V, **75p,** p.p. 5p.

MAINS RELAYS, 200-250V a.c. 2 makes. Heavy duty contacts, **50p,** p.p. 7p.

TELESCOPIC AERIALS
Chromed 7in closed, 28in extended, 6 section ball jointed base, **23p,** p.p. 5p new.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200 Diodes: 1 reed relay: 1 AZ 229 zener ass. capacitor/ resistors. Power supply 22V, 250 m/A d.c. Output 240V a.c., **£1,** p.p. 25p. Ex equip.

WIRING CABLE
Size-1·020. Various colours. 350yds, **60p,** p.p. 28p.

TAPE POSITION INDICATOR
Re-settable 3 digits, **30p,** p.p. 5p.

All orders add 10% V.A.T.

FIELD ELECTRIC LIMITED
3 Shenley Road
Borehamwood, Herts.
Tel. 01-953 6009

SPACEWATCH

BY FRANK W. HYDE

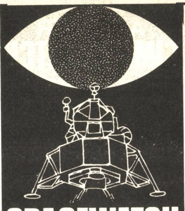

SKYLAB—LAST MISSION

As this is being written the last *Skylab* mission planned before the Soviet–American rendezvous in space, is not quite half way through. The longest single mission of three astronauts will bring to an end the triple series of scientific programmes.

By whatever standards these experiments may be judged they represent one of the major events in the history of the solar system. Some may regard the *Skylab* project as more important than the *Apollo* programme. Certainly, a very comprehensive coverage of observation (and running repairs) will add much to the data so far amassed. It must not, however, be forgotten that side by side with the success story go some rather disquieting happenings.

It is intended that the return of the team will be in early February. However, at the time of writing, there are possibilities that there could be an earlier termination because of certain disciplinary reactions. Perhaps it is to be a blessing, if seen in the broad context of advanced technology.

The problems that have arisen are twofold. There have been technical difficulties and some personnel problems. None of the present crew have flown in space before and this could to some extent explain the behavioural problems.

CREW CONCERN

Mission Control have been concerned about the crew in that they suffered from motion sickness for several days and attempted to conceal this from the physicians monitoring the flight. Perhaps this is understandable since they would be worried about being recalled. On the other hand there were other signs such as proneness to error and poor disposition.

Their sleep sessions have tended to be longer than was thought to be required, compared with the previous crews. They have been moody and temperamental when in contact with control and have complained somewhat bitterly about their workload. Refusal to come in from extra vehicular activities has seemed to show a somewhat antagonistic attitude towards instructions.

The consequences on their work has been very noticeable. The most serious error has been in relation to the operation of the cameras during observation passes of the Earth. The proper filters to six cameras were forgotten. Much of the film will be useless though some may be recoverable using certain special techniques when they are returned to base.

The medical unit in charge at control will be seeking an answer to these rather irrational episodes. Despite this however, it cannot detract from the remarkable *Skylab* project.

Some of the technical problems have been concerned with the gyroscopes. One of these has been out of use since the end of November. The other has tended to show a slowing down. Normally it would have a revolution of 8,200 per minute. It slowed by 14 revolutions and then by a further 10 per minute. This is quite serious and should it continue to fall then the mission could well be curtailed.

PIONEER 10 AND JUPITER

Some of the vital statistics so far recorded during *Pioneer*'s mission to Jupiter have confirmed previous thinking. The magnetic field for example is recorded at 4 gauss. In a recent "SPACEWATCH" mention was made that Dr C. H. Barrow had used a figure of 9 to 10 gauss. Re-examination of his previous papers can now lead to some constructive theories.

The off-set magnetic field confirms Warwick's claim made several years ago. The higher level of the radiation belts has also been confirmed. It is also confirmed that Io has an ionosphere. This supports the earlier data that Io has an influence on the decametre radiation from Jupiter.

It will be some time yet before the accumulated data is to hand for distribution.

Perhaps another important point that might be made is the fact that so far the 8W transmitter has fulfilled its task admirably. It remains to be seen (heard?) how far out it will continue to supply data.

One further important development is that it is now quite definitely confirmed that there are hazards to control, in the magnetosphere of Jupiter. There is the possibility of random effects giving the same sort of command signal to the vehicle.

The case of far out probes such as *Pioneer 10,* introduces the long time period of signal travel. That is 45 minutes out and 45 minutes back. This could be much too long to counteract false signals. To overcome this a method of repeating commands every 30 minutes is being used. By this means the risks are minimised.

MOON AS A STANDARD LAMP

Dr J. Linsky of Boulder, Colorado, has made use of data obtained from the *Apollo* missions and the study of the lunar soil, to set the moon as a standard of comparison for infra-red and microwaves.

The average values have been studied and Linsky's results have shown an accuracy of 4 per cent for wavelengths between 10 micrometres and 1 metre. By averaging the radiation between successive new moons he arrived at a figure for radiation over a lunar day for the central part of the moon's disc. It is possible to use this standard to calibrate the sun and parts of the galaxy.

Linsky is able to fix the brightness at an order of magnitude better than with other methods. Possibilities of a better study of the chromosphere are therefore indicated and perhaps a better view of how the heat transfer shock waves operate.

QUASARS

The see-saw of opinion continues to operate in the controversial field of quasars. In spite of this there is growing confirmation of the claims of the radio astronomers that these are far distant rapidly receding objects.

Recent new work has offered a new dilemma for theorists since in one particular case the observers are faced with deciding as to whether, in certain cases, the quasar is in fact way beyond its apparent position relative to a galaxy or whether Hubbles law is in doubt in such cases.

It still leaves the position largely as before, that of all the new discoveries of other sources such as pulsars, black holes, X-ray stars, etc., the quasar remains the most mysterious. Near or far as to position still remains in doubt when looking at the overall picture.

Constant Current Generators

THE constant current generator is a very useful circuit element, which does not often achieve the recognition it deserves. Fig. 1 shows the symbol used and the voltage-current characteristic of an ideal current source. An ideal current source produces a current which is totally independent of the voltage across the terminals of the source. In other words, the slope resistance or dynamic resistance of the generator is infinite since

$$\text{dynamic resistance } R_d = \frac{\text{change in voltage } (\Delta V)}{\text{change in current } (\Delta I)}$$

Practical current sources, however, have a characteristic of the form shown in Fig. 2. This falls short of the ideal in three main ways:

1. The slope resistance is not infinite, i.e. there is a small change in the current flowing through the device as the voltage across the terminals is altered.

2. Below a certain voltage, called the knee voltage, the slope resistance is reduced because the characteristic curve of any circuit which does not contain its own separate power supply must pass through the origin, i.e. when there is no voltage across it, no current can flow.

3. Above a certain voltage, breakdown will occur and the current will increase sharply.

CURRENT REGULATOR DIODES

The simplest constant current generator available is the current regulator diode. This is a two-terminal device whose symbol is shown in Fig. 3.

The range of current regulator diodes manufactured by Motorola provides current ratings from 220μA to 4·7mA. Their slope resistances vary from 25MΩ for the 220μA diode to 240kΩ for the 4·7mA diode and the knee voltages range from 1V for the lowest current diodes to 2·9V for the 4·7mA diode.

Although these are the easiest current sources to apply, they are very expensive and, in fact, they consist of field effect transistors with their gate and source leads shorted together as described below.

FIELD EFFECT DIODES

The construction of an *n*-channel field effect transistor is shown diagrammatically in Fig. 4. The channel is a bar of *n*-type silicon with a resistance of a few hundred ohms. The drain and source leads are connected to the

Fig. 3. Representative symbol for a current regulator diode

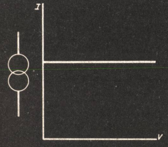

Fig. 1. Voltage/current characteristic of an ideal constant current source with the graphical symbol usually used in diagrams

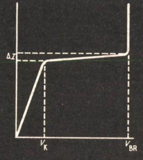

Fig. 2. Voltage/current characteristic of a practical current source

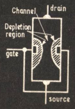

Fig. 4. Construction of a field effect transistor

ends of the bar. Halfway along the bar, two *p*-type regions are diffused into opposite sides of the silicon bar. These are connected together to form the gate.

Thus a diode is produced between the gate and the centre of the channel. This diode, when reverse biased, has a depletion region which increases in size as the reverse bias voltage is increased. The depletion region extends into the channel as shown in Fig. 4.

Because the depletion zone contains almost no current carriers, the effective cross-sectional area of the channel through which current can flow is reduced and the resistance correspondingly increased when the gate diode is reverse biased.

Consider what happens when the gate is connected to the source. When the drain-gate voltage is 0V, the voltage across the gate diode is also 0V and hence there is only a small depletion zone. As the drain voltage is increased, the drain current increases linearly at first because the small depletion zone has little effect on the channel resistance.

However, as the current through the channel increases, a voltage is produced across the resistance of the channel between its mid-point and the source terminal. This reverse biases the gate diode and the consequent increase in the size of the depletion zone increases the channel resistance.

PINCH-OFF

Eventually, the depletion region extends over almost the entire area of the channel. At this point, any further increase in drain voltage has very little effect on the drain current because only a small increase in the size of the zone produces a large change in channel resistance.

The area of operation in which the drain current is virtually unaffected by drain voltage is known as the pinch-off region. The knee voltage at which pinch-off occurs is of the order of a few volts for common f.e.t.s. The drain current, with gate and source connected together and the drain voltage large enough to produce operation in the pinch-off region, is represented by the symbol I_{DSS} and is typically 1–20mA.

The slope resistance of an f.e.t. current source with $V_{GS} = 0V$ as described above is approximately equal to the reciprocal of the low-frequency output admittance y_{OS}.

Table 1: FIELD EFFECT TRANSISTOR PARAMETERS ($\mu S = \mu mho$)

F.E.T. type	$V_{B(DSS)}$	I_{DSS} (mA)	y_{OS} (μS)
2N3819	25V	2–20	50
2N3823	30V	4–20	35
2N4304	30V	0·5–15	50
2N5459	25V	4–16	50
MPF105	25V	4–16	50
BF244	30V	2–25	50
BFW10	30V	8–20	85
BFW11	30V	4–10	50
BFW61	25V	2–20	85

At a voltage of about 25–40V, for low power f.e.t.s, avalanche breakdown occurs and the drain current increases sharply. This voltage is given the symbol $V_{B(DSS)}$. A table listing $V_{B(DSS)}$, I_{DSS} and y_{OS} for several common f.e.t.s is given in Table 1. It should be borne in mind that the value of y_{OS} given in the table is a maximum and most f.e.t.s will have output admittances much lower than the listed values.

EXTERNAL RESISTOR

From the above description of the operation of the f.e.t. constant current source, it can be seen that if an external resistor is added between the source and gate leads as shown in Fig. 5, pinch-off will occur at a lower value of drain current.

Fig. 6 is a graph of the variation of drain current as the source resistor is altered for an MPF102 f.e.t. which had an I_{DSS} of 9·7mA. By using an external resistor the drain current can be set to any value between the leakage current and I_{DSS}. A variable resistor can be used to compensate for the wide spread in I_{DSS} which is found in f.e.t.s.

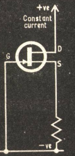

Fig. 5. Constant current generator using a field effect transistor

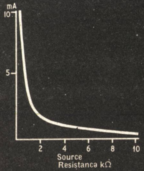

Fig. 6. Graph of current versus source resistance for the circuit in Fig 5

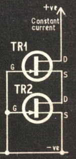

Fig. 7. High slope resistance current source

One advantage of inserting a resistor in series with the source is that the slope resistance of the device is increased. This is because a change in channel current causes a change in the voltage across the resistor which alters the reverse bias on the gate. Obviously, for a given change in current, the voltage change is proportional to the resistance in series with the source.

HIGH SLOPE RESISTANCE

In applications where a very high slope resistance is required, the circuit shown in Fig. 7 can be used. In this circuit, the source resistor is replaced by an f.e.t. current generator which provides a high slope resistance in series with the source of TR1.

For proper operation, the cut-off voltage V_p of TR1 should be greater than that of TR2. The slope resistance can be increased by one or two orders of magnitude using this technique.

The temperature coefficient of drain current depends on the value of drain current, being negative at high currents and positive at low currents. At an intermediate value of drain current $I_{D(0)}$, the two effects causing these changes cancel and the temperature coefficient is approximately zero. The current at which this occurs is given approximately by:

$$I_{D(0)} = \frac{0{\cdot}4}{V_p^2} \times I_{DSS}$$

y AND *h* PARAMETERS

It is often convenient to refer to the characteristics of transistors by means of *y* or *h* parameters. There are four *h* and four *y* parameters for each of the three basic transistor connections.

The four *y* parameters describing a transistor operating in the common emitter configuration are: y_{ie}, y_{fe}, y_{re} and y_{oe}. The second subscript letter "e" refers to the fact that the transistor is in the common emitter connection. Similarly, "b" denotes common base, "s" denotes common source, etc. The first subscript letters refer to input, forward transfer, reverse transfer and output parameters respectively.

Each "y" parameter is the ratio of a current to a voltage. Thus:

y_{ie} is the input admittance (the ratio of input current to input voltage);

y_{fe} is the forward transfer admittance (the ratio of output current to input voltage);

y_{re} is the reverse transfer admittance (the ratio of input current to output voltage);

y_{oe} is the output admittance (the ratio of output current to output voltage).

Whereas *y* parameters are all ratios of currents to voltages, different *h* parameters represent ratios of different quantities. Thus:

h_{ie} is the input impedance (the ratio of input voltage to input current);

h_{fe} is the forward current transfer ratio (the ratio of output current to input current);

h_{re} is the reverse voltage transfer ratio (the ratio of input voltage to output voltage);

h_{oe} is the output admittance.

Although common emitter parameters have been quoted, the definitions are also valid for other connections.

Of the six possible sets of parameters, only *h* and *y* parameters are widely used in transistor circuit analysis. If one set of parameters is known, any other set can be calculated quite easily. This means that the choice of parameters for a given application is largely a matter of convenience.

The characteristics of bipolar transistors are usually described by *h* parameters and those of field effect transistors by *y* parameters.

BIPOLAR TRANSISTORS

A bipolar transistor in either the common base or common emitter configuration can also be used as a constant current source as shown in Fig. 8. Since the collector-base junction is a reverse biased diode, the current through it is only slightly affected by the voltage across it.

The slope resistance in the common base connection is $(h_{fe} + 1)$ times larger than the slope resistance in the common emitter connection. The difference between common base and common emitter circuits lies in the resistances in series with the base and emitter leads.

The circuit in Fig. 9 is a generalised common base or common emitter circuit. If $R_B = 0$ and $R_E = \infty$ the slope resistance is equal to the reciprocal of the low frequency common base output admittance h_{ob}. In practice, provided that R_E is more than a few kilohms, the slope resistance is not appreciably less than this value. If $R_B = \infty$ and $R_E = 0$, the slope resistance equals $1/h_{oe}$. Then h_{oe} and h_{rb} are related by the equation:

$$h_{oe} = h_{ob} \times (h_{fe} + 1).$$

With intermediate values of R_B and R_E the slope resistance lies between these two values. For a BC108, $h_{ob} = 10^{-7}\mu S$ and $h_{oe} = 3 \times 10^{-5}\mu S$.

The circuit of a simple transistor constant current generator is given in Fig. 10. The base voltage is set to 4V by the potential divider across the supply.

Since the BC184 is a silicon transistor, the emitter voltage is about 3·4V. Thus the emitter current is $3{\cdot}4V/6{\cdot}8k\Omega = 500\mu A$ and since $\alpha \simeq 1$, the collector

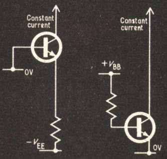

Common emitter Common base

Fig. 8. Transistor constant current generators

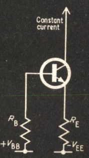

Fig. 9. Generalised common base, common emitter circuit

current is also about 500μA. Because the emitter resistance is 6·8kΩ, the slope resistance of this current source is very high. The knee voltage is about 4V.

The major disadvantage of the circuit in Fig. 10 is that the current is approximately proportional to the supply voltage. To produce a more stable current source, R2 is often replaced by a Zener diode so that the base voltage, and hence the emitter voltage, is less affected by supply voltage variations.

The temperature coefficient of this source depends on the temperature coefficients of the Zener diode and the base-emitter junction. If a Zener of about 4V is used, the temperature coefficients will cancel.

IN INTEGRATED CIRCUITS

Fig. 11 shows the circuit of an interesting transistor current source which is often used in integrated circuits. In this circuit, the base current for the transistor is supplied by part of the current through the resistor. The remainder of the current from the resistor flows through the diode.

In an integrated circuit, since all the transistors and diodes are produced simultaneously on the same chip of silicon, the diode can be made identical to the base-emitter junction of the transistor. Because the diode and the base-emitter diode are connected in parallel, the voltages across the two are equal. Since the two diodes have the same characteristics, the currents through them (I_D and I_E) are also equal.

The current through the diode comes entirely from the resistor but the emitter current in the transistor is provided partly by the resistor and partly by the collector circuit. In other words,

$$\begin{aligned} I_D &= I_E \\ &= I_C + I_B \end{aligned}$$

The base current of the transistor is about one per cent of the emitter current and can be neglected. With this assumption, it can be seen that the collector current of the transistor is equal to the current flowing through the diode. Because the base current is small, almost all of the current flowing through the resistor flows into the diode so that the collector current of the transistor is approximately equal to the current in the resistor.

Circuits of this type have very low knee voltages, typically less than 0·5V. This circuit also has a very low temperature coefficient because the diode and transistor have equal temperature coefficients of voltage which cancel each other.

The breakdown voltage of a transistor- current generator can be anything from 15 to 500V depending on the transistor employed.

SOPHISTICATED CIRCUITS

There are several more complex constant current circuits available which are used where high stability is required. The ring-of-two circuit shown in Fig. 12 is often used as a precision current generator. It is a two-terminal current source because, unlike the transistor circuits described above, no extra supply voltage is necessary.

The operation can be understood if it is considered as two constant current sources, the first consisting of D1, R1 and TR1 and the second containing D2, R2 and TR2. These sources are connected so that each one supplies a constant current to the Zener diode of the other. The knee voltage of the ring-of-two is rather high, and is equal to the sum of the Zener voltages of D1 and D2.

Just as it is possible to construct regulated voltage power supplies, so regulated current supplies can be made.

The current is usually measured by passing it through a resistor and comparing the voltage thus produced with a reference voltage to derive a control signal. This signal is then applied to a bipolar transistor or an f.e.t. which controls the current. A block diagram for such a scheme is shown in Fig. 13. ★

In the concluding part of this article next month, practical applications of constant current sources will be described.

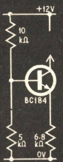

Fig. 10. Simple transistor constant current source

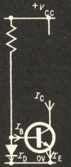

Fig. 11. Matched diode transistor constant current source

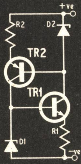

Fig. 12. Ring-of-two constant current generator

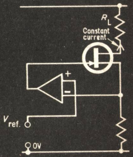

Fig. 13. Stabilised current power supply

ELECTRONIC SNAP

By C. J. ALLEN

THERE are many games in which contestants' reaction times play a vital part; "snap" is an obvious example and a guessing game where the first contestant to press a button is allowed to answer is another. This simple unit has two push buttons and gives a positive indication (by lighting a lamp) of the button which is pressed first.

CIRCUIT DESCRIPTION

The circuit of the Electronic Snap is shown in Fig. 1. It makes use of a single digital integrated circuit type SN7400 which is available for less than 20p. The indicators used are light emitting diodes which are simply diodes which emit light when forward biased.

The SN7400 contains four NAND gates. A NAND gate is one whose output will only go to logic 0 if *both* inputs are logic 1. They are cross-coupled in the circuit so as to form two bistables, circuits which

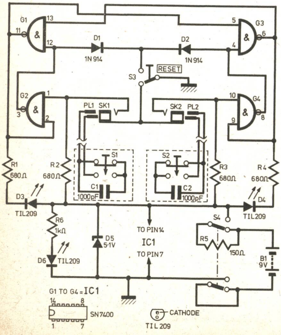

Fig. 1. Circuit diagram of the Electronic Snap

COMPONENTS . . .

Resistors	
R1-R4	680 Ω (4 off)
R5	150 Ω
R6	1 k Ω
All ±10% ¼W carbon	
Capacitors	
C1, C2	1,000pF polystyrene (2 off)
Diodes	
D1, D2	1N914 or any general purpose silicon diode (2 off)
D3, D4, D6	TIL209 or similar light emitting diode (3 off)
D5	5·1V 400mW Zener diode
Integrated Circuit	
IC1	SN7400N Quad 2-input NAND gate
Switches	
S1, S2	Push to changeover (1 pair normally closed, 1 pair normally open) (2 off)
S3	Push to changeover
S4	Miniature d.p.d.t. toggle
Miscellaneous	
B1	9V PP4 battery
0·1in matrix Veroboard 2in × 1½in	
Diecast box 4¼in × 2¼in × 1in	
35mm film cases (2 off)	
3·5mm jack plug and socket (2 off)	

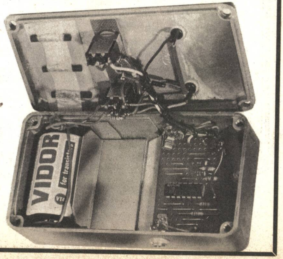

are stable in either of two states. When the reset button is pressed inputs to gates G1 and G3 are taken to logic 0 (less than 0·8V) through diodes D1 and D2. The outputs of G1 and G3 must go to logic 1 regardless of the state of pins 13 and 5.

Switches S1 and S2 are open so the inputs on pin 1 of G2 and pin 10 of G4 are logic 1. Because the outputs of G1 and G3 are logic 1 it follows that all inputs to gates G2 and G4 are logic 1 so their outputs go to logic 0. The circuit will stay in this state even when S3 is released.

Assume S1 is now pressed. One input to G2 goes to logic 0, the output goes to logic 1 causing the output of G1 to go to logic 0 which, in turn, causes l.e.d. D3 to conduct and light up. Pin 5 of G3 is now held at logic 0 so even if S2 is pressed causing the output of G4 to go to logic 1 the output of G3 will stay at logic 1 keeping l.e.d. D4 off.

POWER SUPPLY

Power for the circuit is provided by a nine volt battery which is dropped down to the five volts required by the integrated circuit by the 150Ω resistor R5 and Zener diode D5.

One point that may be noticed is the connection of switches S1 and S2. These are not connected so as just to ground the inputs to G2 and G4 but to provide a very short pulse which is enough to take the inputs to logic 0 but will not drain the battery if the switches are held down.

The switches are connected as changeovers and the very short interval during which the capacitor charges is enough to momentarily take the output to ground.

CONSTRUCTION

The bulk of the circuit is built on a small piece of Veroboard as shown in Fig. 2. Jack plugs are used to connect the switches to the main unit. The switches are mounted in 35mm film cases and the capacitors C1 and C2 are mounted on the switch contacts. ★

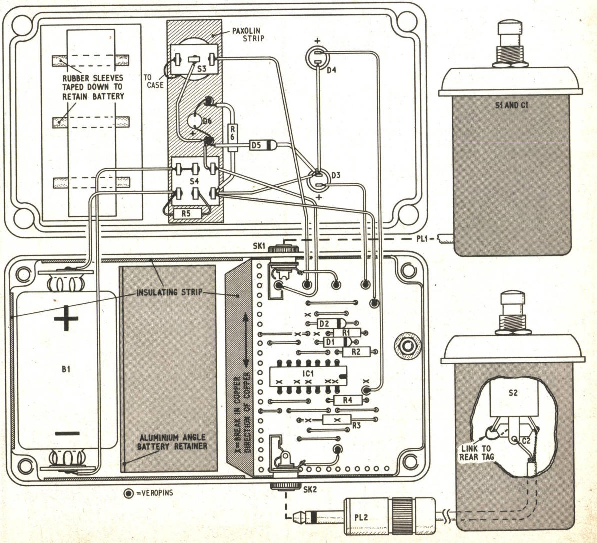

Fig. 2. Layout of the components on the Veroboard and front panel, and interwiring details

SCORPIO Mk.2 IGNITION SYSTEM

By D.S.GIBBS & I.M.SHAW

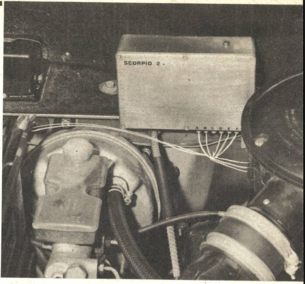

SINCE publication of the original *Scorpio* ignition system, about two and a half years ago, many requests have been received for a six volt version for use on cars and motor cycles with six volt electrical systems.

It is, unfortunately, impractical to build a unit to operate on both 6V and 12V, so two units have been designed with differing component values, and a number of improvements have been made to reduce radio interference and improve tachometer triggering. Both units give substantially the same performance and can be used on either positive or negative earth cars by altering a few connections.

PERFORMANCE

There has been a tremendous rise in interest in capacitor discharge ignition systems over the past few years and their advantages are now widely recognised. The main features are:

(a) Easier starting from cold. The higher spark voltage and faster rise time enables it to fire wet or oiled up plugs. The electronic system can deliver twice the spark voltage of the conventional system into a load of 470kΩ and 40pF—simulating a badly fouled plug.

(b) Smoother running at high speeds. Fig. 6 shows how the electronic system maintains an almost constant spark voltage up to 12,000 r.p.m. for a four cylinder engine (8,000 r.p.m. for six cylinder). This promotes better combustion at high speeds, eliminating misfiring and reducing the level of pollutants in the exhaust.

(c) As a result of the improved combustion there is a small improvement in power and fuel economy.

(d) The contact breaker will remain correctly adjusted for up to 20,000 miles. This keeps the car electrically "in tune", with a consequent improvement in fuel economy.

(e) Spark plug wear is reduced. In the conventional system the spark current is unidirectional and causes deposition of metal from one electrode to the other. In the electronic system the spark current is bidirectional and of much shorter duration. This increases spark plug life and reduces the need for adjustment.

CIRCUIT DESCRIPTION

The circuit of both 12V and 6V versions is the same and is shown in Fig. 1. Transistor TR1 is not required for positive earth operation but it can be left in circuit if desired. This will enable the unit to be used on either positive or negative earth cars merely by changing a few connections.

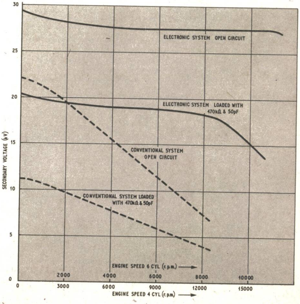

Fig. 6. Graph showing the variation of output voltage with engine speed for conventional and capacitor discharge systems

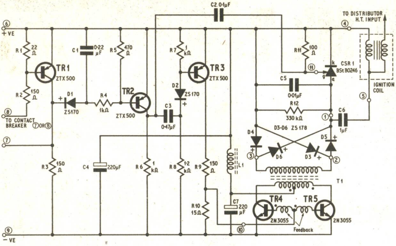

Fig. 1. Circuit diagram of the 12V version of the Scorpio Mk 2 capacitor discharge ignition system.

Refer to blueprint for full constructional details

Please note:* *R12 should be 1W (both versions).
TR3 (6V) should be BFS97 or ***ZTX550.***

The circuit operates as follows (assuming negative earth operation with tag 9 earthed and the contact breaker connected to tag 8):

With the contact breaker closed TR1 is saturated and its collector voltage is close to the positive rail. When the contact breaker opens TR1 turns off and C1 is rapidly charged by R3 and diode D1. This brings TR2 hard on, its collector voltage rises to the positive rail and this positive pulse fires the thyristor CSR1. At the same time TR3 is reverse biased by C3 and remains cut off for about 0·3 milliseconds. This removes the bias from the inverter and prevents the thyristor from latching on.

When the contact breaker points close again TR1 turns hard on, but TR2 remains on for about 0·3 milliseconds—until C1 has discharged through R4 and R5. This effectively prevents contact bounce from retriggering the thyristor at the wrong time. Further noise immunity is provided by C2 and C3, which take about one millisecond to recharge fully after TR2 turns off.

Transistors TR4 and TR5, with the ferrite cored transformer T1, form a very efficient push pull inverter oscillating at about 2kHz. The 400 volt a.c. output is rectified by diodes D3 to D6 and charges up the energy storage capacitor C6 in about 1·5 milliseconds. When the thyristor fires this charged capacitor is thrown directly across the primary of the ignition coil. The primary voltage immediately rises to 400V and this is stepped up to 20 to 30kV at the secondary, forming an arc between the plug electrodes.

CONSTRUCTION

The unit is constructed in a 7¼in × 4½in × 2in diecast box, which acts as a heatsink for TR4, TR5, and the thyristor. Most of the other components are mounted on the printed circuit board shown in Figs. 2 and 3.

Connections to the board are made via turret tags, or the wires can be soldered direct to the board. If turret tags are used they should be expanded with a centre punch after insertion, to lock them in place, and then soldered.

COMPONENTS

The diodes, transistors and resistors are all readily available. Capacitors C1 to C3 are not critical but Mullard type C280 miniature foil types are used in the prototype. The 1µF 440V a.c. rated capacitor (C6) is available from many of the advertisers in P.E. The Siemens thyristor is available from A. M. Marshall and Electrovalue who also supply the Siemens pot core. The address of a supplier for the printed circuit board is shown in the components list. The total cost of the unit is around £8·50.

TRANSFORMER CONSTRUCTION

Details of suitable cores and bobbins are given in the parts list and winding details in Fig. 4. Both types are very similar and give substantially the same perormance.

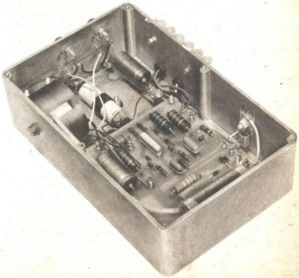

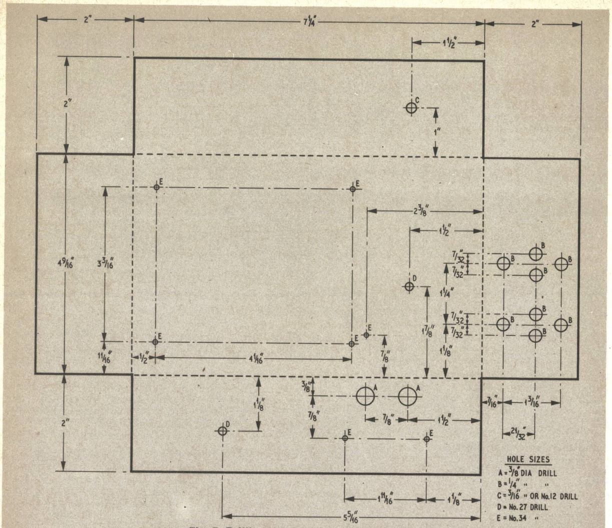

Fig. 7. Drilling details for the diecast box

12V version

First wind on 400 turns of 34 s.w.g. enamelled wire in eight neat layers—taking care not to cross adjacent turns. Insulate the lead out wires with thin sleeving and insulate the whole winding with four turns of thin insulating tape. Then wind on 12 + 12 turns of 20 s.w.g. bifilar (i.e. two wires wound together), and lastly 3 + 3 turns of 30 s.w.g. bifilar. Put coloured sleeving on the wires for identification and to protect them from abrasion against the core and insulate the whole coil with several more turns of insulating tape.

It is a good idea to join the two ferrite cups with a very thin smear of Araldite to prevent the core from making an objectionable whine, but test the transformer before doing this as it will be impossible to separate the core afterwards.

6V version

As above, but with a secondary of 300 turns of 34 s.w.g., a primary of 6 + 6 turns of 18 s.w.g. and a feedback winding of 3 + 3 turns of 30 s.w.g.

ASSEMBLY

Drill the box as shown in Fig. 7, taking special care to deburr the holes for TR4, TR5, and the thyristor. Mount TR4 and TR5 with mica washers and insulators as shown in Fig. 5 and the transformer T1 with a 2BA bolt and spring washer. The stand-off insulator, and capacitor C7 can now be fixed in place and most of the inverter circuit wired up. Filter L1 is fixed with a ½in "p-clip" bolted to the case.

Assemble the printed circuit board and mount with 6BA bolts and ⅜in spacers. Then mount the thyristor with a mica washer and a 4BA nylon bolt. It should be possible to solder the gate and cathode leads of the thyristor directly to tags 11 and 4 respectively on the printed circuit board.

It is advisable to fix down the large capacitor C6 either by tying or by gluing as the considerable vibration puts a great strain on the capacitor leads.

Wire up the circuit as shown in Fig. 5 with 14/0076 connecting wire and mount a six-way 5 amp connector block on the outside of the box for the external connections. Fit two plastic covers to the power transistors to prevent accidental short circuits.

Photograph showing the completed Scorpio Mk 2 ignition system

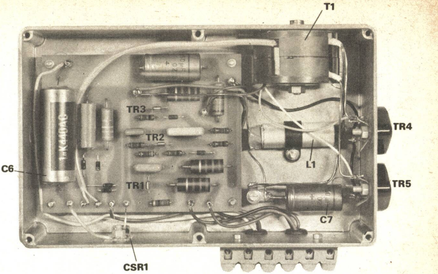

TESTING

Before the unit is installed in the car a few simple tests should be performed to ensure that it is operating correctly.

Temporarily disconnect the anode of the thyristor and connect the car battery to terminals E and F on the connector block, via a 2 amp fuse. The unit should be heard to "sing" immediately and 400V d.c. should appear between tags 1 and 4 on the p.c.b. (6 volt system—300V).

If the inverter has been wired incorrectly it will probably fail to oscillate at all, but if one base winding has been connected the wrong way round the inverter can oscillate on one transistor only. Under these conditions high voltage spikes are produced and up to 800V may appear across tags 1 and 4.

INSTALLATION

Positive earth

The wire or wires connected to the SW or "−" terminal of the ignition coil should be connected to terminal F on the unit instead, and the SW terminal of the coil connected to terminal A. Connect the CB or "+" terminal of the ignition coil to B, the contact breaker to C, and a good earth from the car body or the positive battery terminal to E.

Negative earth

Disconnect the wire or wires to the "+" terminal of the ignition coil and connect them instead to E on the unit. Connect the "+" terminal of the coil to B and the "−" terminal of the coil to A. Connect the contact breaker to D and a good earth to F.

Cold start coils

Some cars are fitted with a cold start coil, consisting of a low voltage coil with a series ballast resistor. The ballast resistor is usually connected to one of the terminals of the coil, but may take the form of a resistance cable. It does not make any significant difference to the spark produced by the unit if the resistor is left in series with the coil, but ensure that the supply current for the unit does not flow through the resistor as there will then be a considerable loss of voltage. In all cases the connection between the starter solenoid and the coil *must* be removed.

SEALING

When the unit is completed and tested and operation is satisfactory the box should be waterproofed to prevent any dampness getting into the electronics. This can be done either using ignition system waterproofing aerosol available under names such as W.D. 40 or "Coldstart", or bath caulking compound. Make sure the grommet holes are sealed as well.

PRECAUTIONS

Because of the very high open circuit voltage produced by this unit *never* attempt to remove the spark plugs whilst the engine is running, since not only is there a danger of breaking down the insulation of the coil, but the experimenter stands a good chance of getting a nasty shock.

In addition the thyristor can be exposed to transient voltages of up to 1,000V under these conditions, and may be destroyed.

TACHOMETERS

There are a large variety of tachometers in use, all differing in their exact requirements, so some experimental work may be necessary to obtain the best results.

There are two possible connection points for current operated tachos (the most common type). The lead from the ignition coil to terminal A on the unit carries a 10 amp short duration pulse and the lead to terminal E (negative earth) or terminal F (positive earth) carries a wider pulse of 4 amps amplitude. In both cases try coupling the wire through the tacho pickup both ways as the polarity of the pulse may be important.

Regarding voltage operated tachos, the high voltage type should operate if connected to terminal B on the unit whilst a low voltage type can be left connected to the contact breaker. If in doubt, try both positions. ★

. . . . never attempt to remove spark plug leads while engine is running

Gerry Brown . . .

ON THE FRINGE

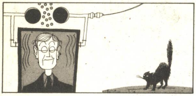

NEGATIVE IONS AGAIN

It seems only recently that we were chatting about the effects that charged atoms and molecules appear to have on us, other animals, and plant life. Since then I have read a number of quite serious reports about these "ionic beasties" and, indeed, discovered in addition that the people at the University of California actually have a faculty there which deals with the subject!

To refresh your memory about ions; generation of airborne ions all begins when sufficient energy is transferred to a gaseous molecule causing it to release an electron. This electron then "climbs aboard" any nearby molecule causing it, in turn, to become charged and in all likelihood convert to a negative ion (by virtue of the charge carried by the electron). The first molecule, however, has, in the process, turned into a positive ion. Umpteen of these molecular collisions occur, with the result that whole layers of species exist having either an overall positive or negative charge.

That, though, is by no means, the end of the story. Water molecules, too, get in on the act and jostle for position around individual ions, so forming somewhat larger ions.

According to Profesor A. Krueger of the University, mentioned earlier, these slightly larger (albeit, still tiny) molecules are of four types, namely $H^+(H_2O)_n$, $(H_3O)^+(H_2O)_n$, $O_2-(H_2O)_n$, and one with a hydroxyl group attached having the formula $OH-(H_2O)_n$. The $_n$ in the formulae has quite a small value.

Apparently, negative ions are the more mobile, when compared with the positive variety, and, since the Earth itself carries a negative charge, the former are repelled from the surface of the ground.

According to the experts, negative ions are decidedly the "good guys", which bears out our earlier thoughts on the subject. Unfortunately, the positive ("bad guys") are in the majority by something like a factor of 1·2 to 1. Pollution, additionally, helps to keep this ratio looking nasty, because, as you will recall, atmospheric dust has the habit of discharging any negative ions with which it comes in contact.

At the present time we can only produce (and successfully maintain) relatively small quantities of the beneficial ions; i.e., in buildings, or in cubicals where the size of the generator/transmission network can be kept within reasonable bounds. However, there ought to be sufficient encouragement for contemplating some really big set-ups. For example, plant growth has been caused to increase by as much as 50 per cent as a result of moderate exposure to air ions. Silkworms, too, hatched out earlier and larval growth was also accelerated. On the other hand, positive ions have been shown to increase the death rate among mice suffering from influenza!

In the final shakedown, it is worthy of mention that negative ions are suspected of lowering the blood serotonin (5-hydroxy tryptamine, 5HT) level, and since this is a hormone which, among other things, appears to be connected with the facilitation of neural signals across the synaptic junctions between nerves, it is not surprising to learn that high negative ion counts can result in profound mental effects. These may range from clearer headedness to a kind of tranquillity.

No amount of persuasion has yet encouraged my editor to change his mind about putting a taboo on a special high-voltage negative ion generator I intended to include. It could no doubt, be lethal in the wrong hands, so I guess his decision is the right one!

MAGNETO-CHEMISTRY

Still on the subject of chemy's, I notice that R. Skorsky of the Alabama University has discovered an interesting effect in ferric oxide, Fe_2O_3. Haematite, for that's it's other name, can, according to him, be reduced at much lower temperatures than previously achieved by simply surrounding the sample in an a.c. field of a few hundred gauss.

Skorsky has a theory that the cause of this effect is due to the increased pressure of hydrogen at the surface of the material resulting from its attraction to the magnetised iron (due to initial reduction of some of the ferric oxide at the beginning of the reaction).

Interestingly enough, C. Peters, over here, at the University of Surrey seems to think that the effect can be expected. His proposal amounts to the fact that since there is a considerable difference in the magnetic properties of the non-reduced material and final product, and because the reaction is going in a "direction" which favours a ferromagnetic substance as an end result, anyway, the outcome will be an *increased* tendency towards production of a magnetic material when a field of sufficient intensity is available. Sounds reasonable!

TAILPIECE

Washington, you'd think, had received its share of trouble. But it would seem the wags haven't finished with 'em yet. Only yesterday I came across this odd bit of logic.

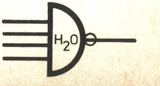

A.C. DETECTOR PROBE

By B. BOWLES

It is often necessary, particularly in radio circuits, to check for the presence of high frequency oscillations but most amateurs do not possess test equipment capable of responding to frequencies greater than a few megahertz. The probe described here will respond to frequencies between 200Hz and 30MHz, allowing use in general a.c. signal tracing. Any a.c. of a few millivolts or more will light a small light emitting diode (l.e.d.). The whole instrument can be held in one hand.

CIRCUIT DESCRIPTION

The complete circuit is shown in Fig. 1. Transistors TR1 and TR2 form a high gain a.c. amplifier which also rectifies the signal to drive the l.e.d. (D2). The configuration is known as a d.c. feedback pair. TR1 is biased just into conduction by feedback from the emitter of TR2. The preset potentiometer VR1 is used to set the d.c. conditions for the circuit. Components R5 and C2 and C3 form a filter which reduces the a.c. feedback so that the a.c. gain of the circuit is not reduced.

The input impedance is roughly equal to the value of R2 since C2 and C3 form a low impedance path for a.c. C3 is used to compensate for the inductive effect of C2 at high frequency. Diode D1 protects the input from negative voltage swings.

RECTIFICATION

The diodes in the emitter of TR2 serve to rectify the signal in the following manner. When the input swings positive TR1 will conduct tending to lower the voltage at TR2 base and by emitter follower action at TR2 emitter as well. The diodes cease to conduct and the voltage at TR2 emitter drops causing the current fed back to TR1 to drop, counteracting the effect of the positive input. If, however, the input goes negative, TR1 will conduct less causing TR2 base to rise. The diodes will, however, maintain the voltage at TR2 emitter almost constant so there will be no negative feedback to the base of TR1.

The circuit thus has high gain when the input goes negative but low gain when it goes positive. Thus an a.c. input will cause TR2 to conduct and hence pass more current through the l.e.d. The resistor in parallel with the l.e.d. allows enough current to pass through the transistor to keep the diodes conducting and the resistor in series limits the maximum l.e.d. current to less than 10mA.

The circuit is so stable that the battery voltage can fall to 7V without affecting performance.

COMPONENTS . . .

R1 4·7kΩ
R2 4·7kΩ
R3 120Ω
R4 1·2kΩ
R5 4·7kΩ
All ±5% $\frac{1}{8}$W carbon

Potentiometer
VR1 5kΩ linear sub-miniature skeleton horizontal mounting

Capacitors
C1 0·22μF
C2 10μF 6·3V tantalum bead
C3 1,000pF ceramic
C4 47μF 10V elect.

Diodes
D1 1N4148
D2 TIL209 light emitting diode
D3 OA91
D4 1N4148

Transistors
TR1, TR2 BC107 *or* BFY90 (2 off)

Miscellaneous
S1 Push-to-make, release-to-break push-button
B1 9V PP3 battery
Veroboard 0·1in matrix 2in × 0·9in
Veropins, 6BA and 8BA nuts and bolts and washers, wire, suitable case (see text)

A.C. DETECTOR PROBE

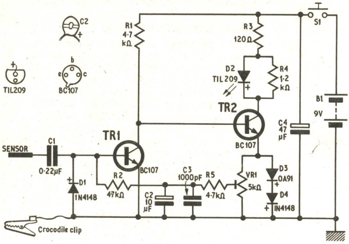

Fig. 1. Circuit diagram of the A.C. Detector Probe

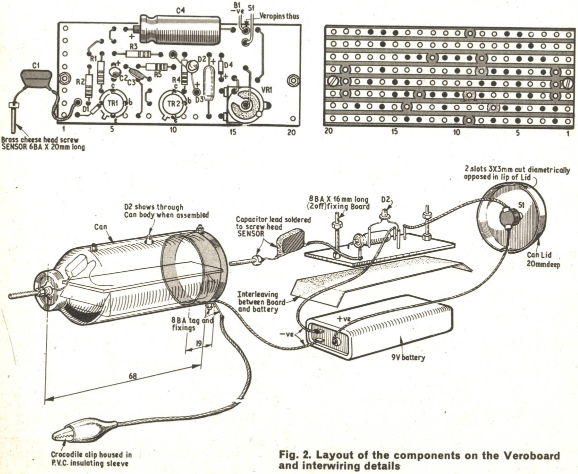
C4
B1
-ve
S1
Veropins thus
C1
R1
R3
R2
C2
C3
R5
D2
D4
R4
D1
TR1
TR2
D3
VR1
b
c
e
1
5
10
15
20
Brass cheese head screw
SENSOR 6BA X 20mm long
20
15
10
5
1
2 slots 3X3mm cut diametrically opposed in lip of Lid
8BA X 16mm long (2off) fixing Board
D2
S1
D2 shows through Can body when assembled
Can
Capacitor lead soldered to screw head SENSOR
Can Lid
20mmdeep
Interleaving between Board and battery
8BA tag and fixings
+ve
-ve
19
9V battery
68
Crocodile clip housed in P.V.C. insulating sleeve

Fig. 2. Layout of the components on the Veroboard and interwiring details

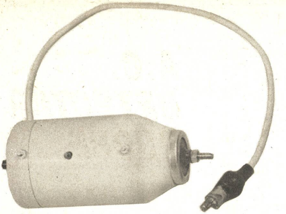

Photograph showing the completed A.C. Detector Probe

CONSTRUCTION

The circuit for the A.C. Detector Probe can be made very compact so that the whole unit can be held in the hand, making it convenient for testing equipment. All the components except the capacitor C1 are mounted on a small piece of Veroboard as shown in Fig. 2. Veropins are used for wire connections to the board. The l.e.d. is mounted on two pins higher than the rest of the board so that it shows through the side of the probe case. Take care not to overheat the l.e.d. when soldering.

Only one end of C1 is connected to the board.

SETTING UP

Before mounting in the case VR1 must be set up.

Connect the battery to the board. The l.e.d. should light with VR1 at one end of the track and extinguish at the other end. If the l.e.d. dims but does not go out, TR1 has low gain and should be replaced.

VR1 should be adjusted so that with no input D2 is just faintly lit. Any a.c. input with a frequency of 200Hz to 10MHz should now cause the l.e.d. to light.

The l.e.d. should flash each time the power is applied, this being due to the charging of C2.

Photograph showing the construction of the A.C. Detector Probe before assembly

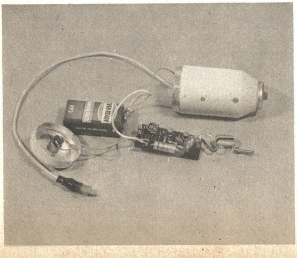

CASE CONSTRUCTION

The prototype case was made from an empty butane lighter fuel container of medium size but any aluminium tube will do. Great care should be taken that there is no gas left in the container.

First pierce the container about five inches from the tip or nozzle. This should be done well away from naked lights, preferably outdoors. Then cut the case into three parts as shown in Fig. 2.

Do not drill the holes yet. After the cutting and any necessary smoothing of the edges, the body of the probe, the end cap and a 19mm ring remain. This ring should be cut with scissors, its ends overlapped and then pushed into the probe body. Mark the overlap, remove the ring and cut off the overlap so that when re-inserted into the tube it fits with the ends butted together. The ring can now be glued into the body leaving about 6mm protruding from the body.

END CAP

This now makes a push-fit seating for the end cap, and provided the cuts have been made square gives the probe a good appearance.

The end cap should now be pushed on and held with adhesive tape and the holes drilled.

The holes in the end cap should now be enlarged into slots so that the end cap can slide over the two bolts which secure it. A hole is also drilled in the end cap to take the push button switch.

The plastic insert in the front of the tube should also be enlarged to 3mm.

FINAL ASSEMBLY

The free end of C1 is soldered to the head of a 12mm 6BA bolt. The solder tag on the mounting bolt should be soldered to the negative line on the board. The battery is then connected up. Some insulating tape is stuck inside the tube in case the circuit should touch, and the board pushed in making sure that the bolt on C1 goes through the end of the tube. The battery is then pushed in with a piece of card between it and the board to stop the metal case shorting the board.

The end cap is now fitted and nuts fitted to the bolts holding the end cap and the probe bolt. Attachment of the earth lead and crocodile clip completes the unit.

USE AND APPLICATIONS

The A.C. Detector Probe is very sensitive and its frequency response extends up to several megahertz. If high voltages are to be measured a resistor can be connected to the probe bolt to act as an attenuator.

Bandwidth can be extended by eliminating D1 and replacing TR1 and TR2 with BFY90 transistors which give high sensitivity up to about 70MHz. Above this frequency the l.e.d. may actually dim when connected to a.c. this being due to phase shift causing the normal rectifying action to be reversed. This is just as valid an indication of the presence of a.c. ★

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit-£24·95! (PLUS VAT)

The Cambridge – new from Sinclair
The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price – and by building it yourself you can save a further £5·50!

Truly pocket-sized
With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

Easy to assemble
All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

Total cost? Just £27·45!
The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32·95 – so you're saving £5·50! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.

Features of the Sinclair Cambridge

- *Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$, weight $3\frac{1}{2}$ oz.
- *Standard keyboard. All you need for complex calculations.
- *Clear-last-entry feature.
- *Fully-floating decimal point.
- *Algebraic logic.
- *Four operators (+, –, x, ÷), with constant on all four.
- *Constant acts as last entry in a calculation.
- *Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- *Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79}.
- *Clear, bright 8-digit display.
- *Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge.
Assembly time is about 3 hours.

Contents:

1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.

This valuable book – free!
If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.

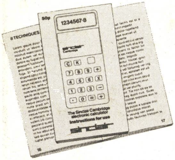

How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations.

Why only Sinclair can make you this offer
The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price.

But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.
And *you* benefit!

Take advantage of this money-back, no-risks offer today
The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £24·95 + £2·50 VAT. (**Total: £27·45**)
Price fully built: £29·95 + £3·00 VAT. (**Total: £32·95**)

PE 374

To: Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

Please send me

☐ a Sinclair Cambridge calculator kit at £24·95 + £2·50 VAT (Total: £27·45)

☐ a Sinclair Cambridge calculator ready built at £29·95 + £3·00 VAT (Total: £32·95)

*I enclose cheque for £ , made out to Sinclair Radionics Ltd, and crossed.

*Please debit my *Barclaycard/Access account. Account number

Name

Address

*Delete as required.

PLEASE PRINT

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

CRYSTAL CALIBRATION OSCILLATOR

by R. A. Penfold

THE PURPOSE of a crystal calibrator is to provide signals at standard frequencies over the medium and short wavebands, in order to allow accurate calibration of a radio receiver dial.

Providing the output from the calibrator is nearly a square wave it will be rich in harmonics (i.e. multiples of the fundamental frequency). A good calibration oscillator of fundamental frequency 200kHz will have harmonics which are reasonably strong right up to the upper limit of the short wave band (30MHz).

Using a crystal means that the fundamental frequency is predetermined, and extremely stable with respect to time and temperature.

In order to allow the signal to be easily identified on a receiver an audio oscillator has been included to modulate the r.f. signal.

CIRCUIT DESCRIPTION

The full circuit diagram is shown in Fig. 1 and can be seen to be divided into two sections, the audio oscillator and the crystal controlled r.f. oscillator. The active elements used in the unit are contained in two integrated circuits type μL914 whose internal circuits are shown in Fig. 2.

The μL914 is intended for use in logic systems and is one of the family of Resistor Transistor Logic (RTL) circuits. It can be adapted for use as an amplifier by inserting a biasing resistor between the collector and the existing base resistor of one of each pair of transistors and ignoring the other, thus forming two, one-transistor amplifiers from each i.c.

CRYSTAL OSCILLATOR

A crystal has the property that at one particular frequency (known as the series resonant frequency) its impedance (resistance to current flow) becomes very low while at all other frequencies its impedance is high.

In the oscillator circuit used in the calibrator the two, one-transistor amplifiers in the μL914 are connected in series *via* the crystal and the capacitor C6.

At the series resonant frequency the impedance of the crystal is sufficiently low for the positive feedback between the two stages to maintain oscillation. Because of the large positive feedback the switching between the two states (transistor on and transistor off) is rapid so that the output is almost square producing the large number of harmonics required. The 200kHz crystal used in the prototype gave enough harmonics to cover the long and medium bands.

AUDIO OSCILLATOR

The other i.c. and its associated components form an audio frequency oscillator with a frequency of about 2kHz. When applied to the crystal oscillator

COMPONENTS . . .

Resistors
R1 2·2kΩ
R2 47kΩ
R3 2·2kΩ
R4 100kΩ
R5 100kΩ
R6 33kΩ
R7 470Ω
R8 100kΩ
All ±10% $\frac{1}{4}$ watt

Capacitors
C1 0·1μF } ceramic
C2 0·1μF } ceramic
C3 120pF
C4 0·047μF ceramic
C5 100μF 10V elect.
C6 2,700pF
C7 0·01μF

Integrated Circuits
IC1, IC2 μL914 or equivalent (2 off)

Crystal
XL1 200kHz crystal with holder (Henry's Radio type FT241A)

Miscellaneous
S1 4-pole 3-way rotary
B1 9V battery type PP4 with clips
SK1 Coaxial panel mounting socket
2·8in × 1·4in Veroboard 0·1in matrix
Aluminium case approx. 4in × 3½in × 2in

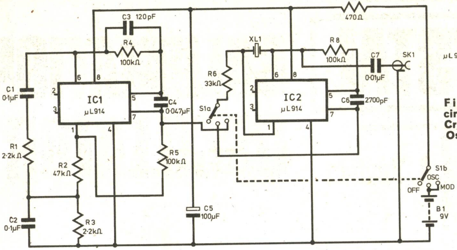

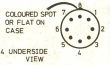

Fig. 1. Complete circuit diagram of the Crystal Calibration Oscillator

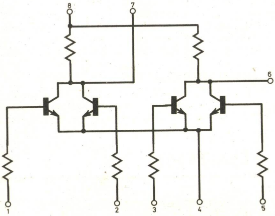

Fig. 2. Circuit diagram showing the internal circuit of the μL914 integrated circuit

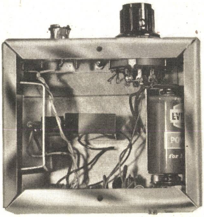

Photograph showing the arrangement of the components in the small aluminium case with the crystal mounted on its bracket

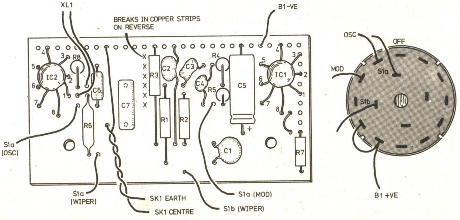

Fig. 3. Constructional details of the Crystal Calibration Oscillator

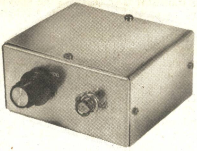

via R6 it varies the amplitude of the r.f. signal so that an audio signal of 2kHz will be heard when the receiver is tuned correctly.

The two amplifiers in the i.c. are connected in series to form an amplifier whose output is in phase with its input. The components C1, R1 and C2, R3 form what is known as a Wien Bridge, and it is these components that determine the frequency.

The switch therefore has three positions, OFF, OSC which gives the unmodulated crystal frequency and MOD which gives this frequency modulated by the oscillator.

Resistor R7 and capacitor C5 are included to reduce the supply voltage down to the 5V required by the i.c.s.

CONSTRUCTION

Construction is simple, all the components except the crystal, switch and output socket being mounted on a piece of Veroboard as shown in Fig. 3.

Any small aluminium case will do providing it is of sufficient size to accommodate all the components. It is wise to obtain a socket with the crystal as soldering to it directly could cause damage. A small bracket to hold the crystal can be mounted on the side of the box as can be seen in the photograph.

The switch used in the prototype is a four-pole three-way type with only two poles used.

USING THE CALIBRATOR

Once the unit has been completed, and all wiring checked for mistakes, a length of lead should be connected to the output socket and the unit turned on.

If the lead is now placed near a medium wave radio receiver, and the receiver is tuned over the band, strong signals from the calibrator should be received at intervals across the dial. Switching on the modulation should produce an audible note on these signals.

Using a 200kHz crystal, harmonics will be generated at 600kHz, 800kHz, 1MHz, 1·2MHz, and 1·6MHz. To find out which is which the receiver should be tuned to a known frequency (say Radio 1 on 1·214MHz) then the dial turned until the nearest signal from the calibrator is received (in the case above this will obviously then be 1·2MHz). Other frequencies can then be ascertained by counting the number of harmonics above or below the known frequency, as each corresponds to a difference of 200kHz.

This method of identification can be used on any band where the exact frequency of a station is known. ★

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.
This is YOUR page and any idea published will be awarded payment according to its merits.

OPTICAL COMMUNICATION SYSTEM

THE circuit described here is for a novel communication system using light beams to carry audio signals. Light emitting diodes (l.e.d.s) are particularly suitable for producing modulated light beams as they produce an intense concentrated spot

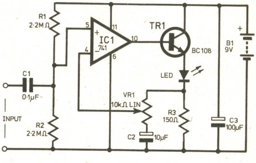

Fig. 1. Transmitter circuit diagram

BOILER GAS VALVE OPERATION AT LOW D.C.

PERHAPS the enclosed circuit idea would be of interest to your readers in view of impeding power cuts this winter. It allows a gas boiler mains operated gas valve, to be operated from a low voltage d.c. supply. The circuit has low battery consumption and low break current to minimise thermostat contact erosion.

I hesitate to recommend exact component values as the circuit was developed hurriedly to be ready for power cuts. In addition it was intended to run from a car battery so I did not bother to optimise the oscillator circuit or the capacitor and charge resistor values for minimum consumption.

I used an available Ferroxcube in the oscillator circuit and I do not know the exact turns ratios. I do not know how much variation exists between individual gas valves so that some experimentation by readers will therefore be required in both these areas.

Fig. 1 shows the circuit where R1 and C1 are included to prevent possible radio interference.

In operation, S1 is first closed charging C5 to about 120V. After a minute or so S2 is operated. The charge on C5 operates the gas valve, the voltage of which is prevented by D1 from falling much of light, have a linear current/light output relationship, and have a good high frequency response (the type of l.e.d. with a plastic diffusing dome is not suitable for use in this circuit).

The circuit shown in Fig. 1 will modulate the light from the l.e.d. using a cystal microphone or a loudspeaker output. IC1 acts as an a.c. amplifier with an input impedance of about 1MΩ. R1 and R2 are biasing resistors and together with IC1 and TR1 they produce a d.c. of 30mA in the l.e.d. VR1 and C2 control the a.c. feedback causing the input signal to be amplified and superimposed upon the bias.

To obtain the maximum range from the transmitter the optical system must be efficient. Either a convex lens or a concave mirror as shown in Fig. 2 can be used to convert the l.e.d. output into a parallel beam.

For efficient reception the light collecting area must be large; the author used a large concave make-up mirror costing 40p, but better quality mirrors will give better results.

The received light is concentrated onto a sensitive photo-Darlington transistor as shown in Fig. 3. Because the transistor is so sensitive the load resistor must be low to prevent saturation in daylight conditions.

At short range the signal across the load resistor is adequate to drive a crystal earpiece, though for longer range an a.c. amplifier and a loudspeaker are needed. The phototransistor output impedance is 1kΩ and most commercially available audio amplifiers are suitable.

The overall distortion is quite low, speech being excellent and music quite acceptable. The main cause of interference is mains lighting but this can be minimised by careful design of the optical system.

Transmitter and receiver must be accurately aligned and the transmitter gain should be carefully adjusted by means of VR1 to give maximum modulation without clipping. Clipping causes obvious distortion and is easily recognised.

J. N. Jones,
Cheshire.

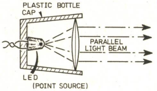

Fig. 2. Typical optical system for the transmitter

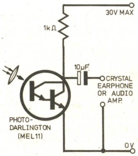

Fig. 3. Receiver circuit diagram

---

below the battery voltage. When the thermostat cuts out C5 recharges ready for the next operation.

C4 was included to adjust the charge rate of C5; it obviously affects the oscillator also and should not be needed in a fully developed design. D1 and D2 should have a minimum p.i.v. of say 200V and 400V respectively. D3 and D4 can be any silicon diodes.

I found that my Potterton boiler gas valve included a rectifier and that it closed at about 70V d.c. and held in at voltages below 11V. The consumption was about 2mA at 12V d.c.

For better economy of operation, a switching circuit might perhaps be devised to switch off the oscillator when the gas valve is energised but I have not tried this.

C. J. Collins,
Letchworth.

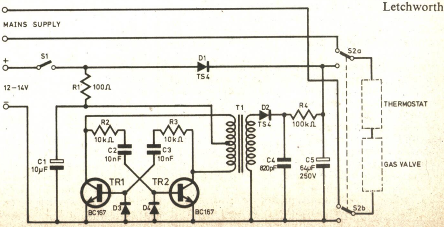

Fig. 1. Circuit for operating gas valve from low voltage d.c. supply

SLOW TIMEBASE OSCILLATOR

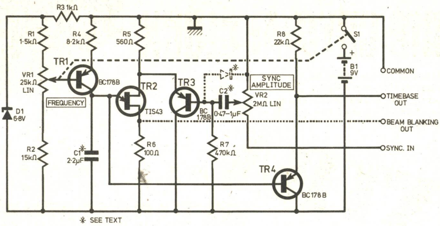

Fig. 1. Circuit diagram of the slow timebase oscillator

The sawtooth generator shown in the circuit diagram Fig. 1 was designed to extend the timebase range of a general purpose oscilloscope down to 1Hz. As well as the linear sawtooth with fast flyback, there is provision for an external synchronising signal and flyback blanking output.

The timing capacitor C1 of the relaxation oscillator, TR2, is charged by a constant current source from TR1. The base potential of TR1, controlling the constant current, is derived from the divider network R1, VR1 and R2. The Zener diode across the divider keeps the voltage at a constant level.

Since the sawtooth output at the emitter of the unijunction is at high impedance, the output is fed to an emitter follower to buffer the output against possible low impedance loads. The output should, however, not be taken to loads of less than 20kΩ impedance.

The synchronising input has a constant input resistance of 2MΩ and a portion of the signal is taken to an emitter follower via VR2 and C2. The effect of the emitter follower output is to modulate the supply voltage to the unijunction in step with the sync signal so that the sawtooth tends to be locked in frequency to the sync signal or a multiple thereof.

For adequate synchronisation even at the lowest frequencies, the input impedance of the emitter follower must be greater than the reactance of the capacitor at the lowest frequency.

The voltage rating of C2 should be sufficient to block the highest d.c. voltages likely to be encountered.

Adequate sync is available with a 0·3 to 1V r.m.s. input, but if higher voltages are used a diode should be wired as shown dotted, see Fig. 1, to prevent transistor emitter/base breakdown.

The frequency range of the oscillator is 1 to 60Hz, but could be extended up to 20kHz by varying the value of the timing capacitor C1. Capacitor C1 should be a low leakage type to ensure good linearity at low frequencies.

One of the many applications would be to use the oscillator for monitoring heart pulses in conjunction with the "Biological Amplifier" published in the January and February '73 issues (no back issues available). Care should be taken to ensure that the output from the Bio-amplifier is a.c. coupled to the vertical input of the monitoring 'scope.

M. H. George,
Upminster,
Essex.

AN IMPROVISED TAPE GUIDE

The drawing in Fig. 1 shows an improvised tape guide with height adjustment.

The guide itself is a ¼in brass binding post and is of the type which is threaded right through. These are obtainable from most well-stocked stationers.

The guide is simply fixed and adjusted by a BA bolt and three nuts.

Paul A. Koh,
Sunbury-on-Thames.

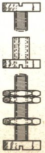

Fig. 1. Construction of the improvised tape guide

NEXT MONTH..

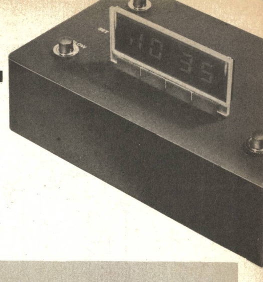

LIQUID CRYSTAL CLOCK

An easy-to-build mains operated digital alarm clock with an attractive crystal display. Besides a rousing audio alarm the clock has facilities to switch appliances at preset times. The display formats may be for 12 or 24 hours.

EXTRA

8 PAGE FEATURE

CAMERA ELECTRONICS

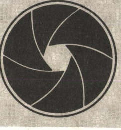

The introduction of electronics into cameras has brought a new degree of simplicity and accuracy to their use.

This special survey takes a selection of commercially available automatic and semi-automatic cameras and describes in detail the operation of the electronics involved.

Plus Special Series...

FIRST STEPS IN CIRCUIT DESIGN

WARNING—If you are a stickler for mathematical rigidity in circuit analyses don't read this novel beginners design series.

A completely fresh approach to design providing a predictable result from simple rules of thumb. Opening articles deal with small signal amplifiers based on popular transistor types.

PRACTICAL
ELECTRONICS

APRIL ISSUE ON SALE MARCH 8, 1974

Subject to the current National industrial situation at the time of going to press

Boolean Algebra—1

By B. J. Wood

A two part article providing an introduction to switching theory and concluding with a practical design of a simple adder/subtractor

George Boole published a treatise "An Investigation of the Laws of Thought" discussing the system now called Boolean Algebra over a century ago in 1861. The basis of his concept is that a statement in words may be represented in the first place by a letter of the alphabet.

Thus we can say that the letter A represents the statement "It is Sunday" and the letter B "It is sunny." These are positive statements and Boole assigned them a value 1.

Using his system it is very simple to identify the opposite statements "It is NOT Sunday" and "It is NOT sunny" by simply putting a bar over the chosen letter thus $\overline{A}$ or $\overline{B}$. This time Boole assigns the value 0 to these negative statements.

To test the system let us assume that we ask the question "Can I mow the lawn?", having set the conditions that one can, but only if it is sunny and also a Sunday.

Thus for a sunny Sunday we have both A and B, or shown mathematically, A.B, where both A and B are 1. Clearly the answer is 1, or positive. If either of the conditions is a negative then the answer will be negative. Thus $\overline{A}.B = 0$ and $A.\overline{B} = 0$ and it is not suitable to mow the lawn.

This type of decision making is called an AND function in which the factors have been multiplied together.

The condition could be "It is Sunday" or "It is sunny" in which case an addition of the two values would be required. If either had a value of 1 the result would be 1. This is called an OR function and in the case of the OR when both are 1 the rather odd result of $1 + 1 = 1$ arises but here the AND and OR are interchangeable.

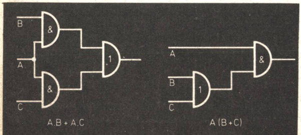

Fig. 1. Two logic diagrams which both represent the same overall function. Note the simpler form of the right-hand version

If the condition "Sunday and dry" is just as suitable for mowing the lawn as "Sunday and sunny" the decision to mow the lawn or not may be stated as A.B + A.C where C means "It is dry". Boolean algebra may be manipulated like any other algebra so that A.(B + C) means the same as A.B + A.C, giving the same arithmetic result.

If there are many conditions and alternatives the algebra can become quite involved. Generally, it is enough to work out one or two decisions at a time and build up the logic gradually.

LOGIC DIAGRAMS

In logic of the electronic kind, diagrams are useful to describe the flow of information. In the initial stages such diagrams contain only simple elements whilst later a whole group of elements may be put into one box and given a label in the same way that a collection of components may be labelled "amplifier". Fig. 1 shows the two ways of connecting AND and OR boxes which will give the same decision, to mow or not to mow the lawn.

The symbols used are fairly simple, being in the form of "D" shapes with inputs to the left and output to the right, a figure in the symbol denotes the number of inputs which must assume a logic 1 state for the output to be logic 1. An & sign in the symbol denotes an AND element.

Thus the operation to decide to mow the lawn under the Sunday and sunny or Sunday and dry conditions can be determined from these diagrams. Notice that the simplification of A.B + A.C to A.(B + C) also simplifies the diagram.

LOGIC ELEMENTS

Logic integrated circuits are available in many forms, simple and complex. They are very convenient packages, reducing external wiring to a minimum. Their low cost allows the constructor to build equipment which, a few years ago, would have been too expensive in terms of time and money. For the moment, however, elements built from discrete components will be discussed and related to the i.c.s as convenient. It does not matter that these devices are not identical as long as they react in the same way.

AND, OR, NOT ELEMENTS

These are the basic devices. More complex devices may be built from them. The AND may be made from diodes and a resistor as in Fig. 2a.

If either of the switches is closed representing an input of a 0 function then the whole of the voltage available from the supply is dropped across R1 and the output is at earth potential. Obviously, closing both switches has the same effect. It is only when both switches are open that a voltage is available at the output terminal.

The presence of this voltage is called logic 1. In its absence the state is logic 0. Why "logic"? Normally, the switches in the diagram are replaced by the outputs of other elements.

In practice absolute voltage levels are not possible at reasonable cost and so the design must allow for fluctuation. Thus logic 0 may be 0·5V or less and logic 1 anything over 2V.

To following elements these values are taken to represent 0 or 1. There is an electrical no-man's-land in between the two values which is avoided by the design and proper use of the devices involved.

AND

To return to the AND element, there is a table at 2a in which the states of A and B are given together with the resultant output for the four possible states of input. Called a truth table, this device shows that for a 1 output all inputs must be at logic 1. For any other combination the output is at logic 0. This applies for two, three or twenty inputs. Note that, to an AND input, an open circuit is a logic 1.

NOT

The NOT is shown at Fig. 2b It is simply an inverter in which, if a logic 1 voltage is applied at the base of the transistor it is switched hard on, the collector bottoms and the output goes to logic 0. If the base is at logic 0 the output is up near the rail voltage.

The second diagram at Fig. 2b is much more like an i.c. inverter in that the transistor is held on with a logic 0 output, unless presented with a logic 0 input. Like the AND, an open circuit input is treated as logic 1.

SYMBOLS

There are conventional symbols used to denote the various elements we have discussed so far as well as others to follow. They are used to avoid the need for either discussing or indeed even showing the actual components used in a particular element such as the diodes or transistors already noted.

Thus the elements AND and NOT, shown in detail at Figs. 2a and 2b may be shown as the two separate 'D' shapes joined together in Fig. 2c. Here the AND element is that with the ampersand (&) inscribed. This is intended to show that the element has inputs which have to be at logic 1 for the output to go to logic 1.

The second element with the small circle on the output line is the NOT element of Fig. 2c. Here the small circle denotes the logic 0 output obtained if the input goes to a logic 1.

NAND

The two elements at Fig. 2c denote NOT AND which is normally known as NAND. In fact this has a new symbol of its own as shown to the right in Fig. 2c, the small circle denoting the NOT output and the ampersand the requirement for logic 1 inputs for this. The truth table shows the outputs obtained for various inputs and it can be seen that only when all inputs are logic 1 will the output be logic 0. Of course, as before the logic 1 input includes an open circuit.

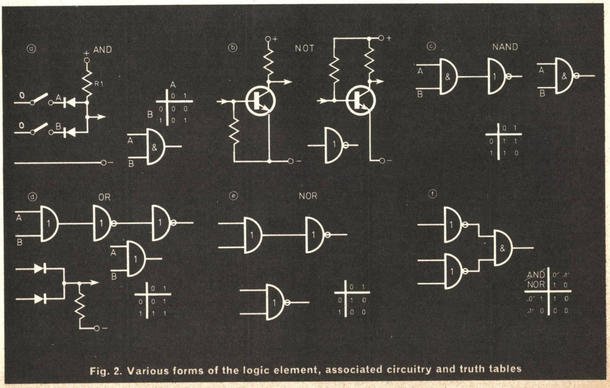

Fig. 2. Various forms of the logic element, associated circuitry and truth tables

OR

In its simplest form the OR element is made from diodes as shown at Fig. 2d. As can be seen these point in the opposite direction from those in the AND element. If a logic 1 appears at any input it becomes available at the output. The OR treats an open circuit as logic 0. In diode form the resistance of the load must be small enough to look like a logic 0 to the following element but large enough to demand only a reasonable current from the input source. The second diagram of Fig. 2d overcomes this difficulty by the introduction of two NOTs.

In this case the first element is a basic threshold element and the number inside denotes the number of inputs which must be at logic 1 for the output to be at logic 1. This element is followed by the two NOT elements and the whole may be shown as below.

NOR

A NOR element is an OR followed by one inverter element as shown at Fig. 2e. Only when all the inputs are at logic 0 is the output at logic 1. Under any other condition, as can be seen from the truth table the output is at logic 0.

INVERTED INPUTS AND OUTPUTS

Suppose that an AND is used with an inverter in each input so that 0 becomes 1 and vice versa. Fig. 2f truth table shows that it becomes a NOR. If, additionally, the output is inverted it then becomes OR. The reader should treat all the other truth tables in a similar fashion. It will be seen that any element may be made to exhibit the characteristics of the other three.

For what follows in this text the important point is that a NAND with inverted inputs becomes an OR. In general the devices to be used will be NANDs with diodes as ANDs when convenient plus NOTs. In the beginning it will be, perhaps, easier to recognise that an OR is required and then use a NAND with inverters in the inputs.

BINARY NUMBERS AND ARITHMETIC

In the kind of logic under discussion there are only the two states 1 and 0. Any process to be handled by the logic must therefore be described in these terms. In everyday arithmetic the radix of 10 is used with ten possible digits of 0 to 9. But if, as with Boolean logic, 2 is used as the radix, only the digits 0 and 1 are possible.

In the scale of 10 the number 286 can be written $(2 \times 10^2) + (8 \times 10^1) + (6 \times 10^0) = 200 + 80 + 6 = 286$.

In the scale of 2 the number 1101 means $(1 \times 2^3) + (1 \times 2^2) + (0 \times 2^1) + (1 \times 2^0) = 8 + 4 + 0 + 1$. (A number to the power of 1 is itself. Any number to the power of 0 is 1).

As a point of interest, decimal-to-binary conversion can be achieved as follows.

CONVERSION

Convert 83 to binary. This may be done mechanically by dividing the number 83 continuously by 2 ignoring remainders until the answer of 1 is reached. Write (—) against odd answers and (0) against even answers. The result looks like this.

83 1
41 1
20 0
10 0
5 1
2 0
1 1

If now the paper is turned so that the (—) against the final answer of 1 is at the left then this is the result in binary:—

1	2	5	10	20	41	83
1	0	1	0	0	1	1

where 1010011 = 64 + 16 + 2 + 1 = 83.

Conversely, to convert binary notation to its decimal counterpart simply multiply the left-most digit by two and add the following binary digit. Multiply the result by two adding the next binary digit and so on until the end is reached as below.

1	1	0	1	0	1
	3	6	13	26	53

The final figure, in this case 53, is the correct answer.

ADDING BINARY NUMBERS

The rules for adition of two binary digits (bits) are 0 + 0 = 0; 0 + 1 = 1; 1 + 1 = 0 and carry 1. Where there is a carry from the previous position it requires the following rules, 0 + 0 + 1 = 1; 0 + 1 + 1 = 0 and carry 1; 1 + 1 + 1 = 1 and carry 1.

Using the rules to add 6 to 7 —

Binary		Decimal
111	=	7
110	=	6
1101	=	13

SUBTRACTION

The rules for subtraction of two binary digits (bits) are 0 − 0 = 0; 1 − 1 = 0; 0 − 1 = 1 and borrow 1, 1 − 0 = 1. Where there is a borrow the following applies, 0 − 0 − 0 = 0; 1 − 0 − 0 = 1; 0 − 1 − 0 = 1 and borrow 1; 1 − 1 − 0 = 0; 1 − 1 − 1 = 1 and borrow 1, etc.

Thus if we subtract 3 from 5:

Binary		Decimal
101	=	5
011	=	3
010	=	2

Of course, problems arise when larger numbers have to be subtracted from smaller numbers. Using decimal notation, the human animal in fact reverses the process, subtracts the smaller from the larger and then calls the result a "negative."

YATES ELECTRONICS

(FLITWICK) LTD.
DEPT. PE, ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request. 10p stamp appreciated.

CALLERS WELCOME Mon.-Sat. 9 a.m.-5 p.m.

PLEASE ADD 10% VAT

RESISTORS

½W Iskra high stability carbon film—very low noise—capless construction
⅛W Mullard CR25 carbon film—very small body size 7·5 x 2·5mm.
½W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price 1–99	Price 100+
½	5%	4·7Ω–2·2MΩ	E24	1p	0·8p
½	10%	3·3MΩ–10MΩ	E12	1p	0·8p
½	2%	10Ω–1MΩ	E24	3·5p	3p
⅛	10%	1Ω– 3·9Ω	E12	1p	0·8p
⅛	5%	4·7Ω–1MΩ	E12	1p	0·8p
4	10%	1Ω–10Ω	E12	6p	5·5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0·5 watt 5% Iskra resistors 5 off each value 4·7Ω to 1MΩ. E12 pack 325 resistors **£2·40.** E24 pack 650 resistors **£4·70.**

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ¼W, lin ½W). Single, **12p.** Dual gang (stereo), **40p.** Single D.P. switch **24p.**

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0·1 matrix).
Sub-miniature 0·1W, **5p** each. Miniature 0·25W, **7p** each.

TRANSISTORS

AC107	15p	AF139	32p	BF177	28p	OC45	12p	2N3710	11p
AC126	12p	AF178	32p	BF178	32p	OC70	12p	2N3711	11p
AC127	15p	AF180	40p	BF179	32p	OC71	12p	2N3819	32p
AC128	15p	AF181	40p	BF180	32p	OC72	12p	2N4062	12p
AC131	12p	BC107	12p	BF181	32p	OC81	12p	2N4286	20p
AC132	12p	BC108	12p	BF194	14p	OC82D	12p	2N4289	20p
AC176	15p	BC109	12p	BF195	14p	2N2646	60p	40360	35p
AC187	22p	BC147	12p	BF197	15p	2N2904	20p	40361	35p
AC188	22p	BC148	12p	BF200	32p	2N2926	10p	40362	40p
AD140	50p	BC149	12p	BFY50	20p	2N3054	58p	40408	40p
AD149	45p	BC157	14p	BFY51	20p	2N3055	60p	ZTX108	15p
AD161	33p	BC158	14p	BFY52	20p	2N3702	13p	ZTX300	15p
AD162	36p	BC159	14p	BUY105		2N3703	12p	ZTX302	20p
AF114	20p	BC187	22p		£2·25	2N3704	13p	ZTX500	15p
AF115	20p	BD131	75p	OC26	45p	2N3705	12p	ZTX503	20p
AF116	20p	BD132	75p	OC28	50p	2N3706	11p		
AF117	20p	BD133	75p	OC35	50p	2N3707	12p		
AF118	38p	BF115	25p	OC42	12p	2N3708	10p		
AF126	20p	BF173	20p	OC44	12p	2N3709	11p		

ZENER DIODES

400mW 5% 3·3V to 30V, **12p.**

WIRE WOUND POTS, 3W, 10, 25,

50Ω and decades to 100kΩ, **35p.**

DIODES

RECTIFIER

BY127	1250V	1A	12p
IN4001	50V	1A	7p
IN4002	100V	1A	8p
IN4004	400V	1A	8p
IN4006	800V	1A	10p
IN4007	1000V	1A	10p

SIGNAL

OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	5p
BA114	8p

BRUSHED ALUMINIUM PANELS

12in × 6in = **25p**; 12in × 2½in = **10p**; 9in × 2in = **7p**

SLIDER POTENTIOMETERS

86mm × 9mm × 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K log. or lin. **40p.**
DUAL GANG, 10K + 10K etc. log. or lin. **60p.**
KNOB FOR ABOVE **12p.**
FRONT PANEL **65p.**
18 Gauge panel 12in × 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THYRISTORS

2N5060 50V 0·8A **30p,**

2N5064 200V 0·8A **47p,**

106F 50V 4A **40p,** 106D 400V 4A **65p.**

ALUMINIUM BOXES

AB7	2¾ × 5½ × 1½in	50p	
AB8	4 × 4 × 1½in	50p	
AB9	4 × 2¾ × 1½in	50p	
AB10	4 × 5¼ × 1½in	50p	
AB11	4 × 2½ × 2in	60p	
AB12	3 × 2 × 1in	44p	
AB14	7 × 5 × 2½in	84p	
AB15	8 × 6 × 3in	£1·08	
AB16	10 × 7 × 3in	£1·22	
AB17	10 × 4½ × 3in	£1·08	
AB18	12 × 5 × 3in	£1·20	
AB19	17 × 8 × 3in	£1·60	

HEATSINKS

2W **24p**	4W **45p**	TO5 clip **5p**	TO1 single **5p**
3W **36p**	6W **60p**	TO18 clip **5p**	TO1 double **8p**

TRANSFORMERS

All have 240V primary

MT30/2	0–12–15–20–24–30V	2A	£2·85
MT50/½	0–19–25–33–40–50V	½A	£1·90
MT50/1	0–19–25–33–40–50V	1A	£2·55
MT50/2	0–19–25–33–40–50V	2A	£3·50
MT60/½	0–24–30–40–48–60V	½A	£2·10
MT60/1	0–24–30–40–48–60V	1A	£2·80
MT60/2	0–24–30–40–48–60V	2A	£3·80

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0·001μF, 0·0015μF, 0·0022μF, 0·0033μF, 0·0047μF, **2½p.** 0·0068μF, 0·01μF, 0·015μF, 0·022μF, 0·033μF, **3p.** 0·047μF, 0·068μF, 0·1μF, **4p.** 0·15μF, **6p.** 0·22μF, **7½p.** 0·33μF, **11p.** 0·47μF, **13p.**

160V: 0·01μF, 0·015μF, 0·022μF, 0·033μF, 0·047μF, 0·068μF, **3p.** 0·1μF **3½p.** 0·15μF **4½p.** 0·22μF, **5p.** 0·33μF, **6p.** 0·47μF, **7½p.** 0·68μF, **11p.** 1·0μF, **13p.**

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0·01μF, 0·015μF, 0·022μF, **3p.** 0·033μF, 0·047μF, 0·068μF, **3½p.** 0·1μF, **4p.** 0·15μF, 0·22μF, **5p.** 0·33μF, **6½p.** 0·47μF, **8½p.** 0·68μF, **11p.** 1·0μF, **13p.** 1·5μF, **20p.** 2·2μF, **24p.**

MYLAR FILM CAPACITORS 100V

0·001μF, 0·002μF, 0·005μF, 0·01μF, 0·02μF, **2½p.** 0·04μF, 0·05μF, 0·068μF, 0·1μF, **3½p.**

CERAMIC DISC CAPACITORS

100pF to 10,000pF, **2p** each.

ELECTROLYTIC CAPACITORS—MULLARD 015/6/7

(μF/V) 1/63, 1·5/63, 2·2/63, 3·3/63, 4·7/63, 6·8/40, 6·8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6·3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6·3, 68/16, 100/4, 100/10, 100/25, 150/6·3, 150/16, 220/4, 220/6·3, 220/16, 330/4, **6p.** 47/63, 100/40 150/25, 220/25, 330/10, 470/6·3, **7p.** 68/63, 150/40, 220/40, 330/16, 1,000/4, **10p.** 470/10, 680/6·3, **11p.** 100/63, 150/63, 220/63, 1,000/10, **12p.** 470/25, 680/16, 1,500/6 3, **13p.** 470/40, 680/25, 1,000/16, 1,500/10, 2,200/6·3, **18p.** 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/6·3, 4,700/4, **21p.**

SOLID TANTALUM BEAD CAPACITORS 12p

0·1μF	35V	2·2μF	35V	22μF	16V
0·22μF	35V	4·7μF	35V	33μF	10V
0·47μF	35V	6·8μF	25V	47μF	6·3V
1·0μF	35V	10μF	25V	100μF	3V

VEROBOARD

	0·1	0·15
2½ × 3¾	22p	16p
2½ × 5	24p	24p
3¾ × 3¾	24p	24p
3¾ × 5	27p	27p
17 × 2½	75p	57½p
17 × 3¾	100p	78p
17 × 5 (plain)	—	82p
17 × 3¾ (plain)	—	60p
17 × 2½ (plain)	—	42p
2½ × 5 (plain)	—	12p
2½ × 3¾ (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2·5mm insulated	8p
Standard insulated	12p	3·5mm insulated	8p
Stereo screened	35p	3·5mm screened	13p
Standard socket	15p	2·5mm socket	8p
Stereo socket	18p	3·5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.
4 way screened cable, **15p**/metre.
6 way screened cable **22p**/metre.

BATTERY ELIMINATOR £1·50

9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF	64V	74p	2500μF	64V	80p	4500μF	16V	50p
2500μF	40V	74p	2800μF	100V	£2·60	4500μF	25V	£1·68
2500μF	50V	58p	3200μF	16V	50p	5000μF	50V	£1·10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0·01μF	10p	0·047μF	13p	0·22μF	20p
0·022μF	12p	0·1μF	13p	0·47μF	22p

POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series Values **4p each.**

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, **£2.** Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector **£5·20.** 12 or 24V battery operated audible alarm **£7·30.** As above for PP9 battery, **£6·40.**

PRINTED BOARD MARKER 97p

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

METERS £1.90

1½in scale 500mA, 1mA, 10mA, 100mA.

BULGIN MAINS CONNECTORS

3 pin 1½A	chassis plug	10p
	line socket	13p
3 pin 3A	chassis plug	10p
	line socket	14p
3 pin 5A	chassis plug	16p
	line socket	18p
3 pin 1½A	chassis socket	18p
	line plug	13p
3 pin 3A	chassis socket	21p
	line plug	23p
2 pin 5A	line plug	20p

THERMISTORS

VA1005	15p
VA1026	15p
VA1033	15p
VA1055S	15p
VA1066S	15p
VA1077	15p
R53	£1·35

WAVECHANGE SWITCH 23p

12W **1p,** 4W **3p,** 2W **2p,** 6W **2p,** 3W **4p.**

LINEAR IC's

709 14 pin dil.	40p
741 8 pin dil.	40p
741 14 pin dil.	38p
723 14 pin dil.	95p
747 14 pin dil.	85p
748 8 pin dil.	45p
Dil. sockets 14 pin and 16 pin	16p

WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

EMI 13 × 8, 3, 8 or 15 ohm	£2·03
EMI 13 × 8, 150 d/c 3, 8 or 15 ohm	£2·25
EMI 13 × 8, 450 t/tw 3, 8 or 15 ohm	£3·60
EMI 13 × 8 type 350 8 ohm	£8·25
EMI $6\frac{1}{2}$in 93850 4 or 8 ohm	£2·80
EMI 8 × 5 d/cone roll/s 8 ohm	£2·50
Baker Group 25 3, 8 or 15 ohm	£6·60
Baker Group 35 3, 8 or 15 ohm	£7·50
Baker De Luxe 12in d/cone	£9·62
Baker Major 12in	£7·50
Kef T27	£4·67
Kef T15	£5·50
Kef B110	£6·16
Kef B200	£7·42
Kef B139	£10·72
Kef DN8	£1·92
Kef DN9	£1·37
Kef DN12	£4·12
Kef DN13	£2·75
Fane Pop 100W 8/15 ohm	£21·45
Fane Pop 60W 8/15 ohm	£12·26
Fane Pop 50W 8/15 ohm	£10·17
Fane Pop 25/2 25W 8/15 ohm	£5·94
Fane Pop 15W 8/15 ohm	£4·40
Fane Crescendo 15in 8 or 15 ohm	£27·50
Fane Crescendo 12A 100W 8 or 15 ohm	£24·20
Fane Crescendo 12B bass	£24·20
Fane 807T 8in d/c roll/s 8 or 15 ohm	£3·85
Fane 808T 8in d/cone 8 or 15 ohm	£2·64
Goodmans Axent 100 tweeter	£6·60
Goodmans 8P 8 or 15 ohm	£3·80
Goodmans 10P 8 or 15 ohm	£4·49
Goodmans 12P 8 or 15 ohm	£11·55
Goodmans 15P 8 or 15 ohm	£17·05
Goodmans 18P 8 or 15 ohm	£29·70
Goodmans Twinaxiom 8	£6·79
Goodmans Twinaxiom 10	£7·61
Elac 9 × 5, 59RM109 15 ohm, 59RM114 8 ohm	£2·53
Elac $6\frac{1}{2}$in d/c roll/s 8 ohm	£3·22
Elac $6\frac{1}{2}$in d/cone 8 ohm	£2·59
Elac 4in tweeter TW4	£1·21
Wharfedale Super 10 RS/DD	£9·80
Coral $6\frac{1}{2}$in d/cone roll/s 8 ohm	£2·42
Siran $6\frac{1}{2}$in 3 or 8 ohm	£1·44
Richard Allan 12in d/c 3 or 15 ohm	£2·20
10in × 6in 3, 8 or 15 ohm	£1·92
8in × 5in 3 or 8 ohm	£1·38
7in × 4in 3 or 8 ohm	£1·38
$2\frac{1}{2}$in 64 ohm or 70mm 80 ohm	65p
Adastra Hiten 10in 10W 8 or 15 ohm	£2·80
Eagle DT33 dome tweeter	£5·45
Eagle HT15 tweeter	£3·66
Eagle CT5 tweeter	£1·25
Eagle CT10 tweeter	£2·54
Eagle MHT10 tweeter	£3·74
Eagle FR4	£4·45
Eagle xover CN23, 28, 216	£1·15
Sp. matching transformer 3–15 ohm	£1·10
Celestion MF1000 25W horn 8 or 15 ohm	£10·45
Celestion PS8 (for Unilex)	£2·16
Celestion G12M 8 or 15 ohm	£12·00
Celestion G12H 8 or 15 ohm	£15·00
Celestion G15C 8 or 15 ohm	£24·00
Celestion G18C 8 or 15 ohm	£33·00

Car Stereo speakers—ask for leaflet.

SPEAKER KITS

Wharfedale Linton 2	£8·75
Wharfedale Glendale 3	£15·75
Wharfedale Dovedale 3	£24·25
Richard Allan Twinkit	£7·95
Richard Allan Triple 8	£11·75
Richard Allan Triple Assem.	£17·50
Richard Allan Super Triple	£20·75
Goodmans DIN 20	£8·58
Fane Mode One	£9·00
Kefkit 2	£24·75
Kefkit 3	£35·50
Peerless 2–8	£5·50
Peerless 10–2	£8·47
Peerless 20–2	£10·41
Helme XLK 25 (pair)	£18·17
Helme XLK 50 (pair)	£37·18

Stephen speaker kits and cabinets—send for free booklet "Choosing a Speaker".

PRICES INCLUDE VAT.

Free with orders over £7—"Hi-fi Loudspeaker Enclosure" book. All units guaranteed new and perfect. Prompt despatch. Carriage and insurance: speakers 35p each, speaker kits 75p each, tweeters and crossovers 20p each.

Carriage and insurance 50p per kit.

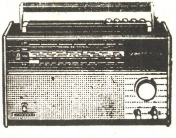

RADIOS/CASSETTES/AMPS

Grundig RF310	£21·25
Grundig Signal 500	£27·00
Grundig Mariner TR865	£32·00
Grundig Elite Boy 500	£27·00
Grundig Melody Boy 500	£27·00
Grundig Melody Boy 1000	£38·75
Grundig Yacht Boy 210	£34·25
Grundig RF430 mains	£27·00
Grundig RF310 mains	£22·75
Grundig Top Boy	£16·75
Grundig Satellit 1000	£121·00
Grundig C230 cassette	£28·00
Grundig C402 cassette	£27·00
Tandberg TP41	£37·75
BASF 9301 radio/cassette	£64·00
Bush VTR178 5 band (inc. AIR)	£29·00
Trio KA2000A	£33·00
Trio KA2002	£41·00
ITT/KB Colt	£9·95
ITT/KB Golf Preset	£21·25
ITT/KB Weekend Auto	£16·00
ITT/KB Europa	£18·00
ITT/KB SL53 cassette	£22·82
ITT/KB Studio 60M cassette	£29·32
ITT/KB Studio 73 stereo cassette	£44·00
Koyo KTR1664 8 waveband	£40·00
Koyo KTR1770 11 waveband	£56·50
Koyo KTR1883 5 band (inc. AIR)	£23·50
GEC 200 Radio/Cassette	£31·00

Prices include VAT.

Carriage and insurance 75p. FREE with each radio—world radio stations book.

PA/DISCO AMPLIFIERS
(carr. and ins. £1)

Baker 100W	£46·00
Linear 30/40	£25·00
Linear 40/60	£30·00
Linear 80/100	£55·00

FREE with speaker orders over £7

"Hi Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.
Carriage and insurance 25p per speaker (tweeters and crossovers 15p). ALL PRICES QUOTED INCLUDE VAT.

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF. Radios, etc.: 10 Swan Street, Wilmslow, Cheshire, SK9 1HF.
Telephone: Wilmslow 29599.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £10 each. Special snip price **£6·33** plus 25p post and insurance. Don't miss this terrific bargain.

12 VOLT $1\frac{1}{2}$ AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price **£2·20,** plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15 amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price **£6·33** plus 65p post.

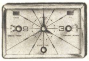

15A ELECTRICAL PROGRAMMER

Learn in your sleep; Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders — have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price **£2·15** + 20p p. & p. or with glass front chrome bezel **83p** extra.

DRILL CONTROLLER
NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. **£1·95.** 13p post and p. Made up model also available. **£2·95.**

THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price **£2·95,** plus 20p post and insurance. Industrial model 5A **£3·30.** Not on plate.

MINIATURE SEALED RELAY

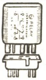

American made. Our Ref.: REL A1. Measures only $\frac{3}{4}$in wide × $\frac{1}{4}$in thick and $\frac{3}{4}$in high and it's a double change over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 9-12 volt will close it. Ideal for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price **28p** including base.

SCORPIO Mk II

As featured this issue! Our 1974 catalogue lists hundreds of bargains and probably many of the parts needed for this project. 66p brings the catalogue and the next 6 monthly supplements.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at **25p** each.

Please add 10% V.A.T.

TERMS: 10% discount if ten of an item ordered, send postage where quoted—other items, post free if order for these items is £6·00, otherwise add 25p.

J. BULL (ELECTRICAL) LTD.

(Dept. P.E.), 7 PARK STREET, CROYDON CRO 1YD
Callers to 102/3 Tamworth Road, Croydon

Whilst a machine can be made to do this it is not part of the present discussion as it is complex and requires very lengthy explanation.

Take the case of subtracting 7 from 3. In decimal the answer is obvious, it is minus 4 (−4). Equally, if you take 5 from 2 the answer is −3. In binary terms using the methods so far discussed this is not so. Thus in the case of 3 − 7:

```
    011
    111
(1) 100
```

And in the case of 2 − 5:

```
    010
    101
(1) 101
```

In both cases there is a borrow 1 with nothing to subtract it from and in fact even if there were more positions to the left the resultant row would be filled with figure 1's with an unsatisfied borrow 1 emerging at the far left.

The same thing happens in decimal notation if one persists in trying to subtract using this type of approach. Thus in decimal the results could be shown as (1)6 and (1)7, the figure in the bracket being the unsatisfied borrow.

In fact the two answers 6 and 7 are the tens complements of the correct answers, subtract the 6 and the 7 from 10 and you have, in positive form, the correct answer.

Similarly, with the binary computation the results must be subtracted from 8 which, in binary is 1000 There are two snags to this situation. First the operator needs to know before the event that a negative result will arise and re-arrange the inputs.

COMPLEMENT

The word complement was mentioned. This is the key to the answer. In the 1 and 0 binary system the 1s complement of 1 is 0 and vice versa.

Ignoring the unsatisfied borrow in the two binary answers, if 1 is changed to 0 and vice versa 100 becomes 011 and 101 becomes 010 or 3 and 2 in decimal, both wrong by being 1 too few. What is really needed is the complement of 7 which can be arranged by subtracting 1 before the complement is taken. To do this the unsatisfied borrow from the left is carried round to the right to form part of the subtraction. Using the examples again—

```
    011      010
    111      101  Subtract
(1) 100  (1) 101
    ↳ 1      ↳ 1  Subtract
    011      100  Answers
    100      011  Complements, both in fact
                                 negative.
```

The complements give the answer in positive form but it is known that the answer is negative because the mode of operation is subtract and there is the borrow 1.

The following table gives all the possible results for the system. The reader is advised to work out columns b, c and d to gain an understanding.

Decimal	a positive	b negative	c neg − 1	d complement of c
0	0000			
1	0001	1111	1110	0001
2	0010	1110	1101	0010
3	0011	1101	1100	0011
4	0100	1100	1011	0100
5	0101	1011	1010	0101
6	0110	1010	1001	0110
7	0111	1001	1000	0111
8	1000			
9	1001			
10	1010			
11	1011			
12	1100			
13	1101			
14	1110			

Next month: Constructional details of a simple adder/subtractor will be given

BOOK REVIEWS

IMPROVING YOUR HI-FI

By John Earl
Published by Fountain Press
203 pages, 8¾in×5½in. Price £3·00

THE title of this book is slightly misleading as the theme is not really improving hi-fi systems but getting the best out of them. Written in a non-technical style, it appears to be directed towards the people who are not satisfied with low-fi but are not *au fait* with all the technicalities and jargon of high-fi and are perhaps not getting all they could from their set-up.

This is strictly a practical book dealing with things like the importance of correct earthing, the need to maintain correct dynamic ranges throughout the system, and the meaning of specifications.

For the non-technical enthusiast this book would be essential reading before he considers buying expensive hi-fi equipment S.R.L.

FET APPLICATIONS HANDBOOK

Edited by Jerome Eimbinder
Published by Foulsham-Tab
350 pages, 8½in × 5½in. Price £1·85

THIS book is a collection of applications data from a wide number of manufacturers and provides an excellent reference work for anyone who is involved in the use of field effect transistors (f.e.t.s).

All types of f.e.t.s are described from the simple junction types to the complementary M.O.S. systems used in the pocket calculators of recent years. Many applications of f.e.t.s are described ranging from voltage controlled resistors to amplifiers, switches and digital circuits. S.R.L.

ESP etc

By Brian Baily...

" . . . more things in heaven and earth . . . "

The first reaction of many readers when they read the above title was probably to ask "What's a subject like this doing in P.E.?" You may well ask. Others may have taken the view that our friend Ed is off his rocker and yet others may take the opposite view, and exclaim "At last Ed has come to his (extra) senses, and allowed publication of this previously 'tabooed' subject."

The fact is, this article was written long before Uri Geller's impressive fork—(if not mind)—bending demonstration on BBC television, but friend Ed was a little sceptical I think before that night when I talked him into viewing it! We must all be grateful for his open-minded approach in allowing this article to appear.

Naturally, there will be those for and those against, but whether you are a sheep or a goat (these are the two rather inappropriate terms that sceptics use to describe the believers and non-believers, respectively) there is always a good reason to give the whole matter another look. Remember, times change, and so do peoples' ideas, evidence, equipment, and even phenomena.

* * *

First, let us get quite clear what is meant by extra-sensory perception (E.S.P.). Take the words literally, and you will get the best definition possible. They mean perception of events (etc.) by some means not obviously connected with any of the five normal senses.

* * *

Let me hasten at this point to make a quick distinction or two. Unfortunately, the Press, Radio, and TV media often treat all subjects which cannot be explained by presently-accepted terms of analysis—witchcraft, black magic, ghosts . . . what-have-you—as E.S.P. This is a great pity, because there are quite different forms of unexplained phenomena, and the only true umbrella titles which could be fairly used to embrace the lot, would be "the occult" (unknown), or "paraphysics."

* * *

However, when writing a subject which must be sensational, so-called evidence is often dragged in from as many different fields as possible to try and get the reader all excited and on the edge of his chair. In fact, the opposite often happens, and many are left believing less one way or the other than when they first started reading!

So, though other subjects come under the above general headings, they are not all E.S.P. Such subjects will be described in this series as the etceteras.

Reasonable Approach

It must always be remembered that there is no commonplace thing of today that, at some time past, was not considered impossible. We are all still learning, and humility is, to the truly rationally-minded, something which can only increase, not decrease, with increased knowledge. Just because humans have relied on speech, sight, etc., for communication and direct physical intervention for getting things done, is not to say that there is no need of a set of equally valid alternatives in his make-up, which needs only to be developed, once discovered—always given he adopts a reasonable approach.

* * *

E.S.P. is nothing new. One can go back to the New Testament, if this is considered far enough, and find references to "gifts of the spirit". I will not digress further, other than to say that evidence of the possibility of E.S.P. has cropped up probably as long as man has inhabited the earth, and in other forms, before.

E.S.P. rarely occurs under controlled laboratory conditions. Read a person's thoughts say, once, and then try to continue the pattern under strict control, and the chances are that you will not succeed again even once. This is the very thing the sceptic looks for, and when it occurs he jumps in with both feet and says "Pooh what did I tell you?" Ok, ok, I say, I am as aware as you that the effect is not repeated under these conditions, but might this not be a point worthy of investigation? "Why?" he would say, and then would come my first analogy, speaking as an electronics bod.

* * *

Take out your comb and comb your hair, or if this is greasy, rub it on your Harris Tweed jacket. The comb is now charged, and you can prove this by picking up small bits of tissue paper from the table. What voltage? Would you believe there's probably more than 5kV on it? There probably is!

Now ask the sceptic to get his voltmeter and place one lead on the gas or water pipe (earth) and the other on the comb and see what he gets. Tell him the meter is at least 20 kilohms per volt. Naturally, he gets no reading. Why, you were on the 250V scale and the needle didn't even flick. Reason is that the meter requires current to flow to operate its needle, and the amount of current required for this is in excess of what the comb could supply despite over 5kV on it, at the point of contact with the meter lead.

* * *

Could E.S.P. be elusive for some similar reason? By this I mean, by trying to "tap" its power to prove an experiment, could we require too much "current" for the source to supply and operate our "meter"? Perhaps the tension caused by the anticipation of all spectators present draws off the very power we are trying to use!

Next month: The Scientists Investigate.

ELECTROVALUE

CATALOGUE 7

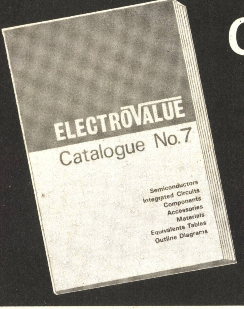

An **A** to **Z** guide to component buying

On the index page of Catalogue 7, between "Aluminium Boxes" and "Zener Diodes" are over 200 references to contents amounting in all to thousands of items, classified, described, often illustrated, and priced. There is a wealth of technical diagrams and data. At 25p, Catalogue 7 is excellent value by any standard. With the 25p Refund Voucher it costs you virtually nothing when you order £5-worth or more.

25p **INCLUDING 25p REFUND VOUCHER AVAILABLE ON ORDERS £5 OR MORE LIST VALUE**

★ *A selection from EV Catalogue 7*

TRANSISTORS
and semi-conductors of many types from simple diodes to ICs photo-sensitive devices, threshold switches, etc., etc.

MINITRON DIGITAL INDICATORS
3015 F Seven segment filament, compatible with standard logic modules. 0–9 and decimal point; 9mm characters in 16 lead DIL (Some alphabetical symbols available), **£1·20.**
Suitable BCD decoder driver, **£1·15.**
3015G showing + or — and 1 and dec. pt, **£1·20.**

DALY ELECTROLYTIC CAPACITORS
in cans, plastic sleeved
1,000mF/25V, **28p;** 2,000mF/25V, **37p;** 5,000mF/25V, **62p;** 1,000mF/50V, **41p;** 2,000mF/50V, **57p;** 5,000mF/50V, **£1·18;** 1,000mF/100V, **82p;** 2,200mF/100V, **£1·56;** 5,000mF/100V, **£2·91.**

POLYESTER CAPACITORS TYPE C280
Radial leads for P.C.B. mounting. Working voltage 250V d.c.
0·01, 0·015, 0·022, 0·033, 0·047, **3p** each; 0·068, 0·1, 0·15, **4p** each; 0·22, **5p;** 0·33, **7p;** 0·47, **8p;** 0·68, **11p;** 1·0, **14p;** 1·5, **21p;** 2·2, **24p.**

SILVERED MICA CAPACITORS
Working voltage 500V d.c.
Values in pF—2·2 to 820 in 32 stages, **6p** each; 1,000, 1,500, **7p** each; 1,800, **8p**; 2,200 **10p;** 2,700, 3,600, **12p** each; 4,700, 5,000, **15p** each; 6,800 **20p;** 8,200, 10,000 **25p** each.

POTENTIOMETERS
ROTARY, CARBON TRACK.
Double wipers for good contact and long working life.
P20 SINGLE linear 100 ohms to 2·2MΩ, **14p** each.
P20 SINGLE log, 4·7kΩ to 2·2MΩ, **14p** each.
JP20 DUAL GANG linear 4·7kΩ to 2·2MΩ **48p** each.
JP20 DUAL GANG log, 4·7kΩ to 2·2MΩ **48p** each.
JP20 DUAL GANG log/antilog 10L, 22K, 47K, 1MΩ only, **48p** each.
JP20 DUAL GANG antilog 10k only **48p.**
2A DP mains switch with any of above **14p** extra.
Decades of 10, 22 and 47 only available in ranges above. **SKELETON CARBON PRESETS 6p** each.

SLIDER POTENTIOMETERS
Linear or log, 10kΩ to 1MΩ in all popular values, **30p** each.
Escutcheon plates, black, white or light grey, **10p** each.
Control knobs blk/wht/red/yel/grn/blue/dk. grey/lt grey, **7p** each.

ELECTROLYTIC CAPACITORS
Axial Lead

uF	3V	6·3V	10V	16V	25V	40V	63V	100V
0·47	—	—	—	—	—	—	**11p**	**8p**
1·0	—	—	—	—	—	**11p**	—	**8p**
2·2	—	—	—	—	**11p**	—	**8p**	**9p**
4·7	—	—	—	**11p**	—	**8p**	**9p**	**8p**
10	—	—	—	—	**8p**	**9p**	**8p**	**8p**
22	—	—	**8p**	—	**9p**	**8p**	**8p**	**10p**
47	**8p**	—	**9p**	**8p**	**9p**	**8p**	**10p**	**13p**
100	**9p**	**8p**	**8p**	**8p**	**9p**	**10p**	**12p**	**19p**
220	**8p**	**8p**	**9p**	**10p**	**10p**	**11p**	**17p**	**28p**
470	**9p**	**10p**	**10p**	**11p**	**13p**	**17p**	**24p**	**45p**
1,000	**11p**	**13p**	**13p**	**17p**	**20p**	**25p**	**41p**	—
2,200	**15p**	**18p**	**23p**	**26p**	**37p**	**41p**	—	—
4,700	**26p**	**30p**	**39p**	**44p**	**58p**	—	—	—
10,000	**42p**	**46p**	—	—	—	—	—	—

This is EV Service

DISCOUNTS
Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14·99. 15% on orders £15 and over.

PACKING & POSTAGE
FREE in U.K. For mail orders for £2 list value and under, there is an additional handling charge of 10p.

GUARANTEE OF QUALITY
All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, "seconds" or sub-standard merchandise is offered for sale.

Prices quoted do not include VAT, for which 10% must be added to total nett value of order. Prices subject to alteration without notice. S.A.E. with written enquiries please.

RESISTORS

Code	Watts	ohms	1–9	10–99 (see note below)	100 up	
C	1/20	82–220K	**9**	**8**	**7·5**	
C	⅓	4·7–470K	**1·3**	**1·1**	**0·9**	**nett**
C	½	4·7–10M	**1·3**	**1·1**	**0·9**	**nett**
C	¾	4·7–10M	**1·5**	**1·2**	**0·97**	**nett**
C	1	4·7–10M	**3·2**	**2·5**	**1·92**	**nett**
MO	½	10–1M	**4**	**3·3**	**2·3**	**nett**
WW	1	0·22–3·9	**7**	**7**	**8**	
WW	3	1–10K	**7**	**7**	**8**	
WW	7	1–10K	**9**	**9**	**8**	

Codes: C—carbon film, high stability, low noise. MO—metal oxide, Electrosil TR5, ultra low noise. WW—wire wound, Plessey.

Values: All E12 except C⅓W, C¾W and MO½W at E.12.
E12, 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82.
E24 as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.
Tolerances—All 5% except MO at 2% and WW at 10% ± 0·05Ω.

Prices and in pennies each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) 100 rates apply to units of 100 only.

ZENER DIODES full range E24 values: 400mW: 2·7V to 36V, **14p** each; 1W: 6·8V to 82V, **21p** each; 1·5W: 4·7V to 75V, **48p** each. Clip to increase 1·5W rating to 3 watts (type 266F) **4p.**

VEROBOARD
Copper clad 0·1 in. matrix—2·5 × 3·75 ins. **24p.** 3·75 × 3·75 ins., **27p.** 2·5 × 5 ins., **27p.** 3·75 × 5ins., **30p.**
Copper clad 0·15 in. matrix—2·5 × 3·75 ins., **18p.** 3·75 × 3·75 ins., **27p.** 2·5 × 5 ins., **27p.** 3·75 × 5 ins., **33p.**
Vero spot face cutter (any matrix), **43p.** 0·040 pins (for 0·1 matrix) per 100, **30p.** 0·052 pins (for 0·15 matrix) per 100, **30p.**

GIRO ACCOUNT No. 38/671/4002

All postal communications, mail orders, etc., to Head Office at Egham address, Dept. PE3.

ELECTROVALUE LTD

28 ST. JUDES ROAD · ENGLEFIELD GREEN · EGHAM · SURREY TW20 0HB
Telephone: Egham 3603 Telex 264475
NORTHERN BRANCH: 680 BURNAGE LANE · BURNAGE · MANCHESTER M19 1NA
Telephone 061-432 4945

Hours of business (both addresses) 9-5.30 p.m. 9-1.30 p.m. Saturdays

U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081

Connoisseur

THE B.D.2 TURNTABLE ASSEMBLY

The famous B.D.2 belt drive turntable with press button speed change has now been developed to feature a newly designed matt and brushed aluminium trim, and the Perspex cover has an easy "hinged-on, hinged-off" movement. The B.D.2 is available as a chassis unit or spring mounted on a wood plinth, as above.

S.A.U.2 PICK-UP ARM

Recognised as one of today's most advanced pick-up arms it features

* Auto-bias Compensator
* Hydraulic Lowering Device
* Precision Balance
* Adjustable Head Shell

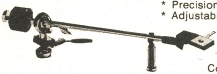

S.C.U.1 STEREO CARTRIDGE

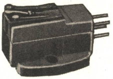

A quality cartridge designed specifically for the person who appreciates his equipment.

Contact your dealer for information or send stamp for a brochure.

A. R. SUGDEN & CO. (ENGINEERS) LTD

Atlas Mill Road, Brighouse HD6 1ER Telephone: Brighouse (04847) 2142. Telegrams and cables: Connoiseur, Brighouse

---

ERSIN
Multicore
5 CORE SOLDER

for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS

Size 5
Savbit alloy
18 swg. **24p**
(illustrated).
Size 19A
60/40 alloy
18 swg. **25p**
Size 15
60/40 alloy
22 swg. **28p**

IDEAL FOR HOME CONSTRUCTORS

Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges, **36p**

Size 12 REEL for Service Engineers and Electricians.
18 swg.
Savbit alloy, **£1·16**

BIB WIRE STRIPPER AND CUTTER

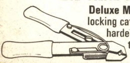

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. **75p**

Prices shown are recommended retail, excluding V.A.T.
From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to
Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP

FERRANTI

Buy from the experts!

- * ALL DEVICES BRAND NEW, TOP GRADE AND TO FULL SPEC.
- * WE HAVE STOCKS OF ALL DEVICES FOR IMMEDIATE DELIVERY.
- * WE CAN SUPPLY ANY FERRANTI DEVICE TO ORDER, Send S.A.E. for quotation.
- * WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS, WITH A STAFF OF EXPERIENCED ENGINEERS.

ZN414 £1·32 WITH CIRCUITS AND DATA

BFS59	**15p**	ZTX310	**9p**	ZTX504	**43p**	ZS170	**10p**
BFS60	**20p**	ZTX311	**10p**	ZTX510	**17p**	ZS171	**13p**
BFS61	**20p**	ZTX312	**10p**	ZTX530	**21p**	ZS172	**16p**
BFS96	**15p**	ZTX313	**11p**	ZTX531	**22p**	ZS174	**17p**
BFS97	**23p**	ZTX314	**13p**	ZTX550	**17p**	ZS176	**23p**
BFS98	**20p**	ZTX320	**31p**	ZTX551	**17p**	ZS178	**38p**
ZTX107	**9p**	ZTX330	**15p**	2N3055	**72p**	ZS270	**11p**
ZTX108	**8p**	ZTX331	**16p**			ZS271	**16p**
ZTX109	**11p**	ZTX382	**13p**	*** DIODES ***		ZS272	**18p**
ZTX212	**14p**	ZTX383	**15p**	ZS120	**8p**	ZS274	**19p**
ZTX213	**14p**	ZTX384	**18p**	ZS121	**10p**	ZS276	**26p**
ZTX214	**15p**	ZTX450	**17p**	ZS122	**13p**	ZS278	**37p**
ZTX300	**12p**	ZTX451	**17p**	ZS123	**16p**		
ZTX301	**13p**	ZTX500	**12p**	ZS124	**18p**	*** ZENERS ***	
ZTX302	**17p**	ZTX501	**13p**	ZS140	**25p**	KS030A to	
ZTX303	**14p**	ZTX502	**17p**	ZS141	**43p**	KS180A	
ZTX304	**21p**	ZTX503	**14p**	ZS142	**33p**	all types	**19p**

MOTOROLA MJE2955 **£1·30**; MJE3055 **72p** each.
RCA PRICES SLASHED! CA3075 **99p**; CA3090Q **£3·25** limited quantity only.
P.E. TRIFFID. ZT1711 **24p**; 2N1132 **25p**.

SCORPIO II P.C.B. 95p; SIEMENS BStB0246 **£1·05**.

FREE! Our comprehensive catalogue giving data and connection diagrams for a wide range of Ferranti semiconductors. Just send S.A.E.

POSTAGE AND PACKING 10p. FREE ON ORDERS OVER £2.
ALL OUR PRICES INCLUDE V.A.T.

DAVIAN ELECTRONICS
PO BOX 38 . OLDHAM , LANCS , OL2 6XJ

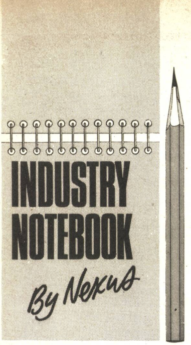

INDUSTRY NOTEBOOK

By Nexus

BEATING THE CLOCK

Coming into service in a few weeks is Cantat 2, the 2,805-mile long transatlantic cable costing £30 million and capable of handling 1,840 telephone conversations simultaneously.

Laying of the cable had its share of drama. The mini-submarine *Pisces 3* sank while burying part of the cable on the UK continental shelf. The two-man crew were rescued, happily, after three days of being trapped on the sea-bed. The craft was also recovered and will be in service again soon.

The cable-laying ship *Mercury* was also damaged in a storm of force 11, forcing her to operate for a time on emergency power. But despite all the upsets, the cable-laying was completed six days ahead of schedule which makes quite a change in a world of go-slow or stop.

The other heartening news out of the *Cantat 2* saga is that because of the vastly increased number of channels available, the new cable is 20 times cheaper per circuit than the transatlantic cable laid between the UK and USA in 1956. But don't expect the cost of a call to go down.

HI-FI HIT

Hi-Fi, like the motor car, has become the index of a nation's prosperity. But what was astonishing in the good old days of 1973 was the number of equipments advertised to the general public—not the addict—at prices of £200 up, and reportedly selling well. Top weight equipment for the real enthusiast was typically Trio's Package 10 quadraphonic package listed by Lasky's at £460 cash or £577·48 on HP. At the bottom of the pack were plenty of modest units around £30.

A survey of the audio market "Finresearch Audio Industry Service" published by Ovum Ltd. at £30 lists 380 companies active in the audio business which has trebled in size in three years. Such was the boom, according to editor Tony Beaumont, that three new companies have been entering the field every week for the past two years.

First "audio separates" I recall was back in 1937 when I was enchanted with the reproduction of 78 r.p.m. discs on the famous corner horn loudspeaker developed by P. A. H. G. Voigt. But I see Ferguson claiming they "invented" what they call Unit Audio just 30 years later in 1967. Claims and counter-claims in the colour ads are numerous and often funny.

This clearly will not be a good year for the audio business. HP restrictions and a general tightening of belts will see to that. But the audio scene will not collapse. It'll still be comparatively big-biz as well as show-biz.

MAINTENANCE PROBLEM

Try to imagine 15,000 fixed transmitter/receivers of powers from five to 300W and 25,000 mobile vehicle-mounted transmitter/receivers. Tack on 30,000 personal portable transmitter/receivers and 200,000 nickel/cadmium batteries to power them. And just add to that little lot 15,000 pocket alarm receivers and all their batteries.

In round figures, this is the size of the maintenance problem of the Home Office Directorate of Telecommunications which looks after the procurement and servicing of Britain's police and firefighting networks as well as a few others.

The problem was discussed in some detail by A. N. Holdstock in a paper given at "Automatic Testing 73", the first full-scale exhibition and conference to be held on the subject. The magnitude of the Home Office's task was such that automatic testing was seen as a solution as early as 1967. Holdstock reports several equipments now in full service but reports that no radio equipment manufacturers are yet designing sets with in-field maintenance by ATE as a prime consideration. Consequently, there are always snags in having to build special jigs and adaptors before ATE can be successfully used in the field.

The next big job is provision of ATE for 1,000 alpha-numeric video-display terminals now being fitted in police stations throughout the country. Each of them has six large PCBs and 530 TTL integrated circuits.

A new and profitable outlet for ATE on production lines is in the automotive industry. No less than six papers were read on the subject including one on the experience of Ford in checking out car electrical systems. Ford will, in fact, move 100 per cent to ATE for this purpose in the UK during this year.

So successful was "Automatic Testing 73" that organiser John Shearsmith has already announced November 5, 1974, as opening day for the next show. The first exhibition attracted 50 companies and 4,000 visitors. Seven hundred delegates attended the technical conference.

INNOVATION

I have to confess that I was one of the sceptics when Advance Electronics went into the calculator business in mid-1972. Like many others I had underrated their ingenuity.

Advance didn't take the easy path by buying off-the-shelf LSI devices. They designed their own in conjunction with General Instrument Microelectronics and did it in such a way that they could be used in many other applications. So watch out for some competitive lines from Advance in business machines.

MINICOMPUTER LEAGUE

A league table of minicomputer manufacturers prepared by Modern Data in the USA shows Digital Equipment Corporation still way ahead with 16,473 units shipped in 1973. Runner up is Data General with 4,230 and Hewlett Packard in third spot has a score of 2,855, marginally ahead of Varian with 2,337. Honeywell ranks only No. 8 with 1,564 while Texas Instruments, mighty in other fields, is bottom and unlucky thirteenth with 452.

Computer Automation, who came to the market with the concept of the Naked Mini, ranks fifth with 1,915 units shipped in the year. Stripped of all frills, the Naked Mini was offered at a rock-bottom price. Since then CA has offered the "Computer-on-a-card" with the whole package on a single printed circuit board, an even lower priced unit for people who want to build a computer into their own equipment.

Digital Equipment still has the stranglehold in minis that IBM has in the larger machine market. But watch out for increased competition and a re-shuffling of positions lower down the table.

PATENTS REVIEW...

AUTOMATIC COMMENTARIES

The Secretary of State for Defence has a new British patent (BP 1 325 161) which concerns automatic machines for playing commentaries to accompany exhibits in museums or exhibitions.

The object of the invention is to provide a replay device which works on the closed loop principle and will always be at the correct start point when brought into action by a new listener. This is relatively easy to achieve if the loop is only to play once, but much more difficult to achieve if the listener is to be afforded the opportunity of listening to the loop more than once.

BP 1 325 161

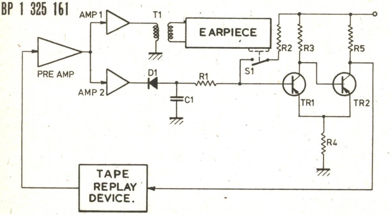

The tape replay device works with an endless loop of magnetic tape and its audio output passes through the pre-amplifier to two amplifiers, see Fig. 1. The output from amplifier 2 is fed to a simple rectifier circuit, D1 and C1, and passed via R1 to a Schmitt trigger circuit, TR1, TR2. The Schmitt trigger is connected to the power supply and controls operation of the tape replay motor.

The switch S1 is mounted as part of a telephone handset and closes when the earpiece is lifted off its rest. The switch is open while the earpiece is on its rest. Amplifier 1 is coupled to the headset earpiece through transformer T1.

When a would-be listener picks up the earpiece S1 closes and the Schmitt trigger changes state to start the tape transport motor. The audio frequencies from the tape are reproduced through the earpiece and used, after rectification, to hold the Schmitt in its active state. This holding action will continue even when the earpiece is returned to its rest.

However, when the audio signals cease, the voltage across C1 dies away and the Schmitt trigger reverts to its former state and the tape motor stops. Thus the loop stops at its start position. The decay time constant of the voltage across C1 must, of course, be long enough to tide over natural pauses in the commentary.

If the listener wishes to hear the commentary through again, then he keeps the earpiece off its rest; the switch S1 holds the trigger circuit active and the loop is replayed.

The patent specification also details a twin channel system which can be used to control visual displays.

SCORING FOR BOXING AND OTHER SPORTS BP 1 325 644

Although BP 1 325 644 from E. J. Sweeny of Ohio, USA, is intended primarily for the scoring of boxing matches by judges, its technology will find wider uses.

The specific intention is to enable three judges to score independently with the sum of their points displayed on a common board.

A master console and three identical scoring booths are spaced round a boxing ring with a visual score board mounted above. A single point will be recorded on the score board only after the master console has received a multiple number of point pulses from the individual scoring booths, e.g. three point pulses must be accumulated from one or more booths before a single point is recorded on the board.

The controls within the booths are duplicated for the two fighters.

VEHICLE GUIDANCE BP 1 320 314

Interest appears to be growing in the technology of automatic vehicle guidance. In BP 1 320 314 Autotrack Systems Ltd., and P.C.D. Ltd., jointly describe the automatic remote control of a tractor ploughing a field. The principle of the invention, however, is much more widely applicable, e.g. garden lawn mowing to model car control.

Guide wires are buried half a metre deep and six metres apart along the routes which the vehicle should take. These guides carry a continuous tone current of 2kHz and the a.c. field that this produces is detected by a detector head on the vehicle.

The detector head has a vertical pick-up coil and a horizontal pick-up coil. With the head exactly above the guide wire there is no phase difference between the outputs of the two coils, but if the head is moved to one side a phase difference appears in the appropriate sense and of magnitude proportional to the distance moved.

The two coils in the patented circuit control solenoids for left and right turn and operate pneumatic, hydraulic or electrical steering gear on board the tractor.

Copies of Patents can be obtained from the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price 25p each

C. T. ELECTRONICS

267 Acton Lane, London W4 5DG
Tel. 01-994 6275

MAIL ORDER DEPT./REGISTERED OFFICE/COMPONENT COUNTER

semiconductors

AC107	35p
AC125	25p
AC126	25p
AC127	27p
AC128	28p
AC176	27p
ACY17	25p
ACY18	30p
ACY19	30p
ACY20	25p
ACY39	55p
ACY21	30p
AD140	60p
AD149	65p
AD161	40p
AD162	40p
ADZ11	£1·80
AF114	25p
AF115	25p
AF116	25p
AF117	25p
AF118	60p
AF172	30p
ASY28	30p
ASZ21	60p
BA102	33p
BA112	50p
BA114	16p
BA156	15p
BC107	12p
BC108	12p
BC109	12p
BC147	12p
BC148	12p
BC149	12p
BC153	15p
BC157	14p
BC158	15p
BC159	15p
BC169C	14p
BC182	14p
BC183	14p
BC184	14p
BC212	14p
BC213	14p
BC214	14p
BC238	12p
BC239	12p
BCY30	40p
BCY31	55p
BCY32	95p
BCY33	45p
BCY34	60p
BCY38	65p
BCY39	£1·00
BCY55	£1·60
BCY70	22p
BCY71	22p
BCY72	25p
BD121	75p
BD123	75p
BD124	80p
BD131	75p
BD132	75p
BD153	75p
BD156	75p
BDY11	£1·40
BDY17	£1·60
BDY19	£1·95
BF152	20p
BF194	14p
BF195	15p
BFX29	30p
BFX84	30p
BFX85	30p
BFX86	30p
BFX88	30p
BFY10	35p
BFY44	50p
BFY50	25p
BFY51	25p
BFY52	25p
BFY53	25p
BFY90	66p
BSW63	65p
BSW68	80p
BSY95A	12p
C111	50p
C426	40p
BY100	15p
BY126	20p
BY127	20p
BY164	65p
IS100	15p
IS103	20p
MJ340	55p
MJ481	95p
MJ2801	£1·25
MJ2901	£2·20
MJE340	50p
MJE370	75p
MJE371	90p
MJE520	65p
MJE2955	£1·95
MJE3055	85p
MM1613	43p
MM1712	60p
MPF102	45p
MPF103 (2N5457)	35p
MPF104 (2N5458)	35p
MPF105 (2N5459)	40p
MPSA06	35p
MPSA16	30p
MPSA56	35p
MPSU06	75p
MPSU56	70p
NKT135	35p
NKT222	25p
NKT401	85p
NKT404	80p
NKT773	30p
NKT774	25p
OA5	20p
OA10	20p
OA47	10p
OA70	12p
OA79	12p
OA81	10p
OA90	10p
OA91	10p
OA200	10p
OA202	10p
OA210	35p
OA211	36p
OC16	90p
OC19	85p
OC22	55p
OC26	65p
OC28	65p
OC35	60p
OC36	65p
OC42	40p
OC44	20p
OC45	20p
OC70	15p
OC71	17p
OC72	20p
OC75	25p
OC76	25p
OC77	40p
OC81	25p
OC83	25p
OC84	25p
OC139	30p
OC140	30p
OC170	25p
OC171	30p
OC200	50p
OC201	60p
OC202	75p
TIP29A	49p
TIP30A	58p
TIP31A	62p
TIP32A	74p
TIP33A	£1·05
TIP34A	£1·55
TIP35A	£3·35
TIP36A	£2·65
TIP41A	75p
TIP42A	90p
TIP29B	58p
TIP30B	66p
TIP31B	70p
TIP32B	82p
TIP33B	£1·12
TIP34B	£1·68
TIP35B	£2·81
TIP36B	£3·64
TIP41B	83p
TIP42B	98p
TIP29C	71p
TIP30C	78p
TIP31C	85p
TIP32C	£1·05
TIP33C	£1·30
TIP34C	£1·90
TIP35C	£3·20
TIP36C	£4·10
TIP41C	95p
TIP42C	£1·10
TIS50	40p
ZTX107	15p
ZTX300	15p
ZTX500	16p
ZTX501	20p
ZTX504	50p
ZTX531	30p
ZTX550	25p
IN659	8p
IN914	8p
IN916	8p
IN4001	8p
IN4002	9p
IN4003	9p
IN4004	10p
IN4005	12p
IN4006	15p
IN4007	18p
IN4148	7p
2N696	25p
2N697	20p
2N698	25p
2N706	12p
2N706A	15p
2N708	15p
2N930	20p
2N1132	25p
2N1302	16p
2N1303	16p
2N1304	25p
2N1305	25p
2N1306	25p
2N1307	25p
2N1308	25p
2N1309	25p
2N1613	25p
2N1711	25p
2N2147	70p
2N2160	65p
2N2217	25p
2N2218	25p
2N2219	25p
2N2222	20p
2N2222A	25p
2N2398	70p
2N2646	50p
2N2846	£1·50
2N2904	25p
2N2905	25p
2N2096	25p
2N2907	25p
2N2926	12p
2N3053	25p
2N3054	65p
2N3055	50p
2N3232	70p
2N3525	95p
2N3702	14p
2N3703	12p
2N3704	12p
2N3705	12p
2N3706	12p
2N3707	12p
2N3708	12p
2N3709	12p
2N3771	£2·70
2N3772	£2·75
2N3773	£2·95
2N3819	35p
2N3820	55p
2N3866	85p
2N3904	22p
2N3905	25p
2N4058	12p
2N4059	12p
2N4060	12p
2N4061	12p
2N4126	17p
2N4286	15p
2N4287	15p
2N4288	15p
2N4289	15p
2N4290	15p
2N4444	£1·90
2N4871	35p
2N4920	60p
2N5191	96p
2N5194	£1·10
40360	50p
40361	50p
40362	55p

DIGITAL INTEGRAL CIRCUITS

SN7400	20p
SN7401	20p
SN7402	20p
SN7403	20p
SN7404	20p
SN7405	20p
SN7406	30p
SN7407	30p
SN7408	20p
SN7409	45p
SN7410	20p
SN7411	23p
SN7412	42p
SN7413	30p
SN7416	30p
SN7417	30p
SN7420	20p
SN7422	48p
SN7423	48p
SN7425	48p
SN7427	42p
SN7428	50p
SN7430	20p
SN7432	42p
SN7433	70p
SN7437	65p
SN7438	65p
SN7440	20p
SN7441AN	75p
SN7442	75p
SN7443	£1·00
SN7445	£2·00
SN7446	£2·00
SN7447	£1·75
SN7448	£1·75
SN7450	20p
SN7451	20p
SN7453	20p
SN7454	20p
SN7460	20p
SN7470	30p
SN7472	30p
SN7473	40p
SN7474	40p
SN7475	55p
SN7476	45p
SN7480	80p
SN7481	£1·25
SN7482	87p
SN7483	£1·00
SN7484	90p
SN7486	45p
SN7490	75p
SN7491AN	£1·00
SN7492	75p
SN7493	75p
SN7494	80p
SN7495	80p
SN7496	£1·00
SN7497	£6·25
SN74100	£2·50
SN74104	£1·45
SN74105	£1·45
SN74107	50p
SN74110	80p
SN74118	£1·00
SN74119	£1·90
SN74121	65p
SN74122	£1·35
SN74123	£2·70
SN74141	£1·00
SN74145	£1·50
SN74150	£3·35
SN74151	£1·10
SN74153	£1·35
SN74154	£2·00
SN74155	£1·55
SN74156	£1·55
SN74157	£1·80
SN74160	£2·60
SN74161	£2·60
SN74162	£3·40
SN74163	£3·40
SN74164	£2·75
SN74165	£4·00
SN74166	£4·00
SN74167	£6·25
SN74170	£4·10
SN74174	£2·00
SN74175	£1·35
SN74176	£1·60
SN74177	£1·60
SN74180	£1·55
SN74181	£7·00
SN74182	£2·00
SN74184	£2·45
SN74185A	£2·40
SN74190	£1·95
SN74191	£1·95
SN74192	£2·00
SN74193	£2·00
SN74194	£2·50
SN74195	£1·85
SN74196	£1·50
SN74197	£1·50
SN74198	£4·60
SN74199	£4·60

TRIACS

SC40D 6A 400V	£1·00
SC40E 6A 500V	£1·20
SC45D 10A 400V	£1·25
SC45E 10A 500V	£1·45
SC50D 15A 500V	£1·85
DIAC	25p

S.C.R.

BTY 79/400R	75p
CRS 1/05	25p
CRS 1/10	30p
CRS 1/20	30p
CRS 1/40	35p
CRS 3/035	30p
CRS 3/10	30p
CRS 3/40	50p
CRS 3/60	60p
CRS 7/400	70p
CRS 7/600	98p
CRS 16/100	65p
CRS 16/200	72p
CRS 16/600	£1·05
C 106D	65p
TIC 44	35p
16RC/20	70p
2N3525	£1·05

LINEAR OP. AMPS

709C TO99/DIL	40p
723C TO99/DIL	£1·05
741C DIL	50p
747C TO99/DIL	£1·10
72748P DIL	65p
723C TO99	£1·05
CA3014	£1·55
CA3018	£1·00
CA3028	£1·20
CA3036	£1·00
CA3046	95p
CA3090	£4·85
CA3048	£2·34
MC1303L	£1·85
MFC4000B	60p
SL403D	£1·50
ZN414	£1·25
LM309K	£1·90
TAD100	£1·90
TOKO FILTER	45p
TAD110	£2·00

ZENER DIODES

BZY88 series 400mW. 3·3-33V. 5%	15p
1·5 Watt range	25p
10 Watt range	45p

L.E.D.

TIL 209 H.P. 5082 28p

L.D.R.

ORP 12 50p

LOW COST OSCILLOSCOPES

Cossor—1035 D.B.; 1049 Mk. 3A, D.B.; 1049 Mk. 4, D.B.

EMI—WM2; WM3B; WM7; WM8; WM16; WM18; WM26.

Solartron—AD557; CD513.2; CD523 S.2; CD643; CD6431.1; CD711 S.2.

All prices and details on application, phone 01-994 6275. Inspection welcome—call at warehouse.

BRIDGE RECTIFIERS

BY164 1·4A, 200V	57p
CIC2-100 2A, 100V	39p
6A, 100V	65p

V.A.T.

Unless otherwise stated all prices are **EXCLUSIVE** of V.A.T. Please add 10% to all orders. Carriage: orders under £5 + 20p. Over £5 post free.

WAREHOUSE

20–24 BEAUMONT ROAD, W.4

SURPLUS COMPONENTS TEST EQUIPMENT, etc., etc.

THOUSANDS OF BARGAINS

Test Equipment ★ Oscilloscopes ★ Signal Generators ★ Counters Cabinets ★ Bridges ★ Meters ★ Transmitters ★ Receivers ★ Power Supplies Laboratory Equipment ★ Galvanometers ★ Audio Equipment ★ Video Equipment ★ Meters ★ Battery Chargers ★ Motors ★ Etc. ★ Etc.

20 TONS OF ELECTRONIC EQUIPMENT

Resistors ★ Relays ★ Capacitors ★ Switches ★ Transformers ★ Meters Potentiometers ★ Component Panels ★ Semiconductors ★ Cable ★ Valves Etc. ★ Etc. ★ Etc.

Regret no lists available. Personal callers only. Cash and Carry only.

AUDIO ACCESSORY SHOP

17 TURNHAM GREEN TERRACE, CHISWICK, W.4

VALVE AMPLIFIERS

5 Watt	£12·50
15 Watt	£24·50
30 Watt	£29·50
50 Watt	£36·25
150 Watt	£75·90
500 Watt	£124·50

TRANSISTOR AMPLIFIERS

FAL Phase 50W	£39·93
FAL Phase 100W	£69·95

DISCO CONSOLES

FAL Disco Mk. 2	£82·99
FAL Power Disco (with 70W. rms. Amp.)	£123·75

HEAVY DUTY LOUDSPEAKERS

★ SPECIAL OFFER PRICE ★

15 in. 70W. E.M.I. 8 ohm .. £19·50

Decca 8in. 10 watt Hi-Fi Speaker, plus matching tweeter, £7·50 complete. Suitable 2-way cross-over .... £1·21

SPEAKER CABINETS

Suitable for any 12 in. speaker, covered in Rexine and Vynair. Size: 18 in. × 18 in. × 8 in. approx. £9·90

DISCO LIGHTING

Sound-Light Module	£7·90
3 Channel Sound-Light	£22·50
Oil Wheel 6 in. dia	£5·25
Suitable ½ rpm Motor	£1·00
Strobe 4 Joule	£25·00
Single Flash Box (100W Red, Blue, Gn., Yel.)	£7·50
Triple Flash Box	£16·25

TEAK VENEERED SPEAKER CABINETS

For 8 × 5 in. speaker	£3·50 each
For 8 in. + Tweeter	£5·00 each
For 13 × 8 in.	£6·50 each
For 12 in. + Tweeter	£9·90 each

ALSO: Audio Connecting Leads, Tape, Cassettes, Stereo Systems, Mixers, Mic. Stands, Speaker Cloth, Turntables, Plinths, Covers, etc., etc.

SGS EA1000 3W AMPLIFIER MODULE

£2·45

HANDBOOK 10p

Solidev 15W, Class B Audio Amp, Thick Film Circuit, £3·65; Handbook, **15p.**

TBA800 5W Audio I.C., **£1·50;** Data, **10p.**

UA041 5W Amplifier Module, **£3·75**

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

Pack No.

1 500 Carbon resistors, ¼, ½, 1, 2 watt.
2 100 Electrolytic Condensers.
3 250 Ceramic, Polystyrene, Silver Mica, etc., Condensers.
4 250 Polyester, Polycarbonate, Paper, etc., Condensers.
5 25 Potentiometers, assorted.
6 250 High-stab. 1%, 2%, 5% resistors.
7 50 Assorted Tagstrips.
8 1lb Assorted nuts, bolts, washers, spacers, etc.
9 25 Assorted switches, rotary, lever, micro, toggle, etc.
10 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED £1 + 25p p.p. per pack, **£5** for 5 packs p/free.

TEST EQUIPMENT

TEKTRONIX Type 109 Pulse Generator	£75
H P Transfer Oscillator, 540B. 100-200 MHz	£100
H P Sweep Oscillator, HO1-686C. 7-11 GHz	£120
H P Sweep Oscillator. 684C. 4-8 GHz	£150
MARCONI VHF-SHF Signal Generator. TF 1058	£200

KLYSTON POWER SUPPLIES

Large selection in stock. **£20** each.

PYE LING Automatic Cycling Oscillator. A.C. 0·1. 5Hz-5LHz	£50
MARCONI TF 1400 Double Pulse Generator	£65
CINTEL 1873 Square Wave and Pulse Generator	£50

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE **£1·50.** 3 for ONLY **55p** + p & p 30p

SPECIAL. As above PLUS Power Transistors ONLY **55p** each + p & p 15p

STABILISED POWER MODULES Complete with circuit diagrams, etc. **99p** each + p & p 15p

PAXOLINE BOARDS 7$\frac{1}{4}$ × 9″ approx. 4 for **30p** + p & p 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16$\frac{1}{2}$ × 4″ approx. 2 for **55p**

DECON-DALO 33pC Marker

Etch resistant printed circuit marker pen **90p** each

VEROBOARDS

Packs containing approx., 50sq. ins. various sizes, all 0·1 matric **55p**

REPANCO CHOKES & COILS

RF Chokes

CH1. 2·5mH **25p** CH2. 5·0mH **25p**
CH3. 7·5mH **25p** CH4. 10mH **25p**
CH5. 1·5mH **25p**

COILS
DRX1 Crystal set **31p** DRR2 Dual range **45p**

COIL FORMERS & CORES

NORMAN $\frac{1}{4}$″ Cores & Formers **7p**
$\frac{3}{8}$″ Cores & Formers **8p**

SWITCHES

DP/DT Toggle **25p** SP/ST Toggle **18p**

FUSES

1$\frac{1}{4}$″ and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1·5A, 2A
QUICK-BLOW **4p** ea. ANTI-SURGE **5p** ea.

EARPHONES

Crystal 2·5mm plug **33p**
Crystal 3·5mm plug **33p**
8 ohms 2·5mm plug **22p**
8 ohms 3·5mm plug **22p**

DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2·5mm and 3·5mm plugs **£1·60**

3-WAY STEREO HEAD-PHONE JUNCTION BOX

H1012 **£1·87**

2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3dB **£1·21**

SELECTED RESISTORS

R1. Our mix, $\frac{1}{2}$ watt carbon—50 for **55p**

CAR STEREO SPEAKERS

(Angled) **£3·85** per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES

(Black Vinyl covered)

No.	Length		Width		Height	Price
BV1	8″	×	5$\frac{1}{4}$″	×	2″	**90p**
BV2	11″	×	6″	×	3″	**£1·20**

ALUMINIUM BOXES

BA1	5$\frac{1}{4}$″	×	2$\frac{3}{4}$″	×	1$\frac{1}{2}$″	**42p**
BA2	4″	×	4″	×	1$\frac{1}{2}$″	**41p**
BA3	4″	×	2$\frac{3}{4}$″	×	1$\frac{1}{2}$″	**41p**
BA4	5$\frac{1}{4}$″	×	4″	×	1$\frac{1}{2}$″	**47p**
BA5	4″	×	2$\frac{1}{2}$″	×	2″	**41p**
BA6	3″	×	2″	×	1″	**34p**
BA7	7″	×	5″	×	2$\frac{1}{2}$″	**66p**
BA8	8″	×	6″	×	3″	**84p**
BA9	6″	×	4″	×	2″	**54p**

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1·84

Chrome Finish Model 60 £1·50

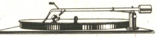

Ref. 36A. Record/Stylus Cleaning Kit **28p**
Ref. 43. Record Care Kit **£2·35**
Ref. 31. Cassette Head Cleaner **54p**
Ref. 32. Tape editing Kit **£1·54**
Model 9. Wire Stripper/Cutter **83p**
Ref. P. Hi-Fi Cleaner **31p**
Ref. 32A. Stylus Balance **£1·36**
Ref. J. Tape Head Cleaning Kit **51p**
Ref. 34. Cassette Case **£1·27**
Ref. 56. Hi-Fi Stereo Hints & Tips **32p**

ANTEX SOLDERING IRONS

X25. 25 watt **£1·93**
CCN 240. 15 watt **£2·15**
Model G. 18 watt **£2·15**
SK2. Soldering Kit **£2·86**
STANDS: ST1 **£1·21.** ST2 **77p**
SOLDER: 18SWG Multicore 7oz **82p**
22SWG 7oz **82p.** 18SWG 22ft **28p**
22SWG Tube **22p**

ANTEX BITS and ELEMENTS

Bits No.		
102	For model CN240 $\frac{3}{32}$″	**ALL 38p each**
102	For model CN240 $\frac{3}{16}$″	
1100	For model CCN240 $\frac{3}{32}$″	
1101	For model CCN240 $\frac{1}{8}$″	
1102	For model CCN240 $\frac{1}{4}$″	
1020	For model G240 $\frac{3}{32}$″	
1021	For model G240 $\frac{1}{8}$″	
1022	For model G240 $\frac{3}{16}$″	
50	For model X25 $\frac{3}{32}$″	
51	For model X25 $\frac{1}{8}$″	
52	For model X25 $\frac{3}{16}$″	

ELEMENTS
ECN 240 **£1·16** ECCN 240 **£1·32**
EG 240 **£1·16** EX 25 **£1·16**

ANTEX HEAT SINKS 10p

VAT included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C1	250	Resistors mixed values approx. count by weight	**0·55**
C2	200	Capacitors mixed values approx. count by weight	**0·55**
C3	50	Precision Resistors 0·1%, 0·01% mixed values	**0·55**
C4	75	$\frac{1}{8}$th W Resistors mixed preferred values	**0·55**
C5	5	Pieces assorted Ferrite Rods	**0·55**
C6	2	Tuning Gangs, MW/LW VHF	**0·55**
C7	7	Pack Wire 50 metres assorted colours	**0·55**
C8	10	Reed Switches	**0·55**
C9	3	Micro Switches	**0·55**
C10	15	Assorted Pots & Pre-Sets	**0·55**
C11	5	Jack Sockets 3 × 3·5m 2 × Standard Switch Type	**0·55**
C12	40	Paper Condensers preferred types mixed values	**0·55**
C13	20	Electrolytics Trans. types	**0·55**
C14	1	Pack assorted Hardware—Nuts/Bolts, Grommets etc.	**0·55**
C15	4	Mains Slide Switches	**0·55**
C16	20	Assorted Tag Strips & Panels	**0·55**
C17	10	Assorted Control Knobs	**0 55**
C18	4	Rotary Wave Change Switches	**0·55**
C19	3	Relays 6—24V Operating	**0·55**
C20	4	Sheets Copper Laminate approx. 10″ × 7″	**0·55**

PLUGS AND SOCKETS

SOCKETS

PS 35 DIN	2 Pin (Speaker)	**0·06**
PS 36 DIN	3 Pin	**0·10**
PS 37 DIN	5 Pin 180°	**0·10**
PS 38 DIN	5 Pin 240°	**0·10**
PS 39	Jack 2·5mm Switched	**0·09**
PS 40	Jack 3·5mm Switched	**0·10**
PS 41	Jack $\frac{1}{4}$″ Switched	**0·17**
PS 42	Jack Stereo Switched	**0·26**
PS 43	Phono Single	**0·06**
PS 44	Phono Double	**0·10**
PS 45	Car Aerial	**0·09**
PS 46	Co-Axial Surface	**0·09**
PS 47	Co-Axial Flush	**0·14**

INLINE SOCKETS

PS 21	D.I.N. 2 Pin (Speaker)	**0·13**
PS 22	D.I.N. 3 Pin	**0·17**
PS 23	D.I.N. 5 Pin 180°	**0·17**
PS 24	D.I.N. 5 Pin 240°	**0·17**
PS 25	Jack 2·5mm Plastic	**0·10**
PS 26	Jack 3·5mm Plastic	**0·12**
PS 27	Jack $\frac{1}{4}$″ Plastic	**0·24**
PS 28	Jack $\frac{1}{4}$″ Screened	**0·28**
PS 29	Jack Stereo Plastic	**0·22**
PS 30	Jack Stereo Screened	**0·32**
PS 31	Phono Screened	**0·14**
PS 32	Car Aerial	**0·15**
PS 33	Co-Axial	**0·17**

PLUGS

PS 1	D.I.N. 2 Pin (Speaker)	**0·11**
PS 2	D.I.N. 3 Pin	**0·12**
PS 3	D.I.N. 4 Pin	**0·15**
PS 4	D.I.N. 5 Pin 180°	**0·14**
PS 5	D.I.N. 5 Pin 240°	**0·15**
PS 6	D.I.N. 6 Pin	**0·15**
PS 7	D.I.N. 7 Pin	**0·15**
PS 8	Jack 2·5mm Screened	**0·10**
PS 9	Jack 3·5mm Plastic	**0·09**
PS 10	Jack 3·5mm Screened	**0·12**
PS 11	Jack $\frac{1}{4}$″ Plastic	**0·13**
PS 12	Jack $\frac{1}{4}$″ Screened	**0·18**
PS 13	Jack Stereo Screened	**0·29**
PS 14	Phono	**0·06**
PS 15	Car Aerial	**0·15**
PS 16	Co-Axial	**0·10**

CABLES

CP 1	Single Lapped Screen	**0·06**
CP 2	Twin Common Screen	**0·08**
CP 3	Stereo Screened	**0·08**
CP 4	Four Core Common Screen	**0·23**
PC 5	Four Core Individually Screened	**0·30**
CP 6	Microphone Fully Braided Cable	**0·10**
CP 7	Three Core Mains Cable	**0·07**
CP 8	Twin Oval Mains Cable	**0·06**
CP 9	Speaker Cable	**0·04**
CP 10	Low Loss Co-Axial	**0·10**

CARBON POTENTIOMETERS

Log and Lin
4·7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M

VC 1	Single Less Switch	**0·14**
VC 2	Single D.P. Switch	**0·26**
VC 3	Tandem Less Switch	**0·44**
VC 4	1K Lin Less Switch	**0·14**
VC 5	100K Log anti-Log	**0·44**

HORIZONTAL CARBON PRESETS

0·1 watt **0·06** each
100, 220, 470, 1K, 2·2K, 4·7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4·7M

BOOK BARGAIN BUN

8 Books comprising
2 Transistor Equivalent Books
1 Radio and Electronic Colour C Data Chart
1 Radio Valve Guide PLUS
3 other Constructional books on R FM Tuners, etc.
Also 1 General Constructional book

Value £3 Our Price £2 10

BP1	Handbook of Transistor Eq and Substitutes
BP2	Handbook of Radio, T.V. an Industrial Tube & Valve E
BP3	Handbook of Tested T Circuits
BP4	International Handbook World's Short Wave, Med Long Wave Radio Stati FM/TV Listings
BP5	Handbook of Simple T Circuits
BP7	Radio & Electronic Colour C Data Chart
BP8	Sound and Loudspeaker Ma
BP9	38 Practical Tested Diode for the Home Constructor
BP11	Practical Transistor Novelty Circuits
129	Universal Gram-Motor Speed Indicator
138	How to make FM & TV Aeri Bands 1, 2 and 3
141	Radio Servicing for Amateur
146	High Fidelity Loudspeaker Enclosures
156	Transistor Circuits Manual N
160	Coil Design & Constructional Manual
161	Radio, TV and Electronics Book
170	Transistor Circuits for Radio Controlled Models
174	Transistor Subminiature Receivers
175	Transistor Test Equipment a Servicing Manual
176	Transistor Audio Amplifier Manual
177	Modern Transistor Circuits fo Beginners
178	A Comprehensive Radio Valv Guide, Book 5
183	How to Receive Foreign T grammes on your set by modifications
185	Tested Shortwave Receiver using MAT's
187	The TSL Mark '4' Valved F and its construction
196	Reactance-Frequency Chart fo Audio & RF use
	Resistor Colour Code Disc Calculator

CARTRIDGES

ACOS GP91-1SC. 200mV at 1·2cms/se
ACOS GP93-1. 280mV at 1cm/sec
ACOS GP96-1. 100mV at 1cm/sec
TTC J-2005. Crystal/Hi Output
TTC J-20 10C Crystal/Hi Output Com

TTC J-200 CS Stereo/Hi Output
TTC J-2105 Ceramic/Med. Output

CARBON FILM RESIST

The E12 Range of Carbon Film Re $\frac{1}{8}$ watt available in PAKS of 50 assorted into the following groups:—

R1 50 Mixed 100 ohms-820 ohms
R2 50 Mixed 1K ohms-8·2K ohms
R3 50 Mixed 10K ohms-82K ohms
R4 50 Mixed 100K ohms-1 Meg. oh

THESE ARE UNBEATABLE PRI LESS THAN 1p EACH INCL.

BI-PAK SUPERIOR QUAL LOW-NOISE CASSETTE

C60, **32p**; C90, **41p**; C120, **52p**

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)
Open Mon.-Thurs. 9.15-6 p.m. Sat. 9.15-5.30. Late Night Shopping until 7 Fri. Tel. 61593

-the lowest prices!

-PAK *QUALITY* COMES TO AUDIO!

AL10/AL20/AL30 UDIO AMPLIFIER MODULES

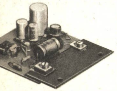

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
ONIC DISTORTION	Po = 3 WATTS f = 1KHz	0·25%
IMPEDANCE	—	8–16 Ω
IMPEDANCE	f = 1KHz	100 k Ω
UENCY RESPONSE —3dB	Po = 2 WATTS	50 Hz–25KHz
TIVITY for RATED O/P	Vs=25V. R1=8 Ω f=1KHz	75mV. RMS
SIONS	—	3″ × 2½″ = 1″

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
um Supply Voltage	25	30	30
put for 2% T.H.D. = 8 Ω f = 1KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

IO AMPLIFIER ULES

3 watts	**£2·19**
5 watts	**£2·59**
10 watts	**£3·01**

VER SUPPLIES

(Use with AL10 & AL20)	**88p**
. (Use with also AL30 & AL50)	**£3·25**
T PANELS PA 12 with Knobs	**£1·00**

PRE-AMPLIFIERS

PA 12.	(Use with AL10 & AL20)	**£4·35**
PA 100.	(Use with AL30 & AL50)	**£13·15**

TRANSFORMERS

T461 (Use with AL10)	**£1·38**	P & P 15p
T538 (Use with AL20)	**£1·93**	P & P 15p
BMT80 (Use with AL30 & AL50)	**£2·15**	P & P 25p

PA12 PRE-AMPLIFIER SPECIFICATION

A12 pre-amplifier has been designed to match into udget stereo systems. It is compatible with the AL 20 and AL 30 audio power amplifiers and it supplied from their associated power supplies. re two stereo inputs, one has been designed for use Ceramic cartridges while the auxiliary input will ost †Magnetic cartridges. Full details are given in cification table. The four controls are, from left to Volume and on/off switch, balance, bass and treble. 2mm × 84mm × 35mm.

Frequency response—
20Hz–50KHz (−3dD)
Bass control—
± 12dB at 60Hz
Treble control—
± 14dB at 14KHz
*Input 1. Impedance
1 Meg. ohm
Sensitivity 300mV
†Input 2. Impedance
30 K ohms
Sensitivity 4mV

LOOK FOR OUR MICONDUCTOR ADVERTISEMENTS IN *actical Wireless* and *RADIO CONSTRUCTOR*

LL PRICES INCLUDE VAT

e STEREO 20

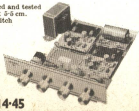

tereo 20" amplifier is mounted, ready wired and tested e-piece chassis measuring 20 cm × 14 cm × 5·5 cm. mpact unit comes complete with on/off switch control, balance, bass and treble controls, ormer, Power supply and Power amps. tively printed front panel and match- trol knobs. The "Stereo 20" has been ed to fit into most turntable plinths t interfering with the mechanism or, tively, into a separate cabinet. t power 20w peak. Input 1 (Cer.) into 1M. Freq. res. 25Hz-25kHz. 2 (Aux.) 4mV into 30K. Harmonic ion. Bass control ± 12dB at 60Hz lly 0·25% at 1 watt. Treble con. B at 14kHz.

£14·45

50W *pk 25w (RMS)*

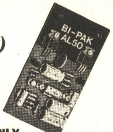

0·1% DISTORTION! HI-FI AUDIO AMPLIFIER

THE AL50

★ Frequency Response 15Hz to 100,000—1dB.

★ Load—3, 4, 8 or 16 ohms.

★ Distortion—better than ·1% at 1KHz,

★ Signal to noise ratio 80dB.

ONLY £3·58 each

★ Supply voltage 10-35 Volts.

★ Overall size 63mm 105mm × 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL8O was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT—TESTED—GUARANTEED.

STABILISED POWER MODULE SPM80

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1·5 amps at 35 volts. Size: 63mm × 105mm × 30mm.
These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disco Systems, Public Address, Intercom Units, etc. Handbook available **10p** **PRICE £3·25**

TRANSFORMER BMT80 £2·15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.
Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

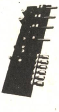

SPECIFICATION

Frequency Response	20Hz—20KHz ± 1dB
Harmonic Distortion	better than 0·1%
Inputs: 1. Tape Head	1·25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1·5 mV into 50K Ω

All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.

Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters: Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than −65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm × 82mm × 35mm

ONLY £13·15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25·30 FREE p. £ p.

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 11p. Overseas add extra for airmail. Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

Now! A FAST *EASY* WAY TO LEARN BASIC RADIO & ELECTRONICS

Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—you learn the *practical* way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified study method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

. . . and what's more, you will **understand exactly what you are doing.** The TECHNATRON Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of "NEW OPPORTUNITIES". This brand new booklet—just out—tells you all about TECHNATRON and B.I.E.T.'s full range of courses.

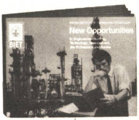

FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BPE47, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR **FREE** BOOK

CL **BPE47**

NAME..................................... AGE..............
(BLOCK CAPITALS)

ADDRESS...

SUBJECT OF INTEREST..

RST

VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS

SPECIAL EXPRESS MAIL ORDER SERVICE

Express postage 1p per transistor, over ten post free
INTEGRATED CIRCUITS 5p + 1p each added

	£p
1N21	0·17
IN23	0·35
IN85	0·88
IN253	0·50
IN256	0·50
IN645	0·16
1N725A	0·20
1N914	0·06
1N4007	0·12
1S113	0·25
IS131	0·13
1S202	0·23
2G371	0·40
2G381	0·22
2G414	0·30
2G417	0·25
2N404	0·22
2N697	0·15
2N698	0·30
2N706	0·10
2N706A	0·12
2N708	0·15
2N709	0·40
2N1091	0·55
2N1131	0·25
2N1132	0·25
2N1302	0·18
2N1303	0·18
2N1304	0·22
2N1305	0·22
2N1306	0·28
2N1307	0·28
2N1308	0·28
2N2147	0·75
2N2148	0·60
2N2160	1·00
2N2218	0·23
2N2219	0·25
2N2369A	0·16
2N2444	1·99
2N2613	0·28
2N2646	0·50
2N2904	0·20
2N2904A	0·25
2N2906	0·20
2N2907	0·23
2N2924	0·18
2N2925	0·15
2N2926	0·10
2N3054	0·50
2N3055	0·60
2N3702	0·11
2N3705	0·15
2N3706	0·11
2N3707	0·13
2N3709	0·10
2N3710	0·11
2N3711	0·11
2N3819	0·35
2N4289	0·20
2N5027	0·53
2N5088	0·33
2S301	0·59
2S304	1·15
2S501	0·75
2S703	1·00
AA129	0·20
AAZ12	0·75
AAZ13	0·10
AC107	0·35
AC126	0·25
AC127	0·25
AC128	0·20
AC187	0·20
AC188	0·20
ACY17	0·35
ACY18	0·27
ACY19	0·27
ACY20	0·22
ACY21	0·22
ACY22	0·16
ACY27	0·25
ACY28	0·25
ACY39	0·65
ACY40	0·22
ACY41	0·22
ACY44	0·32
AD140	0·50
AD149	0·50
AD161	0·39
AD162	0·39
AF106	0·30
AF114	0·25
AF115	0·25
AF116	0·25
AF117	0·20
AF118	0·50
AF119	0·20
AF124	0·30
AF125	0·30
AF126	0·30
AF127	0·30
AF139	0·33
AF178	0·55
AF179	0·65
AF180	0·55
AF181	0·50
AF186	0·40
AFY19	1·13
AFZ11	1·15
AFZ12	2·00
ASY26	0·25
ASY27	0·30
ASY28	0·25
ASY29	0·30
ASY36	0·25
ASY50	0·20
ASY51	0·40
ASY53	0·20
ASY55	0·20
ASY62	0·25
ASY66	0·33
ASZ21	1·00
ASZ23	0·75
AU101	1·50
AUY10	1·00
BC107	0·12
BC108	0·12
BC109	0·12
BC113	0·16
BC115	0·20
BC116	0·20
BC116A	0·23
BC118	0·20
BC121	0·20
BC122	0·20
BC125	0·68
BC126	0·65
BC140	0·55
BC147	0·12
BC148	0·10
BC149	0·12
BC157	0·14
BC158	0·12
BC160	0·63
BC169	0·14
BCY31	0·45
BCY32	1·20
BCY33	0·38
BCY34	0·45
BCY38	0·55
BCY39	1·00
BCY40	0·80
BCY42	0·30
BCY70	0·15
BCY71	0·20
BCZ10	0·60
BCZ11	0·65
BD121	1·00
BD123	1·00
BD124	0·80
BDY11	1·45
BF115	0·22
BF117	0·50
BF167	0·25
BF173	0·28
BF181	0·35
BF184	0·22
BF185	0·22
BF194	0·13
BF195	0·13
BF196	0·15
BF197	0·15
BFS61	0·25
BFS98	0·25
BFX12	0·20
BFX13	0·25
BFX29	0·28
BFX30	0·28
BFX35	0·98
BFX63	0·50
BFX84	0·25
BFX85	0·28
BFX86	0·25
BFX87	0·25
BFX88	0·22
BFY10	1·00
BFY11	0·50
BFY17	0·40
BFY18	0·45
BFY19	0·55
BFY24	0·45
BFY44	1·00
BFY50	0·20
BFY51	0·20
BFY52	0·20
BFY53	0·17
BFY64	0·45
BFY90	0·75
BSX27	0·50
BSX60	0·93
BSX76	0·18
BSY26	0·17
BSY27	0·20
BSY51	0·50
BSY95A	0·12
BSY95	0·12
BT102/500R	0·75
BTY42	0·92
BTY79/100R	0·75
BTY79/400R	1·10
BY100	0·15
BY126	0·14
BY127	0·15
BY182	0·85
BY213	0·25
BYZ10	0·45
BYZ11	0·40
BYZ12	0·40
BYZ13	0·35
BYZ15	1·25
BYZ16	0·60
BYZ88C3V3	0·10
BZY88C3V3	0·10
C111	0·55
CRS1/05	0·30
CRS1/40	0·45
CS4B	1·90
CS10B	3·50
DD000	0·15
DD003	0·15
DD006	0·25
DD007	0·40
DD008	0·38
GD3	0·33
GD4	0·10
GD5	0·33
GD8	0·25
GD12	0·10
GET102	0·50
GET103	0·40
GET113	0·35
GET114	0·30
GET115	0·75
GET116	0·85
GET120	0·50
GET872	0·30
GET875	0·40
GET880	0·55
GET881	0·25
GET882	0·35
GET885	0·40
GEX44	0·08
GEX45/1	0·45
GEX941	0·45
GJ3M	0·50
GJ4M	0·50
GJ5M	0·25
GJ7M	0·50
HG1005	0·50
HS100A	0·20
MAT100	0·20
MAT101	0·25
MAT120	0·20
MAT121	0·25
MJE520	0·65
MJE2955	1·10
MJE3055	0·75
MPF102	0·40
MPF103	0·30
MPF104	0·35
MPF105	0·46
NKT128	0·45
NKT129	0·30
NKT211	0·25
NKT213	0·25
NKT214	0·24
NKT216	0·40
NKT217	0·45
NKT218	1·13
NKT219	0·33
NKT222	0·30
NKT224	0·25
NKT251	0·24
NKT271	0·20
NKT272	0·20
NKT273	0·20
NKT274	0·20
NKT275	0·25
NKT277	0·20
NKT278	0·25
NKT301	0·85
NKT304	0·75
NKT403	0·70
NKT404	0·60
NKT678	0·30
NKT713	0·30
NKT773	0·25
NKT777	0·38
O78B	0·38
OA6	0·12
OA47	0·08
OA70	0·10
OA71	0·20
OA73	0·15
OA74	0·15
OA79	0·10
OA81	0·10
OA85	0·15
OA86	0·15
OA90	0·07
OA91	0·07
OA95	0·07
OA200	0·08
OA202	0·10
OA210	0·20
OA211	0·25
OAZ200	0·50
OAZ201	0·45
OAZ202	0·45
OAZ203	0·45
OAZ204	0·45
OAZ205	0·45
OAZ206	0·45
OAZ207	0·45
OAZ208	0·40
OAZ209	0·40
OAZ210	0·40
OAZ211	0·40
OAZ222	0·45
OAZ223	0·45
OAZ224	0·45
OAZ241	0·25
OAZ242	0·15
OAZ244	0·25
OAZ246	0·15
OAZ290	0·38
OC16	1·00
OC16T	1·00
OC19	0·50
OC20	2·00
OC22	1·00
OC23	1·25
OC24	1·10
OC25	0·40
OC26	0·40
OC28	0·70
OC29	0·65
OC30	0·40
OC35	0·55
OC36	0·65
OC41	0·35
OC42	0·40
OC43	0·70
OC44	0·18
OC44M	0·17
OC45	0·18
OC45M	0·18
OC46	0·27
OC57	0·60
OC58	0·60
OC59	0·60
OC66	0·50
OC70	0·18
OC71	0·15
OC72	0·25
OC73	0·50
OC74	0·30
OC75	0·30
OC76	0·30
OC77	0·55
OC78	0·25
OC79	0·30
OC81	0·28
OC81D	0·28
OC81M	0·20
OC81DM	0·18
OC81Z	0·45
OC82	0·28
OC82D	0·25
OC83	0·25
OC84	0·30
OC114	0·38
OC122	1·00
OC123	1·10
OC139	0·40
OC140	0·65
OC141	0·80
OC169	0·20
OC170	0·25
OC171	0·30
OC200	0·55
OC201	0·80
OC202	0·90
OC203	0·55
OC204	0·65
OC205	1·00
OC206	1·10
OC207	1·00
OC460	0·20
OC470	0·30
OCP71	1·00
ORP12	0·55
ORP60	0·45
ORP61	0·48
PIC44	0·29
SX68	0·20
SX631	0·45
SX635	0·55
SX640	0·75
SX641	0·75
SX642	0·60
SX644	0·85
SX645	0·85
TIS43	0·26
V15/30P	0·75
V30/201P	0·75
V60/201	0·50
V60/201P	0·75
XA101	0·10
XA102	0·18
XA151	0·15
XA152	0·15
XA161	0·25
XA162	0·25
XB101	0·43
XB102	0·30
XB103	0·35
XB113	0·30
XB121	0·43
ZS170	0·10
ZS271	0·18
ZT21	0·25
ZT43	0·25
ZTX107	0·12
ZTX108	0·10
ZTX300	0·14
ZTX304	0·24
ZTX500	0·15
ZTX503	0·16
ZTX531	0·25
INTEGRATED CIRCUITS	
7400	0·20
7401	0·20
7402	0·20
7403	0·20
7404	0·20
7405	0·20
7406	0·40
7407	0·40
7408	0·25
7409	0·33
7410	0·20
7411	0·23
7412	0·28
7413	0·30
7416	0·30
7417	0·30
7420	0·20
7422	0·28
7423	0·40
7425	0·37
7427	0·37
7428	0·43
7430	0·20
7432	0·37
7433	0·43
7437	0·43
7438	0·43
7440	0·20
7441AN	0·85
7442	0·85
7450	0·20
7451	0·20
7453	0·20
7454	0·20
7460	0·20
7470	0·33
7472	0·38
7473	0·44
7474	0·48
7475	0·59
7476	0·45
7480	0·80
7482	0·87
7483	1·20
7484	1·00
7486	0·50
7490	0·75
7491A	1·10
7492	0·75
7493	0·75
7494	0·85
7495	0·85
7496	1·00
7497	4·32
74100	2·16
74107	0·51
74110	0·57
74111	0·86
74118	1·00
74119	1·92
74121	0·57
74122	0·80
74123	1·44
74141	1·00
74145	1·44
74150	2·30
74151	1·15
74154	2·30
74155	1·15
74156	1·15
74157	1·09
74170	2·88
74174	1·80
74175	1·29
74176	1·44
74190	2·30
74191	2·30
74192	2·30
74193	2·30
74194	1·72
74195	1·44
74196	1·58
74197	1·58
74198	3·16
74199	2·88
Plug in sockets—low profile 14 pin DIL	0·15
16 pin DIL	0·17

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only • Tel. 01-677 2424-7

All orders subject to V.A.T. at 10% rate. This must be added to the total order including postage.

MAPLIN ELECTRONIC SUPPLIES

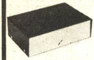

Model 120

LARGE or SMALL Centurion

PROJECTS DESERVE A PROFESSIONAL QUALITY 'INSTRUMENT CASE—4 MODELS

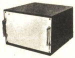

Model 320

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction.

Top. base. sides and detachable rear panel. blue hammer. Detachable aluminium front panel finished in white.

Dimensions in inches.

Model	W	H	D	Price
120	8	2½	6	£1·85
220	8	6	3½	£2·65
221	8	6	6	£2·90
320	12	8	12	£5·75

Chassis for model 320 **£1·75** extra.

Please send s.a.e. for free illustrated leaflet.

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board.

LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3·7in. × 4·5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.

DMO2T (with tremulant) ONLY **£14·25**.

DMO2 (without tremulant) **£12·25**.

★ S.a.e. please for full technical details.

Trade enquiries welcome.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: **£2·63** each OR special price for pack of 12: **£25·00**. S.a.e. please for data sheet.

★SAME DAY SERVICE

MAPLIN: Projected site of London's third airport.

P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We are stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboards.

Send s.a.e. now for our detailed price lists.

YOU SIMPLY MUST SEE OUR PRICES!

Keyboard 49 note C-C	£14·35
uA 7815 (15V 1·5A) voltage regulator	£2·30
741C 8-pin DIL	36p
MFC 6040 electronic attenuator	£0·95
SG 3402N for Ring Modulator	£1·69
CA 3046	69p

CAPACITORS

Sub-miniature
Axial lead electrolytic

Mfd	V	Price	Mfd	V	Price	Mfd	V	Price
1	63	6p	68	6·3	6p			
1·5	63	6p	68	16	6p			
2·2	63	6p	68	63	10p			
3·3	63	6p	100	4	6p			
4·7	63	6p	100	10	6p	470	6·3	6p
6·8	40	6p	100	25	6p	470	10	10p
6·8	63	6p	100	40	6p	470	25	12p
10	25	6p	100	63	12p	470	40	18p
10	63	6p	150	6·3	6p	680	6·3	10p
15	16	6p	150	16	6p	680	16	12p
15	40	6p	150	25	6p	680	25	18p
15	63	6p	150	40	10p	680	40	22p
22	10	6p	150	63	12p	1000	4	10p
22	25	6p	220	4	6p	1000	10	12p
22	63	6p	220	10	6p	1000	16	18p
33	6·3	6p	220	16	6p	1000	25	22p
33	16	6p	220	25	10p	1500	6·3	12p
33	40	6p	220	40	12p	1500	10	18p
47	4	6p	220	63	18p	1500	16	22p
47	10	6p	330	4	6p	2200	6·3	18p
47	25	6p	330	10	6p	2200	10	22p
47	40	6p	330	16	10p	3300	6·3	22p
47	63	6p	330	63	22p	4700	4	22p

PLUGS AND SOCKETS

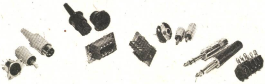

DIN PLUGS

2 pin (1 flat)	8p
3 pin	9p
4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin	10p

DIN Sockets

2 pin	6p
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin	7p

MAINS

P360 3 pin 1·5A chassis plug with line socket. Per pair	28p
SA 2190 3 pin 5A chassis plug	20p
SA 1862 Line socket for above	23p

McMURDO

RP8 8 way chassis plug	47p
RS8 8 way chassis socket	62p

PHONO

Plug plastic	5p
Plug screened	9p
Chassis socket	4p

JACK

Std. ¼" mono plug

Plastic	13p
Screened	17p

Std. ¼" stereo plug

Plastic	16p
Screened	25p

Open mono socket ¼" **10p**; Moulded mono socket ¼" with 2 break contacts **13p**; Moulded stereo socket ¼" with 3 break contacts **18p**; 3·5mm. plug plastic **8p**; screened **11p**; open socket **8p**.

WE KNOW YOU NEED IT!

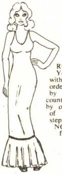

The MES 1974 CATALOGUE IS STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system. EXCITED by our BIG VALUE discount vounchers. STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY **25p** for our beautifully produced catalogue.

and leave the rest to us!

OMNIUM GATHERUM

PP3. 6. etc.. battery clip dual min. **9p.**

PP1. 9. etc.. battery clip separate per pair **6p.**

Pair crocodile clips 1 red. 1 black insulated sleeve **7p.**

Solder Multicore 22 s.w.g. 10 metres **20p**

Silicone grease in special dispenser 20ml **43p.**

Red neon 240V panel mounting **25p.**

Lacing Cord. Strong rayon cored PVC 25m **43p.**

Panel fuse holders 20mm **20p**; 1¼in **35p.**

Transformers

LT700 min. output transformer Pri. 1·2kΩ Sec. 5Ω 200mW **37p.**

Sub-main. Mains Transformer

6–0–6V 100mA **95p,** 12–0–12V 50mA **95p.**
Size: Both approx. 30 × 27 × 25mm.

Min. Mains Transformer

Size: 46 × 31 × 38mm.
0–12V 250mA. 0–12V 250mA **£1·36.**

Mains Transformer MT3AT

Pri. 200–220–240V. Sec. 12–15–20–24–30V 1A **£3·05.**

Mains Transformer MT206AT

Pri. 200–220–240V. Sec. 0–15–20V 1A. 0–15–20V 1A **£3·66.**

Hook-up wire, 7 strand 0·2mm. PVC covered tinned copper wire for light general connexions up to 1·4A. 11 colours: black. blue brown. green. grey. orange. pink. red. violet. white. yellow. 10 metres of any one colour **20p.** Pack of 11 (1 of each colour) 10m. coils **£2·05.**

Single core screened 6p per metre.

Twin individually screened **9p** per metre.

High quality single screened 50Ω 100pF per metre. ideal for high grade audio connexions **15½p** per metre.

Mains 3-core sub-miniature 1A black PVC covered 19 strand 0·1mm per conductor. **6½p** per metre.

POTENTIOMETERS

Rotary miniature carbon track ¼" spindle

Single gang Lin or Log
5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 12p

Dual gang (Stereo) without switch Log or Lin 5k to 2M as above **38p.**

Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above **24p**

PRESETS

Sub-miniature 0·1W Vert or Horiz 100, 250, 500, 1k, 2·5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M **6p**

Wirewound 10% 1W ¼" spindle 10, 50, 100R **34p**; 250, 500, 1k, 5k **33p**; 10k, **37p**; 25k **40p**; 50k **44p**.

RESISTORS

Carbon Film ⅛W	5% 1Ω to 1M; 10% 1·2M to 10M		E12	1p
Carbon Film ¼W	5% 1Ω to 10Ω; 10% 1·2M to 10M		E12	1p
Carbon Film ½W	5% 11Ω to 910k		E12 & E24	1p
Carbon Film 1W	5% 10Ω to 10M		E12	3p
Metal Oxide ½W	2% 10Ω to 1M		E12 & E24	4p
Wirewound 2½W	10% 0·22ohms to 0·47ohms		E12	10p
Wirewound 2½W	5% 1ohm to 270ohms		E12	10p

E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades
E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

LINEARS

LH0042C. TO99 (TO5). FET i/p Op Amp	£3·88
LM301A. 8-pin DIL. Op Amp	55p
MC1303L. 14-pin DIL. Stereo Preamplifier	£1·39
MC1310P. 14-pin DIL. FM Stereo Decoder (no coils needed)	£3·15
MFC4000B. 4-pin case. ¼W Audio Power Amp	38p
MFC8010. 8-pin case. 1W Audio Power Amp	£1·20
MFC9020. 10-lead case. 2W Audio Power Amp	£1·37
NE555V. 8-pin DIL. Precision Timer	79p
NE561B. 16-pin DIL. Phase Locked Loop	£4·48
SG1495D. 14-pin DIL. Fair Quadrant Analogue Multiplier	£2·70
µA723C. TO99 (TO5). 2 to 37V Voltage Regulator	80p
µA723C. 14-pin DIL. 2 to 37V Voltage Regulator	80p
µA741C. 8-pin DIL. Op Amp	36p
µA741C. 14-pin DIL. Op Amp	45p
µA747C. 14-pin DIL. Dual Op Amp	£1·05
µA748C. 8-pin DIL. Op Amp	39p
ZN414. TO5. TRF Radio	£1·20

More linears are listed in the "PE SOUND SYNTHESISER" box. above.

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each **24p.**
Mains rotary DPDT 250V 2A **20p.**

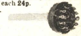

Push to make non-locking **12p**

Slide Miniature DPDT **9p**

Toggle 250V 1·5A with ON/OFF plate **25p.**

Sub-miniature toggle DPDT (12 × 12·5 × 14mm excl. toggle) 250V 3A **66p**

VAT Please add 10% to the final total.

Post and Packing FREE in U.K.
(10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. Tel. Southend-on-Sea 0702 44101

LASKYS

INCORPORATING LASKYS RADIO
AND G. W. SMITH & CO. (RADIO).

AUDIOTRONIC Model ATM1

Top value 10,000 opv pocket multimeter. Ranges:—0/10/50/250/1,000 volt AC and DC. DC current 0-1mA/100mA. Resistance 0/150k ohms. Decibels −10 to +22dB. Size 90x60x28mm. Complete with test leads.

OUR PRICE £2.95 P&P 15p

AUDIOTRONIC Model ATM5

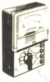

Jewel movement, attractively moulded case with edgwise ohms adjustment. Ranges: 0-3/15/150/300/1200V AC, (2500 opv). 0-6/30/300/600V DC, (5000 opv). 0-300 uA/0-300mA DC. Resistance: x 10 & x 100. −10 to +16dB Supplied with battery test leads and data booklet. Size: 121 x 73 x 29mm

OUR PRICE £3.50 P&P 15p

MODEL TE200

20,000opv. Mirror scale, overload protection. 0/5/25/125/1000V DC. 0/10/50/250/1000V AC. 0/50uA/250mA. 0/60k/6 Meg ohms. −20 to +62dB.

OUR PRICE £4.95 P&P 15p

MODEL U437 MULTIMETER

10,000opv. A first class, instrument manufactured in USSR to the highest standards. Ranges: 2.5/10/50/ 250/500/1000V DC. 2.5/10/50/250/500/1000V AC. DC current 100uA/1/10/100mA/1A. Resistence 300 ohms/3/30/300k/3 Meg. ohms. Complete with batteries, test leads, instructions and a sturdy steel carrying case.

OUR PRICE £4.95 P&P25p

MODEL TH12

20,000 opv. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/150/1000V DC. 0/10/50/250/1000V AC. 0/50uA/25/250mA DC. 0/3k/30k/300k/3 Megohms. −20 to +50dB.

OUR PRICE £5.95 P&P 15p

HIOKI Model 720X VOM

A versatile, accurate measuring instrument. 20,000 opv. 0/5/25/100/500/1000V DC. 0/10.50/250/1000V AC. 0—50uA/250mA. 0—20k/2 Megohms.

OUR PRICE £5.97
P&P 20p

TMK MODEL TW50K

46 ranges, mirror scale. 50k/V DC 50k/V AC. DC Volts: 0.125/0.25/1.25/2.5/5/10/25/50/125/250/500/1000. AC Volts 1.5/3/5/10/25/50/125/250/500/1000. DC current 25/50uA/2.5/5/25/50/250/500mA/5/10A. Resistence: 10k/100k/1 Meg/10 Meg ohms. −20 to +81.5dB.

OUR PRICE £8.50 P&P 17p

ALL PRICES EXCLUDE VAT

U4323 MULTIMETER

20,000opv. Simple unit with audio/IF oscillator. Suitable for general receiver tuning. Ranges: 0.5/2.5/10/50/250/500/1000V DC. 2.5/10/15/250/500/1000V AC. 0.05/0.5/5/50/500mA DC. Resistance: 5/50/500 ohms/5/10/100k ohms/1Meg. Battery operated. Size: 160 x 97 x 40mm. Supplied in carrying case complete with test leads.

OUR PRICE £7.00 P&P 20p

MODEL TE300

30,000opv. Mirror scale. Overload protection. 0/0.6/3/15 60/300/1200V DC. 0/6/30/120/600/1200V AC. 0/30uA/6mA/60mA/300mA/600mA. 0/8k/80k/800k/8 Meg ohms. −20 to +63dB.

OUR PRICE £7.50 P&P 15p

U4324 MULTIMETER

High sensitivity, overload protected. 20,000opv. Ranges: 0.6/1.2/3/12/30/60/120/600/1200V DC. 3/6/15/60/150/300/600/900V AC. Current: 0.06/0.6/6/60/600mA/3A DC. 0.3/3/30/300mA/3A AC. Resistence: 25/500 ohms/0.5/5/50/500k ohms/5 Mohms. Decibels: −10 to +12dB. Size 167 x 98 x 63mm. Supplied complete with test leads, spare diode and instructions.

OUR PRICE £8.00 P&P 20p

U435 MULTIMETER

20,000opv. Overload protected. Ranges: 75mV/2.5/10/25/100/250/500/1000V DC. 2.5/10/25/100/250/500/1000V AC. Current: 50uA/1/5/25/100mA/0.5/2.5A DC. 5/25/100mA/0.5/2.5A AC. Resistance: 0.3/3/30/300k ohms. Size: 205 x 110 x 84mm. Supplied complete with leads, crocodile clips and steel carrying case.

OUR PRICE £8.75 P&P 20p

U4312 MULTIMETER

extremely sturdy instrument for general electrical use. 667opv. 0/0.3/1.5/7.5/30/60/150/300/600/900V DC & 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V AC. 0/300uA/1.5/6/15/150/60/600mA/1/1.5/6A DC. 0/1.5/6/15/60/150/600mA/1.5/6A AC. 0/200/3k/30k ohms. DC accuracy 1%. AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions.

OUR PRICE £9.75 P&P 25p

U91 Clamp VOLT AMMETER

For measuring AC voltage and current without breaking circuit. Ranges: 300/600V AC. Current: 10/25/100/250/500A. Accuracy 4%. Size 283 x 94 x 36mm. Complete with carrying case, leads and fuses.

OUR PRICE £10.50 P&P 20p

MODEL C7080EN

Giant 6" mirror scale. 20,000 opv. 0/0.25/1/2.5/10/50/250/1000/5000V DC. 0/2.5/10/50/250/1000/5000V AC. 0/50uA/1/10/100/500mA/10A DC. 0/2k/200k/20 Meg. −20 to +50dB.

OUR PRICE £13.95 P&P 35p

MODEL 500

30,000 opv with overload protection. Mirror scale. 0/0.5/2.5/10/25/100/250/500/1000V DC. 0/2.5/10/25/100/250/500/1000V AC. 0/50uA/5/50/500mA. 12A DC. 0/60k/6 meg/60 megohms.

OUR PRICE £10.95 Carr. paid
Leather case for above £1.75

KAMODEN 360 MULTIMETER

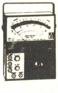

High sensitivity. DC 100kohm/V AC 10kohm/V 5" mirror scale, overload protected. Ranges: 0.5/2.5/10/50/250/1000V DC. 5/10/50/250/1000V AC. Current: 0.01mA/0,5/5/50/500mA/10A. Resistance: 0.1/1/10/100 ohms/1/10/100k ohms/10/100M ohms. Decibels −20 to +62dB. Battery operated. Size: 180 x 140 x 80mm. Supplied complete with, test leads etc.

OUR PRICE £13.95 P&P 25p

HIOKI MODEL 700X

100,000opv. Overload protection. Mirror scale 0.3/0.6/1.2/1.5/3/6/12/30/60/120/300/600/1200V DC. 1.5/3/6/12/30/60/150/300/600/1200V AC. 15/30uA/3/6/30/60/150/500mA/6/12A DC 2k/200k/2M/20MOhms −20 to +63dB.

OUR PRICE £14.95 P&P20p

KAMODEN HM720B FET VOM

Input impedence 10 Megohms. Ranges: 0/.25/1/2.5/10/50/1000V DC. 0/2.5/10 50/250/1000V AC. 0/25uA/2.5/25/250 mA DC. 0/5k/50k/500k/5 M 500 Megohms

OUR PRICE £14.95 P&P 30p

TMK MODEL 117 FET ELECTRONIC VOLTMETER

Battery operated. 11 Meg input, 26 ranges. Large 4¼" mirror scale. Size: 149x117x60mm. 0.3—12000V DC. 3—300V RMS AC. 8—800V P-P. DC current 0.12—12mA. Résistence up to 2000MOhms. Decibels: −20 to +51dB. Supplied complete with leads and instructions.

OUR PRICE £17.50 P&P 20p

KAMODEN 72.200 Multitester

High sensitivity tester. 200,000 opv Overload protected Mirror scale. Ranges:—0/.06/.3 3/30/120/600/1200V DC. 0/3 12/60/300/11200 V AC. 0/6uA/1.2mA/120mA/600mA/12A DC 0/12A AC. −20 to +63dB. 0/2k/200k/2 Meg/200 Megohms.

OUR PRICE £16.95 P&P 30p

370WTR MULTIMETER

Features AC current ranges. 20,000opv. 0/0.5/2.5/10/50/250/500/1000V DC 0/2.5/10/50/250/500/1000V AC. 0/50uA/1/10/100 mA/1/10A DC. 0/100mA/1/10A AC. 0/5k/50k/500k/5 Meg/50 Meg. Decibels: −20 to +62dB.

OUR PRICE £17.50 P&P 25p

U4317 MULTIMETER

High sensitivity instrument for field and laboratory work Knife edge pointer, 86mm. mirror scale. Ranges: 100mV/0.5/2.5/10/25/50/100/250/500/1000 V DC. 0.5/2.5/10/25/50/100/250/500/1000V AC. Current: 50uA/0.5/1/5/10/50/250mA/1/5A DC. 0.25/0.5/1/5/10/50/250mA/1/5A AC. Resistance: 0.5/10/100/200 ohms/1/3/30/300k ohms. Decibels: −5 to +10dB Battery operated. Size: 210 x 115 x 90mm. Supplied in carrying case complete with leads.

OUR PRICE £15.00 P&P 20p

TE40 HIGH SENSITIVITY AC VOLTMETER

10 Meg input. 10 ranges: 0.001/0.03/0.1/0.3/1/3/11/30/100/300V RMS. 5cps—1.2MHz. −40 to +50dB supplied complete with leads and instructions.

OUR PRICE £17.50 P&P 25p

TE65 VALVE VOLTMETER

28 ranges. DC volts 1.5—1500V. AC volts 1.5—1500V. Resistance up to 1000 Megohms, 200/240V AC operation. Complete with probe and instructions.

OUR PRICE £17.50 P&P 30p
Additional probes available: RF £2.12, HV £2.50

TMK LAB TESTER

100,000opv. 6½" scale. Buzzer short circuit check. Sensitivity 100,000 opv DC. 5k/V AC DC Volts: 0.5/2.5/10/50/250/1000V AC. 3/10/50/250/500/1000V DC. current 10/100uA/10/10/100/500mA/2.5/10A. Resistence: 1k/10k/100k/10 Meg/100 Meg ohms. Decibels: −10 to +49dB. Plastic case with carrying handle. Size: 190 x 172 x 99mm.

OUR PRICE £19.95 P&P 25p

MODEL U4311 Sub-standard Multi-range Volt-Ammeter

Sensitivity 330 Ohms/Volt AC and DC. Accuracy 0.5% DC. 1% AC. Scale length: 165mm. 0/300/750uA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5A DC. 0/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5A AC. 0/75/150/300/750mV/1.5/3/7.5/15/30/75/150/300/750V DC. 0/750mV/1.5/3 /7.5/15/30/75/150/300/750V AC. Automatic cut out device. Supplied complete with test leads, manual and test certificates.

OUR PRICE £49.00 P&P 50p

LB3 TRANSISTOR TESTER

Tests ICO and B. PNP/NPN. Operates from 9V battery. Complete with all instructions etc.

OUR PRICE £3.95 P&P 20p

LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with instructions etc.

OUR PRICE £4.50 P&P 20p

U4341 Multimeter & Transistor Tester

27 ranges. 16,700opv. Overload protected. Ranges: 0.3/1.5/6/30/60/150/300/900V DC. 1.5/7.5/30/150/300/750V AC. Current: 0.06/0.6/6/60/600mA DC. 0.3/3/30/300mA AC. Resistance: 0.06/0.6/2/6/20/60/200k ohms/2 Mohms. Battery operated. Supplied complete with probes, leads and steel carrying case. Size: 115 x 215 x 90mm.

OUR PRICE £10.50 P&P 20p

KAMODEN HM350 TRANSISTOR TESTER

High quality instrument to test reverse leak current and DC current. Amplification factor of NPN, PNP, diodes, transistors, SCR's etc. 4" square clear scale meter. Operates from internal batteries. Complete with instructions, leads carrying handle.

OUR PRICE £12.50 P&P 30p

S100TR MULTIMETER—TRANSISTOR TESTER

100,000opv. Mirror scale. Overload protection. 0/0.12/0.6/3/12/30/120/600V DC. 0/6/30/120/600V AC. 0/12/600uA/12/300mA612A DC. 0/10k/1 Meg/100 Meg. −20 to +50dB. 0.01—0.2 MFD. Transistor tester measures Alpha, Beta and ICO. Complete with instructions, batteries and leads.

OUR PRICE £14.95 P&P 25p

Model 449A In Circuit TRANSISTOR TESTER

Checks true AC, Beta in/out. Checks ICO. Checks diodes in/out. Checks SCR etc. Beta HI 10—500 LO 2—50. ICO 0—500uA. 220/240V AC operation.

OUR PRICE £17.50 P&P25p

KAMODEN HMG500 insulation resistance tester

Range 0—1,000 Megohms, 500V. Battery operated. Wide range clear meter 4"x4¾". Complete with deluxe carrying case, batteries and instructions.

OUR PRICE £19.95 P&P 30p

TE16A TRANSISTORISED SIGNAL GENERATOR

5 ranges, 400kHz to 30 MHz. An inexpensive instrument for the handy-man. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. Size: 149 x 149 x 92mm Complete with instructions and leads.

OUR PRICE £8.97 P&P 25p

TE22 SINE SQUARE WAVE AUDIO GENERATOR

Sine 20cps to 200kHz on 4 bands. Square 20 cps to 30 kHz. Output impedence 5000 Ohms. 200/250V AC operation. Supplied brand new guaranteed, with instruction manual and leads.

OUR PRICE £17.50 P&P 37p

ARF 300 AF/RF SIGNAL GENERATOR

All transistorised compact fully portable. AF sinewave 18Hz to 220 kHz. AF square wave 18Hz to 100k Hz. Output Square/Sine wave 10V. P-P RF 100kHz to 200MHz. Output 1V maximum. 220/240V AC operation. Complete with instructions and leads.

OUR PRICE £29.95 P&P 50p

LASKYS

**INCORPORATING LASKYS RADIO
AND G. W. SMITH & CO. (RADIO).**

YAMABISHI VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost.
All models—Input 230V 50/60Hz.
Variable output 0—260V

MODEL S260 GENERAL PURPOSE BENCH MOUNTING

		P&P
1A	£8.75	30p
2.5A	£10.00	35p
5A	£14.70	37p
8A	£25.50	50p
10A	£28.10	75p
12A	£29.50	100p
20A	£72.50	125p
25A	£72.50	130p
40A	£103.10	150p

MODEL S260B Panel Mounting

1A	£8.75	30p
2.5A	£10.00	35p

AT201 Decade ATTENUATOR

Frequency range 0—200kHz. Attenuator 0—111dB, 0.1dB steps. Impedence 600 ohms. Input power maximum 30dBm. Size: 180 x 90 x 55mm.

OUR PRICE £12.50 P&P 37p

BELCO Sine Square Wave CR OSCILLATOR

Sine 18 x 200,000Hz. Square 18 x 20,000 Hz. Maximum output +10dB (10k ohms) Operates from internal batteries. Attractive two tone case. Size: 196 x 127 x 50mm.

OUR PRICE £17.50 P&P 17p

CI5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP Bandwidth: 10MHz. Sensitivity at 100kHz VRMS/mm: 0.1—25. HOR. AMP. Bandwidth: 500kHz. Sensitivity ay 100kHz VRMS/mm: 0.3—25 Preset triggered sweep 1—3000usec. Free running 20—200 kHz in nine ranges. Calibrator pips. 220 x 360 x 430mm. 115—230V AC.

OUR PRICE £39.00 Carr. paid

TO3 Portable OSCILLOSCOPE

3" tube. Y amp sensitivity 0.1Vp-p/CM. Bandwidth: 1.5Hz—1.5MHz. Input Impedence: 2 MOhms, 25pF. X amp. sensitivity: 0.9Vp-p/CM. Bandwidth 1.5Hz—800kHz. Input impedence 2 Meg Ohms, 20pF. Time base, five ranges 10Hz to 300kHz. Synchronisation. Internal or external. Illuminated scale 140 x 215 x 330mm. Weight 15½lbs. 220/240V AC. Supplied brand new with handbook.

OUR PRICE £52.50 P&P 50p

RUSSIAN CI16 Double Beam OSCILLOSCOPE

5 MHz pass band. Separate Y1 and Y2 amplifiers. Rectangular 5" x 4" CRT. Calibrated triggered sweep from 0.2usec to 100 milli-sec/cm. Free running time base, 50Hz—1MHz. Built-in time base Calibrator and amplitude Calibrator. Supplied complete with all accessories and instruction manual.

OUR PRICE £87.00 Carr. paid

MCA220 Automatic Voltage Stabiliser

 

Input 88—125V AC or 176—250 V AC. Output 120V AC or 240V AC. 200V A rating.

OUR PRICE £11.97 P&P 50p

PS100B Regulated POWER SUPPLY UNIT

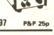

Solid state. Output 6, 9 or 12V DC up to 3 Amp. Meter to monitor current. Input 220/240V AC. Size: 100 x 82 x 159mm.

OUR PRICE £11.97 P&P 25p

PS200 Regulated POWER SUPPLY UNIT

Solid state. Variable output 5—20V DC up to 2 Amp. Independent meters to monitor voltage and current. Output 220/240V AC. Size: 190 x 136 x 98mm.

OUR PRICE £19.95 P&P25p

SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

CLEAR PLASTIC MODEL SD640
Size: 85 x 64mm

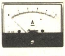

50uA	£3.35
100uA	£3.30
200uA	£3.30
500uA	£3.25
50-0-50uA	£3.35
100-0-100uA	£3.30
1mA	£3.20
5mA	£3.20
10mA	£3.20
50mA	£3.20
100mA	£3.20
500mA	£3.20
1A DC	£3.20
5A DC	£3.20
10A DC	£3.20
5V DC	£3.20
20V DC	£3.20
50V DC	£3.20
300V DC	£3.20
15V AC	£3.30
300V AC	£3.30
VU Meter	£3.45

CLEAR PLASTIC MODEL SW100
Size: 100 x 80mm

50uA	£4.55
100uA	£4.35
500uA	£4.10
50-0-50uA	£4.35
100-0-100uA	£4.30
1mA	£3.95
1A DC	£3.95
5A DC	£3.95
20V DC	£3.95
50V DC	£3.95
300V DC	£3.95
300V AC	£4.00
VU Meter	£4.75

EDGWISE MODEL PE70
Size: 90 x 34mm

50uA	£4.15
100uA	£3.95
200uA	£3.75
500uA	£3.50
50-0-50uA	£3.95
100-0-100uA	£3.85
1mA	£3.50
300V AC	£3.50
VU Meter	£4.25

MODEL ED107 EDUCATIONAL METER
Size: 100 x 90 x 150mm including terminals

A range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The meter movement is easily accessible to demonstrate internal working.

50uA	£7.60
100uA	£7.05
50-0-50uA	£7.05
1A DC	£6.55
5A DC	£6.55
5V DC	£6.55
10V DC	£6.55
15V DC	£6.55
20V DC	£6.55
50V DC	£6.55
300V DC	£6.55
500mA/5A DC	£7.70
5V/50V DC	£7.70
5V/15V DC	£7.70
1A/15A DC	£7.70

CLEAR PLASTIC MODEL 85P
Size: 120 x 110mm

50uA	£4.85
100uA	£4.70
200uA	£4.45
500uA	£4.30
50-0-50uA	£4.70
100-0-100uA	£4.45
500-0-500uA	£4.30
1mA	£4.30
1-0-1mA	£4.30
5mA	£4.30
10mA	£4.30
50mA	£4.30
100mA	£4.30
500mA	£4.30
1A DC	£4.30
5A DC	£4.30
15A DC	£4.30
30A DC	£4.35
10V DC	£4.30
20V DC	£4.30
50V DC	£4.30
150V DC	£4.30
300V DC	£4.30
15V AC	£4.35
300V AC	£4.35
S Meter 1mA	£4.30
VU Meter	£5.00
1A AC	* £4.30
5A AC	* £4.30
10A AC	* £4.30
20A AC	* £4.30
30A AC	* £4.30

*Items with asterisk are Moving Iron type, all others are Moving Coil

CLEAR PLASTIC MODEL SD830
Size: 110 x 83mm

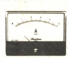

50uA	£3.75
100uA	£3.70
200uA	£3.65
500uA	£3.45
50-0-50uA	£3.75
100-0-100uA	£3.70
1mA	£3.40
5mA	£3.40
10mA	£3.40
50mA	£3.40
100mA	£3.40
500mA	£3.40
1A DC	£3.40
5A DC	£3.40
10A DC	£3.40
5V DC	£3.40
10V DC	£3.40
20V DC	£3.40
50V DC	£3.40
300V DC	£3.40
15V AC	£3.65
300V AC	£3.65
VU Meter	£3.85

CLEAR PLASTIC MODEL 45P
Size: 50 x 50mm

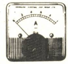

50uA	£3.00
100uA	£2.85
200uA	£2.75
500uA	£2.70
50-0-50uA	£2.90
100-0-100uA	£2.75
500-0-500uA	£2.65
1mA	£2.65
5mA	£2.65
10mA	£2.65
50mA	£2.65
100mA	£2.65
500mA	£2.65
1A DC	£2.65
5A DC	£2.65
10V DC	£2.65
20V DC	£2.65
50V DC	£2.65
300V DC	£2.65
15V AC	£2.70
300V AC	£2.70
S Meter 1mA	£2.75
VU Meter	£3.00
1A AC	* £2.65
5A AC	* £2.65
10A AC	* £2.65
20A AC	* £2.65
30A AC	* £2.65

CLEAR PLASTIC MODEL 38P
Size: 42 x 42mm

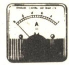

50uA	£2.80
100uA	£2.70
200uA	£2.65
500uA	£2.50
50-0-50uA	£2.75
100-0-100uA	£2.65
500-0-500uA	£2.50
1mA	£2.50
1-0-1mA	£2.50
2mA	£2.50
5mA	£2.50
10mA	£2.50
20mA	£2.50
50mA	£2.50
100mA	£2.50
150mA	£2.50
200mA	£2.50
300mA	£2.50
500mA	£2.50
750mA	£2.50
1A DC	£2.50
2A DC	£2.50
5A DC	£2.50
10A DC	£2.50
15A DC	£2.50
20A DC	£2.50
3V DC	£2.50
10V DC	£2.50
15V DC	£2.50
20V DC	£2.50
50V DC	£2.50
100V DC	£2.50
150V DC	£2.50
300V DC	£2.50
500V DC	£2.50
750V DC	£2.50
15V AC	£2.55
50V AC	£2.55
150V AC	£2.55
300V AC	£2.55
500V AC	£2.55
S Meter 1mA	£2.55
VU Meter	£2.90

CLEAR PLASTIC MODEL SD460
Size: 59 x 46mm

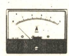

50uA	£3.10
100uA	£3.05
200uA	£3.00
500uA	£2.80
50-0-50uA	£3.10
100-0-100uA	£3.05
1mA	£2.85
5mA	£2.85
10mA	£2.85
50mA	£2.85
100mA	£2.85
500mA	£2.85
1A DC	£2.85
5A DC	£2.85
10A DC	£2.85
5V DC	£2.85
10V DC	£2.85
50V DC	£2.85
300V DC	£2.85
15V AC	£3.00
300V AC	£3.00
VU Meter	£3.20

POSTAGE & PACKING 15p

CLEAR PLASTIC MODEL 65P
Size: 86 x 78mm

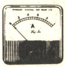

50uA	£4.10
100uA	£3.45
200uA	£3.35
500uA	£3.05
50-0-50uA	£3.45
100-0-100uA	£3.40
500-0-500uA	£2.85
1mA	£2.85
5mA	£2.85
10mA	£2.85
50mA	£2.85
100mA	£2.85
500mA	£2.85
1A DC	£2.85
5A DC	£2.85
10A DC	£2.85
15A DC	£2.85
20A DC	£2.85
30A DC	£3.10
50A DC	£3.20
5V DC	£2.85
10V DC	£2.85
20V DC	£2.85
50V DC	£2.85
150V DC	£2.85
300V DC	£2.85
15V AC	£3.10
50V AC	£3.10
150V AC	£3.10
300V AC	£3.10
500V AC	£3.10
S Meter 1mA	£3.15
VU Meter	£4.10
1A AC	* £2.85
5A AC	* £2.85
10A AC	* £2.85
20A AC	* £2.85
30A AC	* £2.85
50mA AC	* £2.85
100mA AC	* £2.85
200mA AC	* £2.85
500mA AC	* £2.85

BAKELITE MODEL S80 Enlarged Window
Size: 80 x 80mm

50uA	£3.85
100uA	£3.75
500uA	£3.35
50-0-50uA	£3.75
100-0-100uA	£3.65
1mA	£3.00
1A DC	£3.30
5A DC	£3.30
20V DC	£3.30
50V DC	£3.30
300V DC	£3.30
300V AC	£3.30
VU Meter	£4.05

CLEAR PLASTIC MODEL 52P
Size: 60 x 60mm

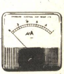

50uA	£3.85
100uA	£3.30
500uA	£2.90
50-0-50uA	£3.35
100-0-100uA	£3.25
1mA	£2.75
5mA	£2.75
10mA	£2.75
50mA	£2.75
100mA	£2.75
500mA	£2.75
1A DC	£2.75
5A DC	£2.75
10V DC	£2.75
20V DC	£2.75
50V DC	£2.75
300V DC	£2.75
15V AC	£2.85
300V AC	£2.85
S Meter 1mA	£2.85
VU Meter	£3.95
1A AC	* £2.75
5A AC	* £2.75
10A AC	* £2.75
20A AC	* £2.75
30A AC	* £2.75

BAKELITE MODEL 65 Size: 80 x 80mm

25uA	£5.05
50uA	£3.90
100uA	£3.30
500uA	£3.00
50-0-50uA	£3.35
100-0-100uA	£3.30
500-0-500uA	£2.85
1mA	£2.85
1-0-1mA	£2.85
5mA	£2.85
10mA	£2.85
50mA	£2.85
100mA	£2.85
500mA	£2.85
1A DC	£2.85
2A DC	£2.85
5A DC	£2.85
15A DC	£2.85
30A DC	£2.85
50A DC	£2.85
5V DC	£2.85
10V DC	£2.85
20V DC	£2.85
50V DC	£2.85
150V DC	£2.85
300V DC	£2.85
30V AC	* £2.85
50V AC	* £2.85
150V AC	* £2.85
300V AC	* £2.85
500V AC	£2.85
VU Meter	£4.00
1A AC	* £2.85
5A AC	* £2.85
10A AC	* £2.85
20A AC	* £2.85
30A AC	* £2.85
50A AC	* £2.85
500mA AC	£2.85
50mV DC	£3.20
100mV DC	£3.20

240° Wide Angle 1mA METERS

MW 1—6 60x60mm
£3.97 P&P 15p
MW 1—8 80x80mm
£4.97 P&P 15p

AUTO TRANSFORMERS

0/115/250V. Step up or step down. Fully shrouded.

80 WATT	£2.75	P&P 18p
150 WATT	£3.50	P&P 18p
300 WATT	£4.50	P&P 23p
500 WATT	£6.95	P&P 33p
1000 WATT	£9.50	P&P 38p
1500 WATT	£12.50	P&P 43p
2250 WATT	£20.95	P&P 50p
5000 WATT	£44.95	P&P £1

ALL PRICES EXCLUDE VAT

Also see following pages

LASKYS

**INCORPORATING LASKYS RADIO
AND G. W. SMITH & CO. (RADIO).**

SWR METER Model SWR3

Handy SWR meter for transmitter antenna alignment, with built-in field strength meter. Accuracy 5%, Impedence 52' Indicator 100uA DC. Full scale 5 section collapsible antenna. Size 145 x 50 x 60mm.

OUR PRICE £4.25 P&P 25p

MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorbtion Wave Meter and Oscillating Detector. Frequency range 440kHz–280MHz in six coils. 500uA meter. 9V battery operation. Size: 180 x 80 x 40mm.

OUR PRICE £15.00 P&P 20p

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing. ¼" diameter shafts. Bulk quantities available.

25 WATT 10/25/50/100/250/500/1000 Ohms **£1.15** P&P 10p

50 WATT 10/25/50/100/250/500/1000/2500/5000 Ohms. **£1.62** P&P 10p

100 WATT 1/5/10/25/50/100/250/500/1000/2500 Ohms **£2.34** P&P 15p

SH628 STEREO HEADPHONES

Outstanding value. With soft ear pads and adjustable headband. 8–16 ohms. 20–20,000Hz. Complete with lead and stereo plug.

OUR PRICE £1.87 P&P 30p

LH02S STEREO HEADPHONES

Light weight headphones with padded ear pieces. 4/16 ohms 20–20,000Hz. Complete with 6' lead and plug.

OUR PRICE £1.97 P&P 30p

TE1018 Deluxe Mono High Impedence Headset.

Sensitive magnetic headset with soft ear pads. Impedence 2,600 ohms (600 ohms DC). Frequency response: 200–4,000Hz.

OUR PRICE £2.25 P&P 30p

DH02S STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable head band. Impedence 8 ohms 20–12,000Hz. Complete with lead and plug.

OUR PRICE £2.25 P&P 30p

BH001 HEADSET and Boom Microphone

Moving coil. Ideal for language teaching, communications etc. Headphone impedence 16 ohms. Microphone impedence 200 ohms.

OUR PRICE £5.95 P&P 30p

ALL PRICES EXCLUDE VAT

Also see previous pages

SUPER VALUE TOP QUALITY TRIO communications equipment

TRIO JR599 RECEIVER

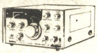

Nine wave-bands covering 1.8–29.7 MHz, 144–146MHz and 10MHz WWV SSB, CW, AM and FM. AF output is more than 1 watt. S Meter. Squelch control. BFO. Variable AF and RF controls. 4–16 ohm output and jack for phones. Power requirement 100/240V AC, 12/14V DC, Size: 270 x 140 x 310mm.

Our Price £132.50 CARR. PAID

TRIO 9R59DS RECEIVER

Four bands covering 550kHz to 30 MHz continuous and electrical bandspread on 10, 15, 20, 40, and 80 mtrs. 8 valve plus 7 diode circuit. 4 to 8 ohm output and phone jack. SSB–CW, ANL, variable BFO. S Meter and separate band spread dial. IF frequency 445kHz, audio output 1½ watt. Variable RF and AF gain controls. 115/250V AC, with instructions.

Our Price £42.50 CARR. PAID

TRIO JR310 SSB RECEIVER

Covers 3.5, 7, 14, 21, 28, 28.5 and 29.1MHz bands and WWV 15MHz. SSB, AM and CW. AF output more than 1W. Crystal controlled BFO for SSB. S Meter, ANL etc. AC 110/120–220/240V. Size: 330 x 179 x 310mm.

OUR PRICE £75.00 Carr. paid

TRIO TR2200 TRANSCEIVER

Fully transistorised portable VHF transceiver Will transmit and receive on six channels between 144–146MHz. 1 watt transmitter. 12V DC internal or external supply. Built-in charger for Ni-Cad cells. Power/volume switch, squelch control, channel selector, mic. socket, earphone/external speaker socket. Complete with microphone and 144.48, 144.72 & 145.32 crystals. Size: 134 x 58 x 180mm.

OUR PRICE £79.50 Carr.paid

UNR30 RECEIVER

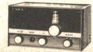

Four bands covering 550 KHz/30MHz BFO. Built-in speaker. Operates from 220/240V AC. Brand new with instructions.

OUR PRICE £15.75 P&P 37p

BELTEK W5400 CAR TRANSCEIVER

Solid state mobile transceiver for 12 volt DC neg. Transmits and receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 1W switchable. Controls: On/off/volume, squelch and channel selector. Internal 3" speaker. Complete with dynamic mic. PTT switch, three sets of crystals for 144.48, 144.6 and 145MHz, mounting bracket and instructions. Size: 150 x 70 x 220mm.

OUR PRICE £75.00 P&P 50p

LAFAYETTE HA600 Receiver

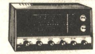

General coverage 150–400kHz, 550 kHz–30MHz. FET front end 2 mechanical filters, product detector. Noise limiter, variable BFO, S Meter, Bandspread and RF gain. 220/240V AC or 12V DC. Brand new with instructions.

OUR PRICE £50.00 P&P 50p

BVD5 Vernier TUNING DIAL

App. 7:1 ratio planetary drive vernier dial. Log scale 0–180 degrees. Blank scales 1–5. Dial size 128 x 76mm. Overall size 190 x 117 x 41mm. deep including knob and coupling. ¼" diam. shaft

OUR PRICE £1.62 P&P 15p

AUDIOTRONIC AHA101 Stereo Headphone Amplifier

All silicon, transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. INPUTS: 5mV and 100mV. OUTPUT: 50mV per channel.

OUR PRICE £7.50 P&P 20p

EMI LOUDSPEAKERS

Model 350 13 x 8" with single tweeter/crossover 20–20,000Hz. 15 watts RMS. Available 8 or 15 ohms.

OUR PRICE £7.25 each P&P 37p

Model 450 13 x 8" with twin tweeter/crossover. 55–13,000Hz. 8 watts RMS. Available 8 or 15 ohms

OUR PRICE £3.62 each P&P 25p

RUH6 Reflex Horn Speaker

Built-in driver unit. Impedence 16 ohms. Power rating 10W. Response 380–7000Hz. Size app. 6" x 6". Weather and shock protected.

OUR PRICE £4.97 P&P 30p

SPECIAL BARGAIN !! STEREOSOUND SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size: 368 x 229 x 190mm. 8 ohms. 8 watts RMS, 16 watts peak. Complete with Din lead.

OUR PRICE £12.95 P&P 50p

HIGH QUALITY CONSTRUCTION KITS

JOSTY KIT

WE ARE APPOINTED STOCKISTS AT ALL BRANCHES

All kits are complete with comprehensive easy to follow instructions and covered by full guarantee.

Post and Packing 15p per kit.

AF20 Mono amplifier	£4.80
AF30 Mono pre-amplifier	£2.61
AF310 Mono amplifier	£5.91
AT5 Auto light control	£2.58
AT30 Photo cell switch unit	£5.70
AT50 400W Light dimmer/ speed control	£4.80
AT55 1,300W Light control/ speed control	£5.70
AT56 2,200W Light dimmer/ speed control	£6.90
AT60 1 channel light control	£7.80
AT65 3 channel light control	£14.55
HF61 MW transistor radio	£3.33
HF65 FM Transmitter	£2.70
HF75 FM transistor radio	£2.88
HF310 FM tuner unit	£15.81
HF325 Deluxe FM tuner unit	£24.12
HF330 FM stereo decoder	£9.96
HF395 Aerial amplifier for AM/FM bands I, II, & III	£1.77
GP310 Stereo pre-amplifier	£21.27
GU330 Tremolo unit	£7.50
NT10 PSU 100mA/9–12V	£6.15
NT300 Professional stabilised PSU. 2 x 30V, 2.2A	£12.51
NT305 Transistor converter 12/15V AC/DC to 6V, 7.5V or 9V DC	£4.50
NT310 PSU 240V AC to 2 x 18V DC at 2A	£4.80
NT315 PSU 240V AC to 4.5–15V DC at 500mA	£9.57
AE1 100mW output stage	£1.65
AE2 Pre-amplifier	£1.26
AE3 Diode receiver	£2.00
AE4 Flasher	£1.09
AE5 Astable multivibrator	£1.05
AE6 Monostable multivibrator	£1.02
AE7 RC generator	£1.06
AE8 Bass filter	99p
AE9 Treble filter	99p
AE10 CCIR filter	99p

NEW FROM JOSTY-KIT 'Amateur Electronics'

The professional book for the amateur —covers the subject from basic principles to advanced electronic techniques. Complete with circuit board for making ten of the kits listed above.

OUR PRICE £3.30 (No VAT)
P & P 25p plus VAT

FRUSTRATED EXPORT ORDER !!

Philco Ford 5245 Mains Tape Recorder.

2 track BSR deck with push button controls for easy operation. Tape counter and volume control Complete with hand microphone, direct recording lead, 1,200' reel of tape and spare reel. 200/250V AC. Fully guaranteed.

OUR PRICE £17.50 P&P 75p

Philco Ford 5248 Mains Tape Recorder.

Four track, two speeds. Piano key type controls, tape counter, recording level meter, volume and tone controls etc. Complete with hand, microphone lead for direct recording 1,800' of tape and spare reel. 200/250V AC. Fully guaranteed.

OUR PRICE £27.50 P&P 75p

KE630 3 Station INTERCOM

Master and two sub-stations. Can be used on desk or wall mounted. Complete with cable and batteries

OUR PRICE £5.25 P&P 50p

SINCLAIR CAMBRIDGE CALCULATOR

To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator.

OUR PRICE £24.95 P&P free

ALSO AVAILABLE READY BUILT
Recommended Price £29.95

OUR PRICE £27.20 P&P 25p

Also available—
SINCLAIR EXECUTIVE
Recommended Price £39.00

OUR PRICE £35.45 P&P 25p

SINCLAIR EXECUTIVE with MEMORY
Recommended Price £49.00

OUR PRICE £44.50 P&P 25p

SPECIAL PURCHASE!! BSR 8 Track Player Chassis

Famous BSR 8track chassis as used in model TD8S complete with silver and black escutcheon, ready to fit into cabinet. Output 125mV. 240V AC. Overall size app. 185 x 215 x 80mm.

OUR PRICE £8.95 P&P50p

MP7 MIXER-PREAMPLIFIER

5 Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. Size: 235 x 127 x 76mm. Inputs: Mics. 3 x 3mV 50k; 2 x 3mV 600 ohms. Phono. Mag. 4mV 50k; Phono Ceramic 100mV 1 Meg. Output 250mV 100k.

OUR PRICE £8.97 P&P 20p

NEW SINCLAIR PROJECT 80 HI-FI MODULES & PACKAGES

Z40 Power Amplifier	£5.45
Z60 Power Amplifier	£6.95
Stereo 80 Pre-Amplifier	£11.95
Active Filter Unit	£6.95
Project 805	£26.95
PZ5 Power Supply	£4.98
PZ6 Power Supply	£7.98
PZ8 Power Supply	£7.98
2 x Z40/Stereo 80/PZ5	£25.00
2 x Z40/Stereo 80/PZ6	£27.75
2 x Z60/Stereo 80/PZ8	£30.45
Transformer for PZ8	£4.05

POST & PACKING 35p each

FM TUNER CHASSIS

6 transistor high quality tuner. Size only 153 x 101 x 63mm 3 IF stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Covers 88–108MHz. Ready built, ready for use. Fantastic value for money.

OUR PRICE £5.95 P&P 20p

A1018 FM TUNER

Specification as above FM chassis but complete in cabinet with on/off switch. Size: 184 x 86 x 127mm.

OUR PRICE £9.65 P&P 30p

Stereo multiplex adapter £4.97

DT55B DIGITAL CLOCK MECHANISM

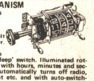

Features 24 hour alarm setting with built in buzzer. On/off and auto alarm 'sleep' switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off radio, TV, light etc. and with auto-switching will turn on again when required. 240V AC operation. Switch rating 250V. 3 Amp.

OUR PRICE £5.95 P&P 30p

BINATONE DS100 Digital Clock

240V mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Size: 159 x 76 x 82mm.

OUR PRICE £4.50 P&P 30p

LASKYS

**INCORPORATING LASKYS RADIO
AND G. W. SMITH & CO. (RADIO).**

AUDIOTRONIC AMR9000
Global AM/FM Portable Radio

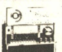

10 wave-bands covering AM: 535–1605kHz. LW: 150–380 kHz. MB 1.6–4MHz. SW1: 4–8MHz. SW2: 8–1.6 MHz. SW3: 16–24MHz. PSB1: 30–50 MHz. PSB2: 148–174MHz. FM: 88–108MHz. Air: 108–136MHz. Feature time zone map and timing dial. Large clear scale. Telescopic aerial and built in aerial. AFC on FM. 6"x4" speaker and personal earpiece. Battery/mains operation. Size: 345 x 133 x 305mm.

OUR PRICE £36.00 P&P 50p

AUDIOTRONIC DOLBY B
Noise Reduction Units

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size: 460 x 203 x 79mm. AC 220/240V

PROCESS 4

For use with semi-professional tape recorders. Frequency response 30Hz –20kHz ± 2dB. S/N better than 70dB. Full source/tape monitoring. Switchable multiplex filter. Supplied with test tape.

OUR PRICE £50.00 P&P 50p

PROCESS 2

For use with cassette and tape recorders. Frequency response 30Hz–20kHz Switchable multiplex filter. 2 Dolby calibration meters. Off tape monitoring. S/N better than 70dB. Supplied complete with test tape or cassette.

OUR PRICE £34.50 P&P 50p

CT5050 Cassette Recorder

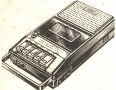

Instant recording and playing. Piano key controls. Automatic level control. Built-in speaker, Complete with remote control microphone, carrying case and shoulder strap.

OUR PRICE £8.50 P&P 50p

AUDIOTRONIC ACD660
Stereo Cassette Deck

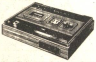

A beautifully styled four track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, normal/chrome tape selector, twin VU meter slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/Din line input sockets, 3.5mm microphone in-sockets etc, etc. Frequency response: 40–12kHz (40–16kHz CrO2), S/N: –45dB. Crosstalk 45dB. Separation: –35dB. Noise limiter –6dB at 10kHz. Complete with connecting leads.

OUR PRICE £39.50 P&P 50p

AUDIOTRONIC LOW NOISE CASSETTES

TYPE	5	10	25
C60	£1.37	£2.61	£6.16
C90	£1.95	£3.70	£8.71
C120	£2.38	£4.50	£10.65

AUDIOTRONIC CrO2 CASSETTES

TYPE	5	10	25
CR60	£3.41	£6.72	£16.63
CR90	£4.63	£9.19	£22.80

AUDIOTRONIC 8 TRACK CARTRIDGES

TYPE	Each	5	10
40M	75p	£3.50	£6.50
80M	99p	£4.70	£8.90

P&P Cassettes 3p, Cartridges 5p each
OVER 10 of either POST FREE!

WALKIE TALKIES

SKYFON 100mW
OUR PRICE £24.95 per pair
P302 Two Channel 300mW
OUR PRICE £52.50 per pair
P1003 Three Channel 1 Watt
OUR PRICE £71.25 per pair
P&P 50p per pair

NB. Licence required for use in UK

1021 Stereo Listening Station

For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. Two gain controls, speakers on off slide switch, stereo headphone socket.

OUR PRICE £2.25 P&P 15p

AUDIOTRONIC STEREO HEADPHONES

LSH20 Individual volume controls. Stereo/mono switch. 8 ohms. 40–19,000Hz.
OUR PRICE £3.75 P&P 30p

LSH30 Open back type. Individual tone and volume controls. 8 ohms. 30–20,000Hz
OUR PRICE £5.95 P&P 30p

LSH40 Two way speaker system Individual volume controls. 8 ohms. 20–20,000Hz
OUR PRICE £7.50 P&P 30p

LSH60 3" speaker units. 8 ohms. Complete with zipped carrying case. 20–20,000Hz.
OUR PRICE £8.95 P&P 30p

LSH50 Electrostatic with self powered energiser. and control unit, with headphone speaker selector. 4–32 ohms 20–24,000Hz.
OUR PRICE £16.95 P&P 30p

LQH400 4 channel dynamic headphones. Each earpeice has four drive units. 4–32 ohms 20–20,000Hz
OUR PRICE £9.95 P&P 30p

EA41 REVERBERATION AMPLIFIER

Self contained, transistorised, battery operated Simply plug in microphone, guitar etc and output to your amplifier. Volume control and depth of reverberation control. Beau-walnut cabinet. 184 x 77 x 108mm.

OUR PRICE £7.50 P&P 20p

SPECIAL BARGAIN! FERGUSON 3406 HI-FI SPEAKERS

High quality 2 way speaker systems. 25 Watts. 4–8 ohms. 40Hz–18kHz. Size: 560 x 340 x 255mm. approx. Wood grain finish with black fronts.

OUR PRICE £29.95 PR. P&P £1

RECORD DECKS

P&P 50p

BSR McDONALD	
C114 Mini	£3.95
C129 Mono	£5.50
C137	£7.00
510/TPD	£12.55
610	£11.30
610/TPD	£15.35
710	£23.10
810	£28.25
MP60	£8.85
MP60/ADC K8	£10.90
MP60/TPD	£14.15
HT70	£11.60
HT70/ADC K7E	£14.25
HT70/TPD	£16.55
CONNOISSEUR	
BD1 Kit	£10.20
BD1 Chassis	£12.50
BD2/SAU2/Chassis	£25.50
BD2/SAU2/Plinth/Cover	£32.25
GARRARD	
1025T Stereo	£4.95
2025TC Less Cartridge	£6.35
2025TC/KS40A	£6.95
SP25 Mk3	£9.25
SP25 Mk3/G800	£10.95
SP25 Mk4	£10.90
SP25 Mk4/M75-6	£13.90
86SB	£20.00
SL65B	£11.15
SL72B	£17.75
SL95B	£28.00
401	£28.60
ZERO 100	£34.10
ZERO 100S	£31.40
ZERO 100SB	£29.20
GOLDRING	
G101 Mk2/P/C	£22.50
GL72	£25.45
GL72P	£33.75
GL75	£32.20
GL75P	£41.65
GL78	£34.60
GL78/P/C	£56.25
GL85/P/C	£72.00

RECORD DECK PACKAGES

BSR McDONALD	P&P 75p
210/SC7M	£7.90
C129	£9.50
MP60/G800	£17.85
MP60/TPD/ADC K8	£16.97
MP60/M44-7	£17.50
HT70/TPD/ADC K7E	£19.20
610/TPD/ADC K8	£19.42
GARRARD	
2025TC/9TA-HC/D	£11.35
SP25 Mk3/G800	£18.15
SP25 Mk3/M44E	£18.25
SP25 Mk3/M44-7	£17.80
SP25 Mk3/M55E	£18.80
SP25 Mk3 Module/M75-6	£19.45
SP25 Mk4/G800	£19.95
SP25 Mk4/AMC 50E (M55E)	£21.30
AP76/G800	£26.75
AP76/G800E	£28.95
AP76/M44-7	£27.50
AP76/M44E	£28.00
AP76/M55E	£28.60
AP76/M75ED	£35.20
AP76/M75EJ	£31.20
GOLDRING	
GL72/G800	£35.65
GL75/G800	£40.90
GL75/G800E	£43.35
GL78/G800	£45.65
GL78/G800E	£48.15
G101/P/C/G800	£23.70
PHILIPS	
GA105/GP200	£12.40
GA205	£17.40
GA207	£20.90
RANK DOMUS	
BD2000	£43.60
BA4000	£53.95
BD6000	£67.50
WHARFEDALE	
Linton W30 Teak	£23.90
Linton W30 White	£25.10

LINEAR 202 STEREO AMPLIFIER

20 Watts RMS Stereo Amplifier with controls for volume, balance, bass and treble, Mono/Stereo switch, loudness and scratch filters. Uses 20 Silicon transistors. Inputs for magnetic and crystal cartridge, Aux. and tape.

OUR PRICE £22.50 P&P 50p

SPECIAL BARGAIN!!
PHONIC 10 Two Way Speakers

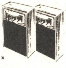

Matched pair of compact book-shelf speakers of unique design. Incorporating a 2" high frequency unit & 6" woofer. 8 ohms impedence. Size: 348 x 228 x 110mm.

OUR PRICE £8.85 Pair P&P 50p

LEAK TRUSPEED Mk3 RECORD DECK PACKAGE

Incorporing low speed synchronous hysteresis motor giving constant turntable speed. 33 and 45 rpm. Cast Alluminium turntable. Fitted Goldring L75 arm and G800 cartridge, complete in plinth with perspex cover. Size 321 x 400 x 191mm inc. cover. AC100-130 and 200-250V.

OUR PRICE £35.95 P&P 75p

AUDIOTRONIC AMC50E
STEREO Magnetic CARTRIDGE

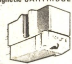

Made by SHURE the AMC50E offers professional performance at a budget price. Frequency response: 20Hz–20kHz. Output voltage 6.6mV. Compliance: 5 x 10–6 cm/dyne. Tracking force ¾ to 2 grammes. Stylus: Eliptical diamond .0007" x .0002".

OUR PRICE £4.50 P&P 12p

AD-76K STEREO MAGNETIC CARTRIDGE

Frequency response 20Hz–20kHz. Output: 5mV (1kHz 5 cm/sec). 0.7 mil conical diamond stylus. Channel separation 20dB. Tracking weight 1½–2½ gms. Original price £3.50

OUR PRICE £1.95 P&P 12p

TELETON F2100 STEREO RECEIVER SYSTEM

6 watts per channel AM/FM Stereo tuner amplifier, Garrard 2025TC record deck with plinth, cover and stereo cartridge, and a pair of Keletron LS50 speakers. SUPER VALUE!

OUR PRICE £48.50 Carr. & Ins. £1.25

ALL PRICES EXCLUDE VAT

CALL INTO YOUR NEAREST BRANCH OR ORDER WITH CONFIDENCE BY MAIL ORDER

CENTRAL LONDON

10 TOTTENHAM CT. RD.	01-637 2232
27 TOTTENHAM CT. RD.	01-636 3715
33 TOTTENHAM CT. RD.	01-636 2605
42/45 TOTTENHAM CT. RD.	01-636 0845
87 TOTTENHAM CT. RD.	01-580 3739
257/8 TOTTENHAM CT. RD.	01-580 0670
21 OLD COMPTON ST.	01-437 9369
3 LISLE ST. WC2	01-437 8204
34 LISLE ST. WC2	01-437 9155
118 EDGWARE RD. W2	01-723 9789
193 EDGWARE RD. W2	01-723 6211
207 EDGWARE RD. W2	01-723 3271
311 EDGWARE RD. W2	01-262 0387
346 EDGWARE RD. W2	01-723 4453
382 EDGWARE RD. W2	01-723 4194
109 FLEET ST. EC4	01-353 5812
152/3 FLEET ST. EC4	01-353 2833
378 HARROW RD. W9	01-286 9530

ESSEX

86 SOUTH ST. ROMFORD	70-20218

SURREY

1046 WHITGIFT CENTRE, CROYDON	01-681 3027
27 EDEN ST. KINGSTON	01-546 7845
32 HILL ST. RICHMOND	01-948 1441

KENT

53/57 CAMDEN RD., TUNBRIDGE WELLS
0892-23242

LEICESTERSHIRE

45 MARKET PLACE, LEICESTER
0533-537678

ALL BRANCHES OPEN FROM
9am to 6pm MON. TO SAT.

HEAD OFFICE AND MAIL ORDER DEPARTMENT

AUDIOTRONIC HOUSE,
THE HYDE INDUSTRIAL ESTATE,
THE HYDE, LONDON NW9 6JJ.
TELEPHONE: 01-205 3735 & 5651.

MAIL ORDER SPECIALISTS
We offer a speedy and efficient service by mail order. Remember to add 10% VAT to total value of goods including carriage and packing and send cash with order to head office. **TO AVOID DELAYS PLEASE PRINT NAME AND ADDRESS CLEARLY IN CAPITALS.**

BARCLAYCARD & ACCESS
Holders welcome call into any branch or telephone your order to head office. **CREDIT TERMS** available for Personal Shoppers on sales of £50 and over

BARGAIN CENTRE
Many special clearance offers and end of stock lines at **87 TOTTENHAM COURT RD. FOR PERSONAL SHOPPERS.**

EXPORT Personal exports arranged for overseas visitors at all our branches. Goods despatched to all parts of the world through our Export Mail Order Department. Immediate attention given to orders.

CHEQUES ACCEPTED FROM PERSONAL SHOPPERS ONLY WITH BANKERS CARD.

All prices correct at 16-1-74 but subject to change. E.& O.E.

PART OF THE AUDIOTRONIC GROUP OF COMPANIES

G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

SPECIAL OFFER ! ! !

SMALL ELECTROLYTICS

Ref. No.	Capacity	Voltage	Price	Ref. No.	Capacity	Voltage	Price
H8/1	1μF	150V	**4p**	H7/4	64μF	15V	**4p**
H8/1A	2μF	150V	**2p**	H7/4A	64μF	35V	**5p**
H8/2	2·2μF	25V	**4p**	H7/5	80μF	16V	**4p**
H8/2A	3·3μF	25V	**4p**	H7/6	100μF	25V	**5p**
H8/3	3μF	50V	**4p**	H7/7	100μF	25V	**4p**
H8/3A	4μF	50V	**4p**	H7/8	125μF	16V	**5p**
H8/4	4·7μF	25V	**4p**	H7/8A	100μF	35V	**6p**
H8/4A	5μF	64V	**4p**	H7/9	100μF	63V	**6p**
H8/5	5μF	10V	**4p**	H7/9A	125μF	4V	**4p**
H8/5A	5μF	150V	**4p**	H7/10	125μF	25V	**6p**
H8/6A	10μF	10V	**4p**	H7/10A	160μF	2·5V	**3p**
H8/7	10μF	70V	**4p**	H7/11	160μF	25V	**6p**
H8/8	16μF	35V	**4p**	H7/11A	150μF	16V	**5p**
H8/8A	16μF	16V	**4p**	H7/13A	200μF	25V	**8p**
H8/9	20μF	6V	**2p**	H7/14	220μF	50V	**10p**
H8/9A	20μF	70V	**4p**	H7/14A	220μF	16V	**6p**
H8/10	22μF	50V	**4p**	H7/15	220μF	25V	**5p**
H8/10A	22μF	100V	**4p**	H7/15A	220μF	35V	**10p**
H8/11	25μF	12V	**4p**	H8/1A	250μF	4V	**3p**
H8/11A	24μF	275V	**4p**	H6/2	250μF	25V	**3p**
H8/12	32μF	15V	**4p**	H6/3A	320μF	2·5V	**3p**
H8/12A	30μF	10V	**4p**	H6/4	320μF	10V	**4p**
H8/13A	32μF	50V	**4p**	H6/4A	330μF	16V	**5p**
H8/14	40μF	25V	**5p**	H6/5	330μF	25V	**10p**
H8/14A	40μF	16V	**4p**	H6/5A	330μF	35V	**15p**
H8/15	47μF	50V	**4p**	H6/8	470μF	25V	**10p**
H8/15A	40μF	35V	**4p**	H6/8A	470μF	35V	**20p**
H7/1	50μF	6V	**3p**	H6/9	500μF	15V	**4p**
H7/1A	50μF	10V	**4p**	H6/9A	400μF	40V	**20p**
H7/2A	64μF	2·5V	**2p**	H6/13A	1000μF	25V	**16p**
H7/3A	64μF	25V	**4p**				

POSTAGE: 15p PER ORDER

ALL GOODS PLUS 10% V.A.T.

MULLARD ELECTROLYTIC CAPACITORS

071 and 072 Series

Type No.	Working Voltage Vdc	Capacitance μF	Max. Ripple Current at 50° C	Weight	Price
071 15332	16	3300	2·4 amps	1oz	**15p**
071 15472	16	4700	3·9 amps	1oz	**17p**
071 15682	16	6800	5·8 amps	1½oz	**22p**
072 15752	16	7500 + 7500	10·5 amps	3oz	**37p**
072 15113	16	11000 + 11000	13·8 amps	4½oz	**49p**
071 16472	25	4700	5·4 amps	1½oz.	**22p**
072 16502	25	5000 + 5000	9·6 amps	3½oz	**37p**
072 16752	25	7500 + 7500	12·6 amps	4½oz	**49p**
071 18681	63	680	2·1 amps	1oz	**15p**

106 and 107 Series

Type No.	Working Voltage Vdc	Capacitance μF	Max. Ripple Current at 50° C	Weight	Price
106 16223	25	22000	17 amps	10oz	**£1·12**
106 17103	40	10000	12 amps	7½oz	**94p**
107 10222	100	2200	10 amps	5½oz	**74p**

Type No.	Voltage	Capacitance	Weight	Price
102 15163	16	16000	8oz	**20p**
104 90003	20	39000	16oz	**30p**
102 16802	25	8000	7oz	**25p**
104 90001	45	20000	16oz	**50p**

A further 10% discount on lots of 100 of any one type.

Please calculate the weight of your order and include appropriate postage.

Not over	Ordinary Parcels	Not over	Ordinary Parcels
1½lb	**16p**	10lb	**37p**
2lb	**21p**	14lb	**47p**
4lb	**25p**	18lb	**57p**
6lb	**29p**	22lb	**67p**

UNIJUNCTION TRANSISTORS similar to 2N2646 **25p**

£1
100 ½ ½ WATT RESISTORS
100 CERAMIC
CAPACITORS
100 DIODES
POSTAGE **15p** PACK No. 1

£1
100 RESISTORS
100 CERAMIC
CAPACITORS
100 POLYSTYRENE
CAPACITORS
POSTAGE **15p** PACK No. 2

£1
1 VERO-BOARD CUTTER
5 2½in x 1in x 0·15 BOARDS
50 SQ.IN "ODD PIECES"
VERO
POSTAGE **15p** PACK No. 3

£1
100 RESISTORS
100 CERAMIC
CAPACITORS
50 MULLARD POLYESTER
CAPACITORS
POSTAGE **15p** PACK No. 4

£1
20 ASSORTED UNUSED
MARKED, TESTED
TRANSISTORS
BC108, ETC.
POSTAGE **15p** PACK No. 5

£1
1 TRANSISTORISED
SIGNAL TRACER KIT
1 TRANSISTORISED
SIGNAL INJECTOR KIT
POSTAGE **15p** PACK No. 6

£1
8 COMPUTER PANELS
CONTAINING MASSES OF
DIODES, TRANSISTORS,
INDUCTORS, RESISTORS
AND CAPACITORS
POSTAGE **25p** PACK No. 7

£1
100 RESISTORS
100 CAPACITORS
(ASSORTED TYPES)
POSTAGE **15p** PACK No. 8

RAYMER ELECTRONICS

RE 500

Advanced integrated Hi-Fi Amplifier only requires connection to mains speaker and input.
Specifications: load imp 4–16 ohm.
Output: 5 watts.
Frequency response 20 Hz to 35kHz ±3dB.
Total distortion less than 1%. I/P Imp 100k ohm Nom. **£6·30.** Post free.
Size: 140 × 80 × 45mm.

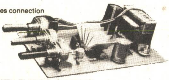

COMPLETE QUADRAPHONIC AMPLIFIER KIT: RE 4K

A Hi-Fi kit comprising CBS SQ decoder, preamplifier and four channel main amplifier. All modules built and tested.
Specifications:
Similar to the Quadrix system (see below) but with *four* channel main amplifier giving 40 watts total peak power.
This is an opportunity to experience quadraphonic sound at the very minimum of cost.

RE QUADRIX

This is a high quality CBS specification SQ decoder with Hi-Fi stereo amplifier. Designed to allow the conversion of any stereo system to full quadraphonic performance with minimum cost. Extraordinary new presence and reality of sound. More than 20 Watts total peak power.

Specifications:

Decoder

I/P impedance	40kΩ
O/P impedance	<300Ω
Nominal I/P	100mV RMS
Front separation	<60dB
Rear separation	<20dB

Amplifier
Power O/P 5W RMS per channel (simultaneously)
Distortion at full O/P less than 1%
Sensitivity for full O/P 100mV
Active tone control Bass ±10bB, Treble ±12dB at 100Hz–10kHz
Load impedance 8–16 ohms

Special Offer **SQ records (full quadraphonic sound) available direct. Comprehensive list free on request.**

GUARANTEE
ALL PRODUCTS ARE GUARANTEED AGAINST FAILURE FOR A PERIOD OF 12 MONTHS AND WILL BE SERVICED FREE OF CHARGE IF PURCHASED DIRECT AND REFUNDED TO US FOR REPAIR.

MICROCHIP I.C.

5 watts RMS
A general purpose Audio i.c. for the constructor capable of 5 watts RMS O/P at less than 1% total distortion, forms an ideal basis for an excellent Hi-Fi system.
Free Data I.C. **£1·50.**
Data, Printed Circuit Board, **75p.**
Post paid.

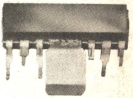

(Power Amp only shown

£39·00. Post free

Power Supply Extra (RE 35 psu)

£49·00. Post free

NAME ....
ADDRESS ....
PLEASE SEND ....
(enclose PO/cheque/M.O.) ....
RAYMER ELECTRONICS LTD.,
Stanley Road, Cambridge CB5 8LB, England.
(0223) 54414. Reg. No. 1021205

PLEASE ADD
10% FOR V.A.T.

***STILL AT £42·50**
Solartron CD 711S.2 Double Beam Oscilloscope D.C.—9 Mc/s; 3 MV/cm; trigger delay; crystal calibrator; 4in flat faced tube. In good working condition. Carr. £1·50.

NEW WIDE RANGE WOBBULATOR
5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10·7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6·3V A.C. and use within minutes of receiving. All this for ONLY **£5·75p.** P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. **£7·85** each. P. & P. 25p (Not cased, not calibrated.)

GRATICULES. 12cm × 14cm high quality plastic **15p** each. P. & P. 5p.
12" Long Persistence Crt, full spec. Price **£7·50** to include V.A.T. & carr.

£1 WORTH OF "UFS". Six brand new capacitors all between 15V and 100V. Total capacitance not less than 7,000mF. P. & P. 45p.

PHOTOMULTIPLIER type 931A **£3·25** each. P. & P. 25p.

ROTARY SWITCH PACK. Six brand new switches (1 ceramic; 1 off, 4 pole, 2 way, etc.), **50p.** P. & P. 20p.

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors ¼ and ½ watt, many high stabs, etc. Fine value at **50p.** P. & P. 17p.

P.C.B. PACKS S & D. Quantity 2sqft—no tiny pieces. **50p** plus P. & P. 20p.

FIBRE GLASS as above **£1** plus P. & P. 20p. Ferric Chloride Resistance Pen FREE (whilst stock lasts) on all purchases of our £1 Fibre Glass pack.

5 CRYSTALS 70 to 90kHz. Our choice, **25p.** P. & P. 15p.

5 MOVING COIL METERS various **£2.** P. & P. 37p.

CAPACITOR PACK—50 Brand new components only **50p.** P. & P. 17p.

POTS—10 different values. Brand new—**50p.** P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, **25p** the lot. P. & P. 10p.

FLAT FACED 4" Twin Beam Tube, type CV2193. Green trace. Brand new **£4** each. P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New **38p** each. Holder **1p** each. Information 5p.

PHOTOCELL equ. OCP71, **13p** each.

PHOTO RESISTOR type Clare 703. Two for **50p.**

MODERN TELEPHONES type 706. Two-tone grey, **£3·75** each. Two-tone green, **£3·75** each. Black, **£2·75** each. P. & P. 25p each.
Also **TOPAZ YELLOW £4·50** each. P. & P. 25p.

IDEAL EXTENSION Telephones with standard GPO type dial, bell and lead coding. **£1·75** each. P. & P. 25p.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY **£3·50.**

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 6.30 p.m. ANY DAY

CHILTMEAD LTD
7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) **Tel.: Reading 582605/65916**

PSYCHEDELIC LIGHTING UNIT IN KIT FORM
Make this fascinating three-channel unit from a kit which contains all components needed to produce an ever changing light display. Takes its drive from the speaker terminals of a record player, tape recorder or portable radio. Will drive a total of 2kW of coloured lamps at 240 volts. Supplied complete with PVC covered steel cabinet with holes ready punched for controls and cable outlets. Master control included. Coloured lamps not supplied.
Price per kit **£11·95**. 240 volt coloured lamps, each **30p.**

METAL CABINETS
These attractive steel cabinets are PVC covered in a range of colours, and offer an economically priced unit for the home constructor. The chassis, which has a white satin PVC finish, provides an easily accessible building area, with an integral fascia panel. The cabinet is supplied complete with stick-on feet.
Colours available include Green, Grey, Black, White and Blue. Every effort will be made to supply a selected colour, but please give alternatives if possible.

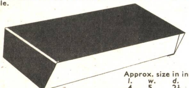

Approx. size in ins. *l.*	*w.*	*d.*	Price
4	5	2½	**75p**
8	6	3	**£1·60**
11	6½	3	**£2·04**

Other sizes to special order. HOLES PUNCHED in front or back panels to your own requirements. Please send S.A.E. for quotation.

FIXED VOLTAGE REGULATORS
TO3 case. Gives stabilised supply. MVR 5 V, MVR 12 V, MVR 15 V.
All priced at **£1·65**

VEROBOARD

	0·1	0·15
2½ × 1in	**7p**	**7p**
2½ × 3¾in	**27p**	**20p**
2½ × 5in	**29p**	**29p**
3¾ × 3¾in	**29p**	**29p**
3¾ × 5in	**31p**	**32p**

D.I.L. REED RELAY
Operates direct from 5 volt TTL logic elements. Normally open contact rated at 0·25A, 100V d.c. Price each **£1·50**

Our CATALOGUE, priced at 25p post free in U.K., shows most of the R.S. range of professional components. Prices include VAT.
All orders over 50p POST FREE—U.K. only. Overseas postage at cost. S.A.E. with all queries please.

CELECTRON-E
P.O. Box No. 1, Llantwit Major, Glamorgan, Wales CF6 9YN

PRACTICAL WIRELESS

SPECIAL SPRING FEATURES!

APRIL ISSUE

Sound to Light Display Control Box
Highlight your parties and discos. Simplified system—easy to make, hours of fun.

Windscreen Wiper Delay
Worn-out wiper blades? Build this easy-to-use wiper control unit.

P.W. CRATA—(Cassette Recorder and Tuner Amplifier). Part 2 of this excellent new design. For more details, see March issue of P.W.

Impedance Matching
Buying hi-fi or building your own? This article irons out the bugs.

SPECIAL TOOL-KIT OFFER—FANTASTIC VALUE . . . EXCELLENT QUALITY.
Superb kit of tools specially available to P.W. readers for constructional projects.

COMING IN MAY ISSUE

Exclusive Supplement. Basic techniques in radio and electronics. Fully illustrated.

Oscilloscope Trace Doubler
Getting the best out of oscilloscopes. Converting single beam to double beam. Double beam converted to show four waveforms simultaneously.

Distortion in Audio Amplifiers
Top author sorts out a misunderstood subject and shows examples with oscillograms.

Car Cassette Power Supply and Audio Booster
Relax with music—without car noise drowning your enjoyment. Useful for car radios, too!

APRIL ISSUE OUT MARCH 1 *ORDER NOW 20p*

The magazine with seven constructional articles every month!

F.M.0. VARICAP TUNER

LP1185/86	**£9.00**/pair
MC131OP	**£3.15** each
MFC4060 (late deliveries)	**78**p
P.C. BOARDS	**£1.87**
READY BUILT BOARDS	**£23.00**
COMPLETE TUNERS IN CABINETS	**£33.00**

NEW! **LP1400 DECODER MODULES**
—LIMITED STOCKS £4.96

Prices include V.A.T. P. & P. 25p.

B. & B. ELECTRONICS

64 MANNERS ROAD, BALDERTON, NEWARK, NOTTS.
Telephone: NEWARK 6895

WINDSCREEN WIPER DELAY KIT

Complete kit of parts including drilled and tinned fibreglass printed circuit board.

The unit provides intermittent wiper operations with a delay up to approximately 60 seconds which can be varied to optimise visibility in conditions of light rain, spray, etc. The original wiper switch overrides when normal operation is required.

£3·60 **including V.A.T. & P. & P. Cash with order.**

Additional relay available for foreign cars £1·10 including V.A.T.

ESSEX X-RAY CO. LTD.
57 THEYDON PARK ROAD, THEYDON BOIS
EPPING, ESSEX CM16 7LR

PHONOSONICS

PCB's AND KITS AT LOW PRICES

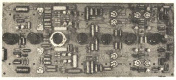

AURORA

Multichannel Sound Controlled Light (PE Apr./Aug. 71). S/c's (excl. SCRs), Rs, Cs, Pots, Cores—8 ch. **£18·42;** 4 ch. **£10·37.** Reg. PSU **£3·65.** PCB—4 ch. control (4¾in × 10¾in) Mk. 2—also holds rotary or slider pots **£2·20.** PCB (4¾in × 5in) Mk. 2—for PSU, Sync Gen, 8 cores, 8 SCRs, **£1·10.** SCRs—1A, **50p.**

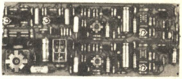

HI-FI TAPE LINK

(PE Mar./Apr. 73). S/c's, i.c.'s, Rs, Cs, Relay and pc-base, Pot Cores and pc-bases, Sw's, Pots, Panel Lamp—Mono, **£11·80;** Stereo, **£18·70.** PSU, **£3·58.** PCB—Main Circuit (3¾in × 9in) (Stereo) also holds relay and cores, **£1·85.** PCB—Sub-Assembly. (2½in × 6½in) (Stereo) Mk. 2 holds Sw, Rs, Cs, Presets and mounts on Sw's, **80p.**

MAILING LIST

New quarterly service
Details with current list

LOUD-HAILER AND SIREN
(Pre-amp and Siren Generator)

(PW Dec. 72). S/c's, Rs, Cs, Pot, PCB (2½in × 2¾in). **£2.20** (While stocks last). Main Amp Module PC5+ obtainable to special order, **£6·25.**

BIOLOGICAL AMPLIFIER

(PE Jan./Feb. 73). P/A Set—S/c's, i.c.'s, Rs, Cs, Pots, PCB (1½in × 3¾in), **£3·20.** O/P Stages (S/c's, Rs, Cs, Pots and Sw's as reqd.). Alphaphone **53p,** Cardiophone **66p,** Freq. Meter **£1·60,** Vis-Feedback **55p.** Audio Amp PC7 avail. to order **£5·20.**

ELECTRONIC PIANO

(PE Sep. 72/Jan. 73). Details in lists.

GEMINI STEREO AMPLIFIER

(PE Nov. 70/Mar. 71) Stereo Sets & PCBs. Pre-amp—S/c's. **£1·80.** Rs, Cs, Pots and Sw's—with ½W MO Rs, **£11·32**—with ½W or ¼W CF Rs, **£9·60.** PCB (3½in × 10¾in) for sets with MO and ¼W Rs, also holds rotary or slider pots and Maka-Sw's, **£1·90.** Main Amp—Rs, Cs, Pots, **£5·39.** PCB (3½in × 5in), **£1·15.** PSU—Rs, Cs, Pot, **£3·97.** PCB (2in × 4in), **65p.**

GEMINI STEREO TUNER

(PE Apr./Jun. 72). PCB as publ., **£1·50.**

MICROPHONE MIXER

(PE Apr. 69). S/c's, Rs, Cs, Pots, PCB (3¾in × 4¼in) also holds 6 rotary or 4 slider pots, **£3·70.**

8 WATT AMPLIFIER

(PW Nov./Dec. 72). Pre-amp—S/c's, Rs, Cs, Pots, Sw—Mono, **£2·50;** Stereo, **£5·45.** PCB (3½in × 7½in) (Stereo) also holds rotary or slider pots and Sw, **£1·50.** Main Amp—S/c's, Rs, Cs, Pot—Mono, **£3·65;** Stereo, **£7·30.** PCB (2½in × 3in) Mono), **60p.**

LOGICAL RADIO CONTROL AND MODEL SERVO CONTROL

(PE Feb./Jun. 72)—Still some PCB's left.

REVERBERATION UNIT

(PW Nov./Dec. 72). S/c's, Rs, Cs, Rotary Pots, T/fmr, **£6·44.** PCB (2in × 11¼in) also holds sliders, **£1·20.** 9in Spring Unit, **£3·75.**

VIBRASONIC GUITAR PRE-AMP

(PW Sept. 70). Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Cs, LDR, Rotary Pots, Lamp, Coupling T/fmr, **£6·97.** PSU, **£3·57.** PCB (3½in × 10¾in) Mk. 2, also holds 7 rotary or slider pots, **£1·75.**

ULTRASONIC TRANSMITTER-RECEIVER

(PE May 72). S/c's, Rs, Cs, Pot, Relay, Dual PCB (2in × 5½in), **£3·90.** T/ducers excluded.

ALSO

PCBs as published (while stocks last) for:
DIGICAL PSU (PE Aug. 72), **50p**
OSCILLOSCOPE P/A (PE Aug. 72), **33p**
TRIFFID (PE Feb. 73), **60p**

AND

DIGITRONIC (PW Mar. 73). Read-out PCB (1¼in × 3½in), **60p.**

TAPE NOISE LIMITER

(PE Feb. 72). S/c's, Rs, Cs, Pot, PCB (1½in × 3in), **£2·30.** Reg. PSU and PCB (1½in × 2½in), **£3·30.**

VERSATILE LIGHT EFFECTS UNIT

Single Channel Sound Controlled Light with built-in variable strobe. (PE June 72). S/c's, Rs, Cs, Pots, T/fmrs, Keyswitch, **£10·38.** PCB (3½in × 7½in) Mk. 2, also holds pots, Sw, T/T7 T/fmr, **£1·50.** SCRs—1A, **50p.**

PHOTOPRINT PROCESS CONTROL

(PE Jan./Feb. 72). For colour and B & W—finds exposure, controls timing, stabs. mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/fmr, **£7·50** PCB (3½in × 5½in) also holds pots, Sw, relay, **£1·20.**

SOUND SYNTHESISER
(PE 1973)

Details of PCBs & Components in lists.

RONDO (PE current series)

PHASING UNIT (PE Sept. 73)

ENLARGER EXPOSURE METER AND THERMOMETER
(PE SEPT. 73)

SEMICONDUCTOR TESTER
(PE OCT. 73)

WIND AND RAIN EFFECTS
(PE OCT. 73)

PROJECT Q4
(PW Quadraphonic System 1973)

DETAILS IN LISTS

SEMICONDUCTORS

AC128	**20p**	ZTX107	**9p**
AC176	**20p**	ZTX503	**14p**
AD161	**40p**	ZTX531	**22p**
BD107	**9p**	2N697	**18p**
BC108	**9p**	2N706	**13p**
BC109	**9p**	2N914	**22p**
BC147	**11p**	2N1304	**20p**
BC148	**11p**	2N1711	**18p**
BC149	**11p**	2N2219	**25p**
BC157	**12p**	2N2905	**23p**
BC158	**12p**	2N2907	**22p**
BC159	**12p**	2N3702	**10p**
BC182L	**11p**	2N3703	**10p**
BC204	**14p**	2N3704	**10p**
BC209c	**14p**	2N3819	**27p**
BC212L	**13p**	2N3823E	**31p**
BC214L	**13p**	2N5777	**40p**
BCY71	**22p**	1N914	**4p**
BFY50	**20p**	1N4001	**6p**
BSY95A	**12p**	1N4002	**7p**
MJE2955	**165p**	1N4004	**8p**
MJE3055	**83p**	1N4005	**10p**
OC28	**45p**	BA145	**17p**
OC71	**12p**	OA91	**7p**
OC84	**24p**	OA200	**7p**
ORP12	**48p**	ZIJ	**50p**
TIS43	**24p**		

CAPACITORS

ELECTROLYTIC (μF/V)

		220/10	**6p**
1·0/63	**6p**	220/16	**6p**
2·2/63	**6p**	220/25	**10p**
4·7/63	**6p**	220/40	**12p**
10/25	**6p**	226/63	**18p**
10/63	**6p**	330/10	**6p**
15/40	**6p**	470/6·3	**6p**
22/10	**6p**	470/25	**12p**
22/25	**6p**	470/40	**16p**
33/6·3	**6p**	500/64	**40p**
33/16	**6p**	680/6·3	**10p**
33/40	**6p**	680/25	**18p**
47/6·3	**6p**	1000/10	**12p**
47/25	**6p**	1000/25	**20p**
47/40	**6p**	1000/40	**40p**
47/63	**6p**	2200/25	**45p**
100/10	**6p**	2200/40	**50p**
100/25	**6p**	3300/63	**130p**
100/40	**6p**	3300/100	**320p**
100/63	**12p**	4700/16	**60p**
150/16	**6p**	4700/25	**75p**
150/63	**12p**	4700/40	**93p**

TANTALUM BEAD (μF/V)

0·1/35	**12p**
0·22/25	**12p**
0·47/35	**12p**
1·0/35	**12p**
1·5/35	**16p**
2·2/35	**12p**
4·7/35	**12p**
10/16	**12p**
10/25	**16p**
15/6·3	**16p**
22/16	**16p**
47/6·3	**16p**
47/16	**25p**

POLYESTER C280AE 250V(μF)

0·01	**3p**
0·015	**3p**
0·022	**3p**
0·033	**3p**
0·047	**3p**
0·068	**3p**
0·1	**4p**
0·15	**5p**
0·22	**5p**
0·33	**7p**
0·47	**9p**
0·68	**11p**
1·0	**14p**

POLYSTYRENE 63V 5% (ρF)
10 to 2200 **3p**; 3300 to 8200 **4p**; 10000 **5p**

RESISTORS (E24 SERIES)
¼W 5% C.F. **1p**; ½W 5% CF. **1p**; ½W 2% M.O. **3½p**

SWITCHES

Makaswitch:	
Shaft assembly	**48p**
Wafers	**33p**
Screens (per pk of 5)	**12p**
Spacers (per pk of 10)	**8p**
Rotary:	
3P4W	**28p**
Multipole Lever:	
4CL/4CL	**£1·30**
4CL/4CN	**£1·30**
Knobs	**6p**
Slide:	
DPDT	**12p**

RELAYS

2PCO 12V	**£1**
4PCO 12V	**£1·30**
Relay base & Clip	**20p**
Reed Relay 6-9V	**85p**

VAT ADD 10%

P. & P. 15p

S.A.E. FOR FREE LIST

GENERAL

All PCBs Fibreglass, Drilled, Roller-Tinned. Layout and Circuit Diagrams Free with each PCB. Unless stated "as published", PCBs are designed by Phonosonics. Pots are rotary unless stated as slider. Prices and deliveries of individual components subject to stock availability. Export: P. & P. extra, VAT: non-applicable.

PHONOSONICS, DEPT. PE23, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW

MAIL ORDER ONLY

CASED AMPLIFIERS

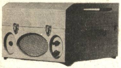

Polished wooden cabinet 14 × 13 × 9in containing a sensitive (20μV) 4 valve amplifier with tone and volume controls. 3W output to 7 × 4in 3Ω speaker. Also included is a non-standard tape deck with solenoid operation. Supplied in good working condition complete with circuit diagram. Standard mains operation. Only **£3** (£1 up to 200 miles, £1·25 over). Suitable cassette **£1.** Spare head **30p;** Amplifier chassis only, complete and tested **£1·65** (40p). 7″ × 4″ speaker **40p** (12p).

7lb BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, crystals, pots, switches, computer panels with transistors and loads of odds and ends. Still only **£1·65** (40p).

COMPUTER PANELS

3lb assorted panels **£1** (30p); 7lb **£2** (40p); 56lb **£13** (c/pd). 12 top quality panels containing power transistors, IC's, trimpots, etc. **£2** (30p); 100 boards **£12** (£1). Pack containing at least 500 components including at least 50 transistors **60p** (20p).

NEW COMPONENTS

SCR's: 200V 5A **40p;** 400V 5A **60p;** BYZ10 1200V 6A **40p;** OC16 **20p;** OC45 **8p;** OC71 **8p;** OC140 **25p;** OC170 **15p;** OC171 **15p;** BFY18 **12p;** BCY72 **8p;** 2N3055 **35p;** XC121 **5p;** BC107 **8p;** 2N3708 **8p;** 741C TO99 or 8 pin DIL **32p;** 100V 8A diodes **20p;** 3·9V or 27V 400mW zeners **7p;** 22V 1W **10p.**

BULK COMPONENTS

500 assorted resistors **£1** (20p); 300 capacitors, all types **£1** (30p); 25 assorted 10X crystals **75p** (30p); 40 assorted pots **£1** (30p).

EX-COMPUTER EQUIPMENT

1200ft ½in tape on 7in NAB spool **68p** (30p); 1800ft ¾in tape on 10½in NAB spool in case **68p** (40p); Screw top electrolytic capacitors: 20,000μF 50V **60p** (25p), 46,500μF 25V **60p** (25p); 35,000μF 15V **40p** (20p); 40,000μF 10V **40p** (20p); 20,000μF 30V **40p** (20p); 25,000μF 25V **40p** (20p).
Fans: 230V 50Hz 6½in dia. blades 2,800 r.p.m. complete with grill and mounting plate **£2·50** (40p).
Heavy duty heat sinks 6 × 5 × 3in with 2 power transistors **80p** (30p).

POWER SUPPLY UNIT

Mains transformer, 2A thermal cut-out, bridge rect. gives 1·7–10·5V with 2 extra caps. Data sheet supplied **75p** (20p).

ODD UNITS

Useful module containing OC35, 2 × OC44, GET103, R's, C's, etc. **40p** (10p). Cat's whisker and crystal **15p;** Unit with 2 modern c/o lever switches, 3 trimpots, etc. **60p** (10p).

ADD 10% TO TOTAL FOR VAT
Carr. in brackets; small parts 5p

GREENWELD (PE10)

24 Goodhart Way, West Wickham, Kent. SHOPS AT: 21 Deptford Broadway SE8. (Tel. 01-692 2009) and 38 Lower Addiscombe Road, Croydon.

TWO NEW SOLDER SIPPERS MAKE DE-SOLDERING QUICK & EASY

Longs

Longs Ltd.
Hanworth Lane
Trading Estate
Chertsey Surrey
KT16 9LZ.

Maxi-Super HT 1810 and Maxi-Mini HT 1800 Solder Sippers

Designed for use when working or re-working P.C. Boards. Permits removal of molten solder from Multi-leg components, enabling easy extraction. The solder is 'sipped' through the nozzle, and automatically ejected when the instrument is next used. A Swiss precision instrument manufactured to a high degree of accuracy.

The anti-corrosive outside casing has a knurled finish for more positive grip, and encases plated internal parts.

The Maxi-Super has been designed with a 3.5 kg. spring action recoilless plunger, whilst the Maxi-Mini with its conveniently shaped operating button, has a 2.5 kg. spring action plunger, protected by a channel guard.

Both models have been designed with an easy-to-replace 'dupont' teflon screw-in nozzle.

PLEASE FORWARD without obligation further details. ☐	PLEASE SUPPLY Maxi-Super HT 1810 at £6.60 ☐	PLEASE SUPPLY Maxi-Mini HT 1800 at £4.95 ☐

I enclose cheque value £________

NAME________ POSITION________

COMPANY________

ADDRESS________

________ SIGNED________

Prices include VAT Reg. England 68496

MEN! GIRLS!

YOU CAN EARN £70p.w.

Plus an exciting life and a secure future.
HOW?

Get into the fabulous Computer Industry now. On the ground floor. While industry, commerce, science and governments are desperately seeking trained personnel. Give us only four to six weeks and we can train you in any one of the three vital careers in computers: (1) Programming (men and girls). (2) Operating (men and girls). (3) Key Punching (girls exclusively).

We are the only training organisation able to make this offer. And our teaching methods succeed because they combine specially prepared courses with equipment such as the unique Eduputer, exclusive to us.

Thanks to our methods, people from all walks of life have exchanged boring, under-paid, insecure jobs for careers that have meaning, prestige and security.

Past performance counts for nothing. Provided you have the aptitude (which we can discover quite simply), there is no reason why you should not get out of the rut and into Tomorrow's World—the fascinating world of Computers.

The moment you qualify—and we will help you do just that—one of our own exclusive appointments agencies will introduce you to opportunities galore. Worldwide. At no cost to you. All part of our continuing service.

What have you to lose by enquiring? Information and advice are yours for the asking. Post the coupon TODAY for full details FREE and without obligation.

London Computer Training Services
S61, Oxford House, 9–15 Oxford Street, W.1.
Telephone 01-437 9906

Please send me your free illustrated brochure on training for Computer Programming (men and girls) ☐
Computer Operating (men and girls) ☐
Key Punching (girls exclusively) ☐
(Tick appropriate box)

Name________
Address________
____
________ Tel.________

Sinclair Project 80

exciting

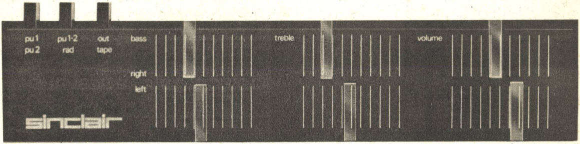

Stereo 80 pre-amplifier/control unit

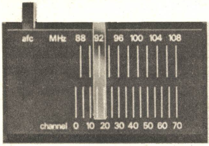

Project 80 tuner

Stereo decoder

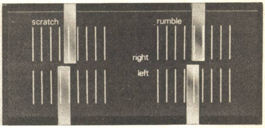

Project 80 Active Filter Unit (AFU)

only $\frac{3}{4}$'' deep x 2'' high

Living with hi-fi takes on new meaning with Sinclair Project 80. The electronics of these revolutionary new modules are all contained within elegantly designed matching cases no more than three-quarters of an inch deep. They are designed for mounting on any appropriate flat surface by means of 6BA bolts extending from the rear of each module and which pass through suitably drilled holes. Connections are taken away out of sight in a similar manner. The possibilities opened up by Project 80 are endless – superb hi-fi systems can be installed in ways hitherto only dreamed about and never before made practical. No more cutting out and shaping to put modules in position. A few holes drilled with the aid of templates supplied and the job is done. Now you need never again be faced with problems of keeping the hi-fi from clashing with carefully thought-out furnishing schemes. (That will surely please wives!) Slider controls have been introduced in place of knobs and all modules in the range incorporate new up-dated circuitry with emphasis on performance standards and built-in protection against overload and shorting. The aim was to re-think modular construction completely – to make it infinitely more versatile, even simpler and more reliable – the result – Project 80 – another triumph for Sinclair, and the most exciting construction modules ever.

the slimmest, most elegant hi-fi modules ever made

Typical Project 80 applications

System	The Units to use	Units cost
Simple battery record player	**Z.40**	**£5·45** +54p V.A.T.
Mains powered record player	**Z.40, PZ.5**	**£10·43** +£1.04 V.A.T.
30W. RMS continuous sine wave stereo amp.	**2 × Z.40s, Stereo 80; PZ.6**	**£30·83** +£3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo amp.	**2 × Z.60s, Stereo 80; PZ.8**	**£33·83** +£3.38 V.A.T.
Indoor P.A.	**Z.60, PZ.8**	**£14·93** +£1.49 V.A.T.

Project 80 FM tuner, decoder, and A.F.U. may be added as required

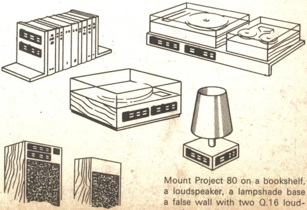

Mount Project 80 on a bookshelf, a loudspeaker, a lampshade base a false wall with two Q.16 loudspeakers . . . almost anywhere.

new thinking in modular hi·fi

Stereo 80 pre-amplifier and control unit

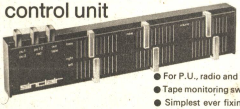

- ● For P.U., radio and tape
- ● Tape monitoring switch
- ● Simplest ever fixing

Each channel has its own separate tone and volume controls operated by sliders, enabling ideal environmental matching to be obtained. A virtual earth input stage forms part of the up-dated circuitry that ensures the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS
Size – 260 × 50 × 20mm ($10\frac{1}{4}$ × 2 × $\frac{3}{4}$ins)
Finish – Black with white indicators and transparent Sliders
Inputs – Magnetic pick-up 3mV RIAA corrected; Ceramic pick-up 300mV Radio 300mV; Tape 30mV
Signal/noise ratio – 60db
Frequency range – 20Hz to 15KHz ± 1dB: 10Hz to 25KHz ± 3dB
Power requirements – 20 to 35 volts
Outputs – 100mV + AB monitoring for tape
Controls – Press button for tape radio and P.U. Sliders for volume, bass (+ 12dB to − 14dB at 100Hz) treble (+ 11dB to − 12dB at 10KHz)

R.R.P. **£11.95** +£1·19 V.A.T.

Project 80 FM tuner and stereo decoder

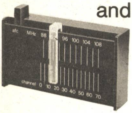

- ● Twin dual varicap tuning: 4 pole ceramic filter: switchable A.F.C.
- ● On the decoder, solid state stereo indicating beacon.

Making the Project 80 F.M. tuner and decoder available separately gives a wider choice of systems and saves money where stereo reception may not be required. The tuner is a triumph of electronic design and assures excellent performance. The decoder gives a 40dB channel separation with 150mV output per channel. Both units may be used with other than Project 80 systems.

TECHNICAL SPECIFICATIONS OF TUNER
Size – 85 × 50 × 20mm ($3\frac{1}{2}$ × 2 × $\frac{3}{4}$ins)
Tuning range – 87·5 to 108 MHz
Detector – I.C. balanced coincidence for good A.M. rejection
One I.C. equal to 26 transistors
Distortion – 0·2% at 1 KHz for 30% modulation
4 pole ceramic filter in I.F. section
Aerial impedance – 75 Ω or 240-300 Ω
Sensitivity – 4 microvolts for 30dB quieting
Output – 300 mV for 30% modulation
Power requirements – 23 to 33 volts

R.R.P. **£11.95** +£1·19 V.A.T.

DECODER
Size – 47 × 50 × 20mm ($1\frac{7}{8}$ × 2 × $\frac{3}{4}$ins)
One 19 transistor I.C.

R.R.P. **£7.45** +0·74 V.A.T.

Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed stockists also offer this guarantee. Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a charge (typically £1·00) will belmade.

sinclair

Sinclair Radionics Ltd. London Road, St. Ives, Huntingdon PE17 4HJ
Telephone St. Ives (0480) 64646

Z.40 & Z.60 power amplifiers

totally short-circuit proof

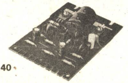

Z.40

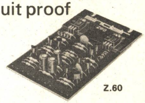

Z.60

Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced.

Z.40 TECHNICAL SPECIFICATIONS
Size – 55 × 80 × 20mm ($2\frac{1}{8}$ × $3\frac{1}{8}$ × $\frac{3}{4}$ins) 9 transistors
Input sensitivity – 100mV
Output – 15 watts RMS continuous into 8 Ω (35v)
Frequency response – 10Hz – 100KHz ± 1dB
Signal/noise ratio – 64dB
Distortion – at 10 watts into 8 Ω less than 0·1%
Power requirements – 12 to 35 volts

Z.60 TECHNICAL SPECIFICATIONS
Size – 55 × 98 × 15mm ($2\frac{1}{8}$ × $3\frac{3}{4}$ × $\frac{3}{4}$ins) 12 transistors
Input sensitivity – 100-250mV
Output – 25 watts RMS continuous into 8 Ω (45V).
Distortion – typically 0·03%
Frequency response – 10Hz to more than 200KHz ± 1dB
Signal/noise ratio – better than 70dB
Built-in protection against transient overload and short circuiting
Load impedance – 4 Ω min; max. safe on open circuit

Z.40 R.R.P. **£5.45** + 0·54 V.A.T.; **Z.60** R.R.P. **£6.95** + 0·69p V.A.T.

Project 80 active filter unit

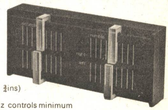

Makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls applied to each channel make it easier to obtain ideal stereo balance.

TECHNICAL SPECIFICATIONS
Size – 108 × 50 × 20mm ($4\frac{1}{4}$ × 2 × $\frac{3}{4}$ins)
Voltage gain – minus 0·2dB
Frequency response – 36Hz to 22KHz controls minimum
Distortion – at 1 KHz – 0·03% using 30V supply
HF cut off (scratch) – 22KHz to 5·5KHz, 12dB/oct. slope
L.F. cut off (rumble) – 28dB at 20Hz, 9dB/oct. slope

- ● For scratch and rumble control
- ● Transistorised active circuitry

R.R.P. **£6.95** +0·69 V.A.T.

Power supply units

PZ.8

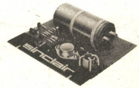

Stabilised. Re-entrant current limiting makes damage from overload or even direct shorting impossible. Normal working voltage (adjustable) 45V.

R.R.P. **£7·98** + 0·79p V.A.T.
Without mains transformer

PZ.5 30V unstabilised
R.R.P. **£4·98** + 0·49p V.A.T.

PZ.6 35V. stabilised
R.R.P. **£7·98** + 0·79p V.A.T.

To SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid ____________________

____

____

for which I enclose Cash/Cheque for £________ including V.A.T.

Name ____________________

Address ____________________

____

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

SITUATIONS VACANT

TECHNICIANS AND ENGINEERS FOR ST. ALBANS AND LUTON

QUALIFIED OR NOT!

OPPORTUNITIES for challenging work on testing and calibrating valve and solid-state electronic measuring equipments embracing all frequencies up to u.h.f. in Production, Service and Calibration departments.

APPLICATIONS are invited from people of all ages with experience or formal training in electronics and from Ex-Services technicians.

HIGHLY COMPETITIVE SALARIES, negotiable and backed by valuable fringe benefits. Overtime normally available.

GENEROUS RE-LOCATION EXPENSES available in most instances.

CONDITIONS excellent; free life assurance, pension schemes, canteen, social club.
37½ hour, 5-day, working week.

WRITE or phone for application forms quoting reference PE743.

mi

MARCONI INSTRUMENTS LTD,
Longacres, St. Albans, Herts
Tel: St. Albans 59292
Luton Airport, Luton, Beds
Tel: Luton 33866

A GEC-Marconi Electronics Company

1971
THE QUEEN'S AWARD TO INDUSTRY 1971

OPPORTUNITIES IN AUSTRALIA for Video/CTV/CCTV Technicians. Progressive company, member of major Australian group expanding rapidly in video field requires experienced technicians in colour TV, video system, closed circuit TV systems including cameras. Top salary, car supplied, assistance in travelling and housing. Locations—Hobart, Melbourne, Sydney. Telephone: ANNE GRAHAM, London 01-636 0541 for further details.

BOOKS AND PUBLICATIONS

DIRECT FROM MANUFACTURER—a comprehensive catalogue of U.H.F. and V.H.F/F.M. aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.I.Y. enthusiast. Complete with useful installation hints. Send **3p** stamp to CLAYDEW ENTERPRISES (P.E.), 261 Hardness Street, London, SE24.

LADDERS

LADDERS, "Special Offer" Unvarnished Triples, 9ft 7in closed—24ft 7in extended. **£18·70** delivered. HOME SALES LADDER CENTRE (PEE2), Haldane (North), Halesfield (1), Telford, Shropshire. Tel. 0952 586644.

FOR SALE

FIBRE OPTICS

Flexible Light Pipe for conveying lights to inaccessible positions. Fibroflex Type 1. Glass 1·14mm effective dia. PVC sheathed. **44p** per metre. (VAT inc.), P. & P. 10p. Any quantity.

Polariser Sheet up to 1 sq. ft. max. size. **16½p** per sq. in. (VAT inc.), P. & P. up to 6 in. square **10p**; over 6 in. square **30p**

★ Cut down glare
★ See those nixie tubes
★ Cross them for light control
★ Make your own strain gauge for plastics and glass

Circuit Board Etching Kits. Full instructions. **£1·37½** (VAT inc.), P. & P. **20p**

Photographic CDS Light Cells—used (with part of original circuit free), **33p** (VAT inc.), Post free.

All items are strictly C.W.O.

From: ARVIN SERVICE COMPANY
12 CAMBRIDGE ROAD
ST. ALBANS

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

TV LINE OUT-PUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey TW9 2EQ
01-948 3702

CATALOGUE NO. 18, Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price **23p,** including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

LABORATORY EQUIPMENT. Cosser oscilloscope **£20.** 4 channel recorder. 4 channel amplifier, Pye current amplifier/voltage supply, all **£30** each. Racal voltage supply **£8** or **£100** lot. Telephone: Worcester 421110 (Evenings).

FOUR CORE Self adhesive ribbon cable, 14mm 1mm. Very unobtrusive and easy to install. Ideal for stereo speaker wiring, intercoms, etc. **6p** per yard. S.A.E. for sample. RCC COMMUNICATIONS, 107 West Street, Ewell, Surrey.

SERVICE SHEETS

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from **5p** with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue **15p.** HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue **15p.** S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

Please mention
PRACTICAL ELECTRONICS
when replying to
ADVERTISEMENTS

EDUCATIONAL

CITY AND GUILDS EXAMINATIONS

Make sure you succeed with an ICS home study course for C & G Electrical Installations, Telecommunications Technicians and Radio Amateurs. Free details from: International Correspondence Schools, Dept. 730D, Intertext House, London, SW8 4UJ.

COLOUR TV SERVICING

Make the most of the current boom. Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers. Also radio and audio courses. Free details from: International Correspondence Schools, Dept. 730D2, Intertext House, London, SW8 4UJ.

TECHNICAL TRAINING

Get the qualifications you need to succeed. Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self build radio kits. Free details: International Correspondence Schools, Dept. 730D3, Intertext House, London, SW8 4UJ.

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

13 WEEKS' full-time Colour TV Servicing course (including Mono revision) for men with a good electronics background.

Next session commences on April 16th.

Prospectus from London Electronics College, Dept. A2, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

OPENSHAW TECHNICAL COLLEGE, Whitworth Street, Manchester, M11 2WH. Evening courses for radio experimenters, including radio, electronics and model control. All facilities available including professional instruction. For further details telephone 061-223 8282.

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

RECEIVERS AND COMPONENTS

R.T. SERVICES
(MAIL ORDER ONLY)
77 Hayfield Rd., Salford 6, Lancs.

Veroboard 6×5 0·1 Matrix, 2 for **£1.** 4×4¼ 0·1 Matrix, 4 for **£1.** 12×3¾ 0·15 Matrix, **75p** each.

Mullard A.M. Module. I.F. Strip, LP1166, **£1·10** inc. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2½×2×1½ in with circuit, **£1·37½** inc. P.P.

Crouzet Geared Motors, 30-60 r.p.m. New, **£1·54** inc. P.P.

UHF TV Tuners. Transistorised, **£1·65** inc. P.P.

VCR138 CRT. New, boxed, **£3·30** inc. P.P.

Transformers. 7·5V + 7·5V ½A, **66p** inc. P.P. 12-0-12V, 100mA, **90p** inc. P.P. 9-0-9V, 100mA, **69p** inc. P.P. 20V, 1A, **88p** inc. P.P.

Transformers. 52-0-52V, 1A + 22-0-22V, 200mA, **£2·20** inc. P.P.

P.C. Board. S/S, 5½ × 5½in, 10 for **70p** inc. P.P.

Panel with 2 SN7490, 2 SN7441 counting circuit with end connector, **£2·20** inc. P.P.

Transistorised Timer. Variable delay. 110 or 250V A.C. input. With instructions. Brand new, **£2** inc. P.P. Size 3″ × 2″ × 2″.

10″ Speaker in Cabinet, 3 Ω with long lead and jack plug made by Pye. Ex-Govt., brand new **£5·50** inc. P.P.

Electrolytic Capacitors, 4,000 MF,50 VW, 4½″ × 1¾″ **75p.** inc. PP.

Ampex Tape 7in. L.P. 1,800ft, **£1·60** inc. P.P.

TUNBRIDGE WELLS. Components from TELESERVICE, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

PRECISION
POLYCARBONATE CAPACITORS

Close tolerance. High stability. Extremely low leakage. All 63V d.c. Plus or minus 1% tolerance: 0·47μF, **56p;** 1·0μF, **66p;** 2·2μF, **80p;** 4·7μF, **£1·30;** 6·8μF, **£1·64;** 10μF, **£2;** 15μF, **£2·75.** Also available ±2% and ±5%, ex. stock.

TANTALUM BEAD CAPACITORS: Values available: 0·1, 0·22, 0·47, 1·0, 2·2, 4·7, 6·8μF at 15V/25V or 35V; 10μF at 16/20V or 25V, 15μF at 10/16V or 20V; 22μF at 6/10V or 16V; 33μF at 6V or 10V; 47μF at 3V or 6V; 100μF at 3V. All at **10p** each; 10 for **95p;** 50 for **£4.**

TRANSISTORS: BC107, BC108, BC109; All at **9p** each; 6 for **51p;** 12 for **96p.** May be mixed for quantity price. BC182 and BC212 at **10p** each; AF178 at **30p** each. All brand new and marked. Full spec. devices.

POPULAR DIODES. IN914, 6p each; 8 for **45p;** 18 for **90p. IN916, 8p** each; 6 for **45p;** 14 for **90p. IS44, 5p** each; 11 for **50p;** 24 for **£1.** All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4·7, 5·6, 6·8, 7·5, 8·2, 9·1, 10, 11, 12, 13·5, 15V. Tol. ±5% at 5mA. All new and marked. Price **7p** each; 6 for **39p;** 14 for **84p.** Special offer 6 of each voltage (66 zeners) **£3·65.**

RESISTORS. Carbon film 5%, ⅓W at 40° C, ½W at 70° C. Range from 2·2Ω to 2·2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at **1p** each; **8p** for 10 of any one value; **70p** for 100 of any one value. Special pack—10 of each value 2·2Ω to 2·2MΩ (730 resistors) **£5.**

440V A.C. CAPACITORS: 0·1μF, size 1⅛in × ½in, **40p;** 0·25μF (1⅜in × ⅝in), **55p;** 0·47 and 0·5μF (1⅜in × ¾in), **66p;** 1·0μF (2in × ¾in), **85p;** 2·0μF (2in × 1in), **£1·15.**

SILICON PLASTIC RECTIFIERS 1·5A. Brand new wire-ended DO27. 100PIV at **7p** each; 4 for **26p.** 400PIV at **8p** each; 4 for **30p;** 800PIV at **11p** each; 4 for **42p.**

7p post and packing on all orders below £5.
Export orders—please add cost of air/sea mail.

PLEASE ADD 10% VAT TO ALL ORDERS
Send S.A.E. for lists of other ex-stock items, L.E.D.'s, disc capacitors, electrolytics, etc. Wholesale price lists available to bona fide companies.

MARCO TRADING
Dept. E3, The Maltings Station Road
Wem, Salop.
Tel. Nantwich (Cheshire) 63291

LARGE COMPUTER PANELS. Average 40 transistors. Plenty of components, **84p** (25p). **AMERICAN PANELS,** 2N series transistors. Quality components, 4, **55p** (10p). **7400 SERIES I.C.S. ON PANEL(S),** 10, **£1** post paid. **M.C. METERS, THREE ASSORTED** 2-3in, **£1·15** (27p). **5-FIGURE RESETTABLE COUNTER.** 18/22V. Works on 12V, **£2·20** (20p). **SILICON DIODES,** 650V 1½A. 10 on tagboard, **35p** (5p). **PANELS WITH 10 S.C.R's** 30V 1½A ferrite cores and 12 transistors, **£1** (10p). **COPPER CLAD PAX. PANELS,** 5½ × 5½in, 6, **45p** c.p. 7½in × 9in **25p.** c.p. 6, **£1·25** c.p. 8½in × 9in. **30p** c.p. 6, **£1·35** c.p. 10in × 9in **35p** c.p. 6, **£1·45** c.p. **WIRE ENDED NEONS,** 10, **50p** (8p). **FOUR PIANO KEY SWITCH WITH INTERLOCK, 33p** (7p). **SILVER MICA CAPACITORS,** 100 assorted, **55p** c.p. **10 ASSORTED MIDGET POTENTIOMETERS 60p** c.p. **VALUPAKS.** From **25p to 75p.** Send 10p stamps for list of these and panels, etc. Refund on purchase.
7lb ASSORTED COMPONENTS, £1·65 c.p.
2lb ASSORTED COMPUTER PANELS £1·65 c.p.

J.W.B. RADIO
2 BARNFIELD CRESCENT, SALE, CHESHIRE M33 1NL
Postage in brackets. Mail order only

DRY REED INSERTS

 

Overall length 1·85″ (Body length 1·1″). Diameter 0·14″. Max. ratings 250v D.C. and 500 mA. Gold clad normally open contacts. **69p** per dozen; **£4·12** per 100; **£30·25** per 1,000; **£275** per 10,000. VAT and post paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34897

BRAND NEW COMPONENTS by return Electrolytics 16V, 25V, 50V—0·47, 1, 2·2, 4·7 10 mF, **4p**; 22, 47, **4½p** (50V, **5p**); 100, **5½p** (50V, **7p**); 220, **6p** (50V, **9p**). Subminiature bead-type tantalums 0·1/35V, 0·22/35V, 0·47/35V, 1/35V, 2·2/35V, 4·7/35V, 10/16V, **8p.** Mylar Film 100V—0·001, 0·002, 0·005, 0·01, 0·02, **2p**; 0·04, 0·05, **3p**; 0·068, 0·1, **3½p**. Polystyrene 63V E12 series 10–1,000pF, **2p**; 1,200–10,000pF, **3p.** Miniature highstab resistors, 5%, E12 series—Carbon Film ⅓W, 1Ω–10MΩ (10% over 1 MΩ). Metal Film ⅛W, 10Ω–2·2MΩ and 1W, 27Ω–10MΩ all **¾p** each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

KX2 GLASS FIBRE P.C. KIT

For transistor and integrated circuits (DIL, TO5, etc.). Track width and spacing capability down to 1mm. Full instructions and all materials supplied, including 3 pieces of 1 oz. copper board 3″ × 4″.

£1·65 plus 10p P. & P.

KELTRONIX LTD.
15 Barra Street, Glasgow G20 0AX

VEROBOARD	0·1	0·15	Plain 0·15
2½in × 5in	**26p**	**26p**	**13p**
2½in × 3¾in	**23p**	**18p**	**12p**
3¾in × 5in	**30p**	**32p**	**20p**
3¾in × 3¾in	**26p**	**26p**	—
Track cutter	**40p**	**40p**	—

MINIATURE CERAMIC CAPACITOR KITS
KIT 1, 10 each E6 value 22pF to 1000pF, 50V. Total 110, **£1·55.**
KIT 2, 25 each E6 value 22pF to 1000pF, 50V. Total, 275 **£3·65.**

SEMICONDUCTORS
8 pin dil 741, **39p;** BC107, **10p;** BC108, **10p;** BC109, **10p;** IN914, **4p.**

SWITCHES
Toggle switch. 250V 1·5A SPST, **18p;** DPDT, **25p.** Slide switch. DPDT miniature or standard, **11p.** Push to make, non-locking, **12p.**

MINIATURE VERTICAL PRESETS
100Ω, 220Ω, 470Ω, 680Ω, 1K, 2·2K, 4·7K, 6·8K, 10K, 22K, 68K, 100K, **4p** each.

NEK ELECTRONICS (P6)
28 Carnegie Road, St. Albans, Herts.
Please add 10p P. & P. Mail order only

COMPONENT SALE

1,000's of components for disposal following wholesaler closing industrial electronics department.

OVER 200 TYPES OF CAPACITOR: Electrolytic, paper, metallised film at knock down prices (e.g. 0·04mfd 150V at 1·5p, 10mfd 16V at 3p).

Also large quantity of switches, fuseholders, semiconductors, variable transformers at unrepeatable prices.

Complete balance of stock must go.

Send 4p in stamps and address for lists.

O & M SERVICES (P.E.)
281A BURY OLD ROAD, PRESTWICH
MANCHESTER, LANCS. M25 5JA

MAINS UNIT FOR TRANSISTOR RADIO ONLY

For single outputs, 6v, 9v, **£2.20**
For two separate outputs, 6v + 6v., 9v + 9v, **£2.75.** P. & P. 20p per unit.
(*Please state outputs reqd.*).
All units are completely isolated from mains by double wound transformer ensuring 100% safety. ALL PRICES INCLUDE VAT.
R.C.S. Products (Radio) Ltd. (Dept. P.E.)
36 Raymond Avenue, South Woodford,
London E18 2HG.

5 N-CHANNEL FETs. Type 3819E (2N3819) for **£1** (inc. VAT). Full spec. transistors complete with circuit details for building voltmeter, timer, ohmmeter, etc. For complete list of FETs and other transistors available send 10p P.O. REDHAWK SALES LTD., 45 Station Road, Gerrards Cross, Bucks. Mail Order Only.

COMPONENTS GALORE. Pack of 500 mixed components. Manufacturers' surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers, etc. Send **£1** + 10p P. & P. C.W.O. to: CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

RADIO & TELEVISION AERIAL BOOSTERS £2·95, five television valves **45p. 50p** bargain transistor packs, bargain **£1** resistor and capacitor packs. UHF-VHF televisions **£7·50.** Carr. £1·50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ POCKET-SIZED **MAXI-VOLT** Big ¼ inch Spark Generator (instant 15,000 volts!) Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz (85g). Send **£1·35** for your Maxi-volt now!

★ UNIQUE **TRANSMITTER/RECEIVER KIT.** No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send **£5·90** for yours now!

★ PSYCHEDELIC **MINI-STROBE KIT.** Take a pocket-sized lightning storm to Disco's and Parties. "BRAIN-FREEZE" 'EM with vari-speed stop-motion flashes. Includes super case, too. Send **£2·20** now!

(All prices include VAT, packing & postage)

Send remittance to:

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh
Ewell, Surrey (Mail order only)

Or for more details, send 15p for lists, plus free design project sheet

---

fibre optic suppliers

LOW COST LED—MLED 500, MV 54
MLED 500 is in TO92 case, for PC board mounting MV 54 is T¾ size, 2mm, miniature. Both emit visible red light. Current requirement 20mA, 150Ω resistors available for 5V d.c. (TTL) operation.

2N5777—SILICON PHOTO DARLINGTON AMPLIFIER
Economical, high sensitivity, TO92, LIGHT DETECTOR

	1	2	5	10	25
MLED500	**22p**	**44p**	**£1·10**	**£2·20**	**£3·74**
MV54	**22p**	**44p**	**£1·10**	**£2·09**	**£3·52**
150Ω	—	—	—	—	**11p**
2N5777	**55p**	**£1·10**	**£2·53**	**£4·62**	**£9·90**

ULTRASONIC TRANSDUCERS—TRANSMITTER RECEIVER PAIR
40kHz for burgular alarm, remote control, novelties. Great value at **£3·85** per trans/receiver pair.

HNCP 37—NEUTRAL CIRCULAR POLARISER
Reduce glare on crt's, meters, displays, panels. 50mm × 50mm (2in), **66p**; 75mm × 75mm, **£1·21**; 150mm × 150mm, **£4·40.**

CROFON 1610—64 FILAMENT LIGHT CONDUIT
1·8mm active dia., 3·3mm o/d. Simply cut to length and conduct light where required. For displays, internal illumination, multiple point lighting. 1 metre, **£1·32**; 2m, **£2·64**; 5m, **£5·50**; 10m, **£10·45.**

FP40—PLASTIC OPTICAL MONO-FIBRE, 1mm DIAMETER
Single strand unjacketed light guide, simple to use. 5 metres, **£1·10**; 10m, **£1·98**; 25m, **£3·85.** FP20 (0·5mm) and FP60 (1·5mm) also available.

MARE'S TAILS FOR DECORATIVE DISPLAYS
7,000 fibres, professionally finished, beautiful. Add lamp, stand, cover to make a Fibre Optic Lamp. Eye catching in boardroom, hall or foyer, **£11·00** each.

All prices shown include P. & P., VAT. C.W.O. please. For full information on our complete range, send 9in × 6in S.A.E. to

FIBRE OPTIC SUPPLIERS (PE)
P.O. Box 702 London W10 6SL

HARDWARE SUPPLIES—Sheet aluminium individual sizes or standard packs, drilled to spec. Screws, nuts, washers, etc., Fascia panels in aluminium individual requirements. Printed circuit boards, one-off or small runs. Printed circuit drafting tapes, etc., **7p** for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks., CV37 9JP.

LOW COST I.C. MOUNTING. I.C. pin sockets in lengths of 100 for **60p** (P. & P. 5p). Quantity rates. S.A.E. details and sample. GASKELL, "Oak Lodge," Tansley, Derbyshire.

MORE RANGES FOR LESS MONEY!

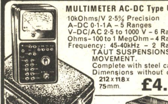

MULTIMETER AC-DC Type U-437
10kOhms/V 2·5% Precision
A–DC 0·1-1A – 5 Ranges
V–DC/AC 2·5 to 1000 V – 6 Ranges.
Ohms–100 to 1 MegOhm – 4 Ranges.
Frequency: 45-40kHz – 2 Ranges.
TAUT SUSPENSIONS MOVEMENT.
Complete with steel case.
Dimensions without case: 212 x 118 x 75mm.
£4.95

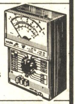

AC/DC Multimeter type U4324
A-DC 0·06-3A – 6 Ranges.
A-AC 0·3-3A – 5 Ranges.
V-DC 0·6-1200 V – 9 Ranges.
V-AC 3-900 V – 8 Ranges.
Frequency: 45 to 20kHz–2 Ranges.
Resistance: 500 Ohm to 5 MOhm–5 Ranges. Decibel: –10 to +12dB –2 Ranges. Accuracy ± 2·5%.
Dimensions: 167 x 98 x 63 mm.
Only **£8.00**

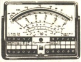

SUPERTESTER 680 R ICE
10 Fields – 80 Ranges: Plus a lot of accessories for measurements of 500A-AC 100 A/DC– Temperature– –50C to +200C– Magnetic fields up to 15 KGauss– Phase indicator– EHT 25kV Electronic Volt Ohm– meter Transistor Diode Tester etc.
Dimensions: 128 x 95 x 32 mm– 300 grams 20kOhm/V Accuracy 1% DC **Ask for free catalogue**
£18.50
Accessories Extra

Add 10% VAT to all items + 35p P & P
ELECTRONIC BROKERS LTD.
49-53 Pancras Road London NW1 2QB. Tel: 837 7781

BUILD THE

TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 & BBC-2 TV

Send s.a.e. for leaflet

Complete kit: Post 35p **£9·80**

Built tested and guaranteed Post 35p **£13·75**

MINIKITS ELECTRONICS, 35g LANGLEY DRIVE, WANSTEAD, LONDON E11 2LN (Mail Order only)

ENAMELLED COPPER WIRE

S.W.G.	*1lb Reel*	*½lb Reel*
10–14	**£1·40**	**80p**
15–19	**£1·40**	**80p**
20–24	**£1·43**	**83p**
25–29	**£1·52**	**91p**
30–34	**£1·57**	**97p**
35–40	**£1·69**	**£1·04**

Please add 10% to all above prices to cover VAT

The above prices cover P. & P. in U.K. Supplied by

INDUSTRIAL SUPPLIES
102 Parrswood Rd., Withington, Manchester 20
Telephone No. 061-224 3553

GLASS FIBRE P.C. BOARD—large supplies available. $\frac{1}{16}$in single sided one ounce copper, **2p** per 3 sq in (under 1ft); **75p** per sq ft (over 1ft). $\frac{1}{16}$ in double sided one ounce copper, **1p** per sq in (under 1ft); **£1** per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. SOLID STATE LIGHTING, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

METER REPAIRS. Ammeters. Voltmeters, Multi-Range meters, etc., also Linear scale Transistorised Ohmmeters for sale. METER REPAIRS, 39 Chesholm Rd., London N16 0DS.

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 76½p)

SEND 5" × 7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

HOLIDAY FOR BOYS. 14/16 years, August 1974. Tuition and practical work in electronics, radio production and tape recording, engineering (Karting) and photography. Eleven days in Norfolk, **£17·50.** Write for free brochure: INTER-SCHOOL CHRISTIAN FELLOWSHIP, c/o 1 Hubbard Road, London, SE27 9PJ.

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M C relays, components, etc. Lower Beeding 236.

BARGAIN LISTS. Connectors, instrument boxes, spark generators, silicon diodes, transistors, new items very low prices. S.A.E. illustrated lists. FREAR, 2 Richmond Terrace, Ulverston, Lancs. LA12 0BU.

VEROSTRIP

LENGTH 8·5"

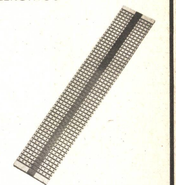

WIDTH 1·5"

Available from your Local Retailer

0·1 and 0·15 pitch Vero Strip is suitable for all applications where Tag Boards can be used.

vero

VERO ELECTRONICS LTD.
INDUSTRIAL ESTATE
CHANDLERS FORD HANTS.

BUILD A CHORDING PROFESSIONAL SYNTHESISER

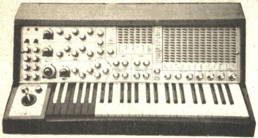

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES
CASH SAVINGS
by buying modules and parts in bulk!
All modules are available separately:
Ring Modulator RM2, **£8.** Voltage-controlled Oscillator VC01, **£10·50,** giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type **£13.** White noise type WN1, **£7.** Voltage-controlled amplifier VCA1, **£10.** Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, **£13.** Voltage-controlled Phase PH1, **£17.** Automatic Announcement Fader module for fading of music by microphone announcement, AF1, **£10.** etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls **£5·50.** REVERB Module and spring unit **£15.** V.A.T. 10% extra. V.A.T. paid orders over **£75.**

The Synthesiser shown above is the **Dewtron** "Apollo" A.1. which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts.

VCO-2 STABLE, PRECISION V/C OSCILLATOR gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. **£24** each or **£27** each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. **£17.** OFT-1 chording module **£9.** Modules (except VCO-1) guaranteed two years.

With over 7 years' unblemished reputation in these pages, ***Dewtron*** *continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading groups. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Send 15p for full catalogue of our famous musical effects.*

D.E.W. LTD. **254 Ringwood Road, FERNDOWN, Dorset BH22 9AR**

OSMABET LTD. We make transformers amongst other things.

AUTO TRANSFORMERS, 110/200/220/240V.
30W, **£1·70**; 50W, **£2·40**; 75W, **£2·85**; 100W, **£3·80**; 500W, **£10·80**; 750W, **£14·25**; 1000W, **£18·00**, etc.
LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6·3V 1·5A, **£1·20**; 3A, **£1·50**; 6A, **£2·55**; 12V 1·5A, **£1·50**; 3A, **£2·55**; 6A CT, **£3·40**; 18V 1·5A CT, **£2·55**; 24V 1·5A CT, **£2·55**; 3A CT, **£3·45**; 5A, **£4·80**; 8A, **£7·35**; 12A, **£10·85**; 40V 3A CT, **£4·50**; 50V 6A CT, **£13·50**; 25V 2A+25V 2A, **£4·90**; 12V 4A+12V 4A, **£4·90.**
LT TRANSFORMERS TAPPED SEC. Prim. 200/240V
0–10–12–14–16–18V 2A, **£2·60**; 4A, **£3·75**;
0–12–15–20–24–30V 2A, **£3·40**; 4A, **£4·50**;
0–5–20–30–40–60V 1A, **£3·40**; 2A, **£4·50**;
0–40–50–60–80–90–100–110V 1A, **£4·90.**
MIDGET RECTIFIER TRANSFORMERS
For FW rect.; 200/240V a.c. 9–0–9V 0·3A, 12–0–12V 0·25A or 20–0–20V 0·15A, **£1·65** each; 9–0–9V 1A, **£1·35**; 12–0–12V 1A or 20–0–20V 0·75A, **£1·50** each.
MAINS TRANSFORMERS
Prim. 200/240V a.c. TX6 sec., 425–0–425 500 Ma, 6·3V CT 6A, 6·3V CT 6A, 0–5–6·3V 3A, **£16·50**; TX1 425–0–425V 250 Ma, 6·3V CT 4A, 6·3V CT 4A, 0–5–6·3V 3A, **£9·75**; MT3 Prim. 0–110–240V sec. 250V 100 Ma, 6·3V 2A, E/S, **£2·70.**
O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec, tapped 3–8–15ohms, A–A 6·6KΩ 30W, **£5·70**; A–A 3KΩ 50W, **£9·00**; 100W (EL34 KT88, etc.), **£15·75**; tapped Multi O/P 10W **£3.**
G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W **35p.**
LOUDSPEAKERS FOR AMPLIFIERS
BAKER 25W, **£6·40**; 35W, **£7·20**; HI-FI Major Module 20W w/tweeter Xover, **£9·20**; Baker speaker lists; FANE 50W, **£10·50**; 60W, **£13·50**; HI-FI speakers, EMI base 13×8in 3 or 15Ω, **£1·60**; 5in 8Ω, **£1·15**; 7×4in 15Ω, **£1·60**; 8×5in 3, 8, 15 or 80Ω, **£1·75** each.
LOUDSPEAKERS
2¼in 8, 16 or 75Ω, 2½in 8 or 25Ω, 2¾in 80Ω, 3in 3, 8, 25 or 35Ω, 3½in 8, 15 or 80Ω **90p** each; 5in 3, 8 or 25Ω, 5×3in 3 or 8Ω, **£1·05**; 7×4in 3 or 15Ω, 6½in 3Ω, 8×2¾in 3Ω, **£1·25**; 10×6in 3Ω, **£1·50.**
SPEAKER MATCHING TRANSFORMERS
12W 3 to 8 or 15Ω up or down **£1·30.**
"INSTANT" BULK TAPE/CASSETTE ERASER
Instant erasure, tape spools, cassettes, demagnetises tape heads. 200/240V a.c. **£3·25.**
RELAYS, SUB-MINIATURE
15, 20 or 30V d.c. 2 CO's **50p** each.
12V d.c. FLUORESCENT LIGHTING
Silicon transistor invertor for 20W tube, **£5·75.**
TAPE RECORDER MOTORS
New, Blowers, fans, etc., 110V a.c. **50p.**
Carriage and VAT on all orders.

S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YG
Tel. 01-958 9314

BAKER 12" MAJOR £9·90

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £12·50

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in × 13in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUDSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W	£8·80	Superb 12 in. 20W	£16·50	New Group 50/12	
Major 12 in. 20W	£9·90	Group 25 12 in. 25W	£8·80	12 in. 50W	£17·60
Deluxe 12 in. 15W	£11·00	Group 35 12 in. 35W	£9.90	30-16000 cps.	

BAKER LOUDSPEAKER CO., BENSHAM MANOR PASSAGE
THORNTON HEATH, SURREY Tel. 01-684-1665
PRICES INCLUDE VAT. HI-FI ENCLOSURE PLANS 42p

PARKERS SHEET
METAL FOLDING
MACHINES
HEAVY VICE
MODELS

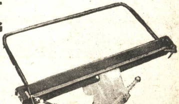

With Bevelled Former Bars

No. 1. Capacity 18 gauge mild steel × 36in. wide ... **£17** carr. 50p
No. 2. Capacity 18 gauge mild steel × 24in. wide ... **£12** carr. 38p
No. 3. Capacity 16 gauge mild steel × 18in. wide ... **£12** carr. 38p

Also new bench models. Capacities 36in. x 18 gauge **£35.** 24in. x 16 gauge **£32.** Carriage 75p. Add 10% VAT to total price of machine and carriage. End folding attachments for radio chassis. Tray and Box making for 36in. model, **27½p** per ft. Other models **17½p.** The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 40.3997

TO SPARK YOUR IMAGINATION!

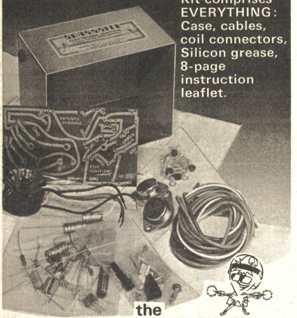

Kit comprises EVERYTHING: Case, cables, coil connectors, Silicon grease, 8-page instruction leaflet.

the SPARKRITE

Electronic Ignition Kit only £9·35

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

• Sustained peak performance. • Up to 20% fuel saving. • Instant all-weather starting. Faster acceleration, higher top speed. • Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price: **£9.35** inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available **£11.55** inc. V.A.T. and postage. **GUARANTEED 5 YEARS.**

ORDER NOW To: ELECTRONICS DESIGN ASSOCIATES,
82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £9·35. Or for ready built unit £11·55.

NAME ....

ADDRESS ....

(Live near Walsall? Call in for an actual workshop demo. It really is convincing).

PE3

'BIG' Discounts

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS	£
EMI 13in × 8in 3, 8 or 15 ohm	
Plain	2·05
With Co-Axial Tweeter	2·20
Twin Tweeter	3·55
Type 350, 8 ohm, 20W	8·00
6½in, 8 ohm, 10W	2·70
8in, 8 ohm, 10W	3·75
12in, 8 ohm, 20W	5·50
8in × 5in, C/Mag. 5W	1·20
8in × 5in, Dual cone 8 ohm, 10W	2·45
ELAC 8in 8 ohm Dual cone	2·10
GOODMANS 6½in 8 ohm Dual cone	1·60
FANE, 7in × 4in, 3 or 8 ohm	1·00
8in Dual cone 8 ohm	2·40
CELESTION 8in, 15 ohm	1·55
ADASTRA 10in, 8 or 15 ohm, 10W	3·05
BAKER GROUP 25 12in, 8 or 15 ohm, 25W	6·45
P. & P.	0·25
5in, 8 ohm, 5W C/Mag.	0·85
2½in, 8 ohm or 64 ohm	0·50
P. & P.	0·10

TWEETER AND CROSSOVER	
EMI 3½in, 3 or 8 ohm C/Mag.	1·00
Cone Tweeter 8 or 15 ohm, 10W	2·40
Cone Tweeter 8 ohm, 3W	1·40
Horn Tweeter 8 ohm, 20W	5·85
Dome Tweeter 8 ohm, 30W	4·85
Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1·05
P. & P.	0·10

KIT FORM CABINETS, TEAK VENEER.	
12in × 12in × 6in with 8in, 8in × 5in or 6½in and 3½in cutout	2·45
17in × 10in × 9in with 8in or 13in × 8in cutout	3·50
18in × 11in × 9in with 13in × 8in cutout for EMI 350	4·25
P. & P. each	0·35

MICROPHONES	
CM20 Crystal Hand	0·50
CM70 Planet stick metal, switch crystal	1·55
DM160 Dynamic uni-dir, ball metal	3·95
UD130 50K/600 ohm, uni-dir, ball metal	4·50
TW206	5·75
CONDENSER MIKE 600 ohm, uni-dir	7·90
Cassette Stick Mike with R. Control on/off switch (2·5 and 3·5mm J/Ply)	1·35
P. & P.	0·15

SOLDERING IRONS	
ANTEX CN240 15W	1·60
SK1 Kit (15 watt iron, 2 spare Bib, etc.)	2·65
X25 25W (low leakage)	1·60
P. & P.	0·10

CARTRIDGES	
ACOS GP91/2SC or GP91/3SC Stereo comp.	1·00
GP93/1 Stereo crystal	1·35
GP94/1 Stereo crystal	1·75
GP95/1	1·35
GP96/1	1·75
GP101	0·75
SONOTONE 9THAC Stereo ceramic, diam.	1·80
19-TI Stereo crystal	0·80
BSR SC5M Stereo ceramic	2·25
SX5H Stereo crystal	1·60
SX5M Stereo crystal	1·60
X5H Mono/stereo	1·25
X5M Mono/stereo	1·25
GOLDRING G800	3·85
G850	2·95
P. & P.	0·05
STYLI FOR ABOVE	
Sapphire **35p** D. Diamond	1·25
GOLDRING G800/G850	1·95

BATTERY ELIMINATORS	
240V input 6, 7·5 or 9 300mA	2·20
12V d.c. input (fits in car lighter socket) 6, 7·5 or 9 d.c. output at 300mA	2·20
P. & P.	0·10

TAPES	Stnd.	LP	DP
5in	45p	55p	70p
5¾in	55p	65p	95p
7in	70p	1·00	1·30
P. & P. 1–3 each			0·09
4 or more lot			0·30

LOW NOISE CASSETTES	1–5	6–10	11–20
C60	35p	33p	30p
C90	45p	43p	40p
C120	55p	52p	50p

Cassette Head Cleaner	0·35
P. & P. 1–5 each	0·03
6–10 lot	0·15
11–20 post free	

PLASTIC LIBRARY CASES for	
5in Reels	0·18
5¾in Reels	0·22
7in Reels	0·25
CASSETTE CASES	0·10
P. & P. 1–3 each 5p; 4 or more	0·20

BIB ACCESSORIES	
Tape Editing Kit, Ref. 23	1·30
Recording Tape Splicer, Ref. 20	1·15
Cassette Tape, Editing, Ref. 24	1·40
Cassette Salvage Kit, Ref. 29	0·40
12's Cassette Case, Ref. 34	1.00
Stylus Balance, Ref. 32A	1·15
Spirit Level, Ref. 46	0·50
Hi-Fi Stereo Test Cassette	1·90
Groove-Kleen Record Cleaner	1·90
P. & P.	0·10

BUDGET SPEAKER SYSTEMS

1. Pr. of 10watt 8ohm 2 speaker system in de luxe teak veneer cabinet 18″ × 11″ × 9″ wired, inc. plugs. **£25·00** per pair.
2. Pr. of 20watt 8ohm 2 speaker system freq. response 50c.p.s. to 17,000c.p.s. Teak veneer cab. 21½″ × 12″ × 9″ with 12ft. cable and plugs. **£29·95** per pair.

**Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED**

Riversdale Electronics

Mail Order Department PE/3
P.O. Box 470, Manchester M60 4BU

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)

13 SOUTH MALL, EDMONTON, N.9 803 1685

"CRESCENT" BUBBLE LIGHT SHOW

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour makes the music you produce more interesting and will appeal to the visual as well as the audio senses.
This budget system compares very favourably with the more sophisticated and much higher priced models.
Specification—Projector: 150W, convection cooled, at 30ft the projected image = 16ft; Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour.
The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, **£15**; 6in Liquid Wheel, **£5**=**£20** + 75p carr.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2¾in × 2¼in × 3½in. Our Price **£2·75** plus 10p P. & P. Same model suitably wired for the Philips Cassette **£3** plus 10p P. & P.

DIGITAL CLOCK KIT

 

24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. **£29·50** + 50p P. & P. Please send S.A.E. if you require more information.

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U.BUILD.IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ THE POWER AMP MODULE TP100W
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm). **£14·28**, carr. 45p.

★ THE PRE-AMP MODULE
Four control pre-amp, Vol., Bass, Treble, Middle controls. Designed to drive most amplifiers using F.E.T. first stage. **£3·96**, carr. 25p.

★ THE POWER SUPPLY MODULE PS100
is supplied complete with the mains transformer. **£9·66**, carr. 50p. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules.
A fantastic bargain. If you purchase all three modules. **£25**, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers.

VAT

Please include 10% VAT on goods plus carriage.

200/250V MAINS RELAY

Heavy duty contacts. 2,500 Ω coil. All new and unused D.P.D.T. mains relays **50p** + V.A.T. Carr. Free. Special quantity price: **£40** per 100 relays.

TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. × 3¼in. × 1½in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for **£2·50** plus 10p P. & P.

MINI LOUDSPEAKERS

2¼in 80 ohm, **50p**; 2¼in 40 ohm, **50p**. Please include 5p P. & P. on each L.S.

CRESCENT "C.300" DISCO CONTROL PACK

A control Unit which when connected to twin decks makes a disco of professional quality. We supply a smart front panel which incorporates controls, switch and input sockets. The control module, I.C. construction incorporating mixing, pre-amp and headphone listening amplifier. The power pack enables this unit to work from the standard mains.
* Inputs include Mic., Tape/Cassette and Twin Decks. * Controls include Mic., Tape, Each Deck,

CRESCENT CATALOGUE

If you construct you should own one. Send **20p**, inc. carriage.

EMI LOUDSPEAKER 450

10W 13in × 8in ± two 2·2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3–8–15 ohm imp.
£3·75 plus 38p P. & P. each.

CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 **28p**, C90 **38p**, C120 **48p** plus 5p P. & P.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

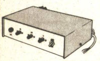

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed)
£18·50 plus 38p P. & P.

If you require more information please send S.A.E.

"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT

This fantastic little box approx. 4″ × 3″ × 2½″ when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts.
Complete with a sensitive level control the unit is fused and cannot harm your amplifier.
A Bargain at **£7·50** plus 10p.

LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output.
With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.

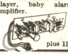

£1·75 plus 13p P. & P.

7in × 4in LOUDSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in × 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: **£1·60**. Free postage on this item.

Dimmit

range of light dimmers

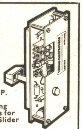

Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppression, 60mm slider range; size 12 × 5 × 4 cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. **£5·50** inc. VAT, add 10p P. & P. Also available in 2kW, with separate heatsink.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for use on lamps, heaters, motors, etc. Rotary and Slider control versions. Ratings: 1,000W, 2,000W.

NEW addition to Dimmit range—Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. Just place unit near any sound source—radio, hi-fi, tv, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Rating 800 watt. Full instructions. **£7·50** inc. VAT, add 10p P. & P. *Send 10p for complete illustrated catalogue and price list.*

YOUNG ELECTRONICS Mail Order Dept.
54 Lawford Road, London NW5 2LN. Telephone 01-267 0201

A Quality 30 MHz Counter for under £100

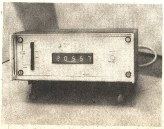

MEMORY DISPLAY
4 GATE TIMES
AUTO INPUT LEVEL
10 mV SENSITIVITY
10 MHz CLOCK
1 Hz RESOLUTION

Shortly available: 200 MHz version at £200

FOR HIRE OR SALES CONTACT: **John Ticehurst**
P.H. Electronics (Sales) Ltd.
Sandwich Industrial Estate
Sandwich, Kent CT13 9LN
Tel.: Sandwich 2517

---

become a RADIO-AMATEUR !

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

RAPY

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME : ____________________

ADDRESS : ____________________ EB34

____________________ BLOCK CAPS please

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

Telephone Corner

COMPLETE TELEPHONES

NORMAL HOUSEHOLD TYPE

EX G.P.O. **Only £1-05p** P. & P. 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only 27 1/2p POST & PACKING 16½p

Tested and Guaranteed Paks

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	55p
B81	10	Reed Switches, 1" long ⅛" dia. Highspeed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight Post & packing 15p.	55p
H4	250	Mixed Resistors. Approx. quantity counted by weight Post & packing 15p.	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945	55p
H41	2	BD131/BD132 Complementary Plastic Transistors	55p

Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	55p

Make a rev counter

for your car

The "TACHO BLOCK". This encapsulated block will turn any 0·1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1-10p each

Ex GPO Push Button Intercom Telephones

Exactly as internal telephone systems still in everyday use where automatic internal exchanges have not yet taken over. Available in 5, 10 or 15 ways. Complete with circuits and instructions. Necessary 24 pair cable **22p** per yard. Price of each instrument is independent of the number of ways.

£2.75 p.p. 38½p

Cable can be sent by Parcel Post. Post and Packing per 50 yds.: **73½p.**
Extension Telephones 71½p each, p.p. 27½p. **£1·37½** for 2, p.p. 55p. These phones are extensions and do not contain bells.

A Cross Hatch Generator £3-85 post paid

A complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. A project in the Sep. '72 edition of Television.

New Paks

Tested & Guaranteed

H63	4	2N3055 Type NPN Sil. power transistors. Below spec. devices	55p
H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66	55p
H66	4	40362. Type PNP Sil. transistors TO-5 can comp. to H65	

Untested, Unmarked

H67	10	3819N Channel FET's plastic case type.	55p

Over 1,000,000 Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

Our very popular 4p Transistors

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR £1-10p PNP 27½p.

High Speed Magnetic Counter

4 digit (non-reset)
24V or 48V (state which)
4×1×1 in. **33p**, p.p. 5p.

Plastic Power Transistors

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1 VCE Min. 15 HFE Min. 15	1–12	13–25	26–50
40 watt	**22p**	**20p**	**18p**
90 watt	**26½p**	**24½p**	**22p**

Range 2 VCE Min. 40 HFE Min. 40	1–12	13–25	26–50
40 watt	**33p**	**31p**	**29p**
90 watt	**38½p**	**36½p**	**33p**

Complementary pairs matched for gain at 3 amps. **11p** extra per pair. Please state NPN or PNP on order.

LM380 AUDIO I.C. as featured in Practical Wireless December issue. Complete with application data, **£1·10.**

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from **11p** each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. his fantastically detailed conversion calilator carries thousands of classified ferences between metric and British (and S.A.) measurements of length, area, lume, liquid measure, weights, etc. cket Size, **15p**, Wall Chart, **18p.**

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at **16½p** each } Now new low
16 pin type at **18p** each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock, details are in our latest catalogue, send for it TODAY using the coupon below.

N.B.—Books are void of V.A.T.

Our famous P1 Pak

is still leading in value

Full of Short Lead Semiconductors and Electronic Components, approx. **170.** We guarantee at least **30** really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

11p P. & P. on this Pak.

Please ask for Pak P.1. only 55p

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME..

ADDRESS ....

....

ALL PRICES INCLUDE 10% V.A.T.

MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co Reg No 820919

Dept. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.
TELEPHONE: SOUTHEND (0702) 46344.

FREE!

Practical Radio & Electronics Certificate course includes a learn while you build ***3 transistor radio kit.*** Everything you need to know about ***Radio & Electronics*** maintenance and repairs for a ***spare time income*** and a ***career*** for a better future.

Over 150 ways to engineer a better future

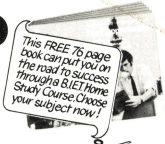
This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained – a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters – and there are many more on file at Aldermaston Court – speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help *you*. **Write to B.I.E.T. Dept. BPE34, Aldermaston Court, Reading RG7 4PF.**

CUT OUT THIS COUPON

Tick or state subject of interest.
Post to address below.

MECHANICAL
Society of Engineers—A.M.S.E. (Mech.) ☐
Institute of Engineers & Technicians (A.M.I.E.) ☐
CITY & GUILDS
Gen. Mech. Eng. ☐
Maintenance Eng. ☐
Welding ☐
Gen. Diesel Eng. ☐
Sheet Metal Work ☐
Eng. Inspection ☐
Eng. Metallurgy ☐

ELECTRICAL & ELECTRONIC
Society of Engineers—A.M.S.E. (Elec.) ☐
CITY & GUILDS
Gen. Electrical Engineering ☐
Electrical Installations ☐
Electrical Maths ☐
Computer Electronics ☐
Electronic Eng. ☐
Practical Radio & Electronics (with kit) ☐

MANAGEMENT & PRODUCTION
Institute of Cost & Management Acctnts. ☐
Computer Programming ☐
Works M'ment. ☐
Work Study ☐
Gen. Production Eng. ☐
Estimating & Planning ☐
Storekeeping ☐
Management Skills ☐
Quality Control ☐

DRAUGHTSMANSHIP
Institute of Engineering Designers (A.M.I.E.D.) ☐
General Draughtsmanship ☐
Elec. Draughtsmanship ☐
Architectural Draughtsmanship ☐
Technical Drawing ☐

RADIO & TELECOMMUNICATIONS
CITY & GUILDS, Radio, TV/Electronics ☐
CITY & GUILDS Telecoms. ☐
Gen. Radio & TV Eng. ☐
Radio Amateurs Exam ☐
Radio Servicing ☐
TV Servicing ☐
Colour TV ☐

AUTOMOBILE & AERONAUTICAL
Institute of the Motor Industry ☐
A.M.I.I. ☐
MAA/IMI ☐
CITY & GUILDS
Auto Eng. ☐
Gen. Auto Eng. ☐
Motor Mechanics ☐
Auto Diesel Eng. ☐
Garage M'ment. ☐
ARB Aero Engineering Certs. ☐
Gen. Aero Eng. ☐

CONSTRUCTIONAL
Society of Engineers—A.M.S.E. (Civ.) ☐
Institute of Building—L.I.O.B. ☐

A.B.T. Clerk of Works ☐
Construction Surveyors Institute—L.C.S.I. ☐
CITY & GUILDS
General Building (all branches) ☐
Heating & Vent. ☐
Inst. Clerk of Works ☐
Site Surveying ☐
Health Engineering ☐
Road Construction ☐
Quantities, Estimates ☐
Hydraulics ☐
Structural Eng. ☐

GENERAL
Agricultural Eng. ☐
Council of Eng. Institutions ☐
Farm Science ☐
Plastics ☐

Supplementary courses for Nat. Certificates.

G.C.E.
– choose from 58 'O' & 'A' level subjects.

Coaching for many exams, including C & G

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE34 QN
Aldermaston Court, Reading RG7 4PF

BPE34

NAME
Block Capitals Please
ADDRESS

OTHER SUBJECTS

AGE

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/sia) Ltd.: South Africa—Central News Agency Ltd. Publishers' Subscription Rate (including postage): Inland £3·25, Overseas £3·50.

Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's

DONT RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES
Order your latest Henry's Catalogue Price 55p post paid
complete with Discount Vouchers

You pay less VAT with Henry's Low Prices

BUILD THE TEXAN

20+20 WATT IC STEREO AMPLIFIER

As featured by
Practical Wireless 1972

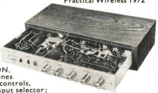

Now built and used by thousands of satisfied customers.

FEATURES: slim design, overall size in cabinet 15¼in × 2¾in × 6⅜in 6-IC's, 10 transistors, stabilisers, Gardeners low field transformer, Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form.

HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES—DEVELOPED TEXAS ENGINEERS FOR PERFORMANCE, BY RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES. On/off switch indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape-head, etc. Constructional details Ref. No. 21, 30p. Distributed by Henry's throughout UK.

FREE Teak cabinet with complete kit.

KIT PRICE **£28·50** (+ VAT + 50p carr/packing) or

built and tested **£35·00** (+ VAT + 50p carr/packing) as illustrated

EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT

DISCO MINI: A complete portable disco, fitted mixer/preamp, 2 decks all facilities	£98·50
As above but with Slider Controls	£118·50
100 watt amplifier for above	£42·50
SDLS100: 100 watt mixer/amplifier with slider controls	£69·00
R50: 50 watt mixer/amplifier	£49·50
R100 100 watt mixer/amplifier	£57·50
DISCO AMP: 100 watt mixer/amplifier chassis unit	£73·00
DISCO MIXER/PREAMPLIFIERS (O/P for up to 6-100 watt amplifiers):	
SDLI (rotary controls):	£49·50
SDLII (slider controls):	£58·50
DISCO VOX (slider controls): The complete disco preamp.	£72·00
DJ100: 100 watt power amplifier for above	£49·50
DJ30L: 3 channel 3kW sound to light	£36·00
DJ40L: as 30L plus built-in microphone	£47·50
DIMAMATIC. 1kW adjustable speed auto dimmer	£25·00
Carlsbro Reverberation Unit	£44·00
SCENE STROBE	£19·00
ROAD STROBE	£25·00
SUPER STROBE	£45·00
Disco anti-feedback microphone	£11·95
Colt 150 watt liquid wheel projector	£22·50
150 watt QI liquid wheel projector	£50·00
150 watt QI cassette wheel projector	£50·00
Spare Effects and Liquid cassettes, large range of patterns	£6·00
Mini spot bank fitted 3 lamps	£12·95
Auto Trilite (mini with flashers)	£17·00
Bubblemaster with 1 gal. liquid	£41·15
MIXERS/MICS/SPEAKERS/LIGHTING U.K.'s largest range of Disco lighting 6in liquid wheels	£5·00

FREE STOCK LIST Ref. No. 18 ON REQUEST AKG/RESLO/DJ/CARLSBRO/EAGLE CHASSIS AND COMPLETE SPEAKER SYSTEMS, MEGAPHONES, TURNTABLES, PUBLIC ADDRESS COMPONENTS, MICS., STANDS, MIXERS, CABINETS

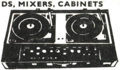

All prices carr. paid (UK) (VAT EXTRA).
Barclaycard/Access call, write or phone your order 01-723 6963—easy terms for callers.

EXCLUSIVE DECCA KELLY SPEAKERS

12 watt speaker Tweeter systems. 8in Bass/Midrobe and Melinex Domed HF radiator plus crossover **£12·50** per pair of systems (carr/packg. 40p) or built into veneered cabinets, size 18 × 12 × 6½in. **£19·50** pair (carr. £1).

HI-FI TAPE EQUIPMENT

U.K.'s largest range with discounts and demonstrations for callers. Latest stock lists on request (Ref. No. 17).
Phone 01-402 4736 for Barclay/Access Card, Direct orders and latest prices.

TRANSISTORS/ SEMICONDUCTORS

U.K.'s largest range for every application. Small quantity discounts. Also Trade, Export and Industrial enquiries invited. Latest stock list (Ref. No. 36). Including valves on request.

ELECTRONICS SUPPLIES

Specialists in electronics for more than 30 years. Trade and industry supplies — every type of component and equipment.

SINCLAIR PROJECT 80

Stereo Preamplifier	£11·95
Audio Filter Unit	£6·95
Z40 15 watt Amplifier	£5·45
Z60 25 watt Amplifier	£6·95
PZ5 Mod. for 1 or 2 Z40	£4·98
PZ6 Mod. (S Tab) 1 or 2 Z40	£7·98
PZ8 Mod. (S Tab) 1 or 2 Z60	£7·98
TRANSFORMER FOR PZ8	£3·95
NEW FM TUNER	£11·95
STEREO DECODER	£7·45

All items post paid.

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise. IF stages. LED indicators, Tuning meter, AFC, Easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size: 8in × 2¾in × 6⅝in. Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5, 30p.) Henry's are sole distributors UK and Europe.

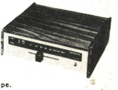

Kit Price **£21·00** (+ VAT)

or built and tested **£24·95** (+ VAT)

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TAPES LTD. TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN ½ REC. PRICES. COMPLETE WITH LIBRARY CASES.

	3 for	6 for	10 for	25 for
C60	£1·00	£1·80	£2·80	£6·75
C90	£1·33	£2·57	£4·20	£10·25
C120	£1·62	£3·15	£5·00	£12·25

Quantity and trade enquiries invited.

LEARN A LANGUAGE—complete with phrase book. German, French, Spanish, Italian. **£1·36** per course. **£5** for any 4.

LOW COST HI-FI SPEAKERS
SPECIAL OFFERS

EMI 13in × 8in—full range speakers (post 20p each or 30p pair); *150TC—8 ohms Twin Cone 10 watt, **£2·20** each or **£4** pair; *450 10 watt c/o Twin Tweeters 3, 8 or 15 ohms, **£3·50** each or **£6·90** pair; EW 15 watt 8 ohms c/o Tweeter, **£4·30** each or **£7·90** pair; 350 20 watt c/o Tweeters 8 or 15 ohms, **£7·50** each or **£14·20** pair.
* Polished wood cabinet **£4·80**, post 35p.

8 ohms full range (post 20p)
FR4 4in 5 watt, **£4**; FR65 6½in 10 watt, **£5·50**; FR8 8in 15 watt, **£6·95**; FR23 9 × 6in 15 watt, **£6·00.**

BASS AND MID RANGE—8 ohms (post 20p)
AA12 5in 15 watt, **£3·30**; B110 5½in 15 watt, **£5·60**; B200 8in 15 watt, **£6·45**; B139/2 13in × 8in 30 watt LF, **£10·25.**

TWEETERS AND CROSSOVERS (post 20p)
K2006 10 watt 8 or 15 ohms, **£2·10**; FHT6 15 watt 8 ohms, **£3·30**; K2011 30 watt 8 ohms, **£4·75**; T27 KEF, **£4·25**; Axent 100 30 watt 8 ohms **£4·90**; K4009 1kHz/5kHz c/o, **£2·20**; SN75 3kHz var. c/o, **£2.**

SPEAKER KITS (carr. etc. 35p)
20-2 8in 30 watt, **£10** each; 20-3 8in 40 watt, **£15** each; LINTON 2 20 watt, **£15·95** pair; GLENDALE 3 30 watt, **£28·95** pair; DOVEDALE 3 50 watt, **£42** pair; KEF KK2, **£20·40** each; KEF KK3, **£32** each.

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size: 4½in long × 2in wide × 11/16in deep.
Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines, etc.

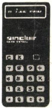

Price **£24·95** (+ VAT)

Also assembled ready to use **£27·20** (+ VAT)

10% VAT TO BE ADDED TO ALL ORDERS. EXPORT SUPPLIED. Prices and descriptions correct at time of proof. Subject to change without notice E & O E. See pages 202 and 203 of this magazine.

Like a permanent job at Henry's? Experienced and trainee salesmen required. Tel. 01-402 8791.

Henry's RADIO LIMITED
[illegible] WARE ROAD, LONDON W2

404-406 Electronic Components and [illegible] 01-402 8381 [illegible] All mail to
309 PA – Disco – Lighting High Pow[illegible] 23 696[illegible] ware Road,
303 Bargains Store (Callers only) [illegible]
Home and Car Entertainment Centres [illegible] now
120 Shaftesbury Avenue, London W1 0[illegible]
104 Burnt Oak Broadway, Burnt Oak, [illegible]
190-194 Station Road, Harrow, Middle[illegible]
354-356 [illegible]ware Road, London W2 01[illegible]
Discount [illegible]
Free at all stores